
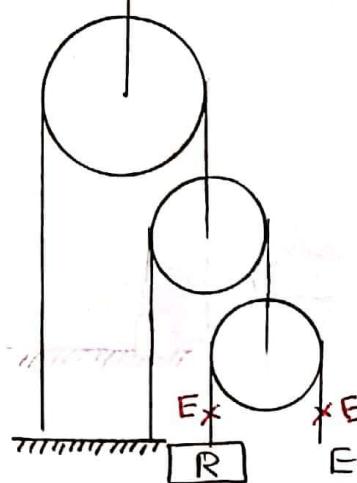



# محمد حسين اوصالی

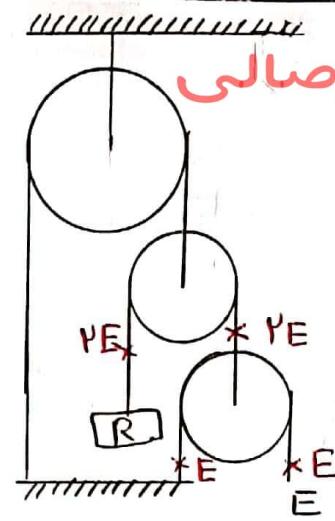


$$\frac{R}{E} = \frac{F}{E} = 1$$




$$\frac{R}{E} = \frac{PE}{E} = P$$

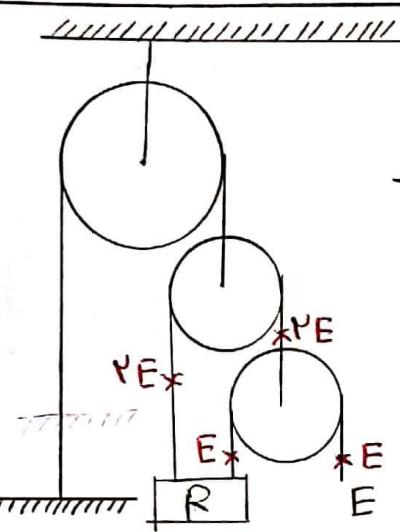


$$\frac{R}{E} = \frac{PE + E}{E} = P$$

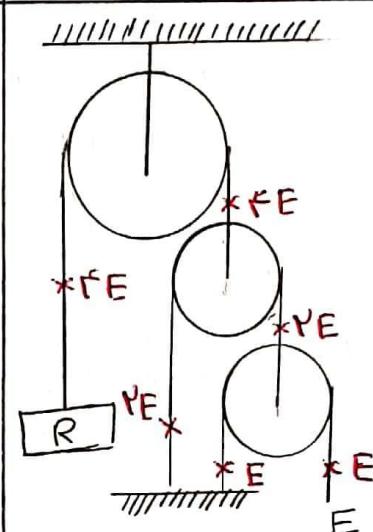


$$\frac{R}{E} = \frac{FE}{E} = F$$

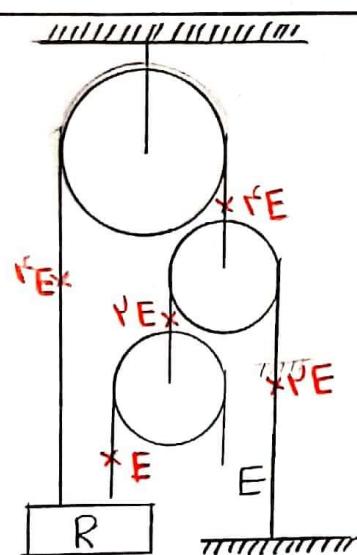


$$\frac{R}{E} = \frac{FE + E}{E} = 2$$

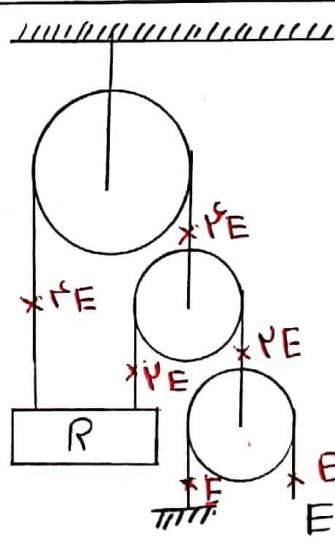

$$\frac{R}{E} = \frac{FE + PE}{E} = 2$$

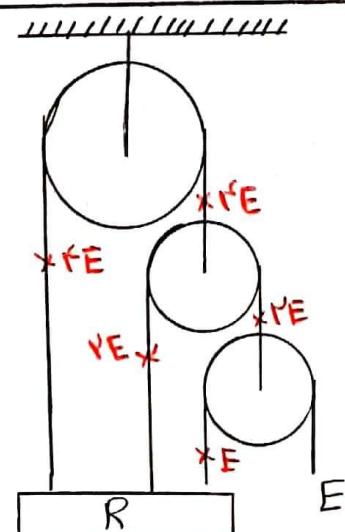

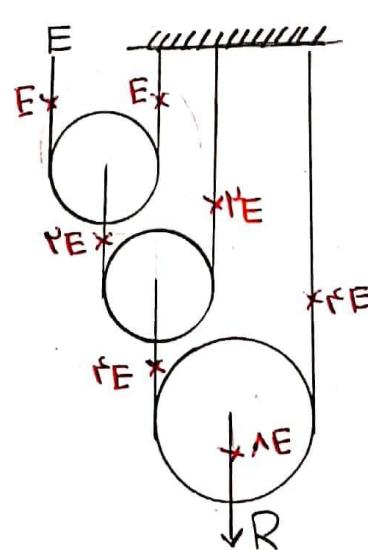
$$\frac{R}{E} = \frac{FE + PE + E}{E} = 3$$




$$\frac{R}{E} = \frac{AE}{E} = A$$


# محمد حسين اوصالی

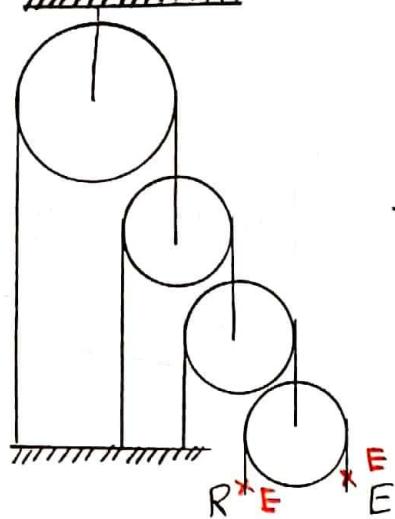


$$\frac{R}{E} = \frac{E}{E} = 1$$

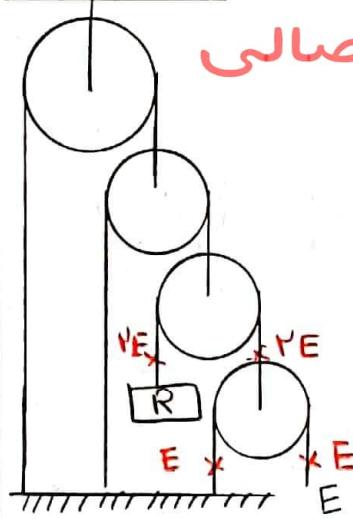


$$\frac{R}{E} = \frac{R_E}{E} = 1$$

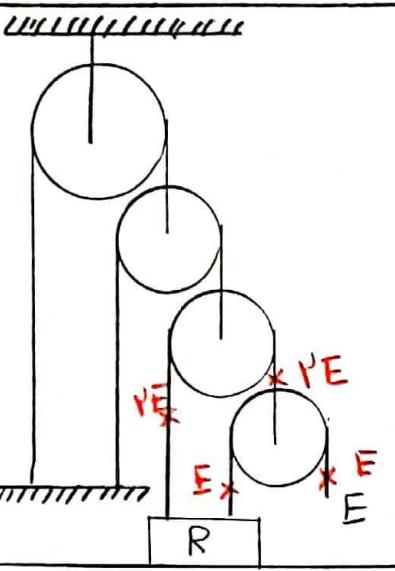


$$\frac{R}{E} = \frac{R_E + E}{E} = 2$$

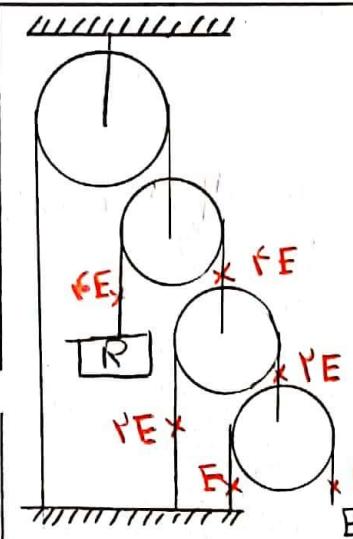


$$\frac{R}{E} = \frac{F_E + E}{E} = 2$$

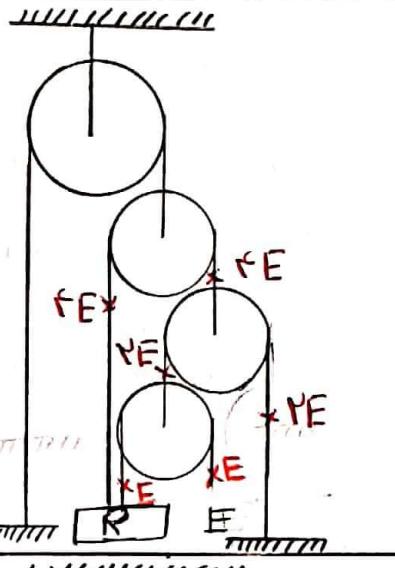


$$\frac{R}{E} = \frac{F_E + E}{E} = 2$$

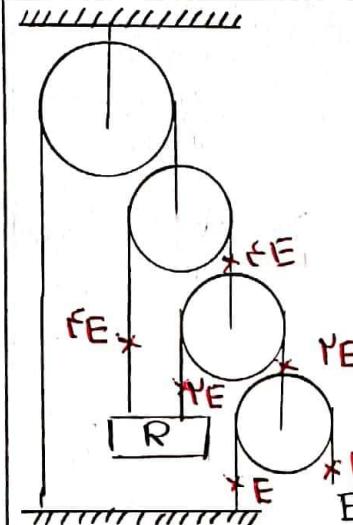
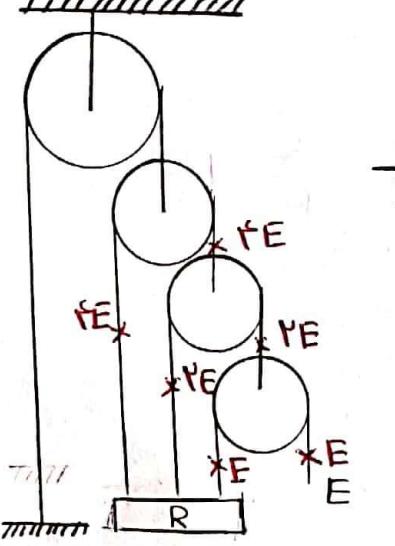
$$\frac{R}{E} = \frac{F_E + R_E}{E} = 2$$



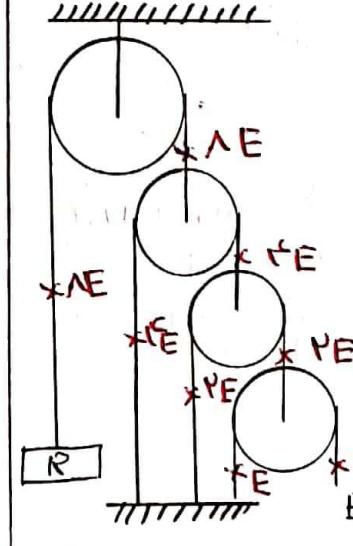
$$\frac{R}{E} = \frac{F_E + R_E + E}{E} = 3$$




$$\frac{R}{E} = \frac{R_E}{E} = 1$$


# محمد حسين اوصالی

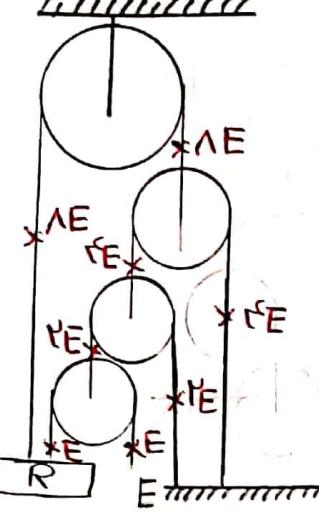

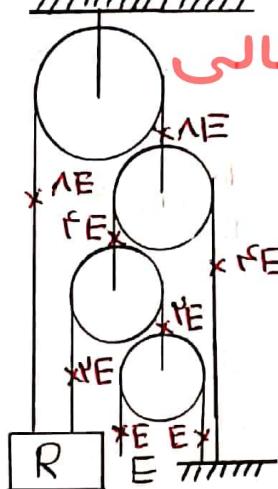
$$\frac{R}{E} = \frac{\lambda E + E}{E} = 9$$



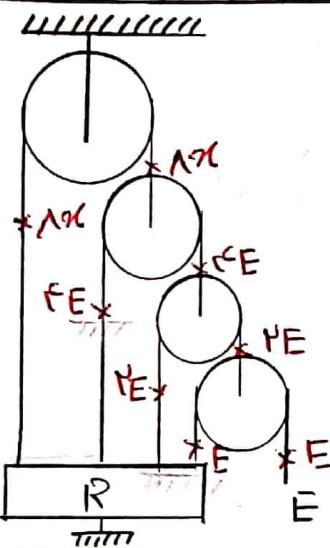
$$\frac{R}{E} = \frac{\lambda E + \mu E}{E} = 10$$



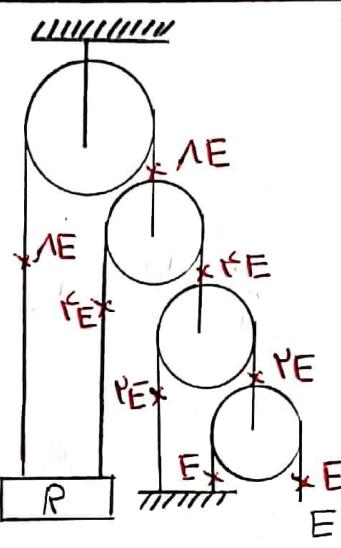
$$\frac{R}{E} = \frac{\lambda E + \mu E + \nu E}{E} = 11$$



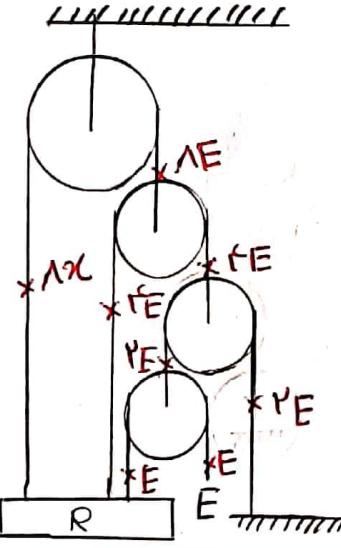
$$\frac{R}{E} = \frac{\lambda E + \mu E + \nu E}{E} = 12$$



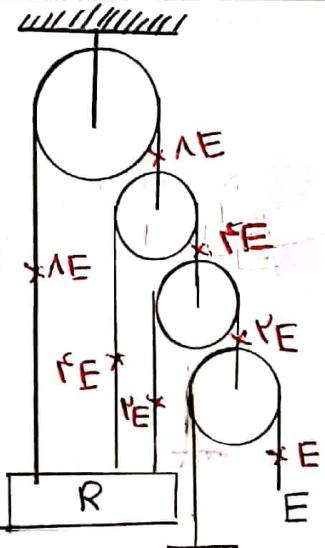
$$\frac{R}{E} = \frac{\lambda E + \mu E + \nu E + \tau E}{E} = 13$$


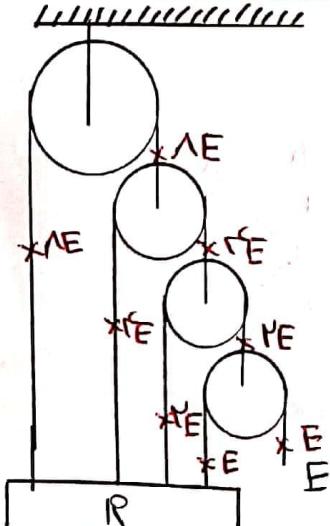
$$\frac{R}{E} = \frac{\lambda E + \mu E + \nu E + \tau E}{E} = 14$$


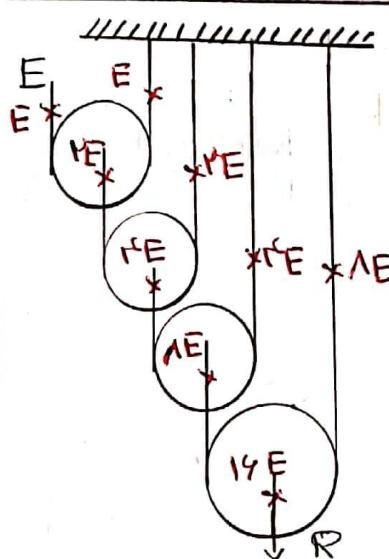
$$\begin{aligned} \frac{R}{E} &= \frac{\lambda E + \mu E + \nu E + \tau E}{E} \\ &= 15 \end{aligned}$$



$$\frac{R}{E} = \frac{14 E}{E} = 15$$