

1-

Obtain the node voltages in the circuit in Fig. 3.4.

**Answer:**  $v_1 = -2 \text{ V}$ ,  $v_2 = -14 \text{ V}$ .

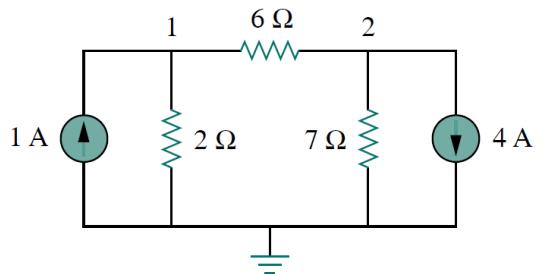


Figure 3.4 For Practice Prob. 3.1.

2-

Find  $v$  and  $i$  in the circuit in Fig. 3.11.

**Answer:**  $-0.2 \text{ V}$ ,  $1.4 \text{ A}$ .

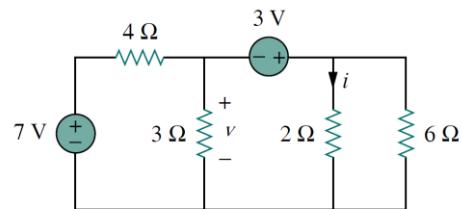


Figure 3.11 For Practice Prob. 3.3.

3-

Find  $v_1$ ,  $v_2$ , and  $v_3$  in the circuit in Fig. 3.14 using nodal analysis.

**Answer:**  $v_1 = 3.043 \text{ V}$ ,  $v_2 = -6.956 \text{ V}$ ,  $v_3 = 0.6522 \text{ V}$ .

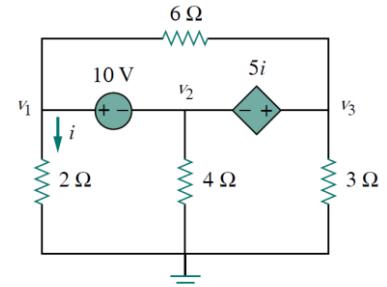


Figure 3.14 For Practice Prob. 3.4.

4-

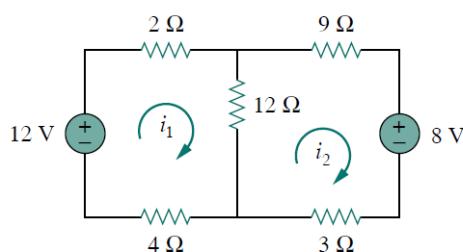


Figure 3.19 For Practice Prob. 3.5.

Calculate the mesh currents  $i_1$  and  $i_2$  in the circuit of Fig. 3.19.

**Answer:**  $i_1 = \frac{2}{3} \text{ A}$ ,  $i_2 = 0 \text{ A}$ .

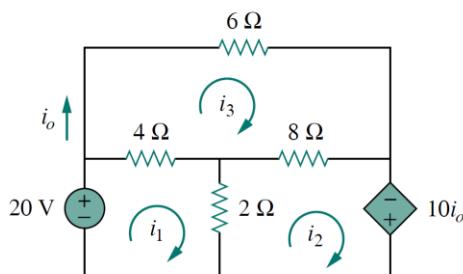



Figure 3.21 For Practice Prob. 3.6.

Using mesh analysis, find  $i_o$  in the circuit in Fig. 3.21.

**Answer:**  $-5 \text{ A}$ .


6-

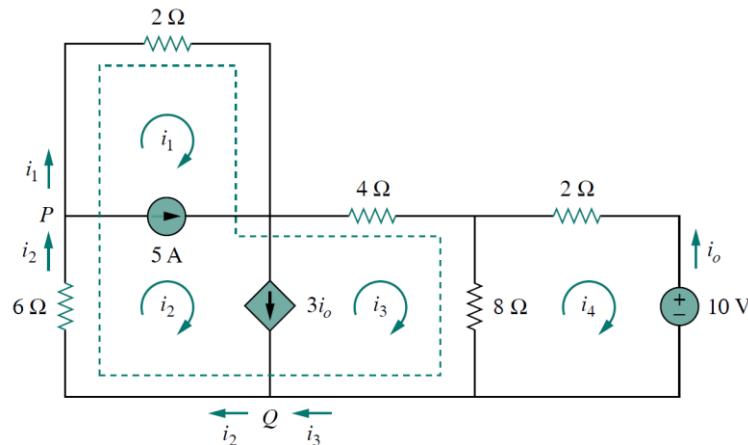For the circuit shown below a) Which analysis is preferable? b) Calculate the mesh currents by employing mesh analysis.



7-


Find  $v_x$  and  $i_x$  in the circuit shown in Fig. 3.91.

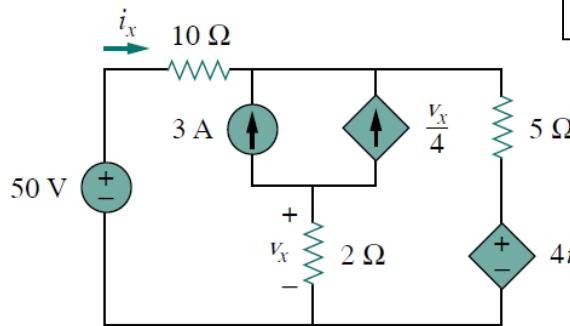

**Figure 3.91** For Prob. 3.49.

8-


Calculate the current gain  $i_o/i_s$  in the circuit of Fig. 3.89.

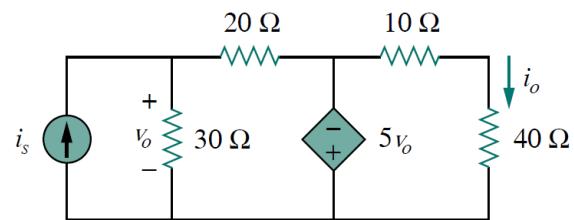

**Figure 3.89** For Prob. 3.47.

9-


Find  $i_1$ ,  $i_2$ , and  $i_3$  in the circuit in Fig. 3.87.

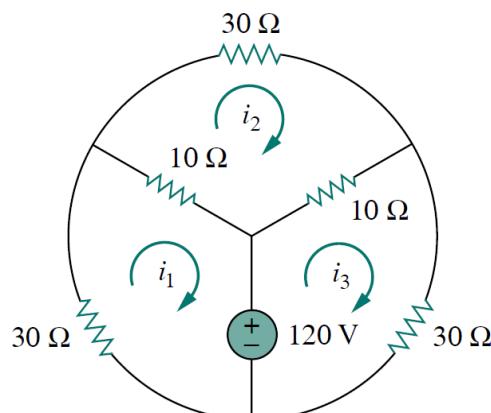

**Figure 3.87** For Prob. 3.44.

10-

Find  $v_o$  and  $i_o$  in the circuit of Fig. 3.92.

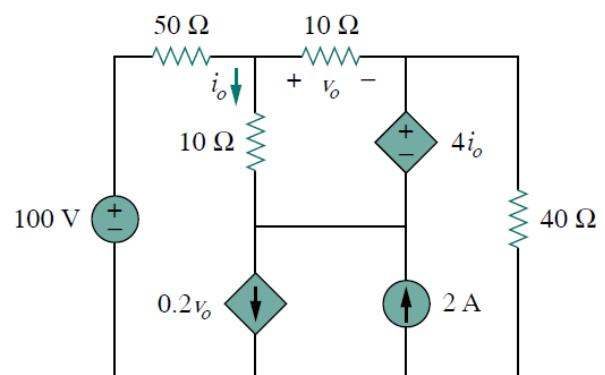

**Figure 3.92** For Prob. 3.50.