

*This page intentionally left blank*



2862458

## PASSIVE DEVICES

An important factor in the success of today's RF integrated circuits has been the ability to incorporate numerous on-chip passive devices, thus reducing the number of off-chip components. Of course, some integrated passive devices, especially in CMOS technology, exhibit a lower quality than their external counterparts. But, as seen throughout this book, we now routinely use hundreds of such devices in RF transceiver design—an impractical paradigm if they were placed off-chip.

This chapter deals with the analysis and design of integrated inductors, transformers, varactors, and constant capacitors. The outline of the chapter is shown below.

| <u>Inductors</u>         | <u>Inductor Structures</u> | <u>Transformers</u>              | <u>Varactors</u>    |
|--------------------------|----------------------------|----------------------------------|---------------------|
| ▪ Basic Structure        | ▪ Symmetric Inductors      | ▪ Structures                     | ▪ PN Junctions      |
| ▪ Inductance Equations   | ▪ Effect of Ground Shield  | ▪ Effect of Coupling Capacitance | ▪ MOS Varactors     |
| ▪ Parasitic Capacitances | ▪ Stacked Spirals          | ▪ Transformer Modeling           | ▪ Varactor Modeling |
| ▪ Loss Mechanisms        |                            |                                  |                     |
| ▪ Inductor Modeling      |                            |                                  |                     |

### 7.1 GENERAL CONSIDERATIONS

While analog integrated circuits commonly employ resistors and capacitors, RF design demands additional passive devices, e.g., inductors, transformers, transmission lines, and varactors. Why do we insist on integrating these devices on the chip? If the entire transceiver requires only one or two inductors, why not utilize bond wires or external components? Let us ponder these questions carefully.

Modern RF design needs *many* inductors. To understand this point, consider the simple common-source stage shown in Fig. 7.1(a). This topology suffers from two serious drawbacks: (a) the bandwidth at node *X* is limited to  $1/[(R_D || r_{O1})C_D]$ , and (b) the voltage headroom trades with the voltage gain,  $g_{m1}(R_D || r_{O1})$ . CMOS technology scaling tends to improve the former but at the cost of the latter. For example, in 65-nm technology with a

 


Figure 7.1 CS stage with (a) resistive, and (b) inductive loads.

 


Figure 7.2 Coupling between bond wires.

1-V supply, the circuit provides a bandwidth of several gigahertz but a voltage gain in the range of 3 to 4.

Now consider the inductively-loaded stage depicted in Fig. 7.1(b). Here,  $L_D$  resonates with  $C_D$ , allowing operation at much higher frequencies (albeit in a narrow band). Moreover, since  $L_D$  sustains little dc voltage drop, the circuit can comfortably operate with low supply voltages while providing a reasonable voltage gain (e.g., 10). Owing to these two key properties, inductors have become popular in RF transceivers. In fact, the ability to integrate inductors has encouraged RF designers to utilize them almost as extensively as other devices such as resistors and capacitors.

In addition to cost penalties, the use of off-chip devices entails other complications. First, the bond wires and package pins connecting the chip to the outside world may experience significant coupling (Fig. 7.2), creating crosstalk between different parts of the transceiver.

### Example 7.1

Identify two undesirable coupling mechanisms if the LO inductor is placed off-chip.

#### Solution:

As illustrated in Fig. 7.3, the bond wire leading to the inductor couples to the LNA input bond wire, producing LO emission and large dc offsets in the baseband. Additionally, the coupling from the PA output bond wire may result in severe LO pulling.

### Example 7.1 (Continued)

 


Figure 7.3 Hypothetical transceiver using an off-chip inductor.

Second, external connections introduce parasitics that become significant at higher frequencies. For example, a 1-nH bond wire inductance considerably alters the behavior of gigahertz circuits. Third, it is difficult to realize differential operation with external loads because of the poor control of the length of bond wires.

Despite the benefits of integrated components, a critical challenge in RF microelectronics has been how to design high-performance circuits with relatively *poor* passive devices. For example, on-chip inductors exhibit a lower quality factor than their off-chip counterparts, leading to higher “phase noise” in oscillators (Chapter 8). The RF designer must therefore seek new oscillator topologies that produce a low phase noise even with a moderate inductor  $Q$ .

**Modeling Issues** Unlike integrated resistors and parallel-plate capacitors, which can be characterized by a few simple parameters, inductors and some other structures are much more difficult to model. In fact, the required modeling effort proves a high barrier to entry into RF design: one cannot add an inductor to a circuit without an accurate model, and the model heavily depends on the geometry, the layout, and the technology’s metal layers (which is the thickest).

It is for these considerations that we devote this chapter to the analysis and design of passive devices.

## 7.2 INDUCTORS

### 7.2.1 Basic Structure

Integrated inductors are typically realized as metal spirals (Fig. 7.4). Owing to the mutual coupling between every two turns, spirals exhibit a higher inductance than a straight line having the same length. To minimize the series resistance and the parasitic capacitance, the spiral is implemented in the top metal layer (which is the thickest).

 


Figure 7.4 Simple spiral inductor.

### Example 7.2

For the three-turn spiral shown in Fig. 7.4, determine the overall inductance.

#### Solution:

We identify the three turns as  $AB$ ,  $BC$ , and  $CD$ , denoting their individual inductances by  $L_1$ ,  $L_2$ , and  $L_3$ , respectively. Also, we represent the mutual inductance between  $L_1$  and  $L_2$  by  $M_{12}$ , etc. Thus, the total inductance is given by

$$L_{tot} = L_1 + L_2 + L_3 + M_{12} + M_{13} + M_{23}. \quad (7.1)$$

Equation (7.1) suggests that the total inductance rises in proportion to the *square* of the number of turns. In fact, we prove in Problem 7.1 that the inductance expression for an  $N$ -turn structure contains  $N(N+1)/2$  terms. However, two factors limit the growth rate as a function of  $N$ : (a) due to the geometry's planar nature, the inner turns are smaller and hence exhibit lower inductances, and (b) the mutual coupling factor is only about 0.7 for adjacent turns, falling further for non-adjacent turns. For example, in Eq. (7.1),  $L_3$  is quite smaller than  $L_1$ , and  $M_{13}$  quite smaller than  $M_{12}$ . We elaborate on these points in Example 7.4.

A two-dimensional square spiral is fully specified by four quantities (Fig. 7.5): the outer dimension,  $D_{out}$ , the line width,  $W$ , the line spacing,  $S$ , and the number of turns,  $N$ .<sup>1</sup>

 


Figure 7.5 Various dimensions of a spiral inductor.

1. One may use the inner opening dimension,  $D_{in}$ , rather than  $D_{out}$  or  $N$ .

The inductance primarily depends on the number of turns and the diameter of each turn, but the line width and spacing indirectly affect these two parameters.

### Example 7.3

The line width of a spiral is doubled to reduce its resistance;  $D_{out}$ ,  $S$ , and  $N$  remain constant. How does the inductance change?

#### Solution:

As illustrated in Fig. 7.6, the doubling of the width inevitably decreases the diameter of the inner turns, thus lowering their inductance, and the larger spacing between the legs reduces their mutual coupling. We note that further increase in  $W$  may also lead to *fewer* turns, reducing the inductance.

 



Figure 7.6 Effect of doubling line width of a spiral.

Compared with transistors and resistors, inductors typically have much greater dimensions ("foot prints"), resulting in a large chip area and long interconnects traveling from one block to another. It is therefore desirable to minimize the outer dimensions of inductors. For a given inductance, this can be accomplished by (a) decreasing  $W$  [Fig. 7.7(a)], or (b) increasing  $N$  [Fig. 7.7(b)]. In the former case, the line resistance rises, degrading the inductor quality. In the latter case, the mutual coupling between the sides of the innermost turns *reduces* the inductance because opposite sides carry currents in opposite directions. As shown in Fig. 7.7(b), the two opposite legs of the innermost turn produce opposing magnetic fields, partially cancelling each other's inductance.

### Example 7.4


Figure 7.8 plots the magnetic coupling factor between two straight metal lines as a function of their normalized spacing,  $S/W$ . Obtained from electromagnetic field simulations, the plots correspond to two cases: each line is  $20\ \mu\text{m}$  or  $100\ \mu\text{m}$  long. (The line width is  $4\ \mu\text{m}$ .) What inner diameter do these plots prescribe for spiral inductors?

(Continues)

 

**Figure 7.7** Effect of (a) reducing the outer dimension and the line width, or (b) reducing the outer dimension and increasing the number of turns.

#### Example 7.4 (Continued)

 

**Figure 7.8** Coupling factor between two straight lines as a function of their normalized spacing.

#### Solution:


We wish to minimize the coupling between the opposite sides of the innermost turn. Relevant to typical inductor designs is the plot for a line length of  $20\ \mu\text{m}$ , suggesting that a diameter of 5 to 6 times  $W$  should be chosen for the inner opening to ensure negligible coupling. It is helpful to remember this rule of thumb.

Even for the basic inductor structure of Fig. 7.5, we must answer a number of questions: (1) How are the inductance, the quality factor, and the parasitic capacitance of the structure calculated? (2) What trade-offs do we face in the choice of these values? (3) What technology and inductor parameters affect the quality factor? These questions are answered in the context of inductor modeling in Section 7.2.6.

## 7.2.2 Inductor Geometries

Our qualitative study of the square spiral inductors reveals some degrees of freedom in the design, particularly the number of turns and the outer dimension. But there are many other inductor geometries that further add to the design space.

Figure 7.9 shows a collection of inductor structures encountered in RF IC design. We investigate the properties of these topologies later in this chapter, but the reader can observe at this point that: (1) the structures in Figs. 7.9(a) and (b) depart from the square shape, (2) the spiral in Fig. 7.9(c) is *symmetric*, (3) the “stacked” geometry in Fig. 7.9(d) employs two or more spirals in *series*, (4) the topology in Fig. 7.9(e) incorporates a grounded “shield” under the inductor, and (5) the structure in Fig. 7.9(f) places two or more spirals in *parallel*.<sup>2</sup> Of course, many of these concepts can be combined, e.g., the parallel topology of Fig. 7.9(f) can also utilize symmetric spirals and a grounded shield.

 

**Figure 7.9** Various inductor structures: (a) circular, (b) octagonal, (c) symmetric, (d) stacked, (e) with grounded shield, (f) parallel spirals.

Why are there so many different inductor structures? These topologies have resulted from the vast effort expended on improving the trade-offs in inductor design, specifically those between the quality factor and the capacitance or between the inductance and the dimensions.

While providing additional degrees of freedom, the abundance of the inductor geometries also complicates the modeling task, especially if laboratory *measurements* are necessary to fine-tune the theoretical models. How many types of inductors and how many different values must be studied? Which structures are more promising for a given circuit application? Facing practical time limits, designers often select only a few geometries and optimize them for their circuit and frequency of interest.

2. The spirals are shorted to one another by vias, although the vias are not necessary.

### 7.2.3 Inductance Equations

With numerous inductors used in a typical transceiver, it is desirable to have closed-form equations that provide the inductance value in terms of the spiral's geometric properties. Indeed, various inductance expressions have been reported in the literature [1–3], some based on curve fitting and some based on physical properties of inductors. For example, an empirical formula that has less than 10% error for inductors in the range of 5 to 50 nH is given in [1] and can be reduced to the following form for a square spiral:

$$L \approx 1.3 \times 10^{-7} \frac{A_m^{5/3}}{A_{tot}^{1/6} W^{1.75} (W + S)^{0.25}}, \quad (7.2)$$

where  $A_m$  is the metal area (the shaded area in Fig. 7.5) and  $A_{tot}$  is the total inductor area ( $\approx D_{out}^2$  in Fig. 7.5). All units are metric.

#### Example 7.5

Calculate the inductor metal area in terms of the other geometric properties.

#### Solution:

Consider the structure shown in Fig. 7.10. We say this spiral has three turns because each of the four sides contains three complete legs. To determine the metal area, we compute the total length,  $l_{tot}$ , of the wire and multiply it by  $W$ . The length from A to B is equal to  $D_{out}$ , from B to C, equal to  $D_{out} - W$ , etc. That is,

$$l_{AB} = D_{out} \quad (7.3)$$

$$l_{BC} = l_{CD} = D_{out} - W \quad (7.4)$$

$$l_{DE} = l_{EF} = D_{out} - (2W + S) \quad (7.5)$$

$$l_{FG} = l_{GH} = D_{out} - (3W + 2S) \quad (7.6)$$

$$l_{HI} = l_{IJ} = D_{out} - (4W + 3S) \quad (7.7)$$

$$l_{JK} = l_{KL} = D_{out} - (5W + 4S) \quad (7.8)$$

$$l_{LM} = D_{out} - (6W + 5S). \quad (7.9)$$

Adding these lengths and generalizing the result for  $N$  turns, we have

$$l_{tot} = 4ND_{out} - 2W[1 + 2 + \dots + (2N - 1)] - 2NW - 2S[1 + 2 + \dots + (2N - 2)] - (2N - 1)S \quad (7.10)$$

$$= 4ND_{out} - 4N^2W - (2N - 1)^2S. \quad (7.11)$$

Since  $l_{tot} \gg S$ , we can add one  $S$  to the right-hand side so as to simplify the expression:

$$l_{tot} \approx 4N[D_{out} - W - (N - 1)(W + S)]. \quad (7.12)$$

#### Example 7.5 (Continued)

The metal area is thus given by

$$A_m = W[4ND_{out} - 4N^2W - (2N - 1)^2S] \quad (7.13)$$

$$\approx 4NW[D_{out} - W - (N - 1)(W + S)]. \quad (7.14)$$

This equation is also used for calculating the area capacitance of the spiral.

 


Figure 7.10 Spiral inductor for calculation of line length.

An interesting property of inductors is that, for a given wire length, width, and spacing, their inductance is a weak function of the number of turns. This can be seen by finding  $D_{out}$  from (7.12), noting that  $A_{tot} \approx D_{out}^2$ , and manipulating (7.2) as follows:

$$L \approx 1.3 \times 10^{-7} \frac{l_{tot}^{5/3}}{\left[ \frac{l_{tot}}{4N} + W + (N - 1)(W + S) \right]^{1/3} W^{0.083} (W + S)^{0.25}}. \quad (7.15)$$

We observe that  $N$  appears only within the square brackets in the denominator, in two terms varying in opposite directions, with the result raised to the power of  $1/3$ . For example, if  $l_{tot} = 2000 \mu\text{m}$ ,  $W = 4 \mu\text{m}$ , and  $S = 0.5 \mu\text{m}$ , then as  $N$  varies from 2 to 3 to 4 to 5, then inductance rises from 3.96 nH to 4.47 nH to 4.83 nH to 4.96 nH, respectively. In other words, a given length of wire yields roughly a constant inductance regardless of how it is “wound.”<sup>3</sup> The key point here is that, since this length has a given series resistance (at low frequencies), the choice of  $N$  only mildly affects the  $Q$  (but can save area).

Figure 7.11 plots the inductance predicted by the simulator ASITIC (described below) as  $N$  varies from 2 to 6 and the total wire length remains at  $2000 \mu\text{m}$ .<sup>4</sup> We observe that  $L$  becomes relatively constant for  $N > 3$ . Also, the values produced by ASITIC are lower than those given by Eq. (7.15).

3. But the number of turns must be at least 2 to create mutual coupling.

4. The outer dimension varies from  $260 \mu\text{m}$  to  $110 \mu\text{m}$  in this experiment.

 


Figure 7.11 Inductance as a function of the number of turns for a given line length.

A number of other expressions have been proposed for the inductance of spirals. For example,

$$L = \frac{\mu_0 N^2 D_{avg} \alpha_1}{2} \left( \ln \frac{\alpha_2}{\rho} + \alpha_3 \rho + \alpha_4 \rho^2 \right), \quad (7.16)$$

where  $D_{avg} = (D_{out} + D_{in})/2$  in Fig. 7.5 and  $\rho$  is the “fill factor” and equal to  $(D_{out} - D_{in})/(D_{out} + D_{in})$  [3]. The  $\alpha$  coefficients are chosen as follows [3]:

$$\alpha_1 = 1.27, \alpha_2 = 2.07, \alpha_3 = 0.18, \alpha_4 = 0.13 \text{ for square shape} \quad (7.17)$$

$$\alpha_1 = 1.07, \alpha_2 = 2.29, \alpha_3 = 0, \alpha_4 = 0.19 \text{ for octagonal shape.} \quad (7.18)$$

Another empirical expression is given by [3]

$$L = 1.62 \times 10^{-3} D_{out}^{-1.21} W^{-0.147} D_{avg}^{2.4} N^{1.78} S^{-0.03} \text{ for square shape} \quad (7.19)$$

$$L = 1.33 \times 10^{-3} D_{out}^{-1.21} W^{-0.163} D_{avg}^{2.43} N^{1.75} S^{-0.049} \text{ for octagonal shape.} \quad (7.20)$$

**Accuracy Considerations** The above inductance equations yield different levels of accuracy for different geometries. For example, the measurements on tens of inductors in [3] reveal that Eqs. (7.19) and (7.20) incur an error of about 8% for 20% of the inductors and an error of about 4% for 50% of the inductors. We must then ask: how much error is tolerable in inductance calculations? As observed throughout this book and exemplified by Fig. 7.1(b), inductors must typically resonate with their surrounding capacitances at the desired frequency. Since a small error of  $\Delta L/L$  shifts the resonance frequency,  $\omega_0$ , by approximately  $\Delta L/(2L)$  (why?), we must determine the tolerable error in  $\omega_0$ .

The resonance frequency error becomes critical in amplifiers and oscillators, but much more so in the latter. This is because, as seen abundantly in Chapter 8, the design of LC oscillators faces tight trade-offs between the “tuning range” and other parameters. Since the tuning range must encompass the error in  $\omega_0$ , a large error dictates a wider tuning range, thereby degrading other aspects of the oscillator’s performance. In practice, the tuning range of high-performance LC oscillators rarely exceeds  $\pm 10\%$ , requiring that both capacitance and inductance errors be only a small fraction of this value, e.g., a few percent. Thus, the foregoing inductance expressions may not provide sufficient accuracy for oscillator design.

Another issue with respect to inductance equations stems from the geometry limitations that they impose. Among the topologies shown in Fig. 7.9, only a few lend themselves to the above formulations. For example, the subtle differences between the structures in Figs. 7.9(b) and (c) or the parallel combination of the spirals in Fig. 7.9(f) may yield several percent of error in inductance predictions.

Another difficulty is that the inductance value also depends on the frequency of operation—albeit weakly—while most equations reported in the literature predict the low-frequency value. We elaborate on this dependence in Section 7.2.6.

**Field Simulations** With the foregoing sources of error in mind, how do we compute the inductance in practice? We may begin with the above approximate equations for standard structures, but must eventually resort to electromagnetic field simulations for standard or nonstandard geometries. A field simulator employs finite-element analysis to solve the steady-state field equations and compute the electrical properties of the structure at a given frequency.

A public-domain field simulator developed for analysis of inductors and transformers is called “Analysis and Simulation of Spiral Inductors and Transformers” (ASITIC) [4]. The tool can analyze a given structure and report its equivalent circuit components. While simple and efficient, ASITIC also appears to exhibit inaccuracies similar to those of the above equations [3, 5].<sup>5</sup>

Following rough estimates provided by formulas and/or ASITIC, we must analyze the structure in a more versatile field simulator. Examples include Agilent’s “ADS,” Sonnet Software’s “Sonnet,” and Ansoft’s “HFSS.” Interestingly, these tools yield slightly different values, partly due to the types of approximations that they make. For example, some do not accurately account for the thickness of the metal layers. Owing to these discrepancies, RF circuits sometimes do not exactly hit the targeted frequencies after the first fabrication, requiring slight adjustments and “silicon iterations.” As a remedy, we can limit our usage to a library of inductors that have been measured and modeled carefully but at the cost of flexibility in design and layout.

## 7.2.4 Parasitic Capacitances

As a planar structure built upon a substrate, spiral inductors suffer from parasitic capacitances. We identify two types. (1) The metal line forming the inductor exhibits parallel-plate and fringe capacitances to the substrate [Fig. 7.12(a)]. If a wider line is chosen to reduce its resistance, then the parallel-plate component increases. (2) The adjacent turns also bear a fringe capacitance, which equivalently appears *in parallel* with each segment [Fig. 7.12(b)].

Let us first examine the effect of the capacitance to the substrate. Since in most circuits, one terminal of the inductor is at ac ground, we construct the uniformly-distributed equivalent circuit shown in Fig. 7.13, where each segment has an inductance of  $L_u$ . Our objective is to obtain a *lumped* model for this network. To simplify the analysis, we make two assumptions: (1) each two inductor segments have a mutual coupling of  $M$ , and (2)

5. In fact, Eqs. (7.19) and (7.20) have been developed based on ASITIC simulations.

 


Figure 7.12 (a) Bottom-plate and (b) interwinding capacitances of an inductor and their models.

 


Figure 7.13 Model of an inductor's distributed capacitance to ground.

the coupling is strong enough that  $M$  can be assumed approximately equal to  $L_u$ . While not quite valid, these assumptions lead to a relatively accurate result.

The voltage across each inductor segment arises from the current flowing through that segment and the currents flowing through the other segments. That is,

$$V_n = j\omega L_n I_n + \sum_{m=1}^{n-1} j\omega I_m M + \sum_{m=n+1}^K j\omega I_m M. \quad (7.21)$$

If  $M \approx L_u$ , then

$$V_n = j\omega \sum_{m=1}^K I_m L_m. \quad (7.22)$$

Since this summation is independent of  $n$ , we note that all inductor segments sustain equal voltages [6]. The voltage at node  $n$  is therefore given by  $(n/K)V_1$ , yielding an electric energy stored in the corresponding node capacitance equal to

$$E_u = \frac{1}{2} C_u \left(\frac{n}{K}\right)^2 V_1^2. \quad (7.23)$$

Summing the energies stored on all of the unit capacitances, we have

$$E_{tot} = \frac{1}{2} C_u \sum_{n=1}^K \left(\frac{n}{K}\right)^2 V_1^2 \quad (7.24)$$

$$= \frac{1}{2} C_u \frac{(K+1)(2K+1)}{6K} V_1^2. \quad (7.25)$$

If  $K \rightarrow \infty$  and  $C_u \rightarrow 0$  such that  $K C_u$  is equal to the total wire capacitance,  $C_{tot}$ , then [6]

$$E_{tot} = \frac{1}{2} \frac{C_{tot}}{3} V_1^2, \quad (7.26)$$

revealing that the equivalent lumped capacitance of the spiral is given by  $C_{tot}/3$  (if one end is grounded).

Let us now study the turn-to-turn (interwinding) capacitance. Using the model shown in Fig. 7.14, where  $C_1 = C_2 = \dots = C_K = C_F$ , we recognize that Eq. (7.22) still applies for it is independent of capacitances. Thus, each capacitor sustains a voltage equal to  $V_1/K$ , storing an electric energy of

$$E_u = \frac{1}{2} C_F \left(\frac{1}{K} V_1\right)^2. \quad (7.27)$$

The total stored energy is given by

$$E_{tot} = K E_u \quad (7.28)$$

$$= \frac{1}{2K} C_F V_1^2. \quad (7.29)$$

Interestingly,  $E_{tot}$  falls to zero as  $K \rightarrow \infty$  and  $C_F \rightarrow 0$ . This is because, for a large number of turns, the potential difference between adjacent turns becomes very small, yielding a small electric energy stored on the  $C_F$ 's.

 


Figure 7.14 Model of an inductor's turn-to-turn capacitances.

In practice, we can utilize Eq. (7.29) to estimate the equivalent lumped capacitance for a finite number of turns. The following example illustrates this point.

### Example 7.6

Estimate the equivalent turn-to-turn capacitance of the three-turn spiral shown in Fig. 7.15(a).

#### Solution:

An accurate calculation would “unwind” the structure, modeling each leg of each turn by an inductance and placing the capacitances between adjacent legs [Fig. 7.15(b)]. Unfortunately, owing to the unequal lengths of the legs, this model entails unequal inductances and capacitances, making the analysis difficult. To arrive at a *uniformly-distributed* model, we select the value of  $C_j$  equal to the average of  $C_1, \dots, C_8$ , and  $L_j$  equal to the total inductance

(Continues)

### Example 7.6 (Continued)

divided by 12. Thus, Eq. (7.29) applies and


$$C_{eq} = \frac{1}{K} C_F \quad (7.30)$$

$$= \frac{1}{8} \frac{C_1 + \dots + C_8}{8} \quad (7.31)$$


$$= \frac{C_1 + \dots + C_8}{64}. \quad (7.32)$$

In general, for an  $N$ -turn spiral,
 
$$C_{eq} = \frac{C_1 + \dots + C_{N^2-1}}{(N^2 - 1)^2}. \quad (7.33)$$



(a)

 

(b)

**Figure 7.15** (a) Spiral inductor for calculation of turn-to-turn capacitances, (b) circuit model.

The frequency at which an inductor resonates with its own capacitances is called the “self-resonance frequency” ( $f_{SR}$ ). In essence, the inductor behaves as a capacitor at frequencies above  $f_{SR}$ . For this reason,  $f_{SR}$  serves as a measure of the maximum frequency at which a given inductor can be used.


### Example 7.7

In analogy with  $Q = L\omega/R_S$  for an inductor  $L$  having a series resistance  $R_S$ , the  $Q$  of an impedance  $Z_1$  is sometimes defined as

$$Q = \frac{\text{Im}\{Z_1\}}{\text{Re}\{Z_1\}}. \quad (7.34)$$

### Example 7.7 (Continued)

Compute this  $Q$  for the parallel inductor model shown in Fig. 7.16(a).

 

**Figure 7.16** (a) Simple tank and (b) behavior of one definition of  $Q$ .

### Solution:

We have

$$Z_1(s) = \frac{R_p L_1 s}{R_p L_1 C_1 s^2 + L_1 s + R_p}. \quad (7.35)$$

At  $s = j\omega$ ,

$$Z_1(j\omega) = \frac{[R_p(1 - L_1 C_1 \omega^2) - jL_1 \omega] j R_p L_1 \omega}{R_p^2 (1 - L_1 C_1 \omega^2)^2 + L_1^2 \omega^2}. \quad (7.36)$$

It follows that

$$Q = \frac{R_p(1 - L_1 C_1 \omega^2)}{L_1 \omega} \quad (7.37)$$

$$= \frac{R_p}{L_1 \omega} \left( 1 - \frac{\omega^2}{\omega_{SR}^2} \right), \quad (7.38)$$

where  $\omega_{SR} = 2\pi f_{SR} = 1/\sqrt{L_1 C_1}$ . At frequencies well below  $\omega_{SR}$ , we have  $Q \approx R_p/(L_1 \omega)$ , which agrees with our definition in Chapter 2. On the other hand, as the frequency approaches  $f_{SR}$ ,  $Q$  falls to zero [Fig. 7.16(b)]—as if the tank were useless! This definition implies that a general impedance (including additional capacitances due to transistors, etc.) exhibits a  $Q$  of zero at resonance. Of course, the tank of Fig. 7.16(a) simply reduces to resistor  $R_p$  at  $f_{SR}$ , providing a  $Q$  of  $R_p/(L_1 \omega_{SR})$  rather than zero. Owing to its meaningless behavior around resonance, the  $Q$  definition given by Eq. (7.34) proves irrelevant to circuit design. We return to this point in Section 7.2.6.

### Example 7.8

In analogy with  $L_1 = \text{impedance}/\omega = (L_1 \omega)/\omega$ , the equivalent inductance of a structure is sometimes defined as  $\text{Im}\{Z_1(j\omega)\}/\omega$ . Study this inductance definition for the parallel tank of Fig. 7.16(a) as a function of frequency.

(Continues)

### Example 7.8 (Continued)

#### Solution:

From Eq. (7.36), we have

$$\frac{\text{Im}\{Z_1(j\omega)\}}{\omega} = \frac{R_p^2 L_1 (1 - L_1 C_1 \omega^2)}{R_p^2 (1 - L_1 C_1 \omega^2)^2 + L_1^2 \omega^2} \quad (7.39)$$

This expression simplifies to  $L_1$  at frequencies well below  $f_{SR}$  but falls to *zero* at resonance! The actual inductance, however, varies only slightly with frequency. This definition of inductance is therefore meaningless. Nonetheless, its value at low frequencies proves helpful in estimating the inductance.

### 7.2.5 Loss Mechanisms

The quality factor,  $Q$ , of inductors plays a critical role in various RF circuits. For example, the phase noise of oscillators is proportional to  $1/Q^2$  (Chapter 8), and the voltage gain of “tuned amplifiers” [e.g., the CS stage in Fig. 7.1(b)] is proportional to  $Q$ . In typical CMOS technologies and for frequencies up to 5 GHz, a  $Q$  of 5 is considered moderate and a  $Q$  of 10, relatively high.

We define the  $Q$  carefully in Section 7.2.6, but for now we consider  $Q$  as a measure of how much energy is *lost* in an inductor when it carries a sinusoidal current. Since only *resistive* components dissipate energy, the loss mechanisms of inductors relate to various resistances within or around the structure that carry current when the inductor does.

In this section, we study these loss mechanisms. As we will see, it is difficult to formulate the losses analytically; we must therefore resort to simulations and even measurements to construct accurate inductor models. Nonetheless, our understanding of the loss mechanisms helps us develop guidelines for inductor modeling and design.

**Metal Resistance** Suppose the metal line forming an inductor exhibits a series resistance,  $R_S$  (Fig. 7.17). The  $Q$  may be defined as the ratio of the desirable impedance,  $L_1 \omega_0$ , and the undesirable impedance,  $R_S$ :

$$Q = \frac{L_1 \omega_0}{R_S} \quad (7.40)$$

For example, a 5-nH inductor operating at 5 GHz with an  $R_S$  of 15.7  $\Omega$  has a  $Q$  of 10.

 


Figure 7.17 Metal resistance in a spiral inductor.

### Example 7.9

Assuming a sheet resistance of 22 m $\Omega/\square$  for the metal,  $W = 4 \mu\text{m}$ , and  $S = 0.5 \mu\text{m}$ , determine if the above set of values is feasible.

#### Solution:

Recall from our estimates in Section 7.2.3, a 2000- $\mu\text{m}$  long, 4- $\mu\text{m}$  wide wire that is wound into  $N = 5$  turns with  $S = 0.5 \mu\text{m}$  provides an inductance of about 4.96 nH. Such a wire consists of  $2000/4 = 500$  squares and hence has a resistance of  $500 \times 22 \text{ m}\Omega/\square = 11 \Omega$ . It thus appears that a  $Q$  of 10 at 5 GHz is feasible.

Unfortunately, the above example portrays an optimistic picture: the  $Q$  is limited not only by the (low-frequency) series resistance but also by several other mechanisms. That is, the overall  $Q$  may fall quite short of 10. As a rule of thumb, we strive to design inductors such that the low-frequency metal resistance yields a  $Q$  about *twice* the desired value, anticipating that other mechanisms drop the  $Q$  by a factor of 2.

How do we reduce the metal dc resistance for a given inductance? As explained in Section 7.2.3, the total length of the metal wire and the inductance are inextricably related, i.e., for a given  $W$ ,  $S$ , and wire length, the inductance is a weak function of  $N$ . Thus, with  $W$  and  $S$  known, a desired inductance value translates to a certain length and hence a certain dc resistance almost regardless of the choice of  $N$ . Figure 7.18 plots the wire resistance of a 5-nH inductor with  $N = 2$  to 6,  $W = 4 \mu\text{m}$ , and  $S = 0.5 \mu\text{m}$ . In a manner similar to the flattening effect in Fig. 7.11,  $R_S$  falls to a relatively constant value for  $N > 3$ .


 


Figure 7.18 Metal resistance of an inductor as a function of number of turns.

From the above discussions, we conclude that the only parameter among  $D_{out}$ ,  $S$ ,  $N$ , and  $W$  that significantly affects the resistance is  $W$ . Of course, a wider metal line exhibits less resistance but a larger capacitance to the substrate. Spiral inductors therefore suffer from a trade-off between their  $Q$  and their parasitic capacitance. The circuit design limitations imposed by this capacitance are examined in Chapters 5 and 8.

As explained in Example 7.3, a wider metal line yields a *smaller* inductance value if  $S$ ,  $D_{out}$ , and  $N$  remain constant. In other words, to retain the same inductance while  $W$  increases, we must inevitably increase  $D_{out}$  (or  $N$ ), thereby increasing the length and counteracting the resistance reduction afforded by a wider line. To illustrate this effect, we can design spirals having a given inductance but different line widths and examine the

 

**Figure 7.19** Metal resistance of an inductor as a function of line width for different number of turns.

resistance. Figure 7.19 plots  $R_S$  as a function of  $W$  for an inductance of 2 nH and with four or five turns. We observe that  $R_S$  falls considerably as  $W$  goes from 3  $\mu\text{m}$  to about 5  $\mu\text{m}$  but begins to flatten thereafter. In other words, choosing  $W > 5 \mu\text{m}$  in this example negligibly reduces the resistance but increases the parasitic capacitance proportionally.

In summary, for a given inductance value, the choice of  $N$  has little effect on  $R_S$ , and a larger  $W$  reduces  $R_S$  to some extent but at the cost of higher capacitance. These limitations manifest themselves particularly at lower frequencies, as shown by the following example.

### Example 7.10

We wish to design a spiral inductor for a 900-MHz GSM system. Is the 5-nH structure considered in Example 7.9 suited to this application? What other choices do we have?

#### Solution:

Since  $Q = L_1\omega_0/R_S$ , if the frequency falls from 5 GHz to 900 MHz, the  $Q$  declines from 10 to 1.8.<sup>6</sup> Thus, a value of 5 nH is inadequate for usage at 900 MHz.

Let us attempt to raise the inductance, hoping that, in  $Q = L_1\omega_0/R_S$ ,  $L_1$  can increase at a higher rate than can  $R_S$ . Indeed, we observe from Eq. (7.15) that  $L_1 \propto l_{tot}^{5/3}$ , whereas  $R_S \propto l_{tot}$ . For example, if  $l_{tot} = 8 \text{ mm}$ ,  $N = 10$ ,  $W = 6 \mu\text{m}$ , and  $S = 0.5 \mu\text{m}$ , then Eq. (7.15) yields  $L \approx 35 \text{ nH}$ . For a sheet resistance of  $22 \text{ m}\Omega/\square$ ,  $R_S = (8000 \mu\text{m}/6 \mu\text{m}) \times 22 \text{ m}\Omega/\square = 29.3 \Omega$ . Thus, the  $Q$  (due to the dc resistance) reaches 6.75 at 900 MHz. Note, however, that this structure occupies a large area. The reader can readily show that the outer dimension of this spiral is approximately equal to 265  $\mu\text{m}$ .

Another approach to reducing the wire resistance is to place two or more metal layers in parallel, as suggested by Fig. 7.9(f). For example, adding a metal-7 and a metal-8 spiral to a metal-9 structure lowers the resistance by about a factor of 2 because metals 7 and 8 are

6. Note that the actual  $Q$  may be even lower due to other losses.


typically half as thick as metal 9. However, the closer proximity of metal 7 to the substrate slightly raises the parasitic capacitance.

### Example 7.11

A student reasons that placing  $m$  spiral inductors in parallel may in fact *degrade* the  $Q$  because it leads to an  $m$ -fold decrease in the inductance but not an  $m$ -fold decrease in resistance. Explain the flaw in the student's argument.

#### Solution:

Since the vertical spacing between the spirals is much less than their lateral dimensions, each two experience a strong mutual coupling (Fig. 7.20). If  $L_1 = L_2 = L_3 = L$  and  $M \approx L$ , then the overall inductance remains equal to  $L$  (why?).

 

**Figure 7.20** Effect of placing tightly-coupled inductors in parallel.

Which approach provides a more favorable resistance-capacitance trade-off: widening the metal line of a single layer or placing multiple layers in parallel? We surmise the latter; after all, if  $W$  is doubled, the capacitance of a single spiral increases by at least a factor of 2, but if metal-7 and metal-8 structures are placed in parallel with a metal-9 spiral, the capacitance may rise by only 50%. For example, the metal-9-substrate and metal-7-substrate capacitances are around 4  $\text{af}/\mu\text{m}^2$  and 6  $\text{af}/\mu\text{m}^2$ , respectively. The following example demonstrates this point.

### Example 7.12

Design the inductor of Example 7.10 with  $W = 3 \mu\text{m}$ ,  $S = 0.5 \mu\text{m}$ , and  $N = 10$ , using metals 7, 8, and 9 in parallel.

#### Solution:

Since  $W$  is reduced from 6  $\mu\text{m}$  to 3  $\mu\text{m}$ , the term  $(W + S)^{0.25}$  in the denominator of Eq. (7.15) falls by a factor of 1.17, requiring a similar drop in  $l_{tot}^{5/3}$  in the numerator so as to obtain  $L \approx 35 \text{ nH}$ . Iteration yields  $l_{tot} \approx 6800 \mu\text{m}$ . The length and the outer dimension are smaller because the narrower metal line allows a tighter compaction of the turns. With three metal layers in parallel, we assume a sheet resistance of approximately  $11 \text{ m}\Omega/\square$ , obtaining  $R_S = 25 \Omega$  and hence a  $Q$  of 7.9 (due to the dc resistance). The parallel combination therefore yields a higher  $Q$ .

(Continues)

### Example 7.12 (Continued)

It is instructive to compare the capacitances of the metal-9 spiral in Example 7.10 and the above multi-layer structure. For the former, the total metal area is  $I_{tot} \cdot W = 48,000 \mu\text{m}^2$ , yielding a capacitance of  $(4 \text{ af}/\mu\text{m}^2) \times 48,000 \mu\text{m}^2 = 192 \text{ fF}$ .<sup>7</sup> For the latter, the area is equal to  $20,400 \mu\text{m}^2$  and the capacitance is  $122.4 \text{ fF}$ .

**Skin Effect** At high frequencies, the current through a conductor prefers to flow at the surface. If the overall current is viewed as many parallel current components, these components tend to repel each other, migrating away so as to create maximum distance between them. This trend is illustrated in Fig. 7.21. Flowing through a smaller cross section area, the high-frequency current thus faces a greater resistance. The actual distribution of the current follows an exponential decay from the surface of the conductor inward,  $J(x) = J_0 \exp(-x/\delta)$ , where  $J_0$  denotes the current density (in  $\text{A}/\text{m}^2$ ) at the surface, and  $\delta$  is the “skin depth.” The value of  $\delta$  is given by

$$\delta = \frac{1}{\sqrt{\pi f \mu \sigma}}, \quad (7.41)$$

where  $f$  denotes the frequency,  $\mu$  the permeability, and  $\sigma$  the conductivity. For example,  $\delta \approx 1.4 \mu\text{m}$  at  $10 \text{ GHz}$  for aluminum. The extra resistance of a conductor due to the skin effect is equal to

$$R_{skin} = \frac{1}{\sigma \delta}. \quad (7.42)$$

Parallel spirals can reduce this resistance if the skin depth exceeds the *sum* of the metal wire thicknesses.

 


Figure 7.21 Current distribution in a conductor at (a) low and (b) high frequencies.

In spiral inductors, the proximity of adjacent turns results in a complex current distribution. As illustrated in Fig. 7.22(a), the current may concentrate near the edge of the wire. To understand this “current crowding” effect, consider the more detailed diagram shown in Fig. 7.22(b), where each turn carries a current of  $I(t)$  [7, 8]. The current in one turn creates a time-varying magnetic field,  $B$ , that penetrates the other turns, generating loops of current.<sup>8</sup> Called “eddy currents,” these components *add* to  $I(t)$  at one edge of the wire and

7. The equivalent (lumped) capacitance of the inductor is less than this value (Section 7.2.4).

8. Faraday’s law states that the voltage induced in a conducting circuit is proportional to the time derivative of the magnetic field.

 


Figure 7.22 (a) Current distribution in adjacent turns, (b) detailed view of (a).

subtract from  $I(t)$  at the other edge. Since the induced voltage increases with frequency, the eddy currents and hence the nonuniform distribution become more prominent at higher frequencies.

Based on these observations, [7, 8] derive the following expression for the resistance of a spiral inductor:

$$R_{eff} \approx R_0 \left[ 1 + \frac{1}{10} \left( \frac{f}{f_{crit}} \right)^2 \right], \quad (7.43)$$

where  $R_0$  is the dc resistance and the frequency  $f_{crit}$  denotes the onset of current crowding and is given by

$$f_{crit} \approx \frac{3.1}{2\pi\mu} \frac{W + S}{W^2} R_{\square}. \quad (7.44)$$

In this equation,  $R_{\square}$  represents the dc sheet resistance of the metal.

### Example 7.13

Calculate the series resistance of the 30-nH inductors studied in Examples 7.9 and 7.12 at 900 MHz. Assume  $\mu = 4\pi \times 10^{-7} \text{ H/m}$ .

#### Solution:

For the single-layer spiral,  $R_{\square} = 22 \text{ m}\Omega/\square$ ,  $W = 6 \mu\text{m}$ ,  $S = 0.5 \mu\text{m}$ , and hence  $f_{crit} = 1.56 \text{ GHz}$ . Thus,  $R_{eff} = 1.03R_0 = 30.3 \Omega$ . For the multilayer spiral,  $R_{\square} = 11 \text{ m}\Omega/\square$ ,  $W = 3 \mu\text{m}$ ,  $S = 0.5 \mu\text{m}$ , and hence  $f_{crit} = 1.68 \text{ GHz}$ . We therefore have  $R_{eff} = 1.03R_0 = 26 \Omega$ .

Current crowding also alters the inductance and capacitance of spiral geometries. Since the current is pushed to the edge of the wire, the equivalent diameter of each turn changes slightly, yielding an inductance different from the low-frequency value. Similarly, as illustrated in Fig. 7.23(a), if a conductor carries currents only near the edges, then its middle section can be “carved out” without altering the currents and voltages, suggesting that the capacitance of this section,  $C_m$ , is immaterial. From another perspective,  $C_m$  manifests itself only if it carries displacement current, which is not possible if the middle section has no current. Based on this observation, [7, 8] approximate the total capacitance,  $C_{tot}$ , to vary

 


Figure 7.23 Reduction of capacitance to the substrate as a result of current crowding.

inversely proportional to the wire resistance:

$$C_{tot} \approx \frac{R_0}{R_{eff}} C_0, \quad (7.45)$$

where  $C_0$  denotes the low-frequency capacitance.

**Capacitive Coupling to Substrate** We have seen in our studies that spirals exhibit capacitance to the substrate. As the voltage at each point on the spiral rises and falls with time, it creates a displacement current that flows through this capacitance and the substrate (Fig. 7.24). Since the substrate resistivity is neither zero nor infinity, this flow of current translates to loss in each cycle of the operation, lowering the  $Q$ .

 


Figure 7.24 Substrate loss due to capacitive coupling.

### Example 7.14

Use a distributed model of a spiral inductor to estimate the power lost in the substrate.

#### Solution:

We model the structure by  $K$  sections as shown in Fig. 7.25(a). Here, each section consists of an inductance equal to  $L_{tot}/K$ , a capacitance equal to  $C_{tot}/K$ , and a substrate resistance equal to  $KR_{sub}$ . (The other loss mechanisms are ignored here.) The factor of  $K$  in  $KR_{sub}$  is justified as follows: as we increase  $K$  for a given inductor geometry (i.e., as the distributed model approaches the actual structure), each section represents a smaller segment of the spiral and hence a smaller cross section area looking into the substrate [Fig. 7.25(b)]. Consequently, the equivalent resistance increases proportionally.

### Example 7.14 (Continued)

 


Figure 7.25 (a) Distributed model of capacitive coupling to the substrate, (b) diagram showing an infinitesimal section.

If we assume perfect coupling between every two inductor segments, then the voltage drop across each segment is given by Eq. (7.22):

$$V_u = \sum_{m=1}^K j\omega I_m L_m, \quad (7.46)$$

where  $I_m$  denotes the current flowing through segment  $L_m$ . Interestingly, due to the uniformly-distributed approximation, all segments sustain equal voltages regardless of the capacitance and resistance distribution. Thus, the voltage at node number  $n$  is given by  $(n/K)V_1$  and the current flowing through the corresponding RC branch by

$$I_{u,n} = \frac{n}{K} \frac{V_1}{KR_{sub} + \left(j\frac{C_{tot}}{K}\omega\right)^{-1}}. \quad (7.47)$$

Since the average power dissipated in the resistor  $KR_{sub}$  is equal to  $|I_{u,n}|^2 R_{sub}$ , the total lost power in the spiral is obtained as

$$P_{tot} = \sum_{n=1}^K |I_{u,n}|^2 KR_{sub} \quad (7.48)$$

$$= \sum_{n=1}^K \frac{V_1^2 KR_{sub}}{K^2 R_{sub}^2 + \left(\frac{C_{tot}}{K}\omega\right)^{-2} K^2} \frac{n^2}{K^2} \quad (7.49)$$


$$= \frac{V_1^2 KR_{sub}}{K^2 R_{sub}^2 + \left(\frac{C_{tot}}{K}\omega\right)^{-2}} \frac{K(K+1)(2K+1)}{6K^2}. \quad (7.50)$$

Letting  $K$  go to infinity, we have

$$P_{tot} = \frac{V_1^2}{R_{sub}^2 + (C_{tot}^2 \omega^2)^{-1}} \frac{R_{sub}}{3}. \quad (7.51)$$

For example, if  $R_{sub}^2 \ll (C_{tot}^2 \omega^2)^{-1}$ , then  $P_{tot} \approx V_1^2 R_{sub} C_{tot}^2 \omega^2 / 3$ . Conversely, if  $R_{sub}^2 \gg (C_{tot}^2 \omega^2)^{-1}$ , then  $P_{tot} \approx V_1^2 / (3R_{sub})$ .

The foregoing example provides insight into the power loss due to capacitive coupling to the substrate. The distributed model of the substrate, however, is not accurate. As depicted in Fig. 7.26(a), since the connection of the substrate to ground is physically far, some of the displacement current flows *laterally* in the substrate. Lateral substrate currents are more pronounced between adjacent turns [Fig. 7.26(b)] because their voltage difference,  $V_1 - V_2$ , is larger than the incremental drops in Fig. 7.26(a),  $V_{n+1} - V_n$ . The key point here is that the inductor-substrate interaction can be quantified accurately only if a three-dimensional model is used, but a rare case in practice.

 


**Figure 7.26** Lateral current flow in the substrate (a) under a branch, and (b) from one branch to another.


**Magnetic Coupling to the Substrate** The magnetic coupling from an inductor to the substrate can be understood with the aid of basic electromagnetic laws: (1) Ampere's law states that a current flowing through a conductor generates a magnetic field around the conductor; (2) Faraday's law states that a time-varying magnetic field induces a voltage, and hence a current if the voltage appears across a conducting material; (3) Lenz's law states that the current induced by a magnetic field generates another magnetic field opposing the first field.

Ampere's and Faraday's laws readily reveal that, as the current through an inductor varies with time, it creates an eddy current in the substrate (Fig. 7.27). Lenz's law implies that the current flows in the opposite direction. Of course, if the substrate resistance were infinity, no current would flow and no loss would occur.

The induction of eddy currents in the substrate can also be viewed as transformer coupling. As illustrated in Fig. 7.28(a), the inductor and the substrate act as the primary and

 

**Figure 7.27** Magnetic coupling to the substrate.

 

**Figure 7.28** (a) Modeling of magnetic coupling by transformers, (b) lumped model of (a).

the secondary, respectively. Figure 7.28(b) depicts a lumped model of the overall system, with  $L_1$  representing the spiral,  $M$  the magnetic coupling, and  $L_2$  and  $R_{sub}$  the substrate. It follows that

$$V_{in} = L_1 s I_{in} + M s I_2 \quad (7.52)$$

$$-R_{sub} I_2 = I_2 L_2 s + M s I_{in}. \quad (7.53)$$

Thus,

$$\frac{V_{in}}{I_{in}} = L_1 s - \frac{M^2 s^2}{R_{sub} + L_2 s}. \quad (7.54)$$


For  $s = j\omega$ ,

$$\frac{V_{in}}{I_{in}} = \frac{M^2 \omega^2 R_{sub}}{R_{sub}^2 + L_2^2 \omega^2} + \left( L_1 - \frac{M^2 \omega^2 L_2}{R_{sub}^2 + L_2^2 \omega^2} \right) j\omega, \quad (7.55)$$

implying that  $R_{sub}$  is transformed by a factor of  $M^2 \omega^2 / (R_{sub}^2 + L_2^2 \omega^2)$  and the inductance is *reduced* by an amount equal to  $M^2 \omega^2 L_2 / (R_{sub}^2 + L_2^2 \omega^2)$ .

### Example 7.15

A student concludes that both the electric coupling and the magnetic coupling to the substrate are eliminated if a grounded conductive plate is placed under the spiral (Fig. 7.29). Explain the pros and cons of this approach.

 

**Figure 7.29** Inductor with a continuous shield.

(Continues)

## Example 7.15 (Continued)

## Solution:

This method indeed reduces the path resistance seen by both displacement and eddy currents. Unfortunately, however, Eq. (7.55) reveals that the equivalent inductance also falls with  $R_{sub}$ . For  $R_{sub} = 0$ ,

$$L_{eq} = L_1 - \frac{M^2}{L_2}. \quad (7.56)$$

Since the vertical spacing between the spiral and the conductive plate ( $\approx 5 \mu\text{m}$ ) is much smaller than their lateral dimensions, we have  $M \approx L_2 \approx L_1$ , obtaining a very small value for  $L_{eq}$ . In other words, even though the substrate losses are reduced, the drastic fall in the equivalent inductance still yields a low  $Q$  because of the spiral's resistance.

It is instructive to consider a few special cases of Eq. (7.54). If  $L_1 = L_2 = M$ , then

$$\frac{V_{in}}{I_{in}} = L_1 s \parallel R_{sub}, \quad (7.57)$$

indicating that  $R_{sub}$  simply appears in parallel with  $L_1$ , lowering the  $Q$ .

## Example 7.16

Sketch the  $Q$  of a given inductor as a function of frequency.

## Solution:

At low frequencies, the  $Q$  is given by the dc resistance of the spiral,  $R_S$ . As the frequency increases,  $Q = L_1\omega/R_S$  rises linearly up to a point where skin effect becomes significant [Fig. 7.30(a)]. The  $Q$  then increases in proportion to  $\sqrt{f}$ . At higher frequencies,  $L_1\omega \gg R_S$ , and Eq. (7.57) reveals that  $R_{sub}$  shunts the inductor, limiting the  $Q$  to

$$Q \approx \frac{R_{sub}}{L_1\omega}, \quad (7.58)$$

which falls with frequency. Figure 7.30(b) sketches the behavior.

 


Figure 7.30 (a) Inductor model reflecting loss at different frequencies, (b) corresponding  $Q$  behavior.

As another special case, suppose  $R_{sub} \ll |L_2 s|$ . We can then factor  $L_2 s$  out in Eq. (7.54) and approximate the result as

$$\frac{V_{in}}{I_{in}} = \left( L_1 - \frac{M^2}{L_2} \right) s + \frac{M^2}{L_2^2} R_{sub}. \quad (7.59)$$

Thus, as predicted in Example 7.15, the inductance is reduced by an amount equal to  $M^2/L_2$ . Moreover, the substrate resistance is transformed by a factor of  $M^2/L_2^2$  and appears in series with the net inductance.

## 7.2.6 Inductor Modeling

Our study of various effects in spiral inductors has prepared us for developing a circuit model that can be used in simulations. Ideally, we wish to obtain a model that retains our physical insights and is both simple and accurate. In practice, some compromise must be made.

It is important to note that (1) both the spiral and the substrate act as three-dimensional distributed structures and can only be approximated by a two-dimensional lumped model; (2) due to skin effect, current-crowding effects, and eddy currents, some of the inductor parameters vary with frequency, making it difficult to fit the model in a broad bandwidth.

## Example 7.17

If RF design mostly deals with narrowband systems, why is a broadband model necessary?

## Solution:

From a practical point of view, it is desirable to develop a broadband model for a given inductor structure so that it can be used by multiple designers and at different frequencies without repeating the modeling effort each time. Moreover, RF systems such as ultra-wideband (UWB) and cognitive radios do operate across a wide bandwidth, requiring broadband models.

Let us begin with a model representing metal losses. As shown in Fig. 7.31(a), a series resistance can embody both low-frequency and skin resistance. With a constant  $R_S$ , the model is valid for a limited frequency range. As explained in Chapter 2, the loss can alternatively be modeled by a parallel resistance [Fig. 7.31(b)] but still for a narrow range if  $R_p$  is constant.

 


Figure 7.31 Modeling loss by (a) series or (b) parallel resistors.

An interesting observation allows us to combine the models of Figs. 7.31(a) and (b), thus broadening the valid bandwidth. The following example serves as the starting point.

### Example 7.18

If the inductance and resistance values in Fig. 7.31 are independent of frequency, how do the two models predict the behavior of the  $Q$ ?

#### Solution:

In Fig. 7.31(a),  $Q = L_1\omega/R_S$ , whereas in Fig. 7.31(b),  $Q = R_p/(L_1\omega)$ ; i.e., the two models predict opposite trends with frequency. (We also encountered this effect in Example 7.16.)

The above observation suggests that we can tailor the frequency dependence of the  $Q$  by merging the two models. Depicted in Fig. 7.32(a), such a model partitions the loss between a series resistance and a parallel resistance. A simple approach assigns half of the loss to each at the center frequency of the band:

$$R'_S = \frac{L_1\omega}{2Q} \quad (7.60)$$

$$R'_p = 2QL_1\omega. \quad (7.61)$$

In Problem 7.2, we prove that the overall  $Q$  of the circuit, defined as  $Im\{Z_1\}/Re\{Z_1\}$ , is equal to

$$Q = \frac{L_1\omega R'_p}{L_1^2\omega^2 + R'_S(R'_S + R'_p)}. \quad (7.62)$$

Note that this definition of  $Q$  is meaningful here because the circuit does not resonate at any frequency. As shown in Fig. 7.32(b), the  $Q$  reaches a peak of  $2\sqrt{R'_p/R'_S}$  at  $\omega_0 = \sqrt{R'_S R'_p}/L_1$ . The choice of  $R'_S$  and  $R'_p$  can therefore yield an accurate variation for a certain frequency range.

 


Figure 7.32 (a) Modeling loss by both series and parallel resistors, (b) resulting  $Q$  behavior.

 


Figure 7.33 (a) Broadband model of inductor, (b) view of a conductor as concentric cylinders, (c) broadband skin effect model.

A more general model of skin effect has been proposed by [9] and is illustrated in Fig. 7.33. Suppose a model must be valid only at dc and a high frequency. Then, as shown in Fig. 7.33(a), we select a series resistance,  $R_{S1}$ , equal to that due to skin effect and shunt the combination of  $R_{S1}$  and  $L_1$  with a large inductor,  $L_2$ . We then add  $R_{S2}$  in series to model the low-frequency resistance of the wire. At high frequencies,  $L_2$  is open and  $R_{S1} + R_{S2}$  embodies the overall loss; at low frequencies, the network reduces to  $R_{S2}$ .

The above principle can be extended to broadband modeling of skin effect. Depicted in Fig. 7.33(b) for a cylindrical wire, the approach in [9] views the line as a set of concentric cylinders, each having some low-frequency resistance and inductance, arriving at the circuit in Fig. 7.33(c) for one section of the distributed model. Here, the branch consisting of  $R_j$  and  $L_j$  represents the impedance of cylinder number  $j$ . At low frequencies, the current is uniformly distributed through the conductor and the model reduces to  $R_1 || R_2 || \dots || R_n$  [9]. As the frequency increases, the current moves away from the inner cylinders, as modeled by the rising impedance of the inductors in each branch. In [9], a constant ratio  $R_j/R_{j+1}$  is maintained to simplify the model. We return to the use of this model for inductors later in this section.

We now add the effect of capacitive coupling to the substrate. Figure 7.34(a) shows a one-dimensional uniformly-distributed model where the total inductance and series resistance are decomposed into  $n$  equal segments, i.e.,  $L_1 + L_2 + \dots + L_n = L_{tot}$  and  $R_{S1} + R_{S2} + \dots + R_{Sn} = R_{S,tot}$ .<sup>9</sup> The nodes in the substrate are connected to one another by  $R_{sub1}, \dots, R_{sub,n-1}$  and to ground by  $R_{G1}, \dots, R_{Gn}$ . The total capacitance between the spiral and the substrate is decomposed into  $C_{sub1}, \dots, C_{subn}$ .

Continuing our model development, we include the magnetic coupling to the substrate. As depicted in Fig. 7.34(b), each inductor segment is coupled to the substrate through a transformer. Proper choice of the mutual coupling and  $R_{subm}$  allows accurate representation of this type of loss. In this model, the capacitance between the substrate nodes is also included.

While capturing the physical properties of inductors, the model shown in Fig. 7.34(b) proves too complex for practical use. The principal issue is that the numerous parameters make it difficult to fit the model to measured data. We must therefore seek more compact models that more easily lend themselves to parameter extraction and fitting. In the first

9. A more accurate model would include mutual coupling such that  $L_{tot} = L_1 + \dots + L_n + nM$ .

 


Figure 7.34 Distributed inductor model with (a) capacitive and (b) magnetic coupling to substrate.

 


Figure 7.35 (a) Compact inductor model, (b) alternative topology.

step, we turn to lumped models. As a simple example, we return to the parallel-series combination of Fig. 7.32(a) and add capacitances to the substrate [Fig. 7.35(a)]. We surmise that  $R'_S$  and  $R'_p$  can represent *all* of the losses even though they do not physically reflect the substrate loss. We also recall from Section 7.2.4 that an equivalent lumped capacitance,  $C_F$ , appears between the two terminals. With constant element values, this model is accurate for a bandwidth of about  $\pm 20\%$  around the center frequency.

An interesting dilemma arises in the above lumped model. We may choose  $C_1$  and  $C_2$  to be equal to half of the total capacitance to the substrate, but our analysis in Section 7.2.4 suggests that, if one terminal is grounded, the equivalent capacitance is *one-third* of the total amount. This is a shortcoming of the lumped model.

Another model that has proved relatively accurate is shown in Fig. 7.35(b). Here,  $R_1$  and  $R_2$  play a similar role to that of  $R_p$  in Fig. 7.35(a). Note that neither model explicitly includes the magnetic coupling to the substrate. The assumption is that the three resistances suffice to represent all of the losses across a reasonable bandwidth (e.g.,  $\pm 20\%$  around the frequency at which the component values are calculated). A more broadband model is described in [10].

**Definitions of  $Q$**  In this book, we have encountered several definitions of the  $Q$  of an inductor:

$$Q_1 = \frac{L\omega}{R_S} \quad (7.63)$$

$$Q_2 = \frac{R_p}{L\omega} \quad (7.64)$$

$$Q_3 = \frac{\text{Im}\{Z\}}{\text{Re}\{Z\}}. \quad (7.65)$$

In basic physics, the  $Q$  of a lossy oscillatory system is defined as

$$Q_4 = 2\pi \frac{\text{Energy Stored}}{\text{Energy Dissipated per Cycle}}. \quad (7.66)$$

Additionally, for a second-order tank, the  $Q$  can be defined in terms of the resonance frequency,  $\omega_0$ , and the  $-3$ -dB bandwidth,  $\omega_{BW}$ , as

$$Q_5 = \frac{\omega_0}{\omega_{BW}}. \quad (7.67)$$

To make matters more complicated, we can also define the  $Q$  of an open-loop system at a frequency  $\omega_0$  as

$$Q_6 = \frac{\omega_0}{2} \frac{d\phi}{d\omega}, \quad (7.68)$$

where  $\phi$  denotes the phase of the system's transfer function (Chapter 8).

Which one of the above definitions is relevant to RF design? We recall from Chapter 2 that  $Q_1$  and  $Q_2$  model the loss by a single resistance and are equivalent for a narrow bandwidth. Also, from Example 7.7, we discard  $Q_3$  because it fails where it matters most: in most RF circuits, inductors operate in resonance (with their own and other circuit capacitances), exhibiting  $Q_3 = 0$ . The remaining three, namely,  $Q_4$ ,  $Q_5$ , and  $Q_6$ , are equivalent for a second-order tank in the vicinity of the resonance frequency.

Before narrowing down the definitions of  $Q$  further, we must recognize that, in general, the analysis of a circuit does *not* require a knowledge of the  $Q$ 's of its constituent devices. For example, the inductor model shown in Fig. 7.34(b) represents the properties of the device completely. Thus, the concept of  $Q$  has been invented primarily to provide intuition, allowing analysis by inspection as well as the use of certain rules of thumb.

In this book, we mostly deal with only one of the above definitions,  $Q_2$ . We reduce any resonant network to a parallel RLC tank, lumping all of the loss in a single parallel resistor  $R_p$ , and define  $Q_2 = R_p/(L\omega_0)$ . This readily yields the voltage gain of the stage

shown in Fig. 7.1(b) as  $-g_m(r_O || R_p)$  at resonance. Moreover, if we wish to compute the  $Q$  of a given inductor design at *different* frequencies, then we add or subtract enough parallel capacitance to create resonance at each frequency and determine  $Q_2$  accordingly.

It is interesting to note the following equivalencies for a second-order parallel tank: for  $Q_2$  and  $Q_3$ , we have

$$Q_2 = 2\pi \frac{\text{Peak Magnetic Energy}}{\text{Energy Lost per Cycle}} \quad (7.69)$$

$$Q_3 = 2\pi \frac{\text{Peak Magnetic Energy} - \text{Peak Electric Energy}}{\text{Energy Lost per Cycle}} \quad (7.70)$$

### 7.2.7 Alternative Inductor Structures

As illustrated conceptually in Fig. 7.9, many variants of spiral inductors can be envisioned that can potentially raise the  $Q$ , lower the parasitic capacitances, or reduce the lateral dimensions. For example, the parallel combination of spirals proves beneficial in reducing the metal resistance. In this section, we deal with several inductor geometries.

**Symmetric Inductors** Differential circuits can employ a single symmetric inductor rather than two (asymmetric) spirals (Fig. 7.36). In addition to saving area, a differential geometry (driven by differential signals) also exhibits a higher  $Q$  [11]. To understand this property, let us use the model of Fig. 7.35(b) with single-ended and differential stimuli (Fig. 7.37). If in Fig. 7.37(a), we neglect  $C_3$  and assume  $C_1$  has a low impedance, then the resistance shunting the inductor at high frequencies is approximately equal to  $R_1$ . That is, the circuit is reduced to that in Fig. 7.37(b).

Now, consider the differential arrangement shown in Fig. 7.37(c). The circuit can be decomposed into two symmetric half circuits, revealing that  $R_1$  (or  $R_2$ ) appears in parallel with an inductance of  $L/2$  [Fig. 7.37(d)] and hence affects the  $Q$  to a lesser extent [11]. In Problem 7.4, we use Eq. (7.62) to compare the  $Q$ 's in the two cases. For frequencies above 5 GHz, differential spirals provide a  $Q$  of 8 or higher and single-ended structures a  $Q$  of about 5 to 6.

 


Figure 7.36 Use of symmetric inductor in a differential circuit.

 


Figure 7.37 (a) Inductor driven by a single-ended input, (b) simplified model of (a), (c) symmetric inductor driven by differential inputs, (d) simplified model of (c).

The principal drawback of symmetric inductors is their large interwinding capacitance, a point of contrast to the trend predicted by Eq. (7.29). Consider the arrangement shown in Fig. 7.38(a), where the inductor is driven by differential voltages and viewed as four segments in series. Modeling each segment by an inductor and including the fringe capacitance between the segments, we obtain the network depicted in Fig. 7.38(b). Note that symmetry creates a virtual ground at node 3. This model implies that  $C_1$  and  $C_2$  sustain large voltages, e.g., as much as  $V_{in}/2$  if we assume a linear voltage profile from node 1 to node 5 [Fig. 7.38(c)].

 


Figure 7.38 (a) Symmetric inductor, (b) equivalent circuit, (c) voltage profile along the inductor.

## Example 7.19

Estimate the equivalent lumped interwinding capacitance of the three-turn spiral shown in Fig. 7.39(a).

 


Figure 7.39 (a) Three-turn symmetric inductor, (b) equivalent circuit, (c) voltage profile along the ladder.

## Solution:

We unwind the structure as depicted in Fig. 7.39(b), assuming, as an approximation, that all unit inductances are equal and so are all unit capacitances. We further assume a linear voltage profile from one end to the other [Fig. 7.39(c)]. Thus,  $C_1$  sustains a voltage of  $4V_{in}/6$  and so does  $C_3$ . Similarly, each of  $C_2$  and  $C_4$  has a voltage of  $2V_{in}/6$ . The total electric energy stored on the four capacitors is therefore equal to

$$E_{tot} = 2 \left[ \frac{1}{2} C \left( \frac{2}{3} V_{in} \right)^2 + \frac{1}{2} C \left( \frac{1}{3} V_{in} \right)^2 \right], \quad (7.71)$$

where  $C = C_1 = \dots = C_4$ . Denoting  $C_1 + \dots + C_4$  by  $C_{tot}$ , we have

$$E_{tot} = \frac{5}{9} \frac{C_{tot}}{4} V_{in}^2, \quad (7.72)$$

and hence an equivalent lumped capacitance of

$$C_{eq} = \frac{5}{18} C_{tot}. \quad (7.73)$$

## Example 7.19 (Continued)

Compared with its counterpart in a single-ended inductor, Eq. (7.32), this value is higher by a factor of  $160/9 \approx 18$ . In fact, the equivalent interwinding capacitance of a differential inductor is typically quite *larger* than the capacitance to the substrate, dominating the self-resonance frequency.

How do we reduce the interwinding capacitance? We can increase the line-to-line spacing,  $S$ , but, for a given outer dimension, this results in smaller inner turns and hence a lower inductance. In fact, Eq. (7.15) reveals that  $L$  falls as  $S$  increases and  $l_{tot}$  remains constant, yielding a lower  $Q$ . As a rule of thumb, we choose a spacing of approximately three times the minimum allowable value.<sup>10</sup> Further increase of  $S$  lowers the fringe capacitance only slightly but degrades the  $Q$ .

Owing to their higher  $Q$ , differential inductors are common in oscillator design, where the  $Q$  matters most. They are typically constructed as octagons (a symmetric version of that in Fig. 7.9(b)) because, for a given inductance, an octagonal shape has a shorter length and hence less series resistance than does a square geometry. (Perpendicular sides provide little mutual coupling.) For other differential circuits, such structures can be used, but at the cost of routing complexity. Figure 7.40 illustrates this point for a cascade of two stages. With single-ended spirals on each side, the lines traveling to the next stage can pass *between* the inductors [Fig. 7.40(a)]. Of course, some spacing is necessary between the lines and the inductors so as to minimize unwanted coupling. On the other hand, with the differential structure, the lines must travel either *through* the inductor or *around* it [Fig. 7.40(b)], creating greater coupling than in the former case.

 


Figure 7.40 Routing of signals to next stage in a circuit using (a) single-ended inductors, (b) a symmetric inductor.

10. But, in some technologies long lines require a wider spacing than short lines, in which case the minimum  $S$  may be 1 to  $1.5 \mu\text{m}$ .

### Example 7.20

If used as the load of differential circuits, single-ended inductors can be laid out with “mirror symmetry” [Fig. 7.41(a)] or “step symmetry” [Fig. 7.41(b)]. Discuss the pros and cons of each layout style.

 


Figure 7.41 Load inductors in a differential pair with (a) mirror symmetry and (b) step symmetry.

#### Solution:

The circuit of Fig. 7.41(a) is relatively symmetric but suffers from *undesirable* mutual coupling between  $L_1$  and  $L_2$ . Since the differential currents produced by  $M_1$  and  $M_2$  flow in *opposite* directions in the spirals, the equivalent inductance seen between  $X$  and  $Y$  is equal to

$$L_{eq} = L_1 + L_2 - 2M, \quad (7.74)$$

where  $M$  denotes the mutual coupling between  $L_1$  and  $L_2$ . With a small spacing between the spirals, the mutual coupling factor,  $k$ , may reach roughly 0.25, yielding  $M = k\sqrt{L_1 L_2} = 0.25L$  if  $L_1 = L_2 = L$ . In other words,  $L_{eq}$  is 25% less than  $L_1 + L_2$ , exhibiting a lower  $Q$ . For  $k$  to fall to a few percent, the spacing between  $L_1$  and  $L_2$  must exceed approximately one-half of the outer dimension of each.

In the topology of Fig. 7.41(b), the direction of currents results in

$$L_{eq} = L_1 + L_2 + 2M, \quad (7.75)$$

increasing the  $Q$ . However, the circuit is less symmetric. Thus, if symmetry is critical [e.g., in the LO buffer of a direct-conversion receiver (Chapter 4)], then we choose the former with some spacing between  $L_1$  and  $L_2$ . Otherwise, we opt for the latter.

Another important difference between two single-ended inductors and one differential inductor is the amount of signal coupling that they inflict or incur. Consider the topology of Fig. 7.42(a) and a point  $P$  on its axis of symmetry. Using the right-hand rule, we observe that the magnetic field due to  $L_1$  points into the page at  $P$  and that due to  $L_2$  out of the page.

 


Figure 7.42 Magnetic coupling along the axis of symmetry with (a) single-ended inductors and (b) a symmetric inductor.

The two fields therefore cancel along the axis of symmetry. By contrast, the differential spiral in Fig. 7.42(b) produces a single magnetic field at  $P$  and hence coupling to other devices even on the line of symmetry.<sup>11</sup> This issue is particularly problematic in oscillators: to achieve a high  $Q$ , we wish to use symmetric inductors but at the cost of making the circuit more sensitive to injection-pulling by the power amplifier.

### Example 7.21

The topology of Fig. 7.43 may be considered a candidate for small coupling. Explain the pros and cons of this structure.

 


Figure 7.43 Inductor with reduced magnetic coupling along axis of symmetry.

#### Solution:

This geometry in fact consists of two single-ended inductors because node  $N$  is a virtual ground. The magnetic fields of the two halves indeed cancel on the axis of symmetry.

(Continues)

11. One can also view the single spiral as a loop antenna.

**Example 7.21** (Continued)

The structure is more symmetric than the single-ended spirals with step symmetry in Fig. 7.42(a). Unfortunately, the  $Q$  of this topology is lower than that of a differential inductor because each half experiences its own substrate loss; i.e., the doubling of the substrate shunt resistance observed in Fig. 7.37 does not occur here. A variant of this structure is described in [12].

**Inductors with Ground Shield** In our early study of substrate loss in Section 7.2.5, we contemplated the use of a grounded shield below the inductor. The goal was to allow the displacement current to flow through a low resistance to ground, thus avoiding the loss due to electric coupling to the substrate. But we observed that eddy currents in a continuous shield drastically reduce the inductance and the  $Q$ .

We now observe that the shield can provide a low-resistance termination for electric field lines even if it is *not* continuous. As illustrated in Fig. 7.44 [13], a “patterned” shield, i.e., a plane broken periodically in the direction perpendicular to the flow of eddy currents, receives most of the electric field lines without reducing the inductance. A small fraction of the field lines sneak through the gaps in the shield and terminate on the lossy substrate. Thus, the width of the gaps must be minimized.

 


Figure 7.44 Inductor with patterned ground shield.

It is important to note that the patterned ground shield only reduces the effect of capacitive coupling to the substrate. The eddy currents resulting from magnetic coupling continue to flow through the substrate as Faraday and Lenz have prescribed.

**Example 7.22**

A student designing a patterned ground shield decides that minimizing the gap width is not a good idea because it increases the capacitance between each two sections of the shield, potentially allowing large eddy currents to flow through the shield. Is the student correct?

**Solution:**

While it is true that the gap capacitance increases, we must note that all of the gap capacitances appear in *series* with the path of eddy currents. The overall equivalent capacitance is therefore very small and the impedance presented to eddy currents quite high.

The use of a patterned shield may increase the  $Q$  by 10 to 15% [13], but this improvement depends on many factors and has thus been inconsistent in different reports [14]. The factors include single-ended versus differential operation, the thickness of the metal, and the resistivity of the substrate. The improvement comes at the cost of higher capacitance. For example, if the inductor is realized in metal 9 and the shield in metal 1, then the capacitance rises by about 15%. One can utilize a patterned  $n^+$  region in the substrate as the shield to avoid this capacitance increase, but the measurement results have not been consistent.

The other difficulty with patterned shields is the additional complexity that they introduce in modeling and layout. The capacitance to the shield and the various losses now require much lengthier electromagnetic simulations.

**Stacked Inductors** At frequencies up to about 5 GHz, inductor values encountered in practice fall in the range of five to several tens of nanohenries. If realized as a single spiral, such inductors occupy a large area and lead to long interconnects between the circuit blocks. This issue can be resolved by exploiting the third dimension, i.e., by stacking spirals. Illustrated in Fig. 7.45, the idea is to place two or more spirals in series, obtaining a higher inductance not only due to the series connection but also as a result of strong mutual coupling. For example, the total inductance in Fig. 7.45 is given by

$$L_{tot} = L_1 + L_2 + 2M. \quad (7.76)$$

Since the lateral dimensions of  $L_1$  and  $L_2$  are much greater than their vertical separation,  $L_1$  and  $L_2$  exhibit almost perfect coupling, i.e.,  $M \approx L_1 = L_2$  and  $L_{tot} \approx 4L_1$ . Similarly,  $n$  stacked spirals operating in series raise the total inductance by approximately a factor of  $n^2$ .

 


Figure 7.45 Stacked spirals.

**Example 7.23**

The five-turn 4.96-nH inductor obtained from Eq. (7.15) in Section 7.2.3 has an outer dimension of

$$D_{out} = \frac{l_{tot}}{4N} + W + (N - 1)(W + S) \quad (7.77)$$

$$= 122 \mu\text{m}. \quad (7.78)$$


Using Eq. (7.15) for the inductance of one spiral, determine the required outer dimension of a four-turn stacked structure having the same  $W$  and  $S$ . Assume two spirals are stacked.

(Continues)

### Example 7.23 (Continued)

#### Solution:

Each spiral must provide an inductance of  $4.96 \text{ nH}/4 = 1.24 \text{ nH}$ . Iteration with  $N = 4$ ,  $W = 4 \mu\text{m}$ , and  $S = 0.5 \mu\text{m}$  in Eq. (7.15) yields  $l_{\text{tot}} \approx 780 \mu\text{m}$  and hence  $D_{\text{out}} = 66.25 \mu\text{m}$ . Stacking thus reduces the outer dimension by nearly a factor of 2 in this case.

 

**Figure 7.46** Equivalent capacitance for a stack of (a) metal-9 and metal-8, or (b) metal-9 and metal-5 spirals.

In reality, the multiplication factor of stacked square inductors is less than  $n^2$  because the legs of one inductor that are perpendicular to the legs of the other provide no mutual coupling. For example, a stack of two raises the inductance by about a factor of 3.5 [6]. The factor is closer to  $n^2$  for octagonal spirals and almost equal to  $n^2$  for circular structures.

In addition to the capacitance to the substrate and the interwinding capacitance, stacked inductors also contain one *between* the spirals [Fig. 7.46(a)].

### Example 7.24

In most circuits, one terminal of the inductor(s) is at ac ground. Which terminal of the structure in Fig. 7.46(a) should be grounded?

#### Solution:

Since  $L_2$  sees a much larger capacitance to the substrate than  $L_1$  does, the terminal of  $L_2$  should be grounded. This is a critical point in the use of stacked inductors.

Using an energy-based analysis similar to that in Section 7.2.4, [6] proves that the equivalent lumped capacitance of the inductor shown in Fig. 7.46(a) is equal to

$$C_{eq} = \frac{4C_1 + C_2}{12}, \quad (7.79)$$

if the free terminal of  $L_2$  is at ac ground.<sup>12</sup> Interestingly, the inter-spiral capacitance has a larger weighting factor than the capacitance to the substrate does. For this reason, if  $L_2$  is moved to lower metal layers [Fig. 7.46(b)],  $C_{eq}$  falls even though  $C_2$  rises. Note that the total inductance remains approximately constant so long as the lateral dimensions are much greater than the vertical spacing between  $L_1$  and  $L_2$ .

### Example 7.25

Compare the equivalent lumped capacitance of single-layer and stacked 4.96-nH inductors studied in Example 7.23. Assume the lower spiral is realized in metal 5 and use the capacitance values shown in Table 7.1.

**Table 7.1** Table of metal capacitances ( $\text{aF}/\mu\text{m}^2$ ).

|         | Metal 8 | Metal 7 | Metal 6 | Metal 5 | Substrate |
|---------|---------|---------|---------|---------|-----------|
| Metal 9 | 52      | 16      | 12      | 9.5     | 4.4       |
| Metal 8 |         | 52      | 24      | 16      | 5.4       |
| Metal 7 |         |         | 88      | 28      | 6.1       |
| Metal 6 |         |         |         | 88      | 7.1       |
| Metal 5 |         |         |         |         | 8.6       |

#### Solution:

For a single metal-9 layer, the total area is equal to  $2000 \mu\text{m} \times 4 \mu\text{m} = 8000 \mu\text{m}^2$ , yielding a total capacitance of 35.2 fF to the substrate. As suggested by Eq. (7.26), the equivalent lumped capacitance is 1/3 of this value, 11.73 fF. For the stacked structure, each spiral has an area of  $780 \mu\text{m} \times 4 \mu\text{m} = 3120 \mu\text{m}^2$ . Thus,  $C_1 = 29.64 \text{ fF}$  and  $C_2 = 26.83 \text{ fF}$ , resulting in

$$C_{eq} = 12.1 \text{ fF}. \quad (7.80)$$

The choice of stacking therefore translates to comparable capacitances.<sup>13</sup> If  $L_2$  is moved down to metal 4 or 3, the capacitance of the stacked structure falls more.

For  $n$  stacked spirals, it can be proved that

$$C_{eq} = \frac{4 \sum_{m=1}^{n-1} C_m + C_{sub}}{3n^2}, \quad (7.81)$$

where  $C_m$  denotes each inter-spiral capacitance [6].

12. If the free terminal of  $L_1$  is grounded, the equivalent capacitance is quite larger.

13. We have neglected the fringe components for simplicity.

How does stacking affect the  $Q$ ? We may surmise that the “resistance-free” coupling,  $M$ , among the spirals raises the inductance without increasing the resistance. However,  $M$  also exists among the turns of a single, large spiral. More fundamentally, for a given inductance, the total wire’s length is relatively constant and independent of how the wire is wound. For example, the single-spiral 4.96-nH inductor studied above has a total length of  $2000\ \mu\text{m}$  and the double-spiral stacked structure in Example 7.23,  $1560\ \mu\text{m}$ . But, with a more realistic multiplication factor of 3.5 for the inductance of two stacked spirals, the total length grows to about  $1800\ \mu\text{m}$ . We now observe that since the top metal layer is typically thicker than the lower layers, stacking tends to *increase* the series resistance and hence decrease the  $Q$ . The issue can be remedied by placing two or more lower spirals in *parallel*. Figure 7.47 shows an example where a metal-9 spiral is in series with the parallel combination of metal-6 and metal-5 spirals. Of course, complex current crowding effects at high frequencies require careful electromagnetic field simulations to determine the  $Q$ .

 


Figure 7.47 Stacked inductor using two parallel spirals in metal 6 and metal 5.

## 7.3 TRANSFORMERS

Integrated transformers can perform a number of useful functions in RF design: (1) impedance matching, (2) feedback or feedforward with positive or negative polarity, (3) single-ended to differential conversion or vice versa, and (4) ac coupling between stages. They are, however, more difficult to model and design than are inductors.

A well-designed transformer must exhibit the following: (1) low series resistance in the primary and secondary windings, (2) high magnetic coupling between the primary and the secondary, (3) low capacitive coupling between the primary and the secondary, and (4) low parasitic capacitances to the substrate. Some of the trade-offs are thus similar to those of inductors.

### 7.3.1 Transformer Structures

An integrated transformer generally comprises two spiral inductors with strong magnetic coupling. To arrive at “planar” structure, we begin with a symmetric inductor and break it at its point of symmetry (Fig. 7.48). Segments  $AB$  and  $CD$  now act as mutually-coupled inductors. We consider this structure a 1-to-1 transformer because the primary and the secondary are identical.

 


Figure 7.48 Transformer derived from a symmetric inductor.

### Example 7.26

What is the relationship between the inductance of the symmetric spiral of Fig. 7.48 and the inductances of the resulting transformer?

#### Solution:

We have

$$L_{AC} = L_{AB} + L_{CD} + 2M, \quad (7.82)$$

where each  $L$  refers to the inductance between its end points and  $M$  to the mutual coupling between  $L_{AB}$  and  $L_{DC}$ . Since  $L_{AB} = L_{CD}$ ,

$$L_{AC} = 2L_{AB} + 2M. \quad (7.83)$$

If  $L_{AC}$  and  $M$  are known, we can determine the inductance of the primary and the secondary.

The transformer structure of Fig. 7.48 suffers from low magnetic coupling, an asymmetric primary, and an asymmetric secondary. To remedy the former, the number of turns can be increased [Fig. 7.49(a)] but at the cost of higher capacitive coupling. To remedy the latter, two symmetric spirals can be embedded as shown in Fig. 7.49(b) but with a slight

 


Figure 7.49 Transformers (a) derived from a three-turn symmetric inductor, (b) formed as two embedded symmetric spirals.

difference between the primary and secondary inductances. The coupling factor in all of the above structures is typically less than 0.8. We study the consequences of this imperfection in the following example.

### Example 7.27

Consider the circuit shown in Fig. 7.50, where  $C_F$  models the equivalent lumped capacitance between the primary and the secondary. Determine the transfer function  $V_{out}/V_{in}$  and discuss the effect of the sub-unity magnetic coupling factor.

 


Figure 7.50 Simple transformer model.

### Solution:

The transformer action gives

$$V_{in} = L_1 s I_1 + M s I_2 \quad (7.84)$$

$$V_{out} = L_2 s I_2 + M s I_1. \quad (7.85)$$

Finding  $I_1$  from Eq. (7.84) and substituting the result in Eq. (7.85), we have

$$I_2 = \frac{V_{out}}{L_2 s} - \frac{M(V_{in} - M s I_2)}{L_1 L_2 s}. \quad (7.86)$$

Also, a KCL at the output node yields

$$(V_{in} - V_{out}) C_F s - I_2 = \frac{V_{out}}{R_L}. \quad (7.87)$$

Replacing  $I_2$  from (7.86) and simplifying the result, we obtain

$$\frac{V_{out}}{V_{in}}(s) = \frac{L_1 L_2 \left(1 - \frac{M^2}{L_1 L_2}\right) C_F s^2 + M}{L_1 L_2 \left(1 - \frac{M^2}{L_1 L_2}\right) C_F s^2 + \frac{L_1 L_2}{R_L} \left(1 - \frac{M^2}{L_1 L_2}\right) s + L_1}. \quad (7.88)$$

It is instructive to examine this transfer function in a few special cases. First, if  $C_F = 0$ ,

$$\frac{V_{out}}{V_{in}} = \frac{M}{\frac{L_1 L_2}{R_L} \left(1 - \frac{M^2}{L_1 L_2}\right) s + L_1}. \quad (7.89)$$

### Example 7.27 (Continued)

suggesting that, since  $k = M/\sqrt{L_1 L_2} < 1$ , the transformer exhibits a low-pass response with a real pole located at

$$\omega_p = \frac{-R_L}{L_2 \left(1 - \frac{M^2}{L_1 L_2}\right)}. \quad (7.90)$$

For example, if  $k = 0.7$ , then  $\omega_p = -1.96 R_L/L_2$ . This pole must lie well above the frequency of operation.

Second, if  $C_F > 0$  but  $M = L_1 = L_2$ , then  $V_{out}/V_{in} = M/L_1 = 1$  regardless of the values of  $C_F$  and  $R_L$ . Thus,  $C_F$  manifests itself because of the sub-unity  $k$ . Since typically  $L_1 = L_2 = L$ , we can express the poles of Eq. (7.88) as

$$\omega_{p1,2} = \frac{1}{2R_L C_F} \left[ -1 \pm \sqrt{1 - \frac{4R_L^2 C_F}{L(1 - k^2)}} \right]. \quad (7.91)$$

Equation (7.88) implies that it is beneficial to reduce  $L_1$  and  $L_2$  while  $k$  remains constant; as  $L_1$  and  $L_2$  (and  $M = k\sqrt{L_1 L_2}$ ) approach zero,

$$\frac{V_{out}}{V_{in}}(s) \approx \frac{M}{L_1}, \quad (7.92)$$

a frequency-independent quantity equal to  $k$  if  $L_1 = L_2$ . However, reduction of  $L_1$  and  $L_2$  also lowers the input impedance,  $Z_{in}$ , in Fig. 7.50. For example, if  $C_F = 0$ , we have from Eq. (7.54),


$$Z_{in} = L_1 s - \frac{M^2 s^2}{R_L + L_2 s}. \quad (7.93)$$

Thus, the number of primary and secondary turns must be chosen so that  $Z_{in}$  is adequately high in the frequency range of interest.


Is it possible to construct planar transformers having a turns ratio greater than unity? Figure 7.51(a) shows an example, where  $AB$  has approximately one turn and  $CD$  approximately two. We note, however, that the mutual coupling between  $AB$  and the inner turn of  $CD$  is relatively weak due to the smaller diameter of the latter. Figure 7.51(b) depicts another 1-to-2 example with a stronger coupling factor. In practice, the primary and secondary may require a larger number of turns so as to provide a reasonable input impedance.

Figure 7.52 shows two other examples of planar transformers. Here, two asymmetric spirals are interwound to achieve a high coupling factor. The geometry of Fig. 7.52(a) can be viewed as two parallel conductors that are wound into turns. Owing to the difference between their lengths, the primary and secondary exhibit unequal inductances and hence a nonunity turns ratio [16]. The structure of Fig. 7.52(b), on the other hand, provides an exact turns ratio of unity [16].


Transformers can also be implemented as three-dimensional structures. Similar to the stacked inductors studied in Section 7.2.7, a transformer can employ stacked spirals for the

 

**Figure 7.51** One-to-two transformers (a) derived from a symmetric inductor, (b) formed as two symmetric inductors.

 

**Figure 7.52** (a) Transformer formed as two wires wound together, (b) alternative version with equal primary and secondary lengths.

 

**Figure 7.53** (a) One-to-one stacked transformer, (b) one-to-two transformer, (c) staggering of turns to reduce coupling capacitance.

primary and the secondary [6]. Figure 7.53(a) shows a 1-to-1 example. It is important to recognize the following attributes: (1) the alignment of the primary and secondary results in a slightly higher magnetic coupling factor here than in the planar transformers of Figs. 7.49 and 7.51; (2) unlike the planar structures, the primary and the secondary can be

symmetric and identical (except for differences in their capacitances); (3) the overall area occupied by 3D transformers is less than that of their planar counterparts.

Another advantage of stacked transformers is that they can readily provide a turns ratio higher than unity [6]. Illustrated in Fig. 7.53(b), the idea is to incorporate multiple spirals in series to form the primary or the secondary. Thus, a technology having nine metal layers can afford 1-to-8 transformers! As shown in [6], stacked transformers indeed provide significant voltage or current gain at gigahertz frequencies. This “free” gain can be utilized between stages in a chain.

Stacked transformers must, however, deal with two issues. First, the lower spirals suffer from a higher resistance due to the thinner metal layers. Second, the capacitance between the primary and secondary is larger here than in planar transformers (why?). To reduce this capacitance, the primary and secondary turns can be “staggered,” thus minimizing their overlap [Fig. 7.53(c)] [6]. But this requires a relatively large spacing between the adjacent turns of each inductor, reducing the inductance.

### 7.3.2 Effect of Coupling Capacitance

The coupling capacitance between the primary and secondary yields different types of behavior with negative and positive mutual (magnetic) coupling factors. To understand this point, we return to the transfer function in Eq. (7.88) and note that, for  $s = j\omega$ , the numerator reduces to

$$N(j\omega) = -L_1L_2 \left( 1 - \frac{M^2}{L_1L_2} \right) C_F\omega^2 + M. \quad (7.94)$$

The first term is always negative, but the polarity of the second term depends on the direction chosen for mutual coupling. Thus, if  $M > 0$ , then  $N(j\omega)$  falls to zero at

$$\omega_z = \sqrt{\frac{M}{L_1L_2 \left( 1 - \frac{M^2}{L_1L_2} \right) C_F}}, \quad (7.95)$$

i.e., the frequency response exhibits a notch at  $\omega_z$ . On the other hand, if  $M < 0$ , no such notch exists and the transformer can operate at higher frequencies. We therefore say “noninverting” transformers suffer from a lower speed than do “inverting” transformers [16].

The above phenomenon can also be explained intuitively: the feedforward signal through  $C_F$  can cancel the signal coupled from  $L_1$  to  $L_2$ . Specifically, the voltage across  $L_2$  in Fig. 7.50 contains two terms, namely,  $L_2j\omega I_2$  and  $Mj\omega I_1$ . If, at some frequency,  $I_2$  is entirely provided by  $C_F$ , the former term can cancel the latter, yielding a zero output voltage.

### 7.3.3 Transformer Modeling

An integrated transformer can be viewed as two inductors having magnetic and capacitive coupling. The inductor models described in Section 7.2.6 therefore directly apply here. Figure 7.54 shows an example, where the primary and secondary are represented by the compact inductor model of Fig. 7.35(b), with the mutual coupling  $M$  and coupling capacitor  $C_F$  added. More details on transformer modeling can be found in [16] and [17].

 


Figure 7.54 Transformer model.

Due to the complexity of this model, it is difficult to find the value of each component from measurements or field simulations that provide only  $S$ - or  $Y$ -parameters for the entire structure. In practice, some effort is expended on this type of modeling to develop insight into the transformer's limitations, but an accurate representation may require that the designer directly use the  $S$ - or  $Y$ -parameters in circuit simulations. Unfortunately, circuit simulators sometimes face convergence difficulties with these parameters.

## 7.4 TRANSMISSION LINES

Integrated transmission lines (T-lines) are occasionally used in RF design. It is instructive to consider a few examples of T-line applications. Suppose a long wire carries a high-frequency signal from one circuit block to another (Fig. 7.55). The wire suffers from inductance, capacitance, and resistance. If the width of the wire is increased so as to reduce the inductance and series resistance, then the capacitance to the substrate rises. These parasitics may considerably degrade the signal as the frequency exceeds several gigahertz.

 


Figure 7.55 Two circuit blocks connected by a long wire.

### Example 7.28

For the wire shown in Fig. 7.55, we also say the current “return path” is poorly-defined. Explain this attribute and its consequences.

#### Solution:

In the ideal situation, the signal current flowing through the wire from block A to block B returns through a ground plane [Fig. 7.56(a)]. In reality, however, due to the wire parasitics

### Example 7.28 (Continued)

and the nonideal ground connection between the two blocks, some of the signal current flows through the substrate [Fig. 7.56(b)]. The complexity of the return path makes it difficult to accurately predict the behavior of the wire at high frequencies. Also, the coupling to the substrate creates leakage of the signal to other parts of the chip.

 


Figure 7.56 (a) Current return path through a ground plane, (b) poor definition of current return path.

If the long wire in Fig. 7.55 is replaced with a T-line and the input port of block B is modified to match the T-line, then the above issues are alleviated. As illustrated in Fig. 7.57, the line inductance and capacitance no longer degrade the signal, and the T-line ground plane not only provides a low-impedance path for the returning current but minimizes the interaction of the signal with the substrate. The line resistance can also be lowered but with a trade-off (Section 7.4.1).

 


Figure 7.57 Two circuit blocks connected by a T-line.

As another example of T-line applications, recall from Chapter 2 that a T-line having a short-circuit termination acts as an inductor if it is much shorter than a wavelength. Thus, T-lines can serve as inductive loads (Fig. 7.58).

 


Figure 7.58 T-line serving as a load inductor.

### Example 7.29

Identify the return path for the signal current that flows through the T-line in Fig. 7.58.

#### Solution:

Since the signal current reaches the  $V_{DD}$  line, a bypass capacitor must be placed between  $V_{DD}$  and ground. Illustrated in Fig. 7.59, such an arrangement must minimize the parasitic inductance and resistance in the return path. Note that low-impedance return paths and hence bypass capacitors are necessary in any high-frequency single-ended stage.

 


Figure 7.59 Return path around a T-line in a CS stage.

How does the  $Q$  of T-line inductors compare with that of spiral structures? For frequencies as high as several tens of gigahertz, the latter provide a higher  $Q$  because of the mutual coupling among their turns. For higher frequencies, it is expected that the former become superior, but actual measured data supporting this prediction are not available—at least in CMOS technology.

T-lines can also transform impedances. As mentioned in Chapter 2, a line of length  $d$  that is terminated with a load impedance of  $Z_L$  exhibits an input impedance of

$$Z_{in}(d) = \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \quad (7.96)$$

where  $\beta = 2\pi/\lambda$  and  $Z_0$  is the characteristic impedance of the line. For example, if  $d = \lambda/4$ , then  $Z_{in} = Z_0^2/Z_L$ , i.e., a capacitive load can be transformed to an inductive component. Of course, the required quarter-wave length becomes practical in integrated circuits only at millimeter-wave frequencies.

### 7.4.1 T-Line Structures

Among various T-line structures developed in the field of microwaves, only a few lend themselves to integration. When choosing a geometry, the RF IC designer is concerned with the following parameters: loss, characteristic impedance, velocity, and size.

Before studying T-line structures, let us briefly look at the back end of CMOS processes. As exemplified by Fig. 7.60, a typical process provides a silicided polysilicon layer and about nine metal layers. The high sheet resistance,  $R_{sh}$ , of poly (10 to 20  $\Omega/\square$ ) makes

 


Figure 7.60 Typical back end of a CMOS process.

it a poor conductor. Each of the lower metal layers has a thickness of approximately  $0.3 \mu\text{m}$  and an  $R_{sh}$  of 60 to 70  $\text{m}\Omega/\square$ . The top layer has a thickness of about  $0.7$  to  $0.8 \mu\text{m}$  and an  $R_{sh}$  of 25 to 30  $\text{m}\Omega/\square$ . Between each two consecutive metal layers lie two dielectric layers: a  $0.7\text{-}\mu\text{m}$  layer with  $\epsilon_r \approx 3.5$  and a  $0.1\text{-}\mu\text{m}$  layer with  $\epsilon_r \approx 7$ .

**Microstrip** A natural candidate for integrated T-lines is the “microstrip” structure. Depicted in Fig. 7.61, it consists of a signal line realized in the topmost metal layer and a ground plane in a lower metal layer. An important attribute of this topology is that it can have minimal interaction between the signal line and the substrate. This is accomplished if the ground plane is wide enough to contain most of the electric field lines emanating from the signal wire. As a compromise between field confinement and the dimensions of the T-line, we choose  $W_G \approx 3W_S$ .

 


Figure 7.61 Microstrip structure.

Numerous equations have been developed in the field of microwaves to express the characteristic impedance of microstrips. For example, if the signal line has a thickness of  $t$  and a height of  $h$  with respect to the ground plane, then

$$Z_0 = \frac{377}{\sqrt{\epsilon_r}} \frac{h}{W_S} \frac{1}{1 + 1.735 \epsilon_r^{-0.0724} (W_e/h)^{-0.836}} \quad (7.97)$$

where

$$W_e = W_S + \frac{t}{\pi} \left( 1 + \ln \frac{2h}{t} \right). \quad (7.98)$$

For example, if  $h = 7 \mu\text{m}$ ,  $t = 0.8 \mu\text{m}$ ,  $\epsilon_r = 4$ , and  $W_S = 4 \mu\text{m}$ , then  $Z_0 \approx 86 \Omega$ . Unfortunately, these equations suffer from errors as large as 10%. In practice, electromagnetic field simulations including the back end details are necessary to compute  $Z_0$ .

### Example 7.30

A short microstrip is used as an inductor resonating with the transistor capacitances in a circuit. Determine the error in the resonance frequency,  $\omega_{res}$ , if the line's characteristic impedance has a 10% error.

#### Solution:

From Eq. (7.96), a T-line with  $Z_L = 0$  and  $2\pi d \ll \lambda$  provides an input impedance of

$$Z_{in} = jZ_0 \tan(\beta d) \quad (7.99)$$

$$\approx jZ_0 \left( 2\pi \frac{d}{\lambda} \right) \quad (7.100)$$

$$\approx j\omega \frac{Z_0 d}{v}, \quad (7.101)$$

i.e., an inductance of  $L_{eq} = Z_0 d / v = L_u d$ , where  $v$  denotes the wave velocity and  $L_u$  the inductance per unit length. Since  $\omega_{res}$  is inversely proportional to  $\sqrt{L_{eq}}$ , a 10% error in  $L_{eq}$  translates to about a 5% error in  $\omega_{res}$ .

The loss of microstrips arises from the resistance of both the signal line and the ground plane. In modern CMOS technologies, metal 1 is in fact thinner than the higher layers, introducing a ground plane loss comparable to the signal line loss.

The loss of a T-line manifests itself as signal attenuation (or bandwidth reduction) if the line simply connects two blocks. With a typical loss of less than 0.5 dB/mm at frequencies of several tens of gigahertz, a microstrip serves this purpose well. On the other hand, if a T-line acts as an inductive load whose  $Q$  is critical, then a much lower loss is required. We can readily relate the loss and the  $Q$ . Suppose a T-line of unit length exhibits a series resistance of  $R_u$ . As shown in Fig. 7.62,

$$\frac{V_{out}}{V_{in}} \approx \frac{R_L}{R_S + R_u + R_L} \quad (7.102)$$

$$\approx \frac{Z_0}{2Z_0 + R_u}. \quad (7.103)$$

 


Figure 7.62 Lossy transmission line.

We find the difference between this result and the ideal value and then normalize to 1/2:

$$\text{Loss} \approx \frac{R_u}{2Z_0 + R_u} \quad (7.104)$$

$$\approx \frac{R_u}{2Z_0}, \quad (7.105)$$

if  $R_u \ll 2Z_0$ . Note that this value is expressed in decibels as  $20 \log(1 - \text{Loss})$  and the result is *negative*. A T-line of unit length has a  $Q$  of

$$Q = \frac{L_u \omega}{R_u} \quad (7.106)$$

$$= \frac{L_u \omega}{2Z_0 \cdot \text{Loss}}. \quad (7.107)$$

### Example 7.31

Consider a microstrip line  $1000 \mu\text{m}$  long with  $Z_0 = 100 \Omega$  and  $L = 1 \text{ nH}$ . If the signal line is  $4 \mu\text{m}$  wide and has a sheet resistance of  $25 \text{ m}\Omega/\square$ , determine the loss and the  $Q$  at 5 GHz. Neglect skin effect and the loss of the ground plane.

#### Solution:

The low-frequency resistance of the signal line is equal to  $6.25 \Omega$ , yielding from Eq. (7.104) a loss of  $0.031 \equiv -0.276 \text{ dB}$ . The  $Q$  is obtained from (7.107) as

$$Q = 5.03. \quad (7.108)$$

In order to reduce the loss of a microstrip, the width of the signal line can be increased (requiring a proportional increase in the width of the ground plane). But such an increase (1) reduces the inductance per unit length (as if multiple signal lines were placed in parallel), and (2) raises the capacitance to the ground plane. Both effects translate to a lower characteristic impedance,  $Z_0 = \sqrt{L_u / C_u}$ . For example, doubling the signal line width roughly halves  $Z_0$ .<sup>14</sup> Equation (7.97) also reveals this rough dependence.

The reduction of the characteristic impedance as a result of widening the signal line does make circuit design more difficult. As noted in Fig. 7.57, a properly-terminated T-line

14. Doubling the width does not reduce  $L_u$  by a factor of 2 because placing two *coupled* wires in parallel does not halve the inductance.

loads the driving stage (block *A*) with a resistance of  $Z_0$ . Thus, as  $Z_0$  decreases, so does the gain of block *A*. In other words, it is the *product* of the gain of block *A* and the inverse loss of the T-line that must be maximized, dictating that the circuit and the line be designed as a single entity.

The resistance of microstrips can also be reduced by stacking metal layers. Illustrated in Fig. 7.63, such a geometry alleviates the trade-off between the loss and the characteristic impedance. Also, stacking allows a narrower footprint for the T-line, thus simplifying the routing and the layout.

 


Figure 7.63 Microstrip using parallel metal layers for lower loss.

### Example 7.32

Transmission lines used to transform impedances are prohibitively long for frequencies up to a few tens of gigahertz. However, the relationship  $v = 1/\sqrt{L_u C_u}$  suggests that, if  $C_u$  is raised, then the wave velocity can be reduced and so can  $\lambda = v/f$ . Explain the practicality of this idea.

#### Solution:

The issue is that a higher  $C_u$  results in a lower  $Z_0$ . Thus, the line can be shorter, but it demands a greater drive capability. Moreover, impedance transformation becomes more difficult. For example, suppose a  $\lambda/4$  line is used to raise  $Z_L$  to  $Z_0^2/Z_L$ . This is possible only if  $Z_0 > Z_L$ .

**Coplanar Lines** Another candidate for integrated T-lines is the “coplanar” structure. Shown in Fig. 7.64, this geometry realizes both the signal and the ground lines in *one plane*, e.g., in metal 9. The characteristic impedance of coplanar lines can be higher than that of microstrips because (1) the thickness of the signal and ground lines in Fig. 7.64 is quite small, leading to a small capacitance between them, and (2) the spacing between the two lines can be large, further decreasing the capacitance. Of course, as  $S$  becomes comparable with  $h$ , more of the electric field lines emanating from the signal wire terminate on the substrate, producing a higher loss. Also, the signal line can be surrounded by ground lines on both sides. The characteristics of coplanar lines are usually obtained by electromagnetic field simulations.

 


Figure 7.64 Coplanar structure.

The loss reduction techniques described above for microstrips can also be applied to coplanar lines, entailing similar trade-offs. However, coplanar lines have a larger footprint because of their lateral spread, making layout more difficult.

**Stripline** The “stripline” consists of a signal line *surrounded* by ground planes, thus producing little field leakage to the environment. As an example, a metal-5 signal line can be surrounded by metal-1 and metal-9 planes and vias connecting the two planes (Fig. 7.65). If the vias are spaced closely, the signal line remains shielded in all four directions.

The stripline exhibits a smaller characteristic impedance than microstrip and coplanar structures do. It is therefore used only where field confinement is essential.

 


Figure 7.65 Stripline structure.

## 7.5 VARACTORS

As described in Chapter 8, “varactors” are an essential component of LC VCOs. Varactors also occasionally serve to tune the resonance frequency of narrowband amplifiers.

A varactor is a voltage-dependent capacitor. Two attributes of varactors become critical in oscillator design: (1) the capacitance range, i.e., the ratio of the maximum and minimum capacitances that the varactor can provide, and (2) the quality factor of the varactor, which is limited by the parasitic series resistances within the structure. Interestingly, these two parameters trade with each other in some cases.

In older generations of RF ICs, varactors were realized as reverse-biased *pn* junctions. Illustrated in Fig. 7.66(a) is one example where the *p*-substrate forms the anode and the *n*<sup>+</sup> contact, the cathode. (The *p*<sup>+</sup> contact provides a low-resistance connection to

 


Figure 7.66 PN junction varactor with (a) one terminal grounded, (b) both terminals floating.

the substrate.) In this case, the anode is “hard-wired” to ground, limiting the design flexibility. A “floating”  $pn$  junction can be constructed as shown in Fig. 7.66(b), with an  $n$ -well isolating the diode from the substrate and acting as the cathode.

Let us examine the capacitance range and  $Q$  of  $pn$  junctions. At a reverse bias of  $V_D$ , the junction capacitance,  $C_j$ , is given by

$$C_j = \frac{C_{j0}}{\left(1 + \frac{V_D}{V_0}\right)^m}, \quad (7.109)$$

where  $C_{j0}$  is the capacitance at zero bias,  $V_0$  the built-in potential, and  $m$  an exponent around 0.3 in integrated structures. We recognize the weak dependence of  $C_j$  upon  $V_D$ . Since  $V_0 \approx 0.7$  to  $0.8$  V and since  $V_D$  is constrained to less than 1 V by today's supply voltages, the term  $1 + V_D/V_0$  varies between approximately 1 and 2. Furthermore, an  $m$  of about 0.3 weakens this variation, resulting in a capacitance range,  $C_{j,max}/C_{j,min}$ , of roughly 1.23. In practice, we may allow the varactor to experience some forward bias (0.2 to 0.3 V), thus obtaining a somewhat larger range.

The  $Q$  of a  $pn$ -junction varactor is given by the total series resistance of the structure. In the floating diode of Fig. 7.66(b), this resistance is primarily due to the  $n$ -well and can be minimized by selecting minimum spacing between the  $n^+$  and  $p^+$  contacts. Moreover, as shown in Fig. 7.67, each  $p^+$  region can be surrounded by an  $n^+$  ring to lower the resistance in two dimensions.

Unlike inductors, transformers, and T-lines, varactors are quite difficult to simulate and model, especially for  $Q$  calculations. Consider the displacement current flow depicted in Fig. 7.68(a). Due to the two-dimensional nature of the flow, it is difficult to determine or compute the equivalent series resistance of the structure. This issue arises partly because the sheet resistance of the  $n$ -well is typically measured by the foundry for contacts having a spacing greater than the depth of the  $n$ -well [Fig. 7.68(b)]. Since the current path in this case is different from that in Fig. 7.68(a), the  $n$ -well sheet resistance cannot be directly applied

 


Figure 7.67 Use of an  $n^+$  ring to reduce varactor resistance.

 


Figure 7.68 Current distribution in a (a) varactor, (b) typical test structure.

to the calculation of the varactor series resistance. For these reasons, the  $Q$  of varactors is usually obtained by measurement on fabricated structures.<sup>15</sup>

In modern RF IC design, MOS varactors have supplanted their  $pn$ -junction counterparts. A regular MOSFET exhibits a voltage-dependent gate capacitance (Fig. 7.69), but the nonmonotonic behavior limits the design flexibility. For example, a voltage-controlled oscillator (VCO) employing such a varactor would generate an output frequency that rises and falls as (the average)  $V_{GS}$  goes from negative to positive values. This nonmonotonic frequency tuning behavior becomes problematic in phase-locked loop design (Chapter 9).


 


Figure 7.69 Variation of gate capacitance with  $V_{GS}$ .

15. Of course, semiconductor device simulators can be used here if the doping levels and the junction depths are known.

 

**Figure 7.70** (a) MOS varactor, (b) operation with negative gate-source voltage, (c) operation with positive gate-source voltage, (d) resulting  $C/V$  characteristic.

A simple modification of the MOS device avoids the above issues. Called an “accumulation-mode MOS varactor” and shown in Fig. 7.70(a), this structure is obtained by placing an NMOS transistor inside an  $n$ -well. If  $V_G < V_S$ , then the electrons in the  $n$ -well are repelled from the silicon/oxide interface and a depletion region is formed [Fig. 7.70(b)]. Under this condition, the equivalent capacitance is given by the series combination of the oxide and depletion capacitances. As  $V_G$  exceeds  $V_S$ , the interface attracts electrons from the  $n^+$  source/drain terminals, creating a channel [Fig. 7.70(c)]. The overall capacitance therefore rises to that of the oxide, behaving as shown in Fig. 7.70(d). (Since the material under the gate is  $n$ -type silicon, the concept of strong inversion does not apply here.)

The  $C/V$  characteristic of MOS varactors has scaled well with CMOS technology generations, approaching its saturated levels of  $C_{max}$  and  $C_{min}$  for  $V_{GS} \approx \pm 0.5$  V in 65-nm devices. These varactors therefore operate with low supply voltages better than their  $pn$ -junction counterparts.

Another advantage of accumulation-mode MOS varactors is that, unlike  $pn$  junctions, they can tolerate both positive and negative voltages. In fact, the characteristic of Fig. 7.70(d) suggests that MOS varactors *should* operate with positive and negative biases so as to provide maximum tuning range. We pursue this point in VCO design in Chapter 8.

Circuit simulations must somehow incorporate the varactor  $C/V$  characteristic of Fig. 7.70(d). In practice, this characteristic is measured on fabricated devices and represented by a table of discrete values. Such a table, however, may introduce discontinuities in the *derivatives* of the characteristic, creating undesirable artifacts (e.g., a high noise floor) in simulations. It is therefore desirable to approximate the  $C/V$  plot by a well-behaved

function. The hyperbolic tangent proves useful here for both its saturating behavior and its continuous derivatives. Noting that  $\tanh(\pm\infty) = \pm 1$ , we approximate the characteristic of Fig. 7.70(d) by

$$C_{var}(V_{GS}) = \frac{C_{max} - C_{min}}{2} \tanh\left(a + \frac{V_{GS}}{V_0}\right) + \frac{C_{max} + C_{min}}{2}. \quad (7.110)$$

Here,  $a$  and  $V_0$  allow fitting for the intercept and the slope, respectively, and  $C_{min}$  and  $C_{max}$  include the gate-drain and gate-source overlap capacitance.

The above varactor model translates to different characteristics in different circuit simulators! For example, HSPICE predicts a narrower oscillator tuning range than Cadence does. Simulation tools that analyze circuits in terms of voltages and currents (e.g., HSPICE) interpret the nonlinear capacitance equation correctly. On the other hand, programs that represent the behavior of capacitors by *charge equations* (e.g., Cadence’s Spectre) require that the model be transformed to a  $Q/V$  relationship. To this end, we recall the general definition of capacitance from  $dQ = C(V)dV$  and write


$$Q_{var} = \int C_{var} dV_{GS} \quad (7.111)$$

$$= \frac{C_{max} - C_{min}}{2} V_0 \ln \left[ \cosh \left( a + \frac{V_{GS}}{V_0} \right) \right] + \frac{C_{max} + C_{min}}{2} V_{GS}. \quad (7.112)$$

In other words, the varactor is represented as a two-terminal device whose charge and voltage are related by Eq. (7.112). The simulation tool then computes the current flowing through the varactor as

$$I_{var} = \frac{dQ_{var}}{dt}. \quad (7.113)$$

The  $Q$  of MOS varactors is determined by the resistance between the source and drain terminals.<sup>16</sup> As shown in Fig. 7.71(a), this resistance and the capacitance are distributed from the source to the drain and can be approximated by the lumped model depicted in Fig. 7.71(b).

 

**Figure 7.71** (a) Effect of distributed resistance in a varactor, (b) lumped model.

16. We assume that the gate resistance is minimized by proper layout.

## Example 7.33

Determine the equivalent resistance and capacitance values in the lumped model of Fig. 7.71(b).

 


Figure 7.72 (a) Distributed model of a varactor, (b) equivalent circuit for half of the structure, (c) canonical T-line structure.

## Solution:

Let us first consider only one-half of the structure as shown in Fig. 7.72(a). Here, the unit capacitances add up to the total distributed capacitance,  $C_{tot}$ , and the unit resistances to the total distributed resistance,  $R_{tot}$ . We turn the circuit upside down, arriving at the more familiar topology illustrated in Fig. 7.72(b). The circuit now resembles a transmission line consisting of series resistances and parallel capacitances. For the general T-line shown in Fig. 7.72(c), it can be proved that the input impedance,  $Z_{in}$ , is given by [18]

$$Z_{in} = \sqrt{\frac{Z_1}{Y_1}} \frac{1}{\tanh(\sqrt{Z_1 Y_1} d)}, \quad (7.114)$$

where  $Z_1$  and  $Y_1$  are specified for unit length and  $d$  is the length of the line. From Fig. 7.72(b),  $Z_1 d = R_{tot}$  and  $Y_1 d = C_{tot} s$ ; thus,

$$Z_{in} = \sqrt{\frac{R_{tot}}{C_{tot} s}} \frac{1}{\tanh(\sqrt{R_{tot} C_{tot} s/4})}. \quad (7.115)$$

At frequencies well below  $1/(R_{tot} C_{tot}/4)$ , the argument of  $\tanh$  is much less than unity, allowing the approximation,

$$\tanh \epsilon \approx \epsilon - \frac{\epsilon^3}{3} \quad (7.116)$$

$$\approx \frac{\epsilon}{1 + \frac{\epsilon^2}{3}} \quad (7.117)$$

## Example 7.33 (Continued)

It follows that

$$Z_{in} \approx \frac{1}{C_{tot} s/2} + \frac{R_{tot}/2}{3}. \quad (7.118)$$

That is, the lumped model of half of the structure consists of its distributed capacitance in series with one-third of its distributed resistance. Accounting for the gray half in Fig. 7.72(b), we obtain

$$Z_{in,tot} \approx \frac{1}{C_{tot} s} + \frac{R_{tot}}{12}. \quad (7.119)$$

The principal difficulty in computing the  $Q$  of MOS varactors (placed inside an  $n$ -well) is that the resistance between the source and drain cannot be directly computed from the MOS transistor characteristics. As with  $pn$  junctions, the  $Q$  of MOS varactors is usually obtained from experimental measurements.

How does the  $Q$  of MOS varactors vary with the capacitance? In the characteristic of Fig. 7.70(d), as we begin from  $C_{min}$ , the capacitance is small and the resistance somewhat large (that of  $n$ -well). On the other hand, as we approach  $C_{max}$ , the capacitance rises and the resistance falls. Consequently, equation  $Q = 1/(RC\omega)$  suggests that the  $Q$  may remain relatively constant. In practice, however, the  $Q$  drops as  $C_{GS}$  goes from  $C_{min}$  to  $C_{max}$  (Fig. 7.73), indicating that the relative rise in the capacitance is greater than the relative fall in the resistance.

 


Figure 7.73 Variation of varactor  $Q$  with capacitance.

As explained in Chapter 8, it is desirable to maximize the  $Q$  of varactors for oscillator design. From our foregoing study of MOS varactors, we conclude that the device length (the distance between the source and drain) must be minimized. Unfortunately, for a minimum channel length, the overlap capacitance between the gate and source/drain terminals becomes a substantial fraction of the overall capacitance, limiting the capacitance range. As illustrated in Fig. 7.74, the overlap capacitance (which is relatively voltage-independent) shifts the  $C/V$  characteristic up, yielding a ratio of  $(C_{max} + 2WC_{ov})/(C_{min} + 2WC_{ov})$ , where  $C_{max}$  and  $C_{min}$  denote the “intrinsic” values, i.e., those without the overlap effect. For a minimum channel length,  $2WC_{ov}$  may even be larger than  $C_{min}$ , thus reducing the capacitance ratio considerably.

 


Figure 7.74 Effect of overlap capacitance on varactor capacitance range.

### Example 7.34

A MOS varactor realized in 65-nm technology has an effective length of 50 nm and a  $C_{ov}$  of  $0.09 \text{ fF}/\mu\text{m}$ . If  $C_{ox} = 17 \text{ fF}/\mu\text{m}^2$ , determine the largest capacitance range that the varactor can provide.

#### Solution:

Assuming a width of  $1 \mu\text{m}$  for the device, we have  $2WC_{ov} = 0.18 \text{ fF}$  and a gate oxide capacitance of  $17 \text{ fF}/\mu\text{m}^2 \times 1 \mu\text{m} \times 50 \text{ nm} = 0.85 \text{ fF}$ . Thus, the minimum capacitance is  $0.18 \text{ fF}$  (if the series combination of the oxide and depletion capacitances is neglected), and the maximum capacitance reaches  $0.85 \text{ fF} + 0.18 \text{ fF} = 1.03 \text{ fF}$ . The largest possible capacitance ratio is therefore equal to  $5.72$ . In practice, the series combination of the oxide and depletion capacitances is comparable to  $2WC_{ov}$ , reducing this ratio to about  $2.5$ .

In order to achieve a larger capacitance range, the length of MOS varactors can be increased. In the above example, if the effective channel length grows to  $100 \text{ nm}$ , then the capacitance ratio reaches  $(1.7 \text{ fF} + 0.18 \text{ fF})/(0.18 \text{ fF}) = 10.4$ . However, the larger source-drain resistance results in a lower  $Q$ . Since the maximum capacitance goes from  $1.03 \text{ fF}$  to  $1.88 \text{ fF}$  and since the channel resistance is doubled, the  $Q$  [ $= 1/(RC\omega)$ ] falls by a factor of  $3.65$ . In other words, an  $m$ -fold increase in the channel length translates to roughly an  $m^2$ -fold drop in the  $Q$ .

The trade-off between the capacitance range and  $Q$  of varactors ultimately leads to another between the tuning range and phase noise of LC VCOs. We study this issue in Chapter 8. At frequencies up to about  $10 \text{ GHz}$ , a channel length of twice the minimum may be chosen so as to widen the capacitance range while retaining a varactor  $Q$  much larger than the inductor  $Q$ .

## 7.6 CONSTANT CAPACITORS

RF circuits employ constant capacitors for various purposes, e.g., (1) to adjust the resonance frequency of LC tanks, (2) to provide ac coupling between stages, or (3) to bypass the supply rail to ground. The critical parameters of capacitors used in RF ICs include the

capacitance density (the amount of capacitance per unit area on the chip), the parasitic capacitances, and the  $Q$ .

### 7.6.1 MOS Capacitors

MOSFETs configured as capacitors offer the highest density in integrated circuits because  $C_{ox}$  is larger than other capacitances in CMOS processes. However, the use of MOS capacitors entails two issues. First, to provide the maximum capacitance, the device requires a  $V_{GS}$  higher than the threshold voltage (Fig. 7.69). A similar “bias” requirement applies to MOS varactors if they are to provide maximum capacitance. Second, the channel resistance limits the  $Q$  of MOS capacitors at high frequencies. From Eq. (7.119), we note that the channel resistance is divided by 12 in the lumped model, yielding

$$Q = \frac{12}{R_{tot}C_{tot}\omega}. \quad (7.120)$$

Both of the above issues make MOS capacitors a poor choice for interstage coupling. Depicted in Fig. 7.75(a) is an example, wherein  $M_3$  sustains a bias gate-source voltage approximately equal to  $V_{DD} - V_{GS2}$  (why?). With typical values of  $V_{DD} = 1 \text{ V}$  and  $V_{GS2} = 0.5 \text{ V}$ ,  $M_3$  suffers from a small overdrive voltage and hence a high channel resistance. Moreover, the nonlinearity of the capacitance of  $M_3$  may manifest itself if the circuit senses large interferers. For these reasons, MOS capacitors rarely serve as coupling devices.

 


Figure 7.75 MOS capacitor used as (a) coupling device (b) bypass component.

One application of MOS capacitors is in supply bypass. As illustrated in Fig. 7.75(b), the supply line may include significant bond wire inductance, allowing *feedback* from the second stage to the first at high frequencies. The bypass capacitor,  $M_3$ , creates a low impedance between the supply and the ground, suppressing the feedback. In this case, the  $Q$  of  $M_3$  is still important: if the equivalent series resistance of the device becomes comparable with the reactance of its capacitance, then the bypass impedance may not be low enough to suppress the feedback.

It is important to note that typical MOS models fail to include the channel resistance,  $R_{on}$ , if the source and the drain are shorted. As illustrated in Fig. 7.75(b) for  $M_3$ ,  $R_{on3}$  is represented as a single lumped component between the two terminals and simply “shorted out” by circuit simulators. For this reason, the designer must compute  $R_{on}$  from I/V characteristics, divide it by 12, and insert the result in series with the MOS capacitor.

## Example 7.35

A MOS capacitor can be constructed as a single transistor of length  $L$  [Fig. 7.76(a)] or  $N$  transistors in parallel, each of length  $L/N$ . Compare the  $Q$ 's of the two structures. For simplicity, assume the effective channel lengths are equal to  $L$  and  $L/N$ , respectively.

## Solution:

The structure of Fig. 7.76(a) exhibits a channel resistance of

$$R_{on,a} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})} \quad (7.121)$$

and each finger in Fig. 7.76(b) a channel resistance of

$$R_{on,u} = \frac{1}{\mu_n C_{ox} \frac{W}{L/N} (V_{GS} - V_{TH})} \quad (7.122)$$

Since  $N$  fingers appear in parallel,  $R_{on,b} = R_{on,u}/N = R_{on,a}/N^2$ . That is, the decomposition of the device into  $N$  parallel fingers reduces the resistance by a factor of  $N^2$ .

 


Figure 7.76 MOS capacitor realized as (a) one long finger, (b) multiple short fingers.

For frequencies up to a few tens of gigahertz, the above decomposition can yield reasonable  $Q$ 's (e.g., 5 to 10), allowing the use of MOS capacitors for supply bypass.

The reader is cautioned that very large MOS capacitors suffer from significant gate leakage current, especially with a  $V_{GS}$  as high as  $V_{DD}$ . This current manifests itself if the system must enter a low-power (standby) mode: the leakage persists as long as  $V_{DD}$  is applied, draining the battery.

 


Figure 7.77 Parallel-plate capacitor.

## 7.6.2 Metal-Plate Capacitors

If the  $Q$  or linearity of MOS capacitors is inadequate, metal-plate capacitors can be used instead. The “parallel-plate” structure employs planes in different metal layers as shown in Fig. 7.77. For maximum capacitance density, all metal layers (and even the poly layer) can be utilized.

## Example 7.36

Show the actual connections necessary among the metal layers shown in Fig. 7.77.

## Solution:

The even-numbered metal layers must be tied to one another and so must the odd-numbered layers. As shown in Figure 7.78, these connections are made by vias. In practice, a row of vias (into the page) is necessary to connect the layers so as to obtain a small series resistance.

 


Figure 7.78 Detailed realization of parallel-plate capacitor.

The  $Q$  and linearity of well-designed parallel-plate capacitors are typically so high that they need not be taken into account. However, even with all metal layers and a poly

layer, parallel-plate structures achieve less capacitance density than MOSFETs do. For example, with nine metal layers in 65-nm technology, the former provides a density of about  $1.4 \text{ fF}/\mu\text{m}^2$  and the latter,  $17 \text{ fF}/\mu\text{m}^2$ .

Parallel-plate geometries also suffer from a parasitic capacitance to the substrate. As illustrated in Fig. 7.79, the capacitance between the lowest plate and the substrate,  $C_p$ , divided by the desired capacitance,  $C_{AB} = C_1 + \dots + C_9$ , represents the severity of this parasitic. In a typical process, this value reaches 10%, leading to serious difficulties in circuit design.

 


Figure 7.79 Bottom-plate parasitic capacitance.

### Example 7.37

We wish to employ capacitive coupling at the input of a stage that has an input capacitance of  $C_{in}$  (Fig. 7.80). Determine the additional input capacitance resulting from the coupling capacitor. Assume  $C_p = 0.1C_c$ .

 


Figure 7.80 Choice of input coupling capacitance value.

### Solution:

To minimize signal attenuation,  $C_c$  must be much greater than  $C_{in}$ , e.g.,  $C_c \approx 5C_{in}$ . Thus,  $C_p = 0.5C_{in}$ , yielding

$$C'_{in} = \frac{C_c C_{in}}{C_c + C_{in}} + 0.5C_{in} \quad (7.123)$$

$$= \frac{4}{3}C_{in}. \quad (7.124)$$

That is, the input capacitance is raised by more than 30%.

 


Figure 7.81 Fringe capacitor structure.

To alleviate the above issue, only a few top metal layers can be utilized. For example, a structure consisting of metal 9 through metal 4 has a density of  $660 \text{ aF}/\mu\text{m}^2$  and a parasitic of  $18 \text{ aF}/\mu\text{m}^2$ , i.e., 2.7%. Of course, the lower density translates to a larger area and more complex routing of signals.

An alternative geometry utilizes the lateral electric field between adjacent metal lines to achieve a high capacitance density. Illustrated in Fig. 7.81, this “fringe” capacitor consists of narrow metal lines with the minimum allowable spacing. This structure is described in Chapter 8.

## REFERENCES

- [1] J. Craninckx and M. S. J. Steyaert, “A 1.8 GHz CMOS Low Phase Noise Voltage-Controlled Oscillator with Prescaler,” *IEEE Journal of Solid-State Circuits*, vol. 30, pp. 1474–1482, Dec. 1995.
- [2] S. Jenei, B. K. J. C. Nauwelaers, and S. Decoutere, “Physics-Based Closed-Form Inductance Expressions for Compact Modeling of Integrated Spiral Inductors,” *IEEE Journal of Solid-State Circuits*, vol. 37, pp. 77–80, Jan. 2002.
- [3] S. S. Mohan et al., “Simple Accurate Expressions for Planar Spiral Inductances,” *IEEE J. Solid-State Circuits*, vol. 34, pp. 1419–1424, Oct. 1999.
- [4] A. Niknejad and R. G. Meyer, “Analysis, Design, and Optimization of Spiral Inductors and Transformers for Si RF ICs,” *IEEE J. Solid-State Circuits*, vol. 33, pp. 1470–1481, Oct. 1998.
- [5] M. Kraemer, D. Dragomirescu, and R. Plana, “Accurate Electromagnetic Simulation and Measurement of Millimeter-Wave Inductors in Bulk CMOS Technology,” *IEEE Topical Meeting on Silicon Monolithic Integrated Circuits in RF Systems*, pp. 61–64, Jan. 2010.
- [6] A. Zolfaghari, A. Y. Chan, and B. Razavi, “Stacked Inductors and 1-to-2 Transformers in CMOS Technology,” *IEEE Journal of Solid-State Circuits*, vol. 36, pp. 620–628, April 2001.
- [7] W. B. Kuhn, “Approximate Analytical Modeling of Current Crowding Effects in Multi-Turn Spiral Inductors,” *IEEE RFIC Symp. Dig. Tech. Papers*, pp. 271–274, June 2000.
- [8] W. B. Kuhn and N. M. Ibrahim, “Analysis of Current Crowding Effects in Multiturn Spiral Inductors,” *IEEE Tran. MTT*, vol. 49, pp. 31–39, Jan. 2001.
- [9] C. S. Yen, Z. Fazarinc, and R. Wheeler, “Time-Domain Skin-Effect Model for Transient Analysis of Lossy Transmission Lines,” *Proc. of IEEE*, vol. 70, pp. 750–757, July 1982.
- [10] Y. Cao et al., “Frequency-Independent Equivalent Circuit Model of On-Chip Spiral Inductors,” *Proc. CICC*, pp. 217–220, May 2002.
- [11] M. Danesh et al., “A Q-Factor Enhancement Technique for MMIC Inductors,” *Proc. IEEE Radio Frequency Integrated Circuits Symp.*, pp. 217–220, April 1998.
- [12] N. M. Neihart et al., “Twisted Inductors for Low Coupling Mixed-signal and RF Applications,” *Proc. CICC*, pp. 575–578, Sept. 2008.

- [13] C. P. Yue and S. S. Wong, "On-Chip Spiral Inductors with Patterned Ground Shields for Si-Based RF ICs," *IEEE J. Solid-State Circuits*, vol. 33, pp. 743–751, May 1998.
- [14] S.-M. Yim, T. Chen, and K. K. O, "The Effects of a Ground Shield on the Characteristics and Performance of Spiral Inductors," *IEEE J. Solid-State Circuits*, vol. 37, pp. 237–245, Feb. 2002.
- [15] Y. E. Chen et al., "Q-Enhancement of Spiral Inductor with  $N^+$ -Diffusion Patterned Ground Shields," *IEEE MTT Symp. Dig. Tech. Papers*, pp. 1289–1292, 2001.
- [16] J. R. Long, "Monolithic Transformers for Silicon RF IC Design," *IEEE J. Solid-State Circuits*, vol. 35, pp. 1368–1383, Sept. 2000.
- [17] J. R. Long and M. A. Copeland, "The Modeling, Characterization, and Design of Monolithic Inductors for Silicon RF ICs," *IEEE J. Solid-State Circuits*, vol. 32, pp. 357–369, March 1997.
- [18] S. Ramo, J. R. Whinnery, and T. Van Duzer, *Fields and Waves in Communication Electronics*, Third Edition, New York: Wiley, 1994.

## PROBLEMS

- 7.1. Extend Eq. (7.1) to an  $N$ -turn spiral and show that  $L_{tot}$  contains  $N(N + 1)/2$  terms.
- 7.2. Prove that the  $Q$  of the circuit shown in Fig. 7.32(a) is given by Eq. (7.62).
- 7.3. Prove that for an  $N$ -turn spiral inductor, the equivalent interwinding capacitance is given by
- $$C_{eq} = \frac{C_1 + \cdots + C_{N^2-1}}{(N^2 - 1)^2}. \quad (7.125)$$
- 7.4. Using Eq. (7.62), compare the  $Q$ 's of the circuits shown in Figs. 7.37(b) and (d).
- 7.5. Consider the magnetic fields produced by the inductors in Fig. 7.41. Which topology creates less net magnetic field at a point far from the circuit but on its line of symmetry?
- 7.6. Repeat Example 7.13 for a 5-nH inductor using a linewidth of 5  $\mu\text{m}$ , a line spacing of 0.5  $\mu\text{m}$ , and four turns. Do the results depend much on the outer diameter?
- 7.7. For the circuit of Fig. 7.28(a), compute  $Y_{11}$  and find the parallel equivalent resistance. Is the result the same as that shown in Eq. (7.55)?
- 7.8. Repeat Example 7.19 for four turns. Is it possible to find an expression for  $N$  turns?
- 7.9. Find the input impedance,  $Z_{in}$ , in Fig. 7.50.
- 7.10. Using the capacitance data in Table 7.1, repeat Example 7.25 for an inductor realized as a stack of four metal layers. Assume the inductance is about 3.5 times that of one spiral.
- 7.11. Suppose an LC VCO (Chapter 8) employs  $pn$ -junction varactors. Determine the bounds on the control voltage and the output swings if the varactors must remain reverse-biased.

## CHAPTER

# 8

## OSCILLATORS

In our study of RF transceivers in Chapter 4, we noted the extensive use of oscillators in both the transmit and receive paths. Interestingly, in most systems, one input of every mixer is driven by a periodic signal, hence the need for oscillators. This chapter deals with the analysis and design of oscillators. The outline is shown below.

| General Principles  | Voltage-Controlled Oscillators   | Phase Noise   | Quadrature VCOs  |
|---|--|---|--|
| <ul style="list-style-type: none"> <li>■ Feedback View</li> <li>■ One-Port View</li> <li>■ Cross-Coupled Oscillator</li> <li>■ Three-Point Oscillators</li> </ul> | <ul style="list-style-type: none"> <li>■ Tuning Limitations</li> <li>■ Effect of Varactor <math>Q</math></li> <li>■ VCOs with Wide Tuning Range</li> </ul> | <ul style="list-style-type: none"> <li>■ Effect of Phase Noise</li> <li>■ Analysis Approach I</li> <li>■ Analysis Approach II</li> <li>■ Noise of Bias Current</li> <li>■ VCO Design Procedure</li> <li>■ Low-Noise VCOs</li> </ul> | <ul style="list-style-type: none"> <li>■ Coupling into an Oscillator</li> <li>■ Basic Topology</li> <li>■ Properties of Quadrature Oscillators</li> <li>■ Improved Topologies</li> </ul> |

### 8.1 PERFORMANCE PARAMETERS

An oscillator used in an RF transceiver must satisfy two sets of requirements: (1) system specifications, e.g., the frequency of operation and the "purity" of the output, and (2) "interface" specifications, e.g., drive capability or output swing. In this section, we study the oscillator performance parameters and their role in the overall system.

**Frequency Range** An RF oscillator must be designed such that its frequency can be varied (tuned) across a certain range. This range includes two components: (1) the system specification; for example, a 900-MHz GSM direct-conversion receiver may tune the LO from 935 MHz to 960 MHz; (2) additional margin to cover process and temperature variations and errors due to modeling inaccuracies. The latter component typically amounts to several percent.