

## Chapter 2, Solution 1

$$v = iR \quad i = v/R = (16/5) \text{ mA} = \underline{\mathbf{3.2 \text{ mA}}}$$

## Chapter 2, Solution 2

$$p = v^2/R \rightarrow R = v^2/p = 14400/60 = \underline{\mathbf{240 \text{ ohms}}}$$

## Chapter 2, Solution 3

$$R = v/i = 120/(2.5 \times 10^{-3}) = \underline{\mathbf{48k \text{ ohms}}}$$

## Chapter 2, Solution 4

- (a)  $i = 3/100 = \underline{\mathbf{30 \text{ mA}}}$   
(b)  $i = 3/150 = \underline{\mathbf{20 \text{ mA}}}$

## Chapter 2, Solution 5


$$n = 9; l = 7; b = n + l - 1 = \underline{\mathbf{15}}$$

## Chapter 2, Solution 6


$$n = 12; l = 8; b = n + l - 1 = \underline{\mathbf{19}}$$
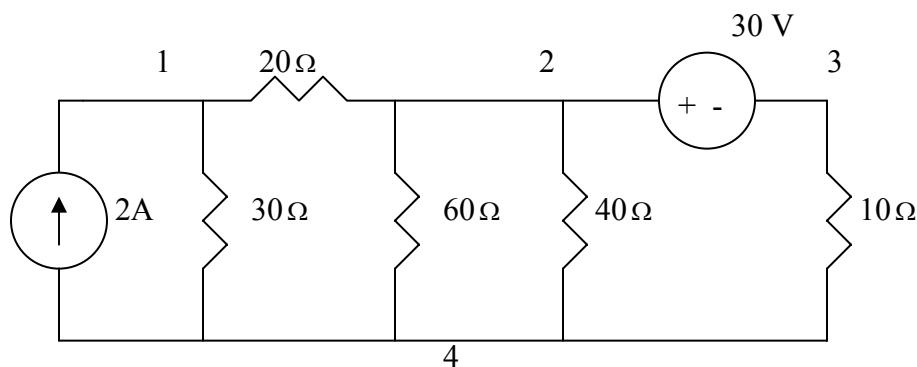
## Chapter 2, Solution 7

7 elements or 7 branches and 4 nodes, as indicated.



## Chapter 2, Solution 8

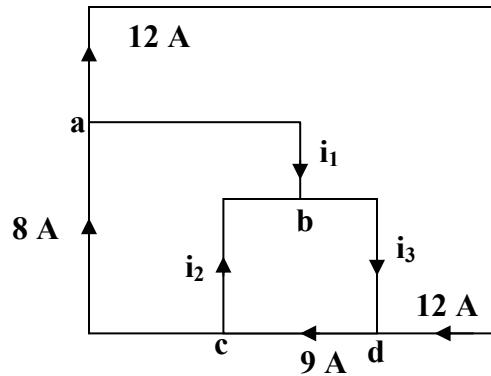


$$\begin{aligned} \text{At node } a, \quad 8 &= 12 + i_1 \longrightarrow i_1 = -4A \\ \text{At node } c, \quad 9 &= 8 + i_2 \longrightarrow i_2 = 1A \\ \text{At node } d, \quad 9 &= 12 + i_3 \longrightarrow i_3 = -3A \end{aligned}$$

## Chapter 2, Solution 9

Applying KCL,

$$\begin{aligned} i_1 + 1 &= 10 + 2 \longrightarrow i_1 = 11A \\ 1 + i_2 &= 2 + 3 \longrightarrow i_2 = 4A \\ i_2 &= i_3 + 3 \qquad \qquad i_3 = 1A \end{aligned}$$

## Chapter 2, Solution 10

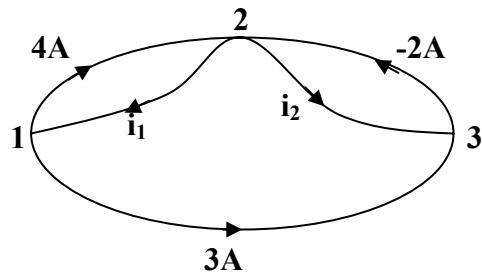


$$\begin{aligned} \text{At node } 1, \quad 4 + 3 &= i_1 \longrightarrow i_1 = 7A \\ \text{At node } 3, \quad 3 + i_2 &= -2 \longrightarrow i_2 = -5A \end{aligned}$$

## Chapter 2, Solution 11

Applying KVL to each loop gives

$$\begin{aligned} -8 + v_1 + 12 &= 0 \longrightarrow v_1 = 4v \\ -12 - v_2 + 6 &= 0 \longrightarrow v_2 = -6v \\ 10 - 6 - v_3 &= 0 \longrightarrow v_3 = 4v \\ -v_4 + 8 - 10 &= 0 \quad \text{---} \quad v_4 = -2v \end{aligned}$$

## Chapter 2, Solution 12

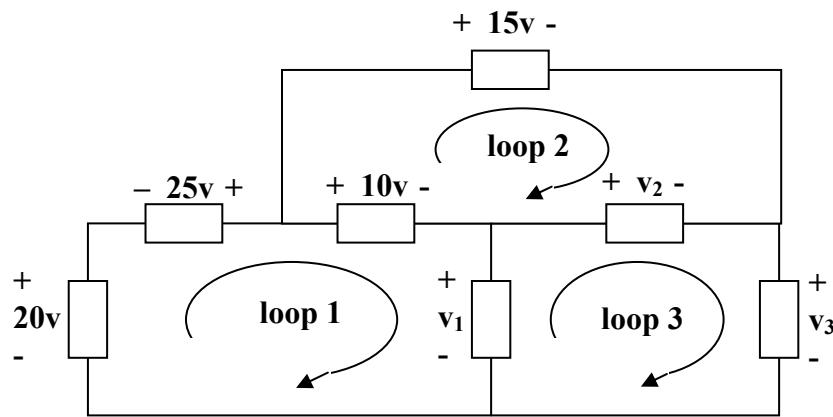


$$\text{For loop 1, } -20 - 25 + 10 + v_1 = 0 \longrightarrow v_1 = 35v$$

$$\text{For loop 2, } -10 + 15 - v_2 = 0 \longrightarrow v_2 = 5v$$

$$\text{For loop 3, } -v_1 + v_2 + v_3 = 0 \longrightarrow v_3 = 30v$$

## Chapter 2, Solution 13

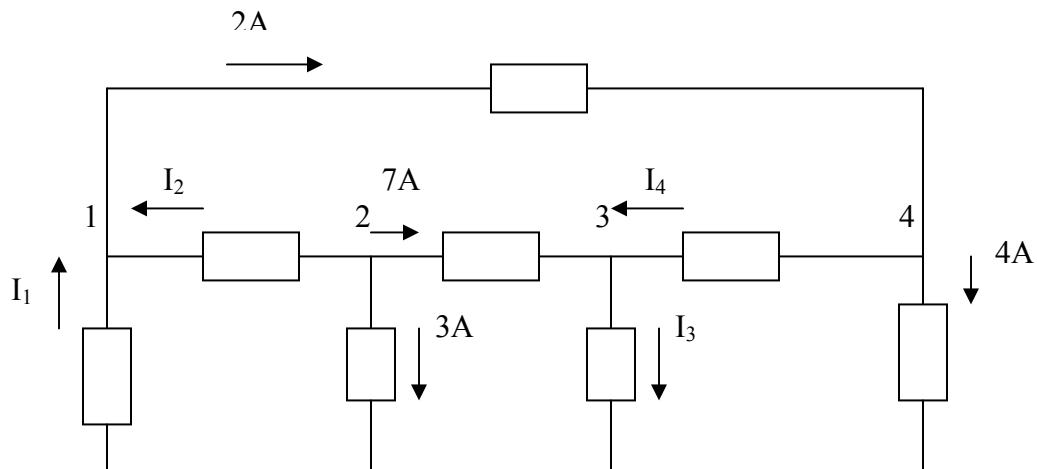

At node 2,

$$3 + 7 + I_2 = 0 \longrightarrow I_2 = -10 A$$

At node 1,

$$I_1 + I_2 = 2 \longrightarrow I_1 = 2 - I_2 = 12 A$$

At node 4,

$$2 = I_4 + 4 \longrightarrow I_4 = 2 - 4 = -2 A$$


At node 3,

$$7 + I_4 = I_3 \longrightarrow I_3 = 7 - 2 = 5 A$$

Hence,

$$\underline{I_1 = 12 A, \quad I_2 = -10 A, \quad I_3 = 5 A, \quad I_4 = -2 A}$$

## Chapter 2, Solution 14

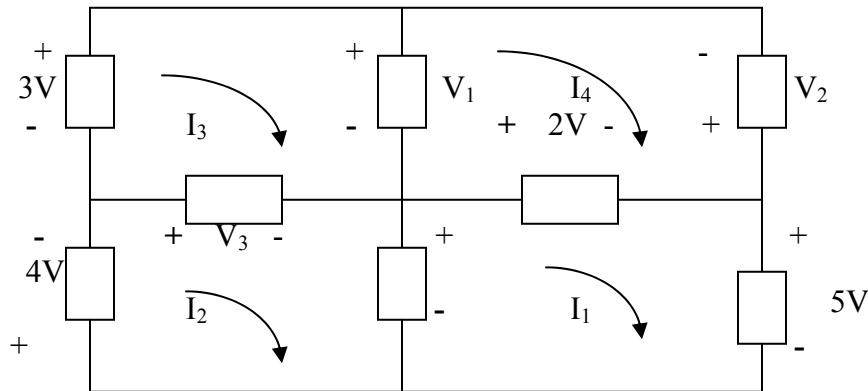

For mesh 1,

$$-V_4 + 2 + 5 = 0 \longrightarrow V_4 = 7 V$$

For mesh 2,

$$+4 + V_3 + V_4 = 0 \longrightarrow V_3 = -4 - 7 = -11 V$$

For mesh 3,

$$-3 + V_1 - V_3 = 0 \longrightarrow V_1 = V_3 + 3 = -8 V$$


For mesh 4,

$$-V_1 - V_2 - 2 = 0 \longrightarrow V_2 = -V_1 - 2 = 6 V$$

Thus,

$$\underline{V_1 = -8 V, \quad V_2 = 6 V, \quad V_3 = -11 V, \quad V_4 = 7 V}$$

## Chapter 2, Solution 15

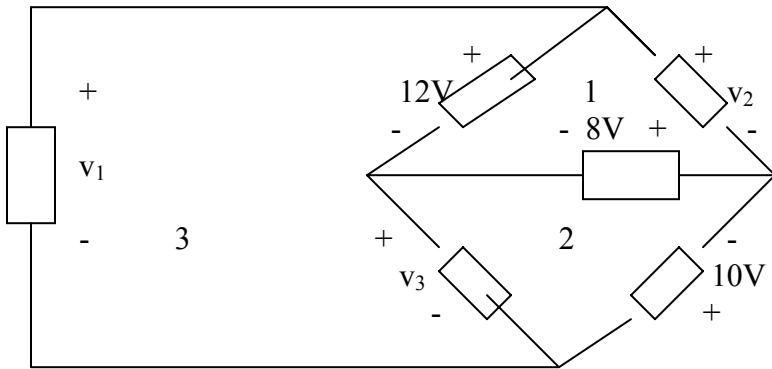

For loop 1,

$$8 - 12 + v_2 = 0 \longrightarrow v_2 = 4V$$

For loop 2,

$$-v_3 - 8 - 10 = 0 \longrightarrow v_3 = -18V$$


For loop 3,

$$-v_1 + 12 + v_3 = 0 \longrightarrow v_1 = -6V$$

Thus,

$$\underline{v_1 = -6V, \quad v_2 = 4V, \quad v_3 = -18V}$$

## Chapter 2, Solution 16

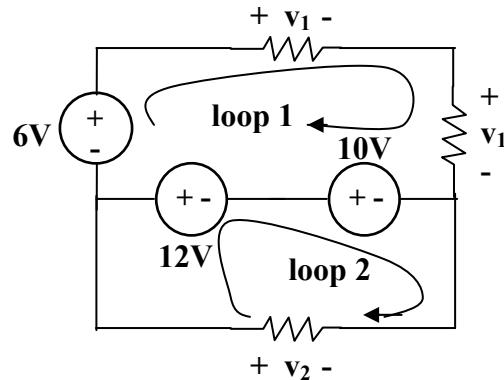


Applying KVL around loop 1,

$$-6 + v_1 + v_1 - 10 - 12 = 0 \longrightarrow v_1 = \underline{\mathbf{14V}}$$

Applying KVL around loop 2,

$$12 + 10 - v_2 = 0 \longrightarrow v_2 = \underline{\mathbf{22V}}$$

## Chapter 2, Solution 17

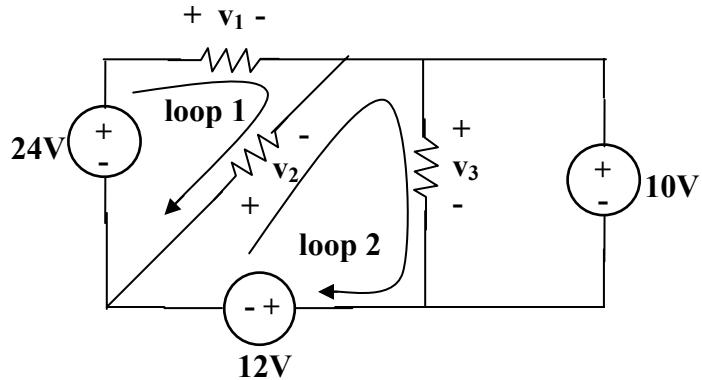

It is evident that  $v_3 = 10\text{V}$

Applying KVL to loop 2,

$$v_2 + v_3 + 12 = 0 \longrightarrow v_2 = -22\text{V}$$

Applying KVL to loop 1,

$$-24 + v_1 - v_2 = 0 \longrightarrow v_1 = 2\text{V}$$

Thus,

$$v_1 = \underline{\underline{2\text{V}}}, v_2 = \underline{\underline{-22\text{V}}}, v_3 = \underline{\underline{10\text{V}}}$$

## Chapter 2, Solution 18

Applying KVL,

$$-30 - 10 + 8 + I(3+5) = 0$$

$$8I = 32 \longrightarrow I = \underline{\underline{4\text{A}}}$$

$$-V_{ab} + 5I + 8 = 0 \longrightarrow V_{ab} = \underline{\underline{28\text{V}}}$$

## Chapter 2, Solution 19

Applying KVL around the loop, we obtain

$$-12 + 10 - (-8) + 3i = 0 \longrightarrow i = -2A$$

Power dissipated by the resistor:

$$p_{3\Omega} = i^2 R = 4(3) = 12W$$

Power supplied by the sources:

$$p_{12V} = 12 (- -2) = 24W$$

$$p_{10V} = 10 (-2) = -20W$$

$$p_{8V} = (- -2) = -16W$$

## Chapter 2, Solution 20

Applying KVL around the loop,

$$-36 + 4i_0 + 5i_0 = 0 \longrightarrow i_0 = 4A$$

## Chapter 2, Solution 21




Apply KVL to obtain

$$-45 + 10i - 3V_0 + 5i = 0$$


But  $v_0 = 10i$ ,

$$-45 + 15i - 30i = 0 \longrightarrow i = -3A$$

$$P_3 = i^2 R = 9 \times 5 = 45W$$

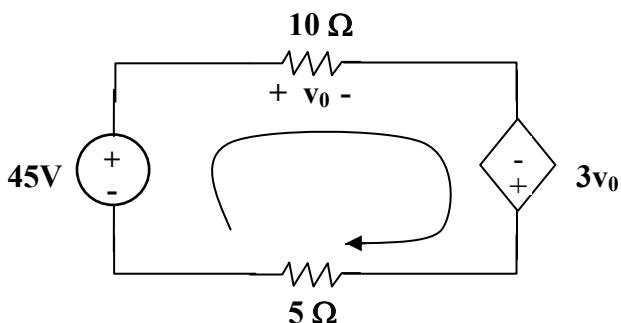

## Chapter 2, Solution 22

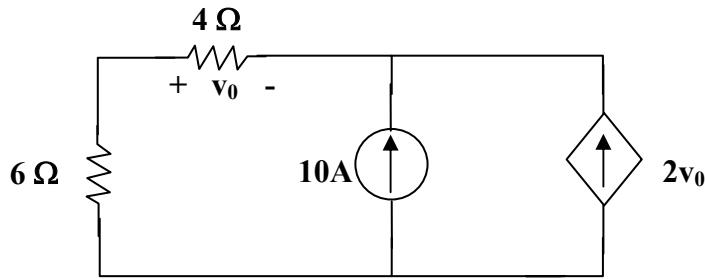

At the node, KCL requires that

$$\frac{v_0}{4} + 10 + 2v_0 = 0 \rightarrow v_0 = \underline{-4.444V}$$

The current through the controlled source is

$$i = 2V_0 = -8.888A$$

and the voltage across it is

$$v = (6 + 4) i_0 = 10 \frac{v_0}{4} = -11.111$$


Hence,

$$p_2 v_i = (-8.888)(-11.111) = \underline{98.75W}$$
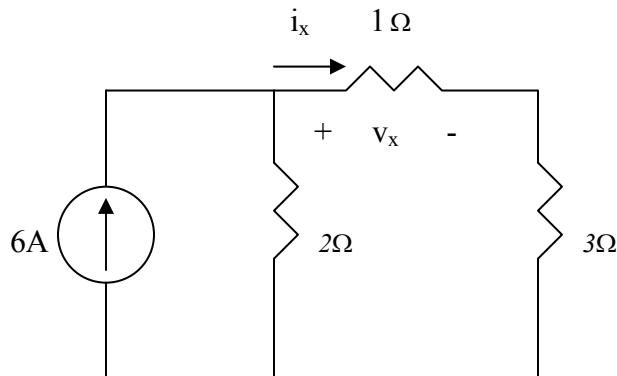
## Chapter 2, Solution 23

$$8//12 = 4.8, \quad 3//6 = 2, \quad (4+2)/(1.2+4.8) = 6//6 = 3$$

The circuit is reduced to that shown below.



Applying current division,

$$i_x = \frac{2}{2+1+3}(6A) = 2A, \quad v_x = li_x = 2V$$

The current through the  $1.2\text{-}\Omega$  resistor is  $0.5i_x = 1A$ . The voltage across the  $12\text{-}\Omega$  resistor is  $1 \times 4.8 = 4.8$  V. Hence the power is

$$P = \frac{v^2}{R} = \frac{4.8^2}{12} = \underline{1.92W}$$

## Chapter 2, Solution 24

$$(a) \quad I_0 = \frac{V_s}{R_1 + R_2}$$

$$V_0 = -\alpha I_0 (R_3 \| R_4) = -\frac{\alpha V_0}{R_1 + R_2} \cdot \frac{R_3 R_4}{R_3 + R_4}$$

$$\frac{V_0}{V_s} = \frac{-\alpha R_3 R_4}{(R_1 + R_2)(R_3 + R_4)}$$

$$(b) \quad \text{If } R_1 = R_2 = R_3 = R_4 = R,$$

$$\left| \frac{V_0}{V_s} \right| = \frac{\alpha}{2R} \cdot \frac{R}{2} = \frac{\alpha}{4} = 10 \longrightarrow \alpha = \underline{40}$$

## Chapter 2, Solution 25

$$V_0 = 5 \times 10^{-3} \times 10 \times 10^3 = 50V$$

Using current division,

$$I_{20} = \frac{5}{5+20}(0.01 \times 50) = \underline{0.1 A}$$

$$V_{20} = 20 \times 0.1 \text{ kV} = \underline{2 \text{ kV}}$$

$$P_{20} = I_{20} V_{20} = \underline{0.2 \text{ kW}}$$

## **Chapter 2, Solution 26**

$$V_0 = 5 \times 10^{-3} \times 10 \times 10^3 = 50V$$

Using current division,

$$I_{20} = \frac{5}{5+20}(0.01 \times 50) = \underline{\underline{0.1\text{ A}}}$$

$$V_{20} = 20 \times 0.1 \text{ kV} = \underline{\underline{2\text{ kV}}}$$

$$P_{20} = I_{20} V_{20} = \underline{\underline{0.2\text{ kW}}}$$

## **Chapter 2, Solution 27**

Using current division,

$$i_1 = \frac{4}{4+6}(20) = \underline{\underline{8\text{ A}}}$$

$$i_2 = \frac{6}{4+6}(20) = \underline{\underline{12\text{ A}}}$$

## **Chapter 2, Solution 28**

We first combine the two resistors in parallel

$$15 \parallel 10 = 6 \Omega$$

We now apply voltage division,

$$v_1 = \frac{14}{14+6}(40) = \underline{\underline{20\text{ V}}}$$

$$v_2 = v_3 = \frac{6}{14+6}(40) = 12 \text{ V}$$

Hence,  $v_1 = \underline{\underline{28\text{ V}}}, v_2 = \underline{\underline{12\text{ V}}}, v_s = \underline{\underline{12\text{ V}}}$

## Chapter 2, Solution 29


The series combination of  $6\ \Omega$  and  $3\ \Omega$  resistors is shorted. Hence

$$i_2 = 0 = v_2$$

$$v_1 = 12, i_1 = \frac{12}{4} = 3\ A$$

Hence  $v_1 = \underline{12\ V}$ ,  $i_1 = \underline{3\ A}$ ,  $i_2 = \underline{0} = v_2$

## Chapter 2, Solution 30

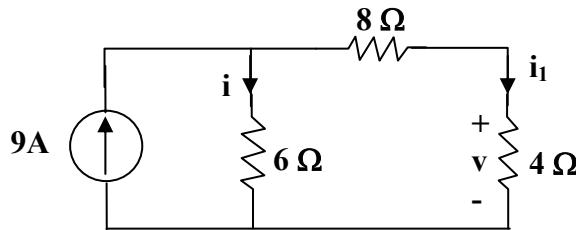

$$\text{By current division, } i = \frac{12}{6+12}(9) = \underline{6\ A}$$

$$i_1 = 9 - 6 = 3\ A, v = 4i_1 = 4 \times 3 = \underline{12\ V}$$

$$p_6 = i^2 R = 36 \times 6 = \underline{216\ W}$$

## Chapter 2, Solution 31

The  $5\ \Omega$  resistor is in series with the combination of  $10\parallel(4+6) = 5\Omega$ .

Hence by the voltage division principle,

$$v = \frac{5}{5+5}(20V) = \underline{10\ V}$$

by ohm's law,

$$i = \frac{v}{4+6} = \frac{10}{4+6} = \underline{1\ A}$$

$$p_p = i^2 R = (1)^2(4) = \underline{4\ W}$$

## Chapter 2, Solution 32

We first combine resistors in parallel.

$$20\parallel 30 = \frac{20 \times 30}{50} = 12 \Omega$$

$$10\parallel 40 = \frac{10 \times 40}{50} = 8 \Omega$$

Using current division principle,

$$i_1 + i_2 = \frac{8}{8+12}(20) = 8A, i_3 + i_4 = \frac{12}{20}(20) = 12A$$

$$i_1 = \frac{20}{50}(8) = \underline{\underline{3.2 A}}$$


$$i_2 = \frac{30}{50}(8) = \underline{\underline{4.8 A}}$$

$$i_3 = \frac{10}{50}(12) = \underline{\underline{2.4 A}}$$

$$i_4 = \frac{40}{50}(12) = \underline{\underline{9.6 A}}$$
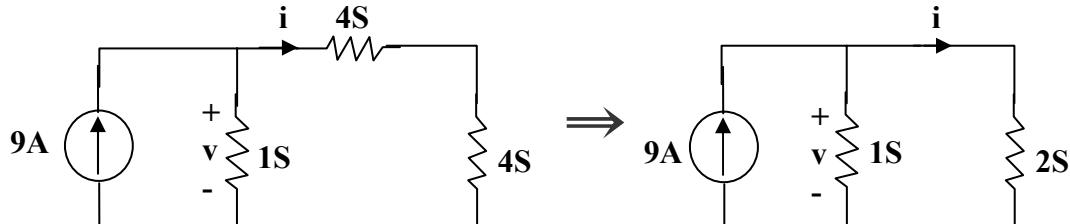
## Chapter 2, Solution 33

Combining the conductance leads to the equivalent circuit below



$$6S\parallel 3S = \frac{6 \times 3}{9} = 25 \text{ and } 25 + 25 = 4 S$$

Using current division,

$$i = \frac{1}{1 + \frac{1}{2}}(9) = \underline{\underline{6 A}}, v = 3(1) = \underline{\underline{3 V}}$$


### Chapter 2, Solution 34

By parallel and series combinations, the circuit is reduced to the one below:

$$10\parallel(2+13) = \frac{10 \times 15}{25} = 6\Omega$$



$$15\parallel(4+6) = \frac{15 \times 15}{25} = 6\Omega$$

$$12\parallel(6+6) = 6\Omega$$

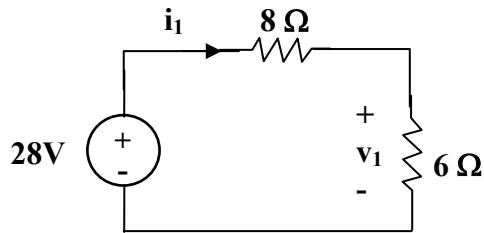

$$\text{Thus } i_1 = \frac{28}{8+6} = 2 \text{ A and } v_1 = 6i_1 = 12 \text{ V}$$

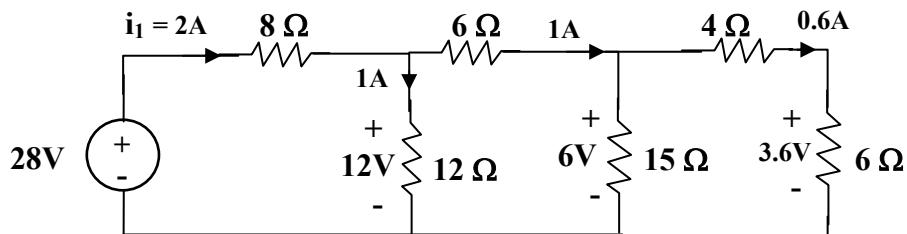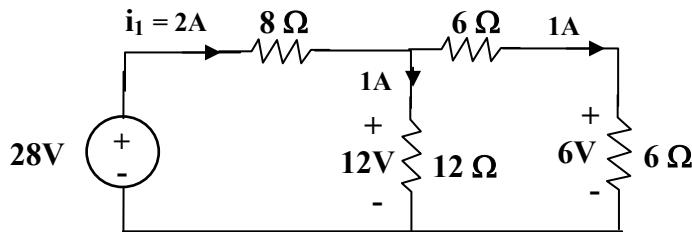We now work backward to get  $i_2$  and  $v_2$ .




$$\text{Thus, } v_2 = \frac{13}{15}(3 \cdot 6) = 3 \cdot 12, i_2 = \frac{v_2}{13} = 0.24$$

$$p_2 = i^2 R = (0.24)^2 (2) = 0.1152 \text{ W}$$

$$i_1 = \underline{\underline{2 \text{ A}}}, i_2 = \underline{\underline{0.24 \text{ A}}}, v_1 = \underline{\underline{12 \text{ V}}}, v_2 = \underline{\underline{3.12 \text{ V}}}, p_2 = \underline{\underline{0.1152 \text{ W}}}$$

### Chapter 2, Solution 35

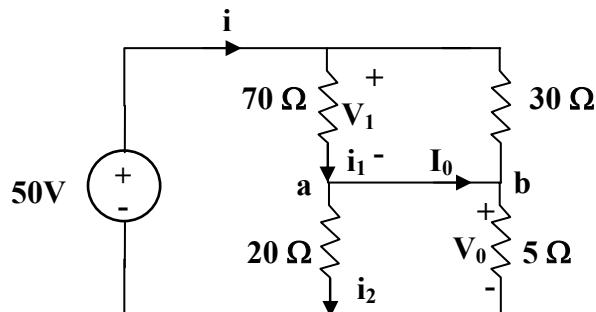

Combining the versions in parallel,

$$70\parallel 30 = \frac{70 \times 30}{100} = 21\Omega , \quad 20\parallel 15 = \frac{20 \times 5}{25} = 4\Omega$$

$$i = \frac{50}{21+4} = 2\text{ A}$$

$$v_i = 21i = 42\text{ V}, v_0 = 4i = 8\text{ V}$$

$$i_1 = \frac{v_1}{70} = 0.6\text{ A}, i_2 = \frac{v_2}{20} = 0.4\text{ A}$$

At node a, KCL must be satisfied

$$i_1 = i_2 + I_0 \longrightarrow 0.6 = 0.4 + I_0 \longrightarrow I_0 = 0.2\text{ A}$$

Hence  $v_0 = \underline{\underline{8\text{ V}}}$  and  $I_0 = \underline{\underline{0.2\text{ A}}}$

## Chapter 2, Solution 36

The  $8\Omega$  resistor is shorted. No current flows through the  $1\Omega$  resistor. Hence  $v_0$  is the voltage across the  $6\Omega$  resistor.

$$I_0 = \frac{4}{2+3\parallel 16} = \frac{4}{4} = 1\text{ A}$$

$$v_0 = I_0 (3\parallel 6) = 2I_0 = \underline{\underline{2\text{ V}}}$$

## Chapter 2, Solution 37

Let  $I$  = current through the  $16\Omega$  resistor. If  $4$  V is the voltage drop across the  $6\parallel R$  combination, then  $20 - 4 = 16$  V in the voltage drop across the  $16\Omega$  resistor.

Hence,  $I = \frac{16}{16} = 1$  A.

But  $I = \frac{20}{16 + 6\parallel R} \rightarrow 1$        $4 = 6\parallel R = \frac{6R}{6 + R}$        $R = \underline{\underline{12 \Omega}}$

## Chapter 2, Solution 38

Let  $I_0$  = current through the  $6\Omega$  resistor. Since  $6\Omega$  and  $3\Omega$  resistors are in parallel.

$$6I_0 = 2 \times 3 \rightarrow R_0 = 1 \text{ A}$$

The total current through the  $4\Omega$  resistor =  $1 + 2 = 3$  A.

Hence

$$v_s = (2 + 4 + 2\parallel 3)(3 \text{ A}) = \underline{\underline{24 \text{ V}}}$$

$$I = \frac{v_s}{10} = \underline{\underline{2.4 \text{ A}}}$$

## Chapter 2, Solution 39

(a)  $R_{eq} = R\parallel 0 = \underline{\underline{0}}$

(b)  $R_{eq} = R\parallel R + R\parallel R = \frac{R}{2} + \frac{R}{2} = \underline{\underline{R}}$

(c)  $R_{eq} = (R + R)\parallel(R + R) = 2R\parallel 2R = \underline{\underline{R}}$

(d)  $R_{eq} = 3R\parallel(R + R\parallel R) = 3R\parallel(R + \frac{1}{2}R)$   
 $= \frac{3Rx\frac{3}{2}R}{3R + \frac{3}{2}R} = \underline{\underline{R}}$

(e)  $R_{eq} = R\parallel 2R\parallel 3R = 3R\parallel \left(\frac{R \cdot 2R}{3R}\right)$

$$= 3R\parallel \frac{2}{3}R = \frac{3Rx\frac{2}{3}R}{3R + \frac{2}{3}R} = \underline{\underline{\frac{6}{11}R}}$$

## Chapter 2, Solution 40

$$R_{eq} = 3 + 4\parallel(2 + 6\parallel 3) = 3 + 2 = \underline{5\Omega}$$

$$I = \frac{10}{R_{eq}} = \frac{10}{5} = \underline{2\text{ A}}$$

## Chapter 2, Solution 41

Let  $R_0$  = combination of three  $12\Omega$  resistors in parallel

$$\frac{1}{R_0} = \frac{1}{12} + \frac{1}{12} + \frac{1}{12} \longrightarrow R_0 = 4$$

$$R_{eq} = 30 + 60\parallel(10 + R_0 + R) = 30 + 60\parallel(14 + R)$$

$$50 = 30 + \frac{60(14 + R)}{74 + R} \longrightarrow 74 + R = 42 + 3R$$

$$\text{or } R = \underline{16\Omega}$$

## Chapter 2, Solution 42

$$(a) \quad R_{ab} = 5\parallel(8 + 20\parallel 30) = 5\parallel(8 + 12) = \frac{5 \times 20}{25} = \underline{4\Omega}$$

$$(b) \quad R_{ab} = 2 + 4\parallel(5 + 3)\parallel 8 + 5\parallel 10\parallel(6 + 4) = 2 + 4\parallel 4 + 5\parallel 5 = 2 + 2 + 2.5 = \underline{6.5\Omega}$$

## Chapter 2, Solution 43

$$(a) \quad R_{ab} = 5\parallel 20 + 10\parallel 40 = \frac{5 \times 20}{25} + \frac{400}{50} = 4 + 8 = \underline{12\Omega}$$

$$(b) \quad 60\parallel 20\parallel 30 = \left( \frac{1}{60} + \frac{1}{20} + \frac{1}{30} \right)^{-1} = \frac{60}{6} = 10\Omega$$

$$R_{ab} = 80\parallel(10 + 10) = \frac{80 + 20}{100} = \underline{16\Omega}$$


## Chapter 2, Solution 44

(a) Convert T to Y and obtain

$$R_I = \frac{20 \times 20 + 20 \times 10 + 10 \times 20}{10} = \frac{800}{10} = 80\Omega$$

$$R_2 = \frac{800}{20} = 40\Omega = R_3$$

The circuit becomes that shown below.

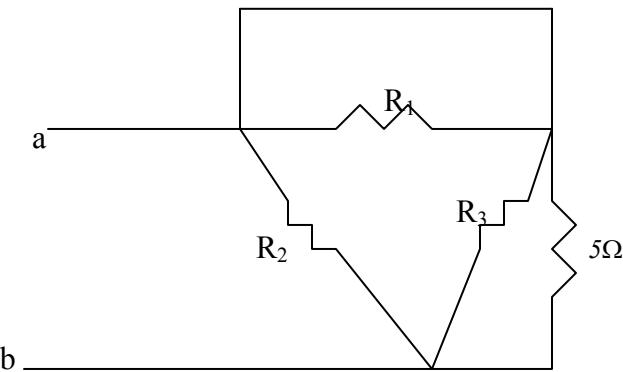

$$R_1//0 = 0, \quad R_3//5 = 40//5 = 4.444\Omega$$

$$R_{ab} = R_2 // (0 + 4.444) = 40 // 4.444 = 4\Omega$$


$$(b) 30//(20+50) = 30//70 = 21\Omega$$

Convert the T to Y and obtain

$$R_I = \frac{20 \times 10 + 10 \times 40 + 40 \times 20}{40} = \frac{1400}{40} = 35\Omega$$


$$R_2 = \frac{1400}{20} = 70\Omega, \quad R_3 = \frac{1400}{10} = 140\Omega$$

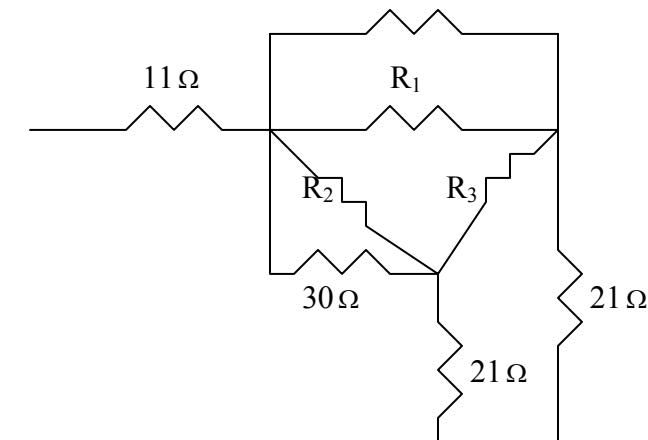The circuit is reduced to that shown below.




Combining the resistors in parallel

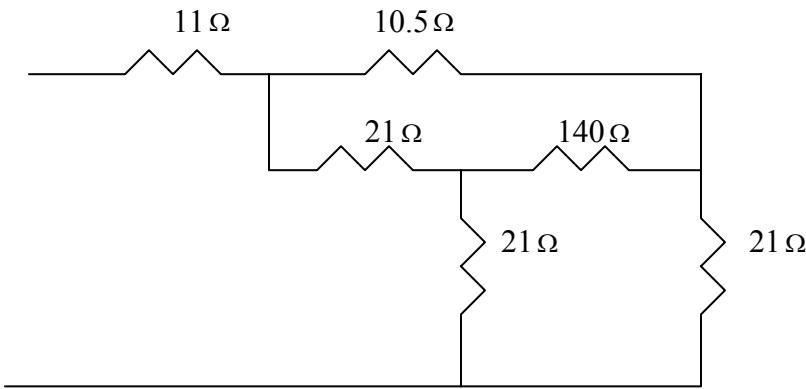$R_1//15 = 35//15 = 10.5$ ,  $30//R_2 = 30//70 = 21$   
leads to the circuit below.



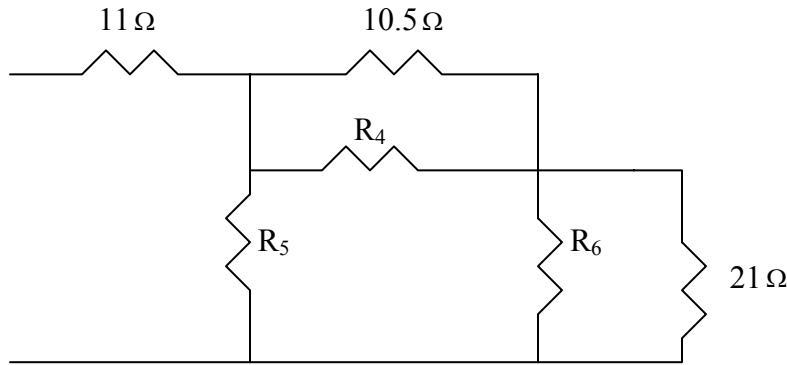Converting the T to Y leads to the circuit below.



$$R_4 = \frac{2I \times 140 + 140 \times 2I + 2I \times 2I}{2I} = \frac{632I}{2I} = 30I \Omega = R_6$$

$$R_5 = \frac{632I}{140} = 45.15$$

$$10.5//30I = 10.15, \quad 30I//21 = 19.63$$

$$R_5//(10.15 + 19.63) = 45.15//29.78 = 17.94$$

$$R_{ab} = 11 + 17.94 = \underline{28.94 \Omega}$$

### Chapter 2, Solution 45

$$(a) \quad 10//40 = 8, \quad 20//30 = 12, \quad 8//12 = 4.8$$

$$R_{ab} = 5 + 50 + 4.8 = \underline{59.8 \Omega}$$

(b) 12 and 60 ohm resistors are in parallel. Hence,  $12//60 = 10$  ohm. This 10 ohm and 20 ohm are in series to give 30 ohm. This is in parallel with 30 ohm to give  $30//30 = 15$  ohm. And  $25//(15+10) = 12.5$ . Thus

$$R_{ab} = 5 + 12.8 + 15 = \underline{32.5 \Omega}$$

### Chapter 2, Solution 46

$$(a) \quad R_{ab} = 30\parallel 70 + 40 + 60\parallel 20 = \frac{30 \times 70}{100} + 40 + \frac{60 + 20}{80}$$

$$= 21 + 40 + 15 = \underline{\mathbf{76 \Omega}}$$

(b) The 10- $\Omega$ , 50- $\Omega$ , 70- $\Omega$ , and 80- $\Omega$  resistors are shorted.

$$20\parallel 30 = \frac{20 \times 30}{50} = 12\Omega$$


$$40\parallel 60 = \frac{40 \times 60}{100} = 24$$

$$R_{ab} = 8 + 12 + 24 + 6 + 0 + 4 = \underline{\mathbf{54 \Omega}}$$
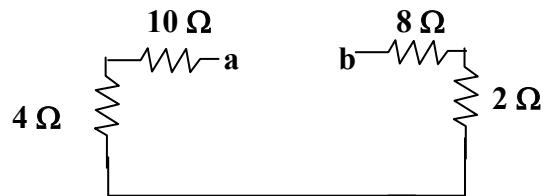
### Chapter 2, Solution 47

$$5\parallel 20 = \frac{5 \times 20}{25} = 4\Omega$$

$$6\parallel 3 = \frac{6 \times 3}{9} = 2\Omega$$



$$R_{ab} = 10 + 4 + 2 + 8 = \underline{\mathbf{24 \Omega}}$$

### Chapter 2, Solution 48

$$(a) \quad R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{100 + 100 + 100}{10} = 30$$

$$R_a = R_b = R_c = \underline{\underline{30 \Omega}}$$

$$(b) \quad R_a = \frac{30 \times 20 + 30 \times 50 + 20 \times 50}{30} = \frac{3100}{30} = 103.3 \Omega$$

$$R_b = \frac{3100}{20} = 155 \Omega, \quad R_c = \frac{3100}{50} = 62 \Omega$$

$$R_a = \underline{\underline{103.3 \Omega}}, \quad R_b = \underline{\underline{155 \Omega}}, \quad R_c = \underline{\underline{62 \Omega}}$$

### Chapter 2, Solution 49

$$(a) \quad R_1 = \frac{R_a R_c}{R_a + R_b + R_c} = \frac{12 + 12}{36} = 4 \Omega$$

$$R_1 = R_2 = R_3 = \underline{\underline{4 \Omega}}$$

$$(b) \quad R_1 = \frac{60 \times 30}{60 + 30 + 10} = 18 \Omega$$


$$R_2 = \frac{60 \times 10}{100} = 6 \Omega$$

$$R_3 = \frac{30 \times 10}{100} = 3 \Omega$$

$$R_1 = \underline{\underline{18 \Omega}}, \quad R_2 = \underline{\underline{6 \Omega}}, \quad R_3 = \underline{\underline{3 \Omega}}$$
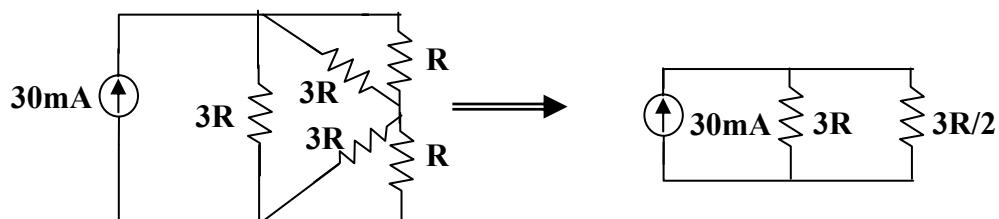
### Chapter 2, Solution 50

Using  $R_\Delta = 3R_Y = 3R$ , we obtain the equivalent circuit shown below:



$$3R \parallel R = \frac{3RxR}{4R} = \frac{3}{4}R$$

$$3R \parallel (3RxR)/(4R) = 3/(4R)$$

$$3R \left( \frac{3}{4}R + \frac{3}{4}R \right) = 3R \parallel \frac{3}{2}R = \frac{3Rx\frac{3}{2}R}{3R + \frac{3}{2}R} = R$$


$$P = I^2R \longrightarrow 800 \times 10^{-3} = (30 \times 10^{-3})^2 R$$

$$R = \underline{\underline{889 \Omega}}$$

### Chapter 2, Solution 51

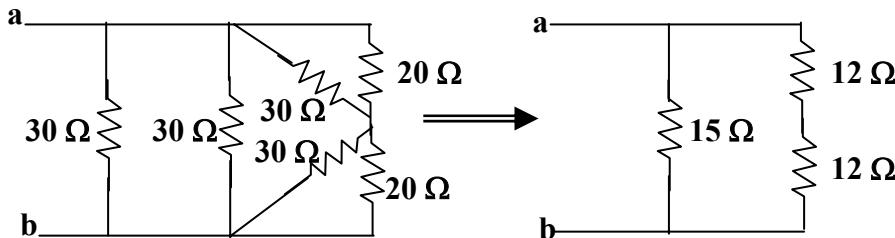(a)  $30 \parallel 30 = 15\Omega$  and  $30 \parallel 20 = 30x20/(50) = 12\Omega$

$$R_{ab} = 15 \parallel (12+12) = 15 \times 24 / (39) = \underline{\underline{9.31 \Omega}}$$



(b) Converting the T-subnetwork into its equivalent  $\Delta$  network gives


$$R_{a'b'} = 10 \times 20 + 20 \times 5 + 5 \times 10 / (5) = 350 / (5) = 70 \Omega$$

$$R_{b'c'} = 350 / (10) = 35 \Omega, R_{a'c'} = 350 / (20) = 17.5 \Omega$$

Also  $30 \parallel 70 = 30 \times 70 / (100) = 21 \Omega$  and  $35 / (15) = 35 \times 15 / (50) = 10.5$


$$R_{ab} = 25 + 17.5 \parallel (21 + 10.5) = 25 + 17.5 \parallel 31.5$$
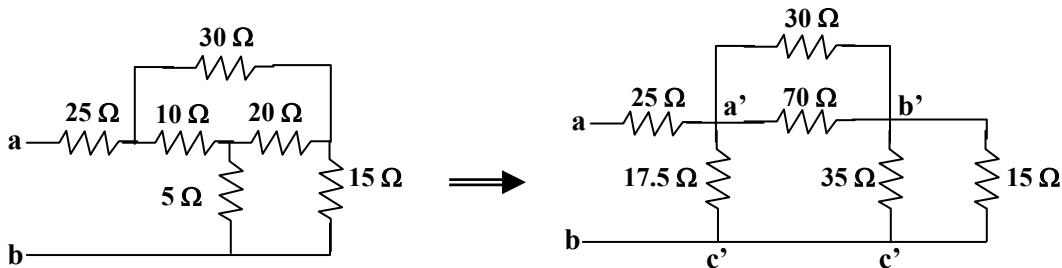
$$R_{ab} = \underline{\underline{36.25 \Omega}}$$



## Chapter 2, Solution 52

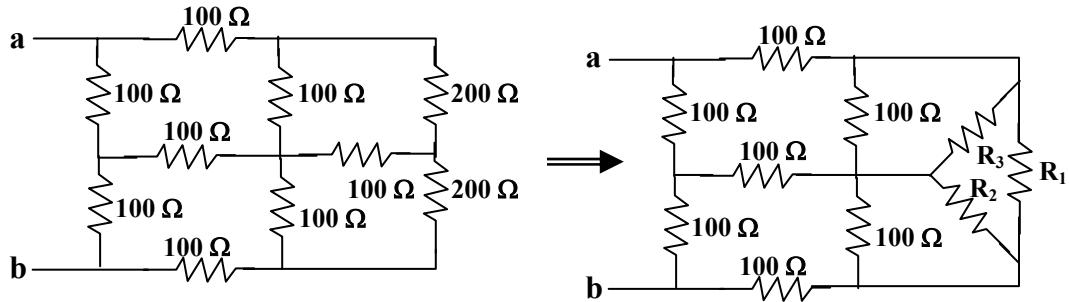(a) We first convert from T to  $\Delta$ .




$$R_1 = \frac{100 \times 200 + 200 \times 200 + 200 \times 100}{100} = \frac{80000}{100} = 800 \Omega$$


$$R_2 = R_3 = 80000/(200) = 400$$

$$\text{But } 100\parallel 400 = \frac{100 \times 400}{500} = 80 \Omega$$

We connect the  $\Delta$  to Y.

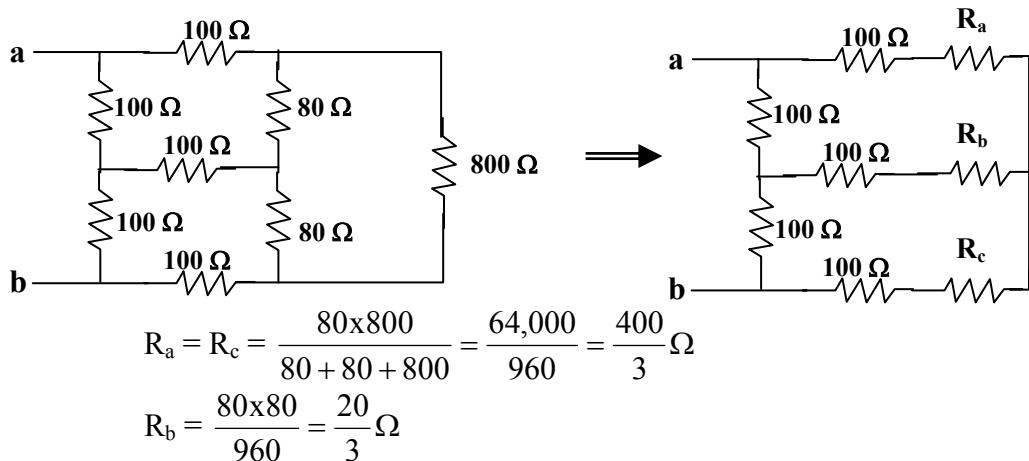

We convert T to  $\Delta$ .

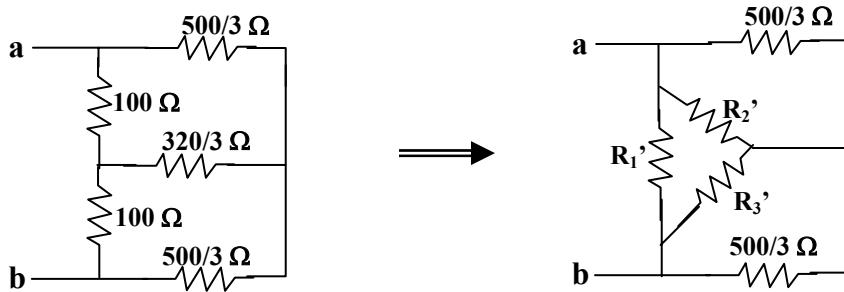


$$R_1' = \frac{100 \times 100 + 100 \times \frac{320}{3} + 100 \times \frac{320}{3}}{\frac{320}{3}} = \frac{94,000 / (3)}{320 / (3)} = 293.75 \Omega$$

$$R_2' = R_3' = \frac{94,000 / (3)}{100} = 313.33$$

$$940 / (30) \parallel 500 / (3) = \frac{940 / (3) \times 500 / (3)}{1440 / (3)} = 108.796$$

$$R_{ab} = 293.75 \parallel (2 \times 108.796) = \frac{293.75 \times 217.6}{511.36} = \underline{125 \Omega}$$

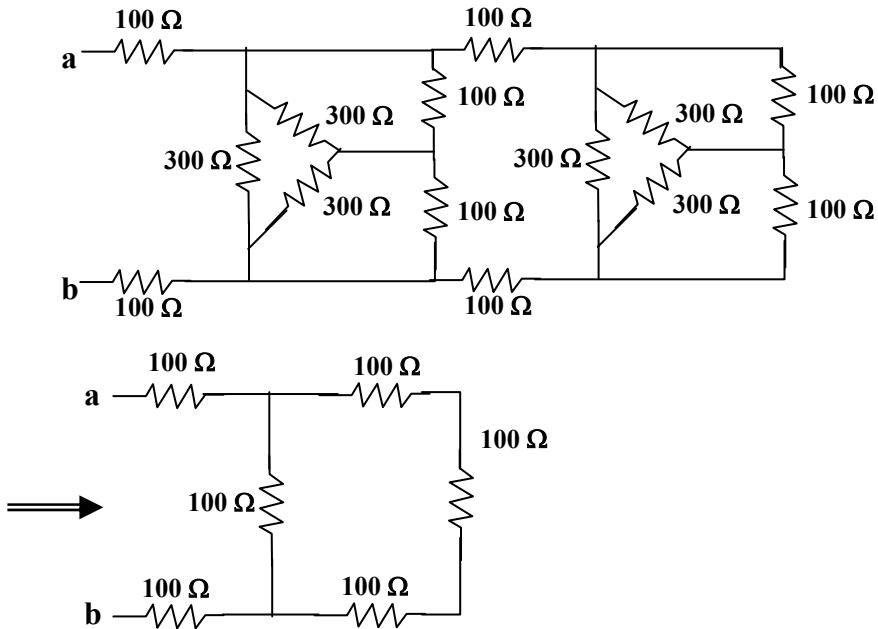
(b) Converting the  $T_s$  to  $\Delta_s$ , we have the equivalent circuit below.



$$300 \parallel 100 = 300 \times 100 / (400) = 75, \quad 300 \parallel (75 + 75) = 300 \times 150 / (450) = 100$$


$$R_{ab} = 100 + 100 \parallel 300 + 100 = 200 + 100 \times 300 / (400)$$

$$\underline{R_{ab} = 2.75 \Omega}$$

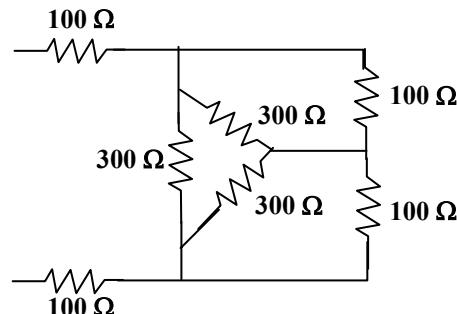

## Chapter 2, Solution 53

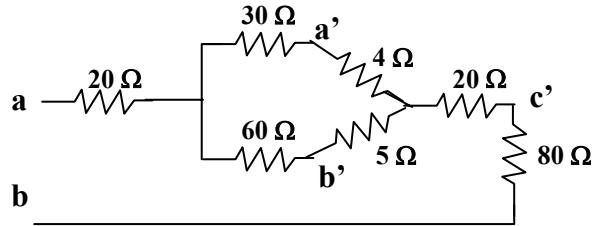(a) Converting one  $\Delta$  to T yields the equivalent circuit below:



$$R_{a'n} = \frac{40 \times 10}{40 + 10 + 50} = 4\Omega, R_{b'n} = \frac{10 \times 50}{100} = 5\Omega, R_{c'n} = \frac{40 \times 50}{100} = 20\Omega$$


$$R_{ab} = 20 + 80 + 20 + (30 + 4)\parallel(60 + 5) = 120 + 34\parallel65$$

$$R_{ab} = \underline{\underline{142.32 \Omega}}$$

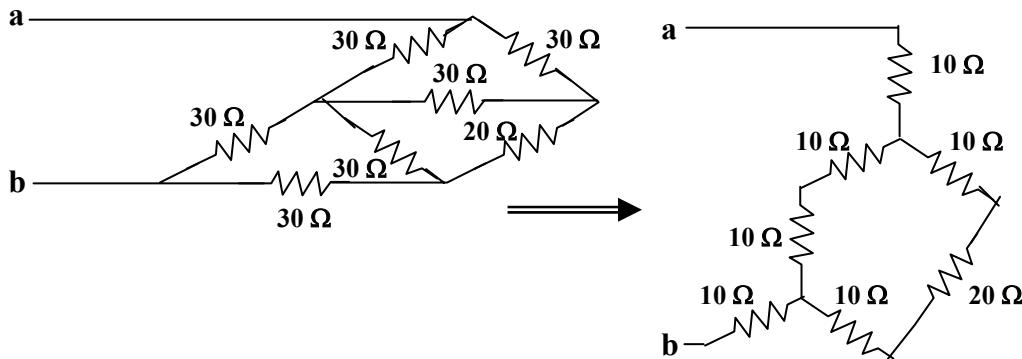(a) We combine the resistor in series and in parallel.

$$30\parallel(30 + 30) = \frac{30 \times 60}{90} = 20\Omega$$

We convert the balanced  $\Delta$ s to Ts as shown below:



$$R_{ab} = 10 + (10 + 10)\parallel(10 + 20 + 10) + 10 = 20 + 20\parallel40$$

$$\underline{\underline{R_{ab} = 33.33 \Omega}}$$


## Chapter 2, Solution 54

$$(a) R_{ab} = 50 + 100 / /(150 + 100 + 150) = 50 + 100 / /400 = \underline{\underline{130\Omega}}$$

$$(b) R_{ab} = 60 + 100 / /(150 + 100 + 150) = 60 + 100 / /400 = \underline{\underline{140\Omega}}$$

## Chapter 2, Solution 55

We convert the T to  $\Delta$ .

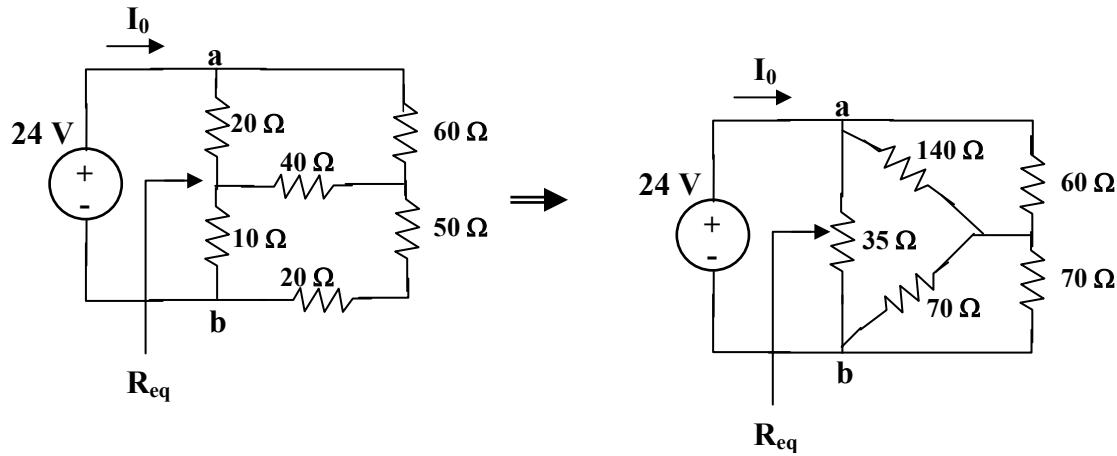

$$R_{ab} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{20 \times 40 + 40 \times 10 + 10 \times 20}{40} = \frac{1400}{40} = 35\Omega$$

$$R_{ac} = 1400/(10) = 140\Omega, R_{bc} = 1400/(40) = 35\Omega$$


$$70\parallel 70 = 35 \text{ and } 140\parallel 160 = 140 \times 60 / (200) = 42$$

$$R_{eq} = 35\parallel(35+42) = 24.0625\Omega$$

$$I_0 = 24/(R_{ab}) = \underline{\underline{0.9774A}}$$
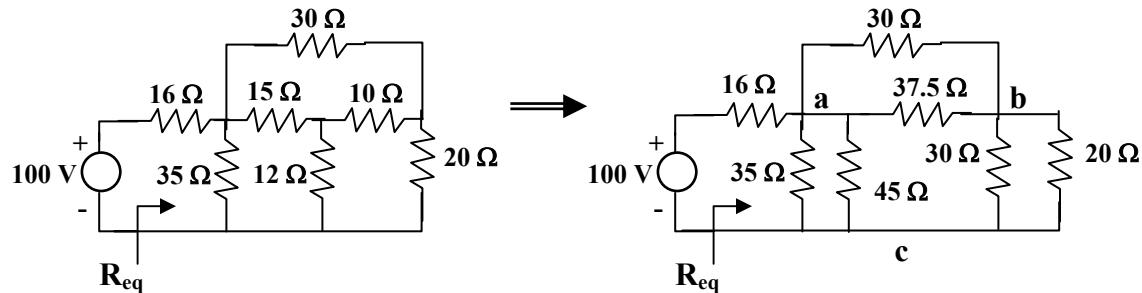
## Chapter 2, Solution 56

We need to find  $R_{eq}$  and apply voltage division. We first transform the Y network to  $\Delta$ .



$$R_{ab} = \frac{15 \times 10 + 10 \times 12 + 12 \times 15}{12} = \frac{450}{12} = 37.5\Omega$$

$$R_{ac} = 450/(10) = 45\Omega, R_{bc} = 450/(15) = 30\Omega$$

Combining the resistors in parallel,

$$30\parallel 20 = (600/50) = 12 \Omega,$$

$$37.5\parallel 30 = (37.5 \times 30 / 67.5) = 16.667 \Omega$$


$$35\parallel 45 = (35 \times 45 / 80) = 19.688 \Omega$$

$$R_{eq} = 19.688\parallel(12 + 16.667) = 11.672 \Omega$$

By voltage division,

$$v = \frac{11.672}{11.672 + 16} 100 = \underline{\underline{42.18 \text{ V}}}$$

### Chapter 2, Solution 57

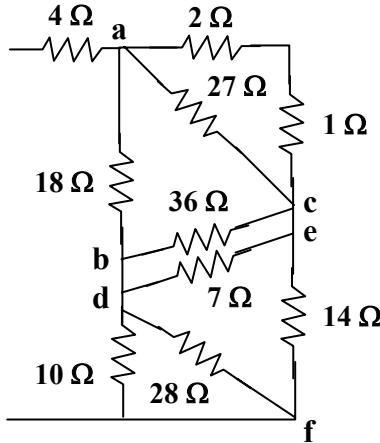

$$R_{ab} = \frac{6 \times 12 + 12 \times 8 + 8 \times 6}{12} = \frac{216}{12} = 18 \Omega$$

$$R_{ac} = 216/(8) = 27 \Omega, R_{bc} = 36 \Omega$$


$$R_{de} = \frac{4 \times 2 + 2 \times 8 + 8 \times 4}{8} = \frac{56}{8} = 7 \Omega$$

$$R_{ef} = 56/(4) = 14 \Omega, R_{df} = 56/(2) = 28 \Omega$$

Combining resistors in parallel,

$$10\parallel 28 = \frac{280}{38} = 7.368 \Omega, 36\parallel 7 = \frac{36 \times 7}{43} = 5.868 \Omega$$
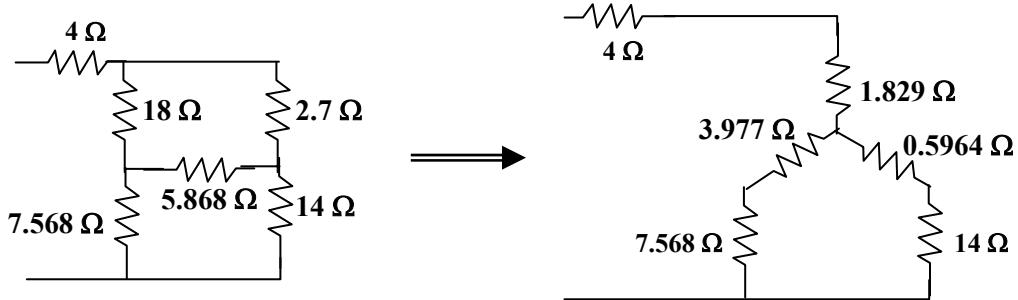
$$27\parallel 3 = \frac{27 \times 3}{30} = 2.7 \Omega$$



$$R_{an} = \frac{18 \times 2.7}{18 + 2.7 + 5.867} = \frac{18 \times 2.7}{26.567} = 1.829 \Omega$$

$$R_{bn} = \frac{18 \times 5.868}{26.567} = 3.977 \Omega$$

$$R_{cn} = \frac{5.868 \times 2.7}{26.567} = 0.5904 \Omega$$


$$R_{eq} = 4 + 1.829 + (3.977 + 7.368) \parallel (0.5964 + 14)$$

$$= 5.829 + 11.346 \parallel 14.5964 = \underline{\underline{12.21 \Omega}}$$

$$i = 20 / (R_{eq}) = \underline{\underline{1.64 A}}$$
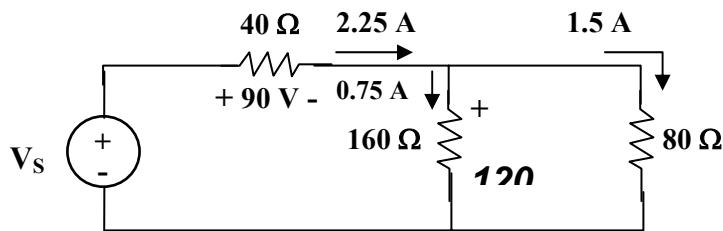
### Chapter 2, Solution 58

The resistor of the bulb is  $120 / (0.75) = 160\Omega$



Once the  $160\Omega$  and  $80\Omega$  resistors are in parallel, they have the same voltage  $120V$ . Hence the current through the  $40\Omega$  resistor is

$$40(0.75 + 1.5) = 2.25 \times 40 = 90$$

Thus

$$v_s = 90 + 120 = \underline{\underline{210 V}}$$

## Chapter 2, Solution 59

Total power  $p = 30 + 40 + 50 + 120 \text{ W} = vi$

$$\text{or } i = p/(v) = 120/(100) = \underline{\underline{1.2 \text{ A}}}$$

## Chapter 2, Solution 60

$$\begin{aligned} p &= iv & i &= p/(v) \\ i_{30\text{W}} &= 30/(100) = \underline{\underline{0.3 \text{ A}}} \\ i_{40\text{W}} &= 40/(100) = \underline{\underline{0.4 \text{ A}}} \\ i_{50\text{W}} &= 50/(100) = \underline{\underline{0.5 \text{ A}}} \end{aligned}$$

## Chapter 2, Solution 61

There are three possibilities

(a) Use  $R_1$  and  $R_2$ :

$$R = R_1 \parallel R_2 = 80 \parallel 90 = 42.35\Omega$$

$$p = i^2 R$$

$$i = 1.2\text{A} + 5\% = 1.2 \pm 0.06 = 1.26, 1.14\text{A}$$

$$p = 67.23\text{W} \text{ or } 55.04\text{W}, \text{ cost} = \$1.50$$

(b) Use  $R_1$  and  $R_3$ :

$$R = R_1 \parallel R_3 = 80 \parallel 100 = 44.44 \Omega$$

$$p = I^2 R = 70.52\text{W} \text{ or } 57.76\text{W}, \text{ cost} = \$1.35$$

(c) Use  $R_2$  and  $R_3$ :

$$R = R_2 \parallel R_3 = 90 \parallel 100 = 47.37\Omega$$

$$p = I^2 R = 75.2\text{W} \text{ or } 61.56\text{W}, \text{ cost} = \$1.65$$

Note that cases (b) and (c) give  $p$  that exceed 70W that can be supplied.  
Hence case (a) is the right choice, i.e.

**R<sub>1</sub> and R<sub>2</sub>**

## Chapter 2, Solution 62

$$p_A = 110 \times 8 = 880 \text{ W}, \quad p_B = 110 \times 2 = 220 \text{ W}$$

$$\text{Energy cost} = \$0.06 \times 360 \times 10 \times (880 + 220)/1000 = \underline{\underline{\$237.60}}$$

### Chapter 2, Solution 63

Use eq. (2.61),

$$R_n = \frac{I_m}{I - I_m} R_m = \frac{2 \times 10^{-3} \times 100}{5 - 2 \times 10^{-3}} = 0.04 \Omega$$
$$I_n = I - I_m = 4.998 \text{ A}$$
$$p = I_n^2 R = (4.998)^2 (0.04) = 0.9992 \approx \underline{\mathbf{1 W}}$$

### Chapter 2, Solution 64

$$\text{When } R_x = 0, i_x = 10 \text{ A} \quad R = \frac{110}{10} = 11 \Omega$$

$$\text{When } R_x \text{ is maximum, } i_x = 1 \text{ A} \longrightarrow R + R_x = \frac{110}{1} = 110 \Omega$$

$$\text{i.e., } R_x = 110 - R = 99 \Omega$$

$$\text{Thus, } R = \underline{\mathbf{11 \Omega}}, \quad R_x = \underline{\mathbf{99 \Omega}}$$

### Chapter 2, Solution 65

$$R_n = \frac{V_{fs}}{I_{fs}} - R_m = \frac{50}{10 \text{ mA}} - 1 \text{ k}\Omega = \underline{\mathbf{4 \text{ k}\Omega}}$$

### Chapter 2, Solution 66

$$20 \text{ k}\Omega/\text{V} = \text{sensitivity} = \frac{1}{I_{fs}}$$

$$\text{i.e., } I_{fs} = \frac{1}{20} \text{ k}\Omega/\text{V} = 50 \mu\text{A}$$

$$\text{The intended resistance } R_m = \frac{V_{fs}}{I_{fs}} = 10(20 \text{ k}\Omega/\text{V}) = 200 \text{ k}\Omega$$

$$(a) \quad R_n = \frac{V_{fs}}{i_{fs}} - R_m = \frac{50 \text{ V}}{50 \mu\text{A}} - 200 \text{ k}\Omega = \underline{\mathbf{800 \text{ k}\Omega}}$$

$$(b) \quad p = I_{fs}^2 R_n = (50 \mu\text{A})^2 (800 \text{ k}\Omega) = \underline{\mathbf{2 \text{ mW}}}$$

## Chapter 2, Solution 67

(a) By current division,

$$i_0 = 5/(5+5) (2 \text{ mA}) = 1 \text{ mA}$$
$$V_0 = (4 \text{ k}\Omega) i_0 = 4 \times 10^3 \times 10^{-3} = \underline{\underline{4 \text{ V}}}$$

(b)  $4\text{k}\parallel 6\text{k} = 2.4\text{k}\Omega$ . By current division,

$$i'_0 = \frac{5}{1+2.4+5} (2\text{mA}) = 1.19 \text{ mA}$$

$$v'_0 = (2.4 \text{ k}\Omega)(1.19 \text{ mA}) = \underline{\underline{2.857 \text{ V}}}$$

(c) % error =  $\left| \frac{v_0 - v'_0}{v_0} \right| \times 100\% = \frac{1.143}{4} \times 100 = \underline{\underline{28.57\%}}$

(d)  $4\text{k}\parallel 30 \text{ k}\Omega = 3.6 \text{ k}\Omega$ . By current division,

$$i'_0 = \frac{5}{1+3.6+5} (2\text{mA}) = 1.042 \text{ mA}$$

$$v'_0 (3.6 \text{ k}\Omega)(1.042 \text{ mA}) = 3.75 \text{ V}$$

% error =  $\left| \frac{v - v'_0}{v_0} \right| \times 100\% = \frac{0.25 \times 100}{4} = \underline{\underline{6.25\%}}$

## Chapter 2, Solution 68

(a)  $40 = 24\parallel 60\Omega$

$$i = \frac{4}{16+24} = \underline{\underline{0.1 \text{ A}}}$$

(b)  $i' = \frac{4}{16+1+24} = \underline{\underline{0.09756 \text{ A}}}$

(c) % error =  $\frac{0.1 - 0.09756}{0.1} \times 100\% = \underline{\underline{2.44\%}}$

## Chapter 2, Solution 69

With the voltmeter in place,

$$V_0 = \frac{R_2 \| R_m}{R_1 + R_s + R_2 \| R_m} V_s$$

where  $R_m = 100 \text{ k}\Omega$  without the voltmeter,

$$V_0 = \frac{R_2}{R_1 + R_2 + R_s} V_s$$

(a) When  $R_2 = 1 \text{ k}\Omega$ ,  $R_2 \| R_m = \frac{100}{101} \text{ k}\Omega$

$$V_0 = \frac{\frac{100}{101}}{\frac{100}{101} + 30} (40) = \underline{1.278 \text{ V (with)}}$$

$$V_0 = \frac{1}{1 + 30} (40) = \underline{1.29 \text{ V (without)}}$$

(b) When  $R_2 = 10 \text{ k}\Omega$ ,  $R_2 \| R_m = \frac{1000}{110} = 9.091 \text{ k}\Omega$

$$V_0 = \frac{9.091}{9.091 + 30} (40) = \underline{9.30 \text{ V (with)}}$$

$$V_0 = \frac{10}{10 + 30} (40) = \underline{10 \text{ V (without)}}$$

(c) When  $R_2 = 100 \text{ k}\Omega$ ,  $R_2 \| R_m = 50 \text{ k}\Omega$

$$V_0 = \frac{50}{50 + 30} (40) = \underline{25 \text{ V (with)}}$$

$$V_0 = \frac{100}{100 + 30} (40) = \underline{30.77 \text{ V (without)}}$$

## Chapter 2, Solution 70


(a) Using voltage division,

$$v_a = \frac{12}{12 + 8} (25) = \underline{15V}$$

$$v_b = \frac{10}{10 + 15} (25) = \underline{10V}$$


$$v_{ab} = v_a - v_b = 15 - 10 = \underline{5V}$$

(b)

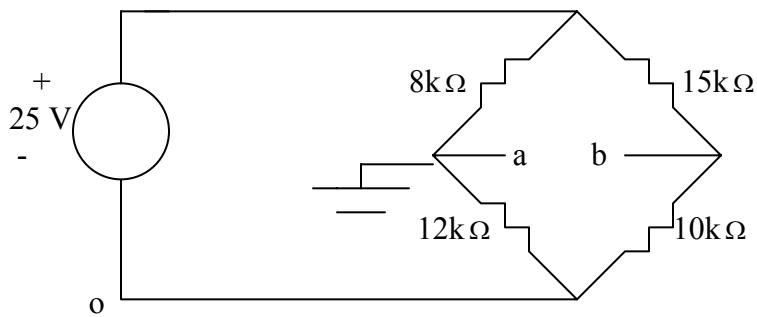

$$v_a = 0, \quad v_b = 10V, \quad v_{ab} = v_a - v_b = 0 - 10 = -10V$$

### Chapter 2, Solution 71

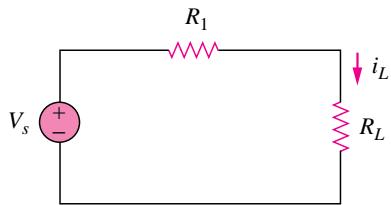


Given that  $v_s = 30 \text{ V}$ ,  $R_I = 20 \Omega$ ,  $I_L = 1 \text{ A}$ , find  $R_L$ .

$$v_s = i_L(R_I + R_L) \longrightarrow R_L = \frac{v_s}{i_L} - R_I = \frac{30}{1} - 20 = 10 \Omega$$

## Chapter 2, Solution 72

The system can be modeled as shown.

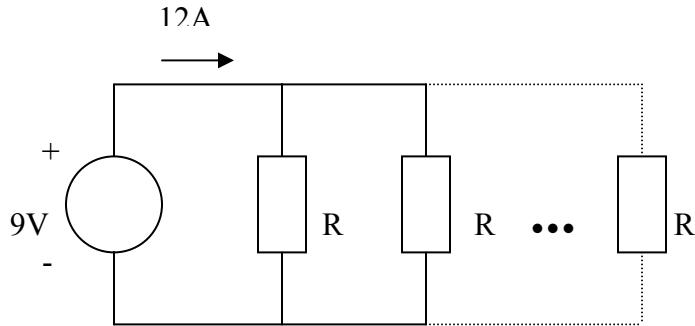

The  $n$  parallel resistors  $R$  give a combined resistance of  $R/n$ . Thus,

$$9 = 12 \times \frac{R}{n} \quad \longrightarrow \quad n = \frac{12 \times R}{9} = \frac{12 \times 15}{9} = 20$$

## Chapter 2, Solution 73

By the current division principle, the current through the ammeter will be one-half its previous value when

$$\begin{aligned} R &= 20 + R_x \\ 65 &= 20 + R_x \longrightarrow R_x = \underline{\underline{45 \Omega}} \end{aligned}$$

## Chapter 2, Solution 74

With the switch in high position,

$$6 = (0.01 + R_3 + 0.02) \times 5 \longrightarrow R_3 = \underline{\underline{1.17 \Omega}}$$

At the medium position,


$$6 = (0.01 + R_2 + R_3 + 0.02) \times 3 \longrightarrow R_2 + R_3 = 1.97$$

$$\text{or } R_2 = 1.97 - 1.17 = \underline{\underline{0.8 \Omega}}$$

At the low position,

$$\begin{aligned} 6 &= (0.01 + R_1 + R_2 + R_3 + 0.02) \times 1 \longrightarrow R_1 + R_2 + R_3 = 5.97 \\ R_1 &= 5.97 - 1.97 = \underline{\underline{4 \Omega}} \end{aligned}$$

### Chapter 2, Solution 75

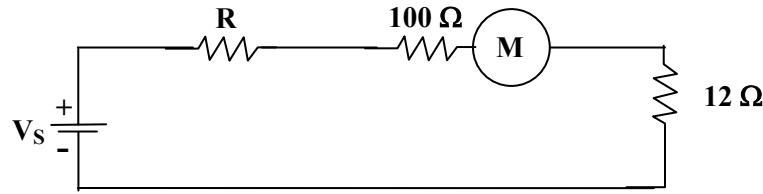

(a) When  $R_x = 0$ , then

$$I_m = I_{fs} = \frac{t}{R + R_m} \longrightarrow R_2 = \frac{E^2}{I_{fs}} - R_m = \frac{2}{0.1 \times 10^3} - 100 = 19.9 \text{ k}\Omega$$

(b) For half-scale deflection,  $I_m = \frac{I_{fs}}{2} = 0.05 \text{ mA}$

$$I_m = \frac{E}{R + R_m + R_x} \longrightarrow R_x = \frac{E}{I_m} - (R + R_m) = \frac{2}{0.05 \times 10^{-3}} - 20 \text{ k}\Omega = \underline{\underline{20 \text{ k}\Omega}}$$

### Chapter 2, Solution 76

For series connection,  $R = 2 \times 0.4 \Omega = 0.8 \Omega$

$$P = \frac{V^2}{R} = \frac{(120)^2}{0.8} = \underline{\underline{18 \text{ k}\Omega \text{ (low)}}$$

For parallel connection,  $R = 1/2 \times 0.4 \Omega = 0.2 \Omega$

$$P = \frac{V^2}{R} = \frac{(120)^2}{0.2} = \underline{\underline{72 \text{ kW} \text{ (high)}}$$

### Chapter 2, Solution 77

(a)  $5 \Omega = 10 \parallel 10 = 20 \parallel 20 \parallel 20 \parallel 20$

i.e., four 20 Ω resistors in parallel.

(b)  $311.8 = 300 + 10 + 1.8 = 300 + 20 \parallel 20 + 1.8$

i.e., one  $300\Omega$  resistor in series with  $1.8\Omega$  resistor and a parallel combination of two  $20\Omega$  resistors.

(c)  $40 \text{ k}\Omega = 12 \text{ k}\Omega + 28 \text{ k}\Omega = 24 \parallel 24 \text{ k} + 56 \text{ k} \parallel 50 \text{ k}$


i.e., Two  $24\text{k}\Omega$  resistors in parallel connected in series with two  $50\text{k}\Omega$  resistors in parallel.

(d)  $42.32 \text{ k}\Omega = 42l + 320$   
 $= 24k + 28k = 320$   
 $= 24k = 56k \parallel 56k + 300 + 20$

i.e., A series combination of  $20\Omega$  resistor,  $300\Omega$  resistor,  $24\text{k}\Omega$  resistor and a parallel combination of two  $56\text{k}\Omega$  resistors.

## Chapter 2, Solution 78

The equivalent circuit is shown below:

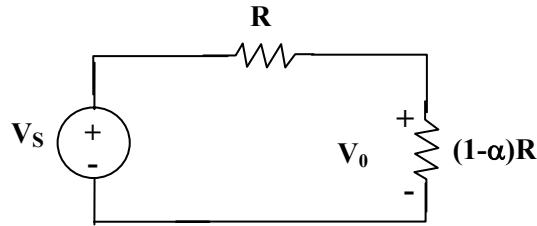

$$V_0 = \frac{(1-\alpha)R}{R + (1-\alpha)R} V_s = (1-\alpha)R_0 V_s$$

$$\underline{\underline{\frac{V_0}{V_s} = (1-\alpha)R}}$$

## Chapter 2, Solution 79

Since  $p = v^2/R$ , the resistance of the sharpener is

$$R = v^2/(p) = 6^2/(240 \times 10^{-3}) = 150\Omega$$

$$I = p/(v) = 240 \text{ mW}/(6\text{V}) = 40 \text{ mA}$$



Since  $R$  and  $R_x$  are in series,  $I$  flows through both.

$$IR_x = V_x = 9 - 6 = 3 \text{ V}$$

$$R_x = 3/(I) = 3/(40 \text{ mA}) = 3000/(40) = \underline{\underline{75 \Omega}}$$
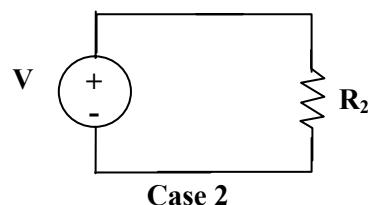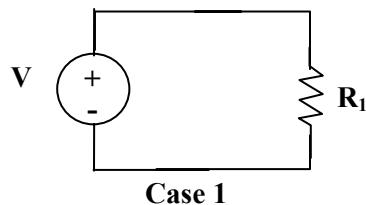
## Chapter 2, Solution 80

The amplifier can be modeled as a voltage source and the loudspeaker as a resistor:



$$\text{Hence } p = \frac{V^2}{R}, \quad \frac{p_2}{p_1} = \frac{R_1}{R_2} \rightarrow p_2 = \frac{R_1}{R_2} p_1 = \frac{10}{4}(12) = \underline{\underline{30 \text{ W}}}$$

## Chapter 2, Solution 81

Let  $R_1$  and  $R_2$  be in  $k\Omega$ .

$$R_{eq} = R_1 + R_2 \parallel 5 \quad (1)$$

$$\frac{V_o}{V_s} = \frac{5 \parallel R_2}{5 \parallel R_2 + R_1} \quad (2)$$


$$\text{From (1) and (2), } 0.05 = \frac{5 \parallel R_1}{40} \quad 2 = 5 \parallel R_2 = \frac{5R_2}{5 + R_2} \text{ or } R_2 = 3.33 \text{ k}\Omega$$

$$\text{From (1), } 40 = R_1 + 2 \quad R_1 = 38 \text{ k}\Omega$$

Thus  $R_1 = 38 \text{ k}\Omega$ ,  $R_2 = 3.33 \text{ k}\Omega$


## Chapter 2, Solution 82

(a)

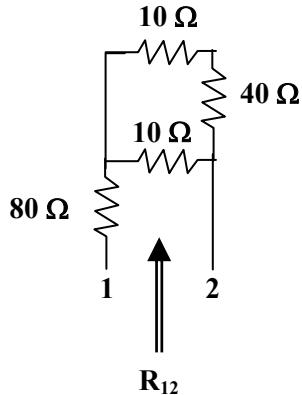


$$R_{12} = 80 + 10 \parallel (10 + 40) = 80 + \frac{50}{6} = \underline{\underline{88.33 \Omega}}$$

(b)

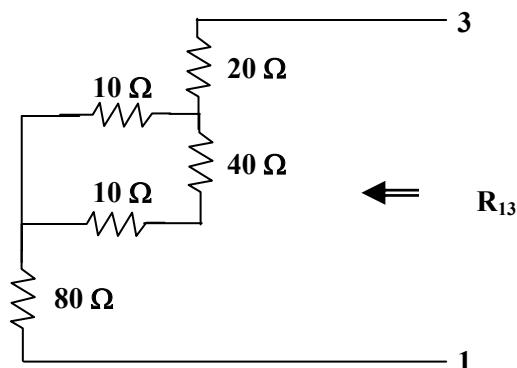

$$R_{13} = 80 + 10 \parallel (10 + 40) + 20 = 100 + 10 \parallel 50 = \underline{\underline{108.33 \Omega}}$$

(c)

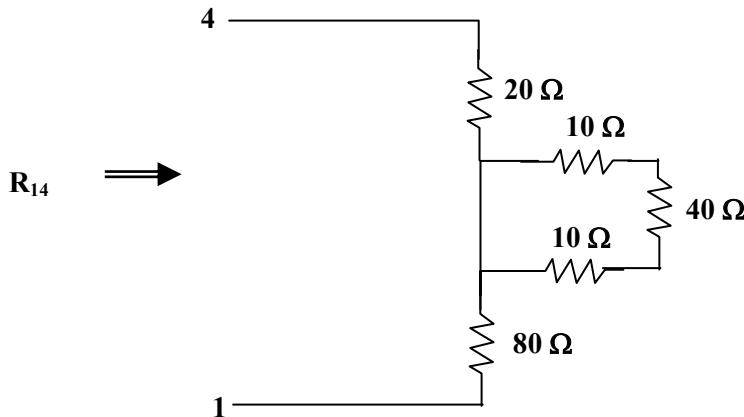


$$R_{14} = 80 + 0 \parallel (10 + 40 + 10) + 20 = 80 + 0 + 20 = \underline{\underline{100 \Omega}}$$

### Chapter 2, Solution 83

The voltage across the tube is  $2 \times 60 \text{ mV} = 0.06 \text{ V}$ , which is negligible compared with 24 V. Ignoring this voltage amp, we can calculate the current through the devices.

$$I_1 = \frac{p_1}{V_1} = \frac{45 \text{ mW}}{9 \text{ V}} = 5 \text{ mA}$$
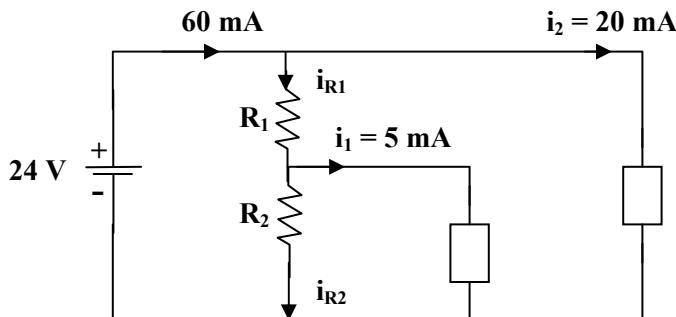
$$I_2 = \frac{p_2}{V_2} = \frac{480 \text{ mW}}{24 \text{ V}} = 20 \text{ mA}$$



By applying KCL, we obtain

$$I_{R_1} = 60 - 20 = 40 \text{ mA} \text{ and } I_{R_2} = 40 - 5 = 35 \text{ mA}$$

$$\text{Hence, } I_{R_1} R_1 = 24 - 9 = 15 \text{ V} \longrightarrow R_1 = \frac{15 \text{ V}}{40 \text{ mA}} = \underline{\underline{375 \Omega}}$$

$$I_{R_2} R_2 = 9 \text{ V} \longrightarrow R_2 = \frac{9 \text{ V}}{35 \text{ mA}} = \underline{\underline{257.14 \Omega}}$$