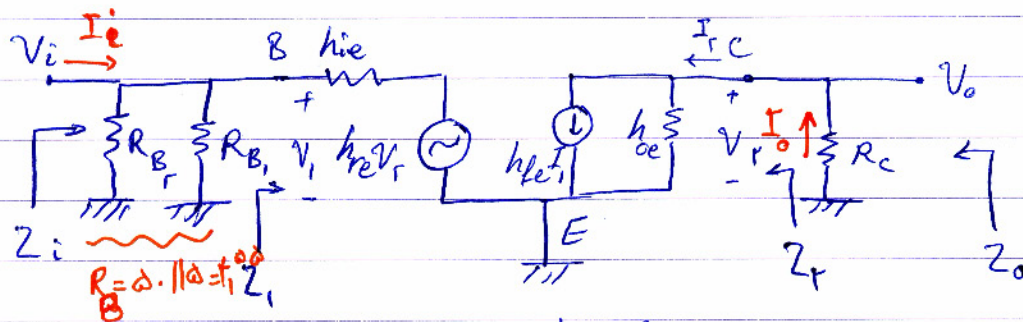


$$\left\{ \begin{array}{l} h_{ie} = 1 \text{ k}\Omega \\ h_{re} = 2 \times 10^{-4} \\ h_{fe} = 100 \\ h_{oe} = 20 \mu\text{A/V} \end{array} \right.$$



$$A_v = \frac{V_o}{V_i} = \frac{V_r}{V_i} = \frac{-h_{fe} R_c}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_c} = -241.44$$

$$Z_i = h_{ie} - \frac{h_{fe} h_{re} R_c}{1 + h_{oe} R_c} = 1491 \Omega$$


تقریباً

$$A_i = \frac{I_o}{I_i} = \frac{I_r}{I_i} \times \frac{I_1}{I_i} = \frac{I_r}{I_i} \times \frac{I_1}{I_i} = \frac{h_{fe}}{1 + h_{oe} R_c} \times \frac{R_B}{R_B + Z_i} = 20.1 \text{ V}$$


$$Z_i = R_B \parallel Z_1 = 1.92 \text{ k}\Omega$$

$$Z_r = \frac{1}{h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s}} = 10 \text{ k}\Omega$$
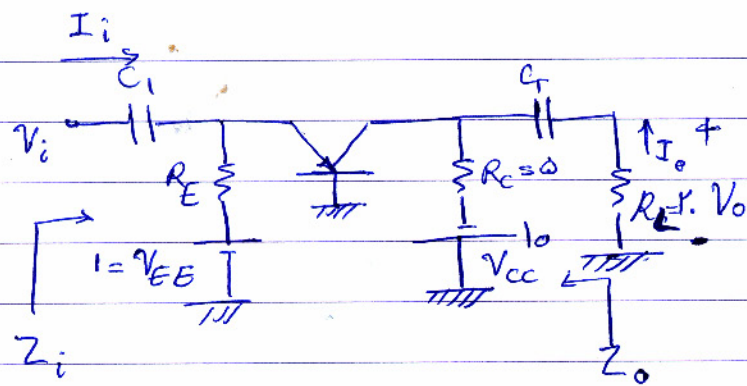
$$Z_o = R_c \parallel Z_r = 4.9 \text{ k}\Omega$$


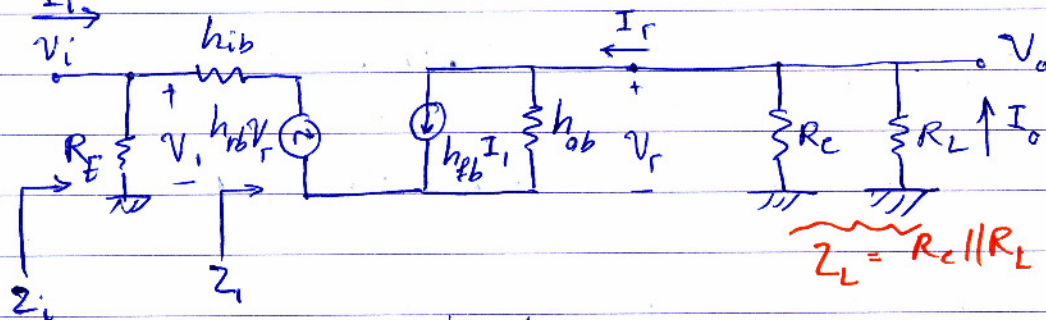
$$\left\{ \begin{array}{l} h_{ib} = 1 \text{ k}\Omega \\ h_{rb} = 0 \dots \times 10^{-4} \\ h_{ob} = 1 \text{ pA/V} \\ h_{fb} = -199 \end{array} \right.$$



$$Z_1 = h_{ib} - \frac{h_{fb} h_{rb} Z_L}{1 + h_{ob} Z_L} = 1 \text{ k}\Omega$$

$$Z_i = R_E || Z_1 = 19.1 \text{ k}\Omega$$

$$A_I = \frac{I_o}{I_i} \times \frac{I_1}{I_b} \times \frac{I_r}{I_c} = \frac{I_1}{I_i} \times \frac{I_r}{I_b} \times \frac{I_o}{I_c} = \frac{R_E}{R_E + Z_1} \times \frac{R_C}{R_C + R_L} \times \frac{h_{fb}}{1 + h_{ob} Z_L}$$

$$\Rightarrow \boxed{A_I = -199}$$

$$A_v = \frac{v_o}{v_i} = \frac{v_r}{v_i} = \frac{-h_{fb} Z_L}{h_{ib} + (h_{ib} h_{ob} - h_{rb} h_{fb}) Z_L} = \boxed{99}$$

$$Z_o = \frac{1}{h_{ob} - \frac{h_{fb} h_{rb}}{h_{ib} + 0}} = 199 \text{ k}\Omega$$


$$Z_o = 0 \text{ k}\Omega || Z_1 = \boxed{19.1 \text{ k}\Omega}$$

مثال: مدار زیر را در یک ترانزیستور با مدل dc، Q را بر دست آورده پس تحلیل ac کنید

$$(\beta+1)R_E \gg R_{B_r}$$

با توجه به این که

مرحله اول

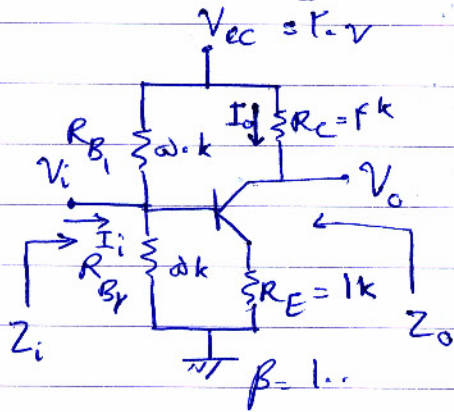

$$V_B = \frac{10}{10+10} \times 10 = 5V$$


$$V_E = V_B - 0.7V = 5V - 0.7V = 4.3V$$

$$I_E = \frac{V_E}{R_E} = \frac{4.3V}{1k} = 4.3mA = I_C$$

$$-V_{cc} + R_C I_C + V_{CE} + R_E I_E = 0$$

$$V_{CE} = 10V - 4.3V = 5.7V$$
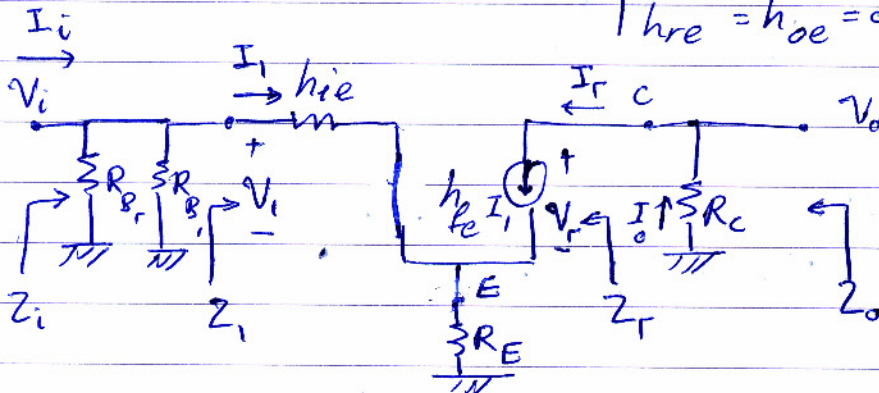
$$\begin{cases} h_{ie} = \frac{r_e}{I_C} \times \beta = 1.37k\Omega \\ h_{fe} \approx 100 \\ h_{re} = h_{oe} = 0 \end{cases}$$



$$Z_i = h_{ie} + (1+\beta)R_E = 1.37k\Omega + 101 \times 1k = 102.37k\Omega$$

$$Z_o = R_C \parallel 102.37k\Omega = 1k\Omega$$

$$A_v = \frac{V_o}{V_i} = ? \quad V_o = -I_o R_c = -h_{fe} I_1 R_c$$

$$-V_i + h_{ie} I_1 + (I_1 + h_{fe} I_1) R_E = 0$$


$$I_1 = \frac{V_i}{h_{ie} + (h_{fe} + 1) R_E} \Rightarrow V_o = -h_{fe} R_c \times \frac{V_i}{h_{ie} + (h_{fe} + 1) R_E}$$

$$\Rightarrow A_v = \frac{V_o}{V_i} = \frac{-h_{fe} R_c}{h_{ie} + (h_{fe} + 1) R_E}$$

$$A_I = \frac{I_o}{I_i} = ? \quad I_o = I_c = h_{fe} I_1 \Rightarrow \frac{I_c}{I_1} = h_{fe}$$

$$= \frac{I_c}{I_1} \times \frac{I_1}{I_i}$$
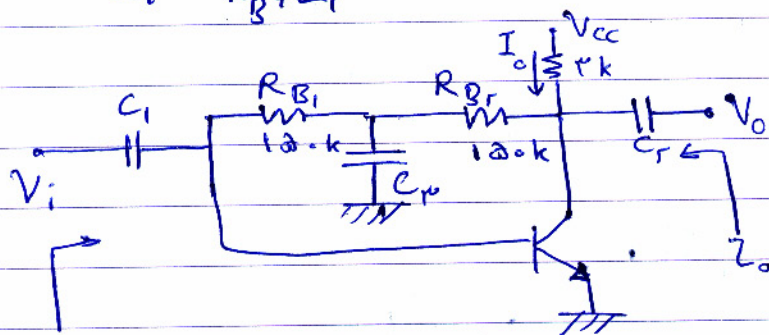
$$\frac{I_1}{I_i} = \frac{R_B}{R_B + Z_i} \Rightarrow A_I = h_{fe} \times \frac{R_B}{R_B + Z_i}$$



...
 $\left. \begin{array}{l} h_{fe} = \beta \\ h_{ie} = 1k \end{array} \right\}$

