
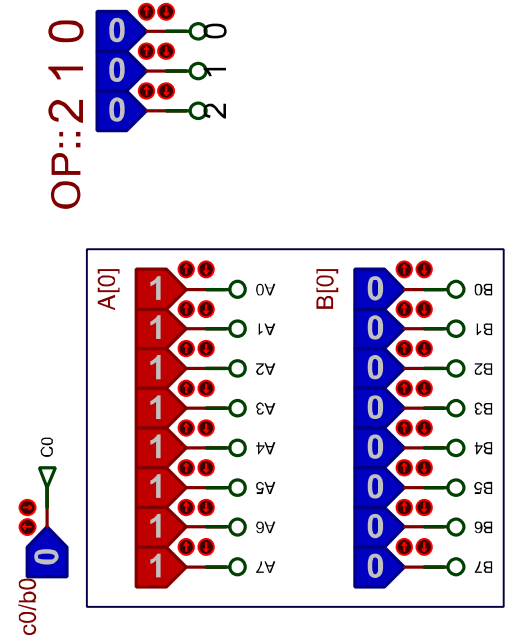


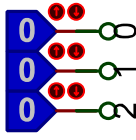
- 0 ==> A plus B
- 1 ==> A-->RIGHT
- 2 ==> A and B
- 3 ==> A or B
- 4 ==> A xor B
- 5 ==> A - B
- 6 ==> A \* B
- 7 ==> LEFT<--A



OP::2 1 0




نتیجه ی نهایی

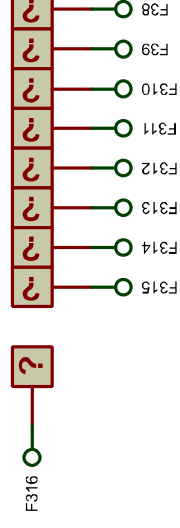


این هشت بیت فقط هنگام ضرب معتبرند

ALU1

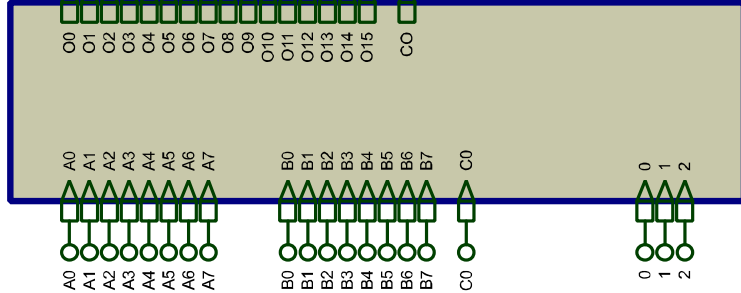

ALU12

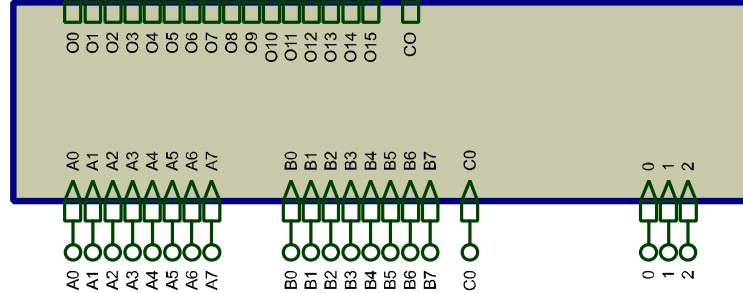

ALU13

