

8.1

$$V_{in} = I_{in} (Z_{in} + G_{22}) + G_{21} V_{out}$$

$$\frac{V_{out} - A_o I_{in} Z_{in}}{Z_{out}} = -G_{11} V_{out} - G_{12} I_{in}$$

$$\Rightarrow I_{in} \left(\frac{A_o Z_{in}}{Z_{out}} - G_{12} \right) = V_{out} \left(\frac{1}{Z_{out}} + G_{11} \right)$$

$$V_{in} = V_{out} \left[G_{21} + \frac{(Z_{in} + G_{22}) \left(\frac{1}{Z_{out}} + G_{11} \right)}{\frac{A_o Z_{in}}{Z_{out}} - G_{12}} \right]$$



$$\frac{V_{out}}{V_{in}} = \frac{\frac{A_o Z_{in} - G_{12} Z_{out}}{Z_{out}}}{G_{21} \left(\frac{A_o Z_{in}}{Z_{out}} - G_{12} \right) + (Z_{in} + G_{22}) \left(\frac{1}{Z_{out}} + G_{11} \right)}$$

$$A_{v, open} = \frac{1}{Z_{out}} (A_o Z_{in} - G_{12} Z_{out}) \cdot \frac{1}{Z_{in} + G_{22}} \cdot \frac{1}{\frac{1}{Z_{out}} + G_{11}}$$

$$= \frac{G_{11}^{-1}}{G_{11}^{-1} + Z_{out}} \cdot \frac{1}{Z_{in} + G_{22}} (A_o Z_{in} - G_{12} Z_{out})$$

if $G_{12} \ll A_o Z_{in} / Z_{out}$ then the second term can be neglected

8.2

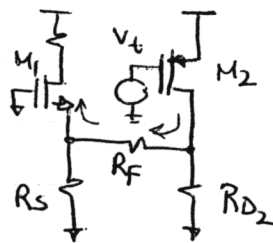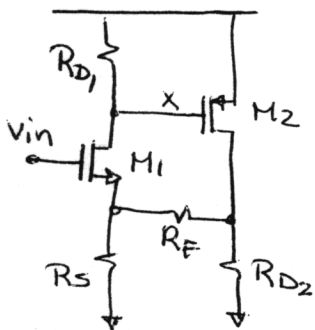

The current through R_{S1} :

$$= \frac{g_{m2} \cdot V_t \cdot R_{D2}}{R_{D2} + R_F + (R_S \parallel \frac{1}{g_{m2}})}$$

The current through M_1 :

$$= \frac{g_{m2} V_t R_{D2}}{R_{D2} + R_F + (R_S \parallel \frac{1}{g_{m2}})} \cdot \frac{R_S}{R_S + \frac{1}{g_{m2}}}$$


This current is multiplied by R_{D1} to produce V_f

loop gain: $\frac{g_{m2} R_{D2} R_S R_{D1}}{(R_{D2} + R_F)(R_S + \frac{1}{g_{m2}}) + R_S \cdot \frac{1}{g_{m2}}}$

This result is accurate, whereas $G_{21} A_{v,open}$ is approximate because it neglects the signal propagating thru the feedback network from the input to the output.

8.3

voltage-current

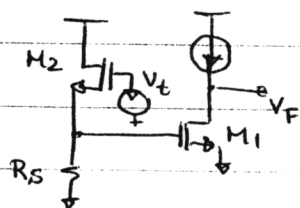

loop gain: $\frac{R_S}{R_S + \frac{1}{g_{m2}}} \cdot g_{m1} r_{o1}$

$$\frac{v_{in}}{R_S} \times (R_S \parallel \frac{1}{g_{m2}}) g_{m1} r_{o1} = V$$

$$\Rightarrow \left. \frac{v_{out}}{\frac{v_{in}}{R_S}} \right|_{open} = g_{m1} r_{o1} (R_S \parallel \frac{1}{g_{m2}})$$


$$Z_{in,open} = \frac{1}{g_{m2}}$$

$$Z_{out,open} = r_{o1}$$

$$\left. \frac{v_{out}}{\frac{v_{in}}{R_S}} \right|_{closed} = \frac{1}{g_{m2}} \Rightarrow A_{v,closed} = \frac{1}{g_{m2} R_S}$$

$$Z_{in,closed} = 0 \quad r_{o1} \rightarrow \infty$$
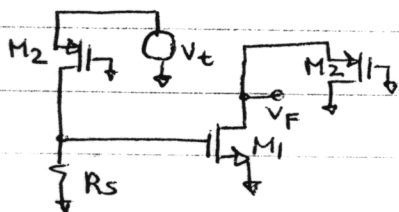
$$Z_{out,closed} = \frac{R_S + \frac{1}{g_{m2}}}{g_{m1} R_S} = \frac{1}{g_{m1}} + \frac{1}{g_{m1} g_{m2} R_S}$$



$$\frac{v_F}{V_t} = g_{m2} R_S \frac{g_{m1}}{g_{m2}} = g_{m1} R_S$$

$$Z_{in,open} = r_{o2}$$


$$Z_{out,open} = \frac{1}{g_{m2}}$$

$$\left. \frac{v_{out}}{\frac{v_{in}}{R_S}} \right|_{open} = R_S \cdot \frac{g_{m1}}{g_{m2}}$$

$$A_{v,closed} = \frac{g_{m1}/g_{m2}}{1 + g_{m1} R_S}$$

$$Z_{in,closed} = \infty$$
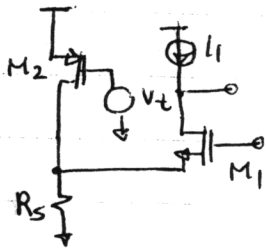
$$Z_{out,closed} = \frac{1}{g_{m2}(1 + g_{m1} R_S)}$$




$$R_S g_{m2} V_t \frac{r_{o1}}{R_S + \frac{1}{g_{m1}}} = V_F \Rightarrow \text{loop gain: } \frac{R_S g_{m2} r_{o1}}{R_S + \frac{1}{g_{m1}}}$$

$$R_{out,open} = g_{m1} r_{o1} R_S + r_{o1} + R_S \approx g_{m1} r_{o1} R_S$$

$$R_{in,open} = \frac{1}{g_{m1}}$$

$$\frac{V_{out}}{V_{in}} \Big|_{open} = \frac{r_{o1}}{R_S + \frac{1}{g_{m1}}}$$
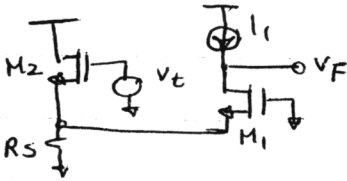
$$r_{o1} \rightarrow \infty \quad A_V = \frac{1}{R_S g_{m2}} \quad R_{in} = 0 \quad R_{out} = \frac{g_{m1} (R_S + \frac{1}{g_{m1}})}{g_{m2}}$$



$$\text{loop gain: } V_t \cdot \frac{R_S \parallel \frac{1}{g_{m1}}}{\frac{1}{g_{m2}} + R_S \parallel \frac{1}{g_{m1}}} \cdot g_{m1} r_{o1} = V_F$$

$$R_{in,open} = \frac{1}{g_{m1} + g_{m2}}$$

$$R_{out,open} = g_{m1} r_{o1} (R_S \parallel \frac{1}{g_{m2}})$$


$$A_{V,open} \Rightarrow \frac{V_{in}}{R_S} (R_S \parallel \frac{1}{g_{m2}}) \times g_{m1} r_{o1} = V_{out} \Rightarrow A_{V,open} = \frac{g_{m1} r_{o1} (R_S \parallel \frac{1}{g_{m2}})}{R_S}$$

$$r_{o1} \rightarrow \infty \quad A_{V,closed} = \frac{(R_S \parallel \frac{1}{g_{m2}}) (\frac{1}{g_{m2}} + R_S \parallel \frac{1}{g_{m1}})}{R_S (R_S \parallel \frac{1}{g_{m1}})}$$

$$R_{in,closed} = 0$$


$$R_{out,closed} = \frac{(R_S \parallel \frac{1}{g_{m2}}) (\frac{1}{g_{m2}} + R_S \parallel \frac{1}{g_{m1}})}{R_S \parallel \frac{1}{g_{m1}}}$$

8.4

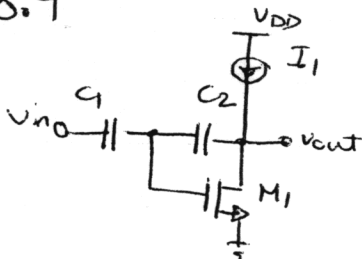

$$R_{in} = \frac{1}{C_1 S} + \frac{1}{g_m}$$

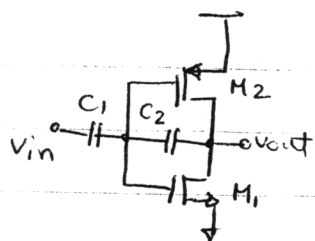
$$R_{out} = \frac{r_o}{1 + \frac{C_2}{C_1 + C_2} g_{m1} r_o} = \frac{C_1 + C_2}{g_{m1} C_2}$$



using the results in part (a)

$$R_{in} = \frac{1}{C_1 s} + \frac{1}{g_{m1} + g_{m2}}$$
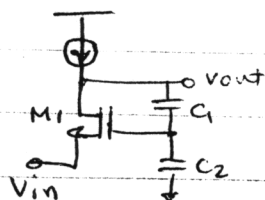
$$R_{out} = \frac{C_1 + C_2}{(g_{m1} + g_{m2}) C_2}$$



$$\text{loop gain} = g_{m1} r_o \frac{C_1}{C_1 + C_2}$$

$$R_{in \text{ closed}} = \frac{1}{g_{m1}} + \frac{1}{C_2 s}$$

$$R_{out \text{ closed}} = \frac{r_o}{1 + g_{m1} r_o \frac{C_1}{C_1 + C_2}} = \frac{C_1 + C_2}{g_{m1} C_1}$$

8.5

$$- \frac{1}{\left(1 + \frac{1}{g_{m1} r_{o1}}\right) \frac{C_2}{C_1} + \frac{1}{g_{m1} r_{o1}}} = -0.95 \frac{C_1}{C_2} \Rightarrow \frac{C_1}{C_2} = 1.63$$

$g_{m1} r_{o1} = 50$

Open loop output impedance: r_o

$$\text{loop gain: } \frac{C_2}{C_1 + C_2} g_m r_o$$

$$\text{closed loop } R_{out} = \frac{r_o}{1 + \frac{C_2}{C_1 + C_2} g_m r_o} = 0.49 r_o$$

8.6

$$R_{in, closed} = \frac{1}{g_{m1}} \cdot \frac{1}{1 + g_{m2} R_D \frac{C_1}{C_1 + C_2}} \quad I_1 = I_2 \Rightarrow g_{m2} = \sqrt{2} g_{m1}$$

$$= \frac{1}{g_{m1}} \cdot \frac{1}{1 + 1000 \sqrt{2} g_{m1}} = 50 \Rightarrow g_{m1} = 3.42 \text{ mV}$$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \Rightarrow I_D = \frac{(3.42 \times 10^{-3})^2}{2 \times 1.342 \times 10^{-4} \times 100} = 435 \mu A$$

8.7

$$\frac{V_x}{I_x} = \frac{R_D}{1 + \frac{g_{m2} R_S (g_{m1} + g_{mb1}) R_D}{(g_{m1} + g_{mb1}) R_S + 1}} \cdot \frac{C_1}{C_1 + C_2} \quad R_D \rightarrow \infty = \frac{(g_{m1} + g_{mb1}) R_S + 1}{g_{m2} R_S (g_{m1} + g_{mb1})} \cdot \frac{C_1 + C_2}{C_1}$$

$$\text{if } (g_{m1} + g_{mb1}) R_S \gg 1 \Rightarrow \frac{V_x}{I_x} = \frac{1}{g_{m2}} \cdot \frac{C_1 + C_2}{C_1}$$

8.8

If f_{-3dB} of each stage is ω_0

$$\left| \frac{1}{\left(1 + \frac{s}{\omega_0}\right)^n} \right| = \frac{1}{\sqrt{2}} \Rightarrow \left(1 + \left(\frac{\omega}{\omega_0}\right)^2\right)^n = 2$$

if we indicate the Gain f_{-3dB} as $k = \text{const}$

$$\Rightarrow \left(\frac{K}{\omega_0}\right)^n = 500$$

$$\Rightarrow \frac{\ln 2}{\ln(1 + (\frac{\omega}{\omega_0})^2)} = \frac{\ln 500}{\ln(\frac{K}{\omega_0})} \Rightarrow 1 + (\frac{\omega}{\omega_0})^2 = \left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}}$$

$$\Rightarrow \omega = \omega_0 \sqrt{\left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} - 1}$$


$$\frac{d\omega}{d\omega_0} = 0 \Rightarrow \sqrt{\left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} - 1} + \frac{\omega_0}{2} \cdot \frac{1}{\sqrt{\left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} - 1}} \cdot \left(-\frac{\ln 2}{\ln 500} \cdot \frac{1}{\omega_0} \cdot \left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}}\right) = 0$$

$$\Rightarrow \left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} - 1 - \frac{1}{2} \frac{\ln 2}{\ln 500} \left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} = 0 \Rightarrow \frac{K}{\omega_0} = 1.67$$

$\Rightarrow$ Gain per stage = 1.67

Stage BW = 598 MHz

8.9

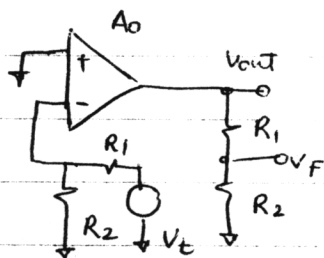

$$A_{open} = A_0 \frac{R_2}{R_1 + R_2 + R_0}$$

$$R_{out, open} = R_0 \parallel (R_1 + R_2)$$

Loop gain =

$$\left(\frac{R_2}{R_1 + R_2}\right) A_0 \left(\frac{R_2}{R_0 + R_1 + R_2}\right)$$

$$A_{closed} = \frac{A_0 \frac{R_2}{R_0 + R_1 + R_2}}{1 + \left(\frac{R_2}{R_1 + R_2}\right) A_0 \left(\frac{R_2}{R_0 + R_1 + R_2}\right)}$$

$$R_{out, closed} = \frac{R_0 \parallel (R_1 + R_2)}{1 + \left(\frac{R_2}{R_1 + R_2}\right) A_0 \left(\frac{R_2}{R_0 + R_1 + R_2}\right)}$$


8.10

$$\frac{1 + \frac{C_2}{C_1}}{\left(1 + \frac{C_2}{C_1}\right) \frac{1}{g_{m1}(r_{o2} \parallel r_{o4})} + 1} = 0.95 \left(1 + \frac{C_2}{C_1}\right)$$

↑
5% gain error

$$g_{m1}(r_{o2} \parallel r_{o4}) \approx 24.4$$
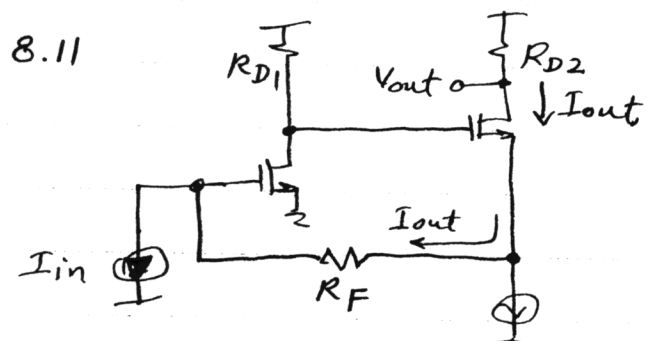
$$\Rightarrow 1 + \frac{C_2}{C_1} \leq 1.28$$



I_{out} fully flows through $R_F \Rightarrow I_{out} = I_{in}$
and $V_{out} = I_{out} \cdot R_{D2}$.

Thus, the transimpedance is equal to R_{D2} .
(continued on next page)

8.11 (cn'td)

$$-\underbrace{(I_{out} R_S + V_{nRS} + V_{nRF} + V_{n1})}_{V_Y} g_{m1} R_D \xrightarrow{+V_{nRD} + V_{n2}} V_X$$

$$(V_X - V_Y) g_{m2} = I_{out}$$

$$\Rightarrow g_{m2} [(I_{out} R_S + V_{nRS} + V_{nRF} + V_{n1})(-g_{m1} R_D) + V_{nRD} + V_{n2} - (I_{out} R_S + V_{nRS})] = I_{out}$$

$$\Rightarrow I_{out} [1 + g_{m2} R_S (g_{m1} R_D + 1)] = g_{m2} \left[-g_{m1} R_D - 1 \right] V_{nRS} - g_{m1} R_D V_{nRF} - g_{m1} R_D V_{n1} + V_{nRD} + V_{n2}$$

$$\Rightarrow I_{out} = \frac{g_{m2} [-(1 + g_{m1} R_D) V_{nRS} - g_{m1} R_D V_{nRF} - g_{m1} R_D V_{n1} + V_{nRD} + V_{n2}]}{1 + g_{m2} R_S (1 + g_{m1} R_D)}$$


If we apply a current of I_{in} to the input, the resulting output current is obtained as :

$$\left\{ \underbrace{[(I_{in} + I_{out}) R_S + I_{in} R_F]}_{V_X} (-g_{m1} R_D) - \underbrace{(I_{in} + I_{out}) R_S}_{V_Y} \right\} g_{m2} = I_{out}$$


$$\frac{I_{out}}{I_{in}} = \frac{[-g_{m1} R_D (R_S + R_F) - R_S] g_{m2}}{1 + g_{m2} R_S (1 + g_{m1} R_D)}$$

Dividing the output noise current by the gain yields the input-referred noise current:
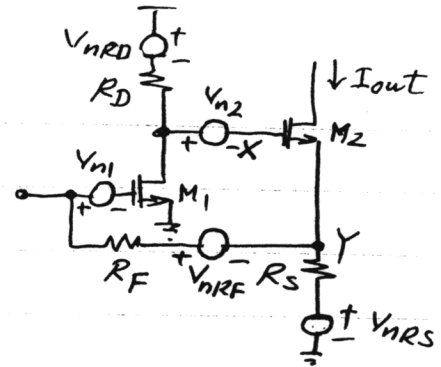
$$I_{n,in} = \frac{-(1 + g_{m1} R_D) V_{nRS} - g_{m1} R_D V_{nRF} - g_{m1} R_D V_{n1} + V_{nRD} + V_{n2}}{-g_{m1} R_D (R_S + R_F) - R_S}$$



8.12

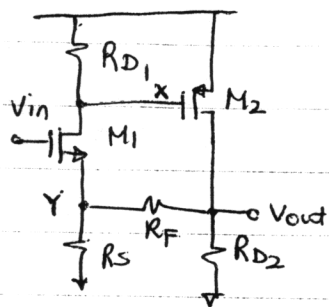

$$I_{D2} = 1 \text{ mA} \Rightarrow \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_X - |V_{TP}|)^2 = 1 \text{ mA}$$

$$\Rightarrow V_X = 1.478$$

$$I_{D1} = 761 \mu\text{A}$$

$$\begin{cases} \frac{V_Y}{2\text{k}} + \frac{V_Y - V_{out}}{2\text{k}} = 761 \mu\text{A} & \Rightarrow V_{out} = 1.841 \\ \frac{V_{out}}{2\text{k}} + \frac{V_{out} - V_Y}{2\text{k}} = 1 \text{ mA} & \Rightarrow V_Y = 1.681 \end{cases}$$

$$I_{D1} = 0.761 \text{ mA} \Rightarrow \frac{1}{2} \times 1.342 \times 10^{-4} \times 100 (V_{in} - V_Y - V_{TN})^2 = 0.761 \text{ mA}$$

$$V_{in} - V_Y = 1.037 \Rightarrow V_{in} = 2.717 \text{ V}$$

$$G_{21} = 0.5$$

$$\begin{cases} g_{m1} = \frac{2 \times 0.761 \text{ mA}}{1.037 - 0.7} = 4.52 \text{ mS} \\ g_{m2} = \frac{2 \times 1 \text{ mA}}{1.522 - 0.8} = 2.77 \text{ mS} \end{cases}$$

$$A_{v_{open}} = \frac{-2\text{k}}{1\text{k} + \frac{1}{4.52 \text{ mS}}} \left[-2.77 \left[2\text{k} \parallel 4\text{k} \right] \right] = 6.048$$

$$A_{v_{closed}} = \frac{6.048}{1 + 3.024} = 1.503$$

8.13

problem 8.9


$$R_{out} = \frac{R_o (R_1 + R_2)}{R_o + R_1 + R_2 + \frac{R_2^2}{R_1 + R_2} \cdot \frac{A_o}{1 + \frac{s}{\omega_o}}}$$

Zero: ω_o

$$\text{pole: } \omega_o + \frac{A_o R_2^2}{(R_1 + R_2)(R_o + R_1 + R_2)} \omega_o$$


$$\text{DC value: } \frac{R_o (R_1 + R_2)}{R_o + R_1 + R_2 + A_o R_2^2 / (R_1 + R_2)}$$
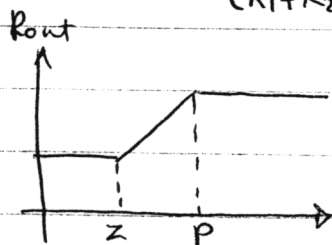
$$\text{final value: } R_o \parallel (R_1 + R_2)$$



The output impedance is less reduced, as the loop gain gets smaller.

8.12

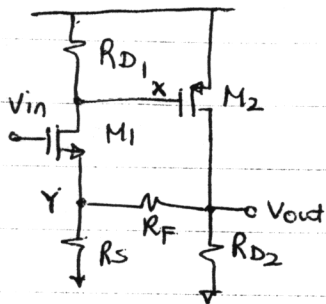

$$I_{D2} = 1 \text{ mA} \Rightarrow \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_X - |V_{TP}|)^2 = 1 \text{ mA}$$

$$\Rightarrow V_X = 1.478$$

$$I_{D1} = 761 \mu\text{A}$$

$$\begin{cases} \frac{V_Y}{2\text{k}} + \frac{V_Y - V_{out}}{2\text{k}} = 761 \mu\text{A} \Rightarrow V_{out} = 1.841 \\ \frac{V_{out}}{2\text{k}} + \frac{V_{out} - V_Y}{2\text{k}} = 1 \text{ mA} \Rightarrow V_Y = 1.681 \end{cases}$$

$$I_{D1} = 0.761 \text{ mA} \Rightarrow \frac{1}{2} \times 1.342 \times 10^{-4} \times 100 (V_{in} - V_Y - V_{TN})^2 = 0.761 \text{ mA}$$

$$V_{in} - V_Y = 1.037 \Rightarrow V_{in} = 2.717 \text{ V}$$

$$G_{21} = 0.5$$

$$\begin{cases} g_{m1} = \frac{2 \times 0.761 \text{ mA}}{1.037 - 0.7} = 4.52 \text{ mS} \\ g_{m2} = \frac{2 \times 1 \text{ mA}}{1.522 - 0.8} = 2.77 \text{ mS} \end{cases}$$


$$A_{V_{open}} = \frac{-2\text{k}}{1\text{k} + \frac{1}{4.52 \text{ mS}}} \left[-2.77 \left[2\text{k} \parallel 4\text{k} \right] \right] = 6.048$$

$$A_{V_{closed}} = \frac{6.048}{1 + 3.024} = 1.503$$

8.13


problem 8.9

$$R_{out} = \frac{R_o (R_1 + R_2)}{R_o + R_1 + R_2 + \frac{R_2^2}{R_1 + R_2} \cdot \frac{A_o}{1 + \frac{s}{\omega_o}}}$$

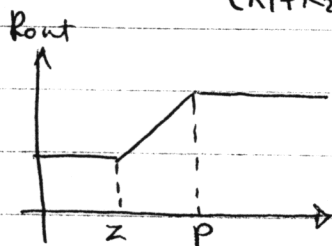
Zero: ω_o pole: $\omega_o + \frac{A_o R_2^2}{(R_1 + R_2)(R_o + R_1 + R_2)} \omega_o$ DC value: $\frac{R_o (R_1 + R_2)}{R_o + R_1 + R_2 + A_o R_2^2 / (R_1 + R_2)}$ final value: $R_o \parallel (R_1 + R_2)$ 

The output impedance is less reduced, as the loop gain gets smaller.

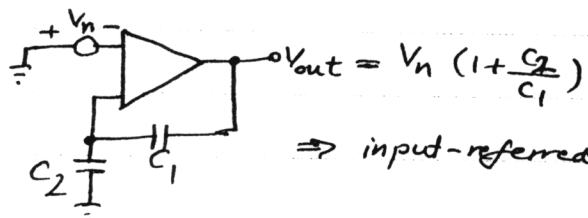8.14 The input-referred noise voltage of the circuit is the same as that of the open-loop circuit:


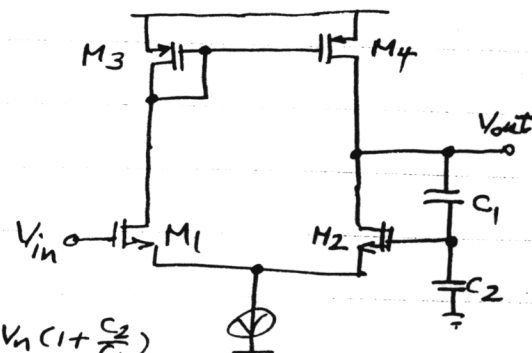
$$\Rightarrow \text{input-referred noise} = \frac{V_n(1 + \frac{C_2}{C_1})}{1 + \frac{C_2}{C_1}} = V_n$$



The noise produced by M_1 - M_4 referred to the input is:

$$\overline{V_n^2} = 4kT \left(\frac{2}{3g_{m1,2}} + 2 \frac{2g_{m3,4}}{3g_{m1,2}^2} \right) + 2 \frac{K_N}{(WL)_{1,2} C_{ox} f} + 2 \frac{K_P}{(WL)_{3,4} C_{ox} f} \times \frac{g_{m3,4}^2}{g_{m1,2}^2}$$

8.15


a) $Z_{in, open} = R_o$

$$Z_{in, closed} = \frac{R_o}{1 + G_{m1} G_{m2} R_o \frac{R_o}{1 + R_o C_1 s}} = \frac{R_o(1 + R_o C_1 s)}{R_o C_1 s + 1 + G_{m1} G_{m2} R_o^2}$$

Zero: $\frac{1}{R_o C_1}$

Pole: $\frac{1 + G_{m1} G_{m2} R_o^2}{R_o C_1}$

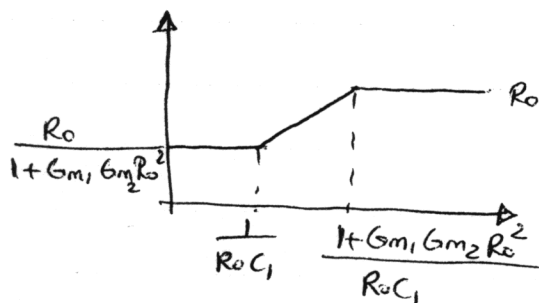DC: $\frac{R_o}{1 + G_{m1} G_{m2} R_o^2}$ Final: R_o



b) Heavy feedback at lower frequency. As frequency increases, feedback weakens since the output impedance of the feedforward amplifier reduces

8.15 (c) For input-referred noise voltage, we short the input,


$$\text{hence } \overline{V_{n,out}^2} = 4kT \times 2 \left(\frac{2}{3}g_m + \frac{1}{R_0} \right) \left(R_0 \parallel \frac{1}{C_1 s} \right).$$

Dividing this by the voltage gain, $g_m \left(R_0 \parallel \frac{1}{C_1 s} \right)^2$, we have

$$\overline{V_{n,in}^2} = 8kT \left(\frac{2}{3g_m} + \frac{1}{g_m^2 R_0} \right).$$

For the input noise current, we leave the input open.

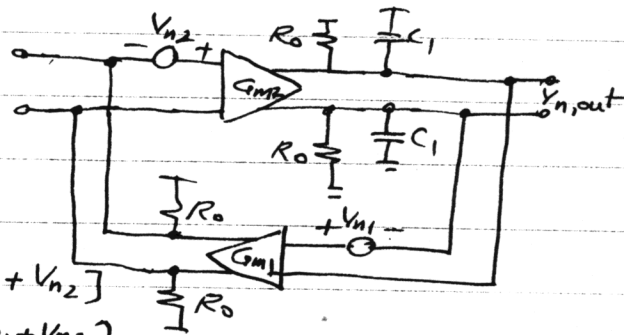Here, V_{n1} and V_{n2} represent the input noise of each differential pair (including the noise of resistors).



$$\begin{aligned} -V_{n,out} &= G_{m2} \left(R_0 \parallel \frac{1}{C_1 s} \right) \left[(V_{n,out} + V_{n1}) G_{m1} R_0 + V_{n2} \right] \\ \Rightarrow V_{n,out} &= - \frac{G_{m2} \left(R_0 \parallel \frac{1}{C_1 s} \right) (G_{m1} R_0 V_{n1} + V_{n2})}{1 + G_{m2} \left(R_0 \parallel \frac{1}{C_1 s} \right) G_{m1} R_0} \end{aligned}$$

If we apply current between the two input terminals with value I_{in} , the output voltage is obtained as:

$$\begin{aligned} -V_{out} &= (V_{out} G_{m1} + I_{in}) R_0 \cdot G_{m2} \left(R_0 \parallel \frac{1}{C_1 s} \right) \\ \Rightarrow \frac{V_{out}}{I_{in}} &= - \frac{G_{m2} R_0 \left(R_0 \parallel \frac{1}{C_1 s} \right)}{1 + G_{m1} G_{m2} R_0 \left(R_0 \parallel \frac{1}{C_1 s} \right)} \end{aligned}$$

Dividing $V_{n,out}$ by this gain gives the input-referred noise

$$\text{current: } I_{n,in} = \frac{G_{m1} R_0 V_{n1} + V_{n2}}{R_0} \Rightarrow \overline{I_{n,in}^2} = G_{m1}^2 \overline{V_{n1}^2} + \frac{\overline{V_{n2}^2}}{R_0^2}$$


8.16

a) Due to symmetry of the π network, no current flows through R_F .

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - R_{S1} I_{D1} - V_{Tn})^2 = 0.5 \text{ mA}$$

$$(V_{in} - 2.2)^2 = \frac{2 \times 0.5 \times 10^{-3}}{1.342 \times 10^{-4} \times 100} \Rightarrow V_{in} = 2.473 \text{ V}$$
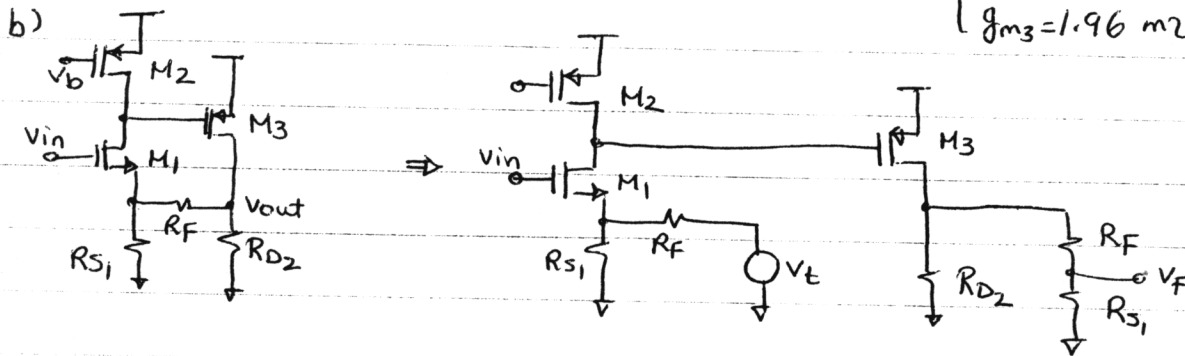
$$\begin{cases} g_{m1} = 3.66 \text{ mS} \\ g_{m2} = 1.96 \text{ mS} \\ g_{m3} = 1.96 \text{ mS} \end{cases} \begin{cases} r_{o1} = 20 \text{ k}\Omega \\ r_{o2} = 10 \text{ k}\Omega \\ r_{o3} = 10 \text{ k}\Omega \end{cases}$$



$$A_{v_{open}} = \frac{r_{o2}}{R_{S1} \parallel R_F + \frac{1}{g_{m1}}} \times g_{m3} [r_{o3} \parallel R_{D2} \parallel (R_F + R_{S1})] = 18.42$$


$$R_{out_{open}} = r_{o3} \parallel R_{D2} \parallel (R_F + R_{S1}) = 1.667 \text{ k}\Omega$$

$$\begin{aligned} \text{Loop gain: } \frac{V_t}{R_F} \times (R_F \parallel R_{S1}) \times \frac{r_{o2}}{R_{S1} \parallel R_F + \frac{1}{g_{m1}}} \times g_{m3} [r_{o3} \parallel R_{D2} \parallel (R_F + R_{S1})] \times \frac{R_{S1}}{R_F + R_{S1}} \\ = V_F \Rightarrow \text{loop gain} = 4.605 \end{aligned}$$

$$A_v = \frac{18.42}{1 + 4.605} = 3.286$$

$$R_{out} = \frac{1.667 \text{ k}\Omega}{1 + 4.605} = 297 \Omega$$

8.17

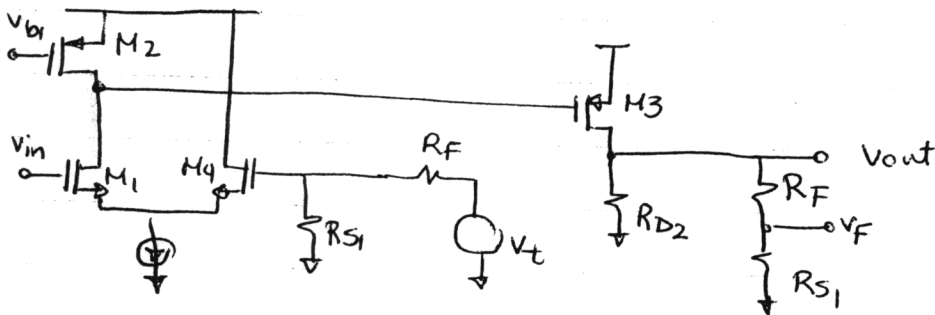

$$\begin{aligned}
 r_{o1} &= r_{o4} = 20k \\
 r_{o3} &= 10k \quad r_{o2} = 10k \\
 g_{m1} &= g_{m4} = 3.66 \text{ mS} \\
 g_{m2} &= g_{m3} = 1.96 \text{ mS}
 \end{aligned}$$

$$A_{v_{open}} = \frac{1}{2} g_{m1} (r_{o1} \parallel r_{o2}) g_{m3} (r_{o3} \parallel R_{D2} \parallel (R_F + R_{S1})) = 39.85$$

$$R_{out} = r_{o3} \parallel R_{D2} \parallel (R_F + R_{S1}) = 1.667k$$

$$V_t \frac{R_{S1}}{R_{S1} + R_F} \times \frac{g_{m1}}{2} \times (r_{o1} \parallel r_{o2}) g_{m3} (r_{o3} \parallel R_{D2} \parallel (R_F + R_{S1})) \frac{R_{S1}}{R_{S1} + R_F} = V_F$$

$$\text{loop gain} = 9.96$$

$$A_v = \frac{39.85}{1 + 9.96} = 3.63$$

$$R_{out} = \frac{1.667k}{1 + 9.96} = 153\Omega$$

Smaller output impedance compared to 8.16.

8.14

8.18

$$a) I_{Dn} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GSn} - V_{THn})^2 \Rightarrow V_{GSn} = 0.973V$$

$$V_{GSp} = 1.311 \Rightarrow 3 - V_b = 1.311 \Rightarrow V_b = 1.69$$

$$V_{in} = R_1 \times I + V_{GSn}$$

$$M_3: \text{saturation} \Rightarrow -V_A + V_b > |V_{THp}| \Rightarrow V_A < 1.689 - 0.8 = 0.889$$


$$M_4: \text{saturation} \Rightarrow -V_{out} + V_b > V_{THp} \Rightarrow V_{out} < 0.889 \Rightarrow R_1 I < 0.889 \Rightarrow R_1 < 177$$

$$M_1: \text{saturation} \Rightarrow V_A > R_1 I + (V_{GS1} - V_{THn}) \Rightarrow 0.273 + R \times 0.5m < 0.889$$

$$\Rightarrow R_1 < 1232$$

$$M_2: \text{saturation: } V_{out} = R_1 I > V_A - V_{tn} \Rightarrow R_1 > \frac{0.889 - 0.7}{0.5 \times 10^{-3}} = 378 \Omega$$
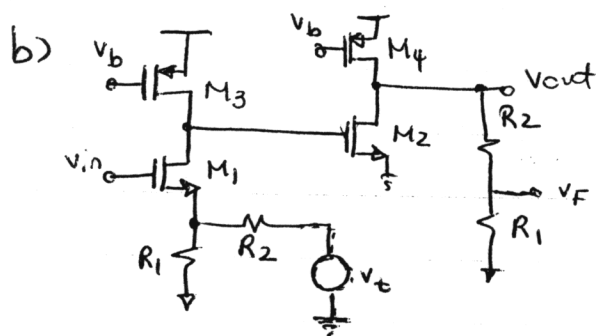
$$378 \leq R_1 \leq 1232 \Rightarrow 1.162 \leq V_{in} \leq 1.589$$



$$R_1 = 805 \Omega$$

$$r_{o1} = r_{o2} = 20k$$

$$g_{m1} = 3.66 mS$$

$$r_{o3} = r_{o4} = 10k$$

$$g_{m2} = 3.66 mS$$

$$\text{open loop gain} = \frac{r_{o3}}{R_1 \parallel R_2 + \frac{1}{g_{m1}}} \times g_{m2} (r_{o4} \parallel (R_1 + R_2) \parallel r_{o2}) = 97.6$$

$$\text{Output impedance} = r_{o4} \parallel (R_1 + R_2) \parallel r_{o2} = 2422 \Omega$$


$$\text{loop gain: } \frac{V_t}{R_2} \times (R_1 \parallel R_2) \times \frac{r_{o3}}{R_1 \parallel R_2 + \frac{1}{g_{m1}}} \times g_{m2} (r_{o4} \parallel (R_1 + R_2) \parallel r_{o2}) \frac{R_1}{R_1 + R_2} = V_F$$

$$\Rightarrow \text{loop gain} = \frac{1}{3000} \times 635 \times 97.6 \times \frac{805}{3805} = 4.37$$


$$A_v = \frac{97.6}{1 + 4.37} = 18.17$$

$$R_{out} = \frac{2422}{1 + 4.37} = 451 \Omega$$


8.19

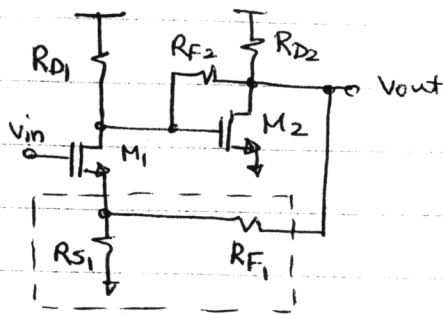

Voltage - Voltage

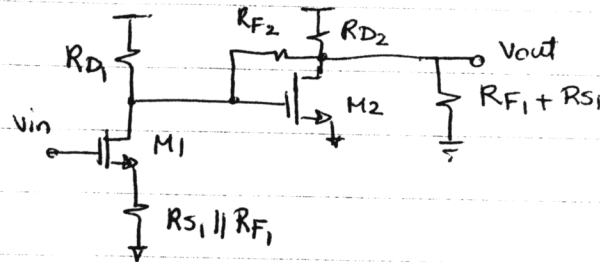

next we consider

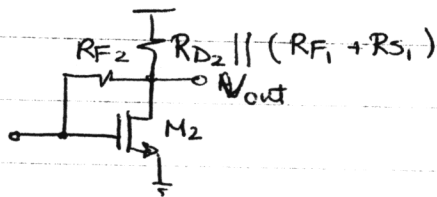

$$R_{in2} = \frac{R_{F2}}{1 + g_{m2} [R_{D2} \parallel (R_{F1} + R_{S1})]} = 261 \Omega$$

$$R_{out2} = \frac{R_{D2} \parallel (R_{F1} + R_{S1})}{1 + g_{m2} [R_{D2} \parallel (R_{F1} + R_{S1})]} = 174 \Omega$$


$$A_{v2} = \frac{R_D}{R_D + R_{F2}} (-g_{m2} R_{F2} + 1) = -3.6$$

$$R_D = R_{D2} \parallel (R_{F1} + R_{S1}) = 1333$$

$$\text{Open loop gain} = - \frac{R_{D1} \parallel R_{in2}}{R_{S1} \parallel R_{F1} + \frac{1}{g_{m1}}} \cdot A_{v2} = \frac{231}{1000 + 200} \times 3.6 = 0.69$$

$$\text{Open loop output impedance} = R_{out2} = 174 \Omega$$

loop gain:

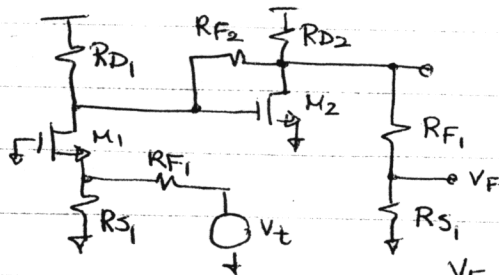

$$\frac{V_t}{R_{F1}} \times (R_{S1} \parallel R_{F1}) \times \frac{R_{D1}}{R_{S1} \parallel R_{F1} + \frac{1}{g_{m1}}} \times A_{v2} \times \frac{R_{S1}}{R_{S1} + R_{F1}} = V_F$$

$$\frac{V_F}{V_t} = \frac{1}{2000} \times 1000 \times \frac{1000}{1200} \times 3.6 \times \frac{1}{2} = 0.75$$

$$A_{v_{closed}} = \frac{0.69}{1 + 0.75} = 0.394$$

$$R_{out_{closed}} = \frac{174}{1 + 0.75} = 99.5 \Omega$$

8.20

$$I_{D1} = I_{D2} \Rightarrow V_{in} = 1.2538 \Rightarrow I_D = 2.316 \text{ mA}$$

$$g_{m1} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{THn}) = 1.342 \times 10^{-4} \times 100 \times (1.2538 - 0.7) = 7.432 \text{ mS}$$

$$g_{m2} = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{THp}) = 3.835 \times 10^{-5} \times 100 \times (3 - 1.2538 - 0.8) = 3.628 \text{ mS}$$

$$r_{o1} = \frac{1}{\lambda_1 I_{D1}} = \frac{1}{0.1 \times 2.316 \times 10^{-3}} = 4.317 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_2 I_{D2}} = \frac{1}{0.2 \times 2.316 \times 10^{-3}} = 2.159 \text{ k}\Omega$$

(a)

$$a) A_v = -(g_{m1} + g_{m2})(r_{o1} \parallel r_{o2}) = -(7.432 + 3.628)1.439 = -15.91$$

$$R_{out} = r_{o1} \parallel r_{o2} = 1439 \Omega$$

$$b) A_v = \frac{1}{R_1} \cdot \frac{-(R_1 \parallel R_2)(g_{m1} + g_{m2})(R_2 \parallel r_{o1} \parallel r_{o2})}{1 + (g_{m1} + g_{m2})(R_2 \parallel r_{o1} \parallel r_{o2}) \frac{R_1}{R_1 + R_2}}$$

(eq. 8.70)


$$= \frac{1}{1} \times \frac{0.909(7.432 + 3.628)1.258}{1 + (7.432 + 3.628)1.258 \times \frac{1}{11}} = 5.58$$

$$R_{out} = \frac{R_2 \parallel r_{o1} \parallel r_{o2}}{1 + (g_{m1} + g_{m2})(R_2 \parallel r_{o1} \parallel r_{o2}) \frac{R_1}{R_1 + R_2}} = 1.258 \text{ k}\Omega / 2.26 = 556 \Omega$$

$$R_{out} = 1.258 \text{ k}\Omega / 2.26 = 556 \Omega$$

(b) We figure out sensitivity for (b), (a) is a special case where

$$R_1 = 0 \quad R_2 = \infty$$

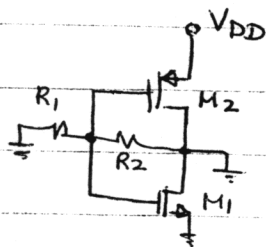


$$G_m = g_{m2}$$

$$R_{out} = \text{same as before}$$

$$A_v = \frac{g_{m2}(R_2 \parallel r_{o1} \parallel r_{o2})}{1 + (g_{m1} + g_{m2})(R_2 \parallel r_{o1} \parallel r_{o2}) \frac{R_1}{R_1 + R_2}} = \frac{3.628 \times 1.258}{1 + 13.913 \times \frac{1.258}{11}} = 1.76$$

if $R_1 = 0$ and $R_2 = \infty$
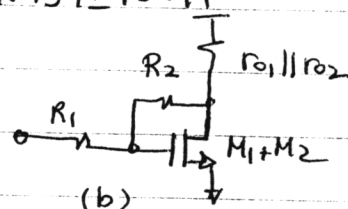
$$A_v = g_{m2}(r_{o1} \parallel r_{o2}) = 3.628 \times 1.439 = 5.217$$



8.21



$$a) \quad \overline{V_{out}^2} = 4KT \frac{2}{3} (g_{m1} + g_{m2}) (r_{o1} || r_{o2})^2$$

$$\overline{V_{in}^2} = \frac{4KT \frac{2}{3}}{g_{m1} + g_{m2}} =$$

$$b) \quad \overline{V_{in}^2} = 4KT R_1 + \frac{\left[\frac{4KT}{R_2} + 4KT \frac{2}{3} (g_{m1} + g_{m2}) \right] R_o^2}{A_v^2} = 4KT R_1 + \frac{\frac{4KT}{R_2} + 4KT \frac{2}{3} (g_{m1} + g_{m2})}{\left(\frac{R_2}{R_1 + R_2} \right)^2 (g_{m1} + g_{m2})}$$

$$= 4KT R_1 + \frac{4KT \frac{2}{3}}{g_{m1} + g_{m2}} + \frac{4KT/R_2}{\left(\frac{R_2}{R_1 + R_2} \right)^2 (g_{m1} + g_{m2})^2}$$

8.22

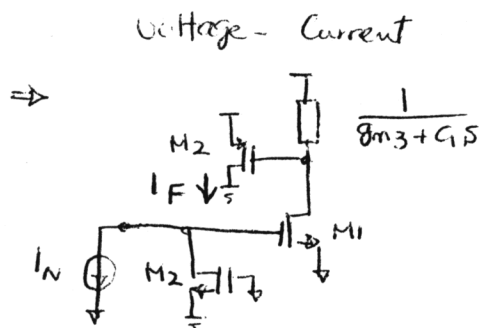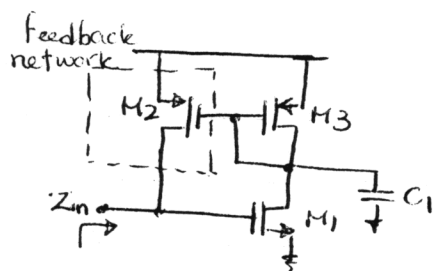

$$\left| \frac{I_F}{I_N} \right| = r_{o2} \cdot g_{m1} \cdot \frac{1}{g_{m3} + C_1 s} \cdot g_{m2}$$


$$Z_{in, open} = r_{o2}$$

$$Z_{in, closed} = \frac{r_{o2}}{1 - r_{o2} g_{m1} g_{m2} \frac{1}{g_{m3} + C_1 s}} = - \frac{g_{m3} + C_1 s}{g_{m1} g_{m2}} \quad r_{o2} \rightarrow \infty$$

$$= - \frac{g_{m3}}{g_{m1} g_{m2}} - \underbrace{\frac{C_1}{g_{m1} g_{m2}}}_s$$

8.23

Very low freq.

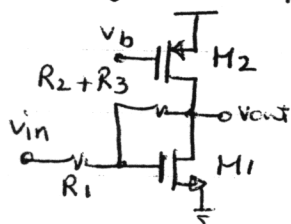


eq. (8.70)

$$A_v = \frac{1}{R_1} \cdot \frac{-(R_1 \parallel (R_2 + R_3)) g_{m1} (R_2 + R_3)}{1 + g_{m1} (R_2 + R_3) \frac{R_1}{R_1 + R_2 + R_3}}$$

$$= -\frac{1}{2k} \frac{(2114) \frac{1}{200} \times 4k}{1 + \frac{1}{200} \times 4k \times \frac{1}{3}}$$

$$= -1.739$$

very high freq.

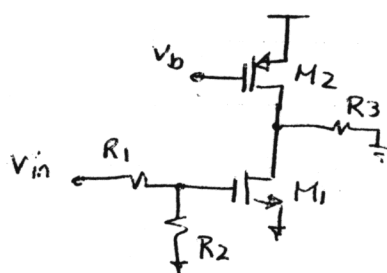

$$A_v = \frac{R_2}{R_1 + R_2} (-g_{m1} R_3)$$


$$= \frac{1}{2} \left(-\frac{1}{200} \times 2000 \right) = -5$$

Chapter 9

Problem 9.1

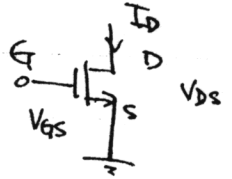(a) For a MOSFET in triode region,

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad (*)$$



Transconductance, $g_m = \frac{\partial I_D}{\partial V_{GS}}$ (from definition)

$$\frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} V_{DS}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{DS}$$

Output resistance, $r_o = \frac{\partial V_{DS}}{\partial I_D}$

Take derivative of (*) on both sides



$$1 = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T - V_{DS}) \frac{\partial V_{DS}}{\partial I_D}$$


$$r_o = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T - V_{DS})}$$

we know in saturation,

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) \quad \&$$



$$r_o = \frac{1}{\lambda I_D}$$

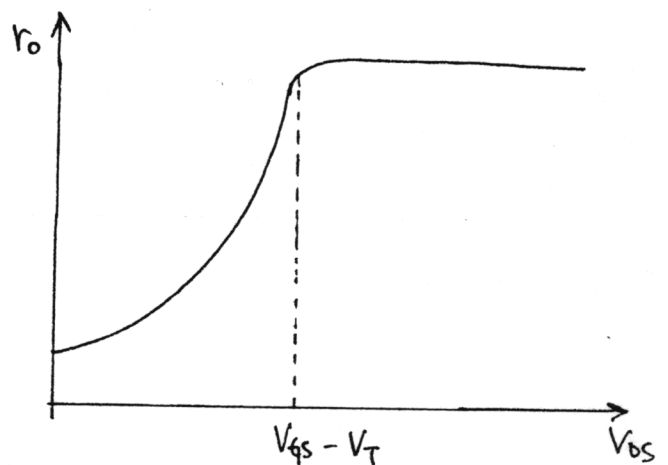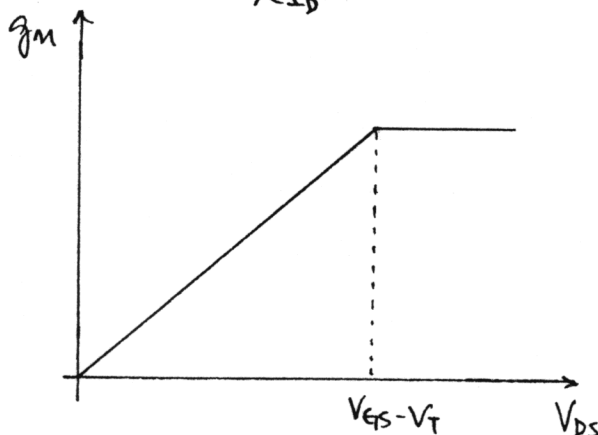

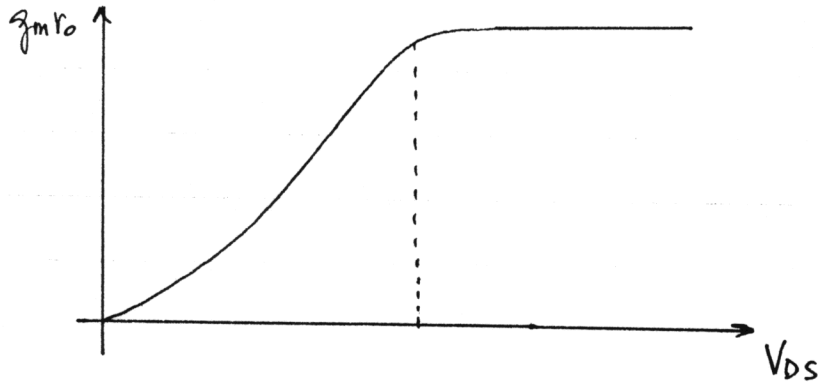

9.1 (b)

Use half-circuit concept:

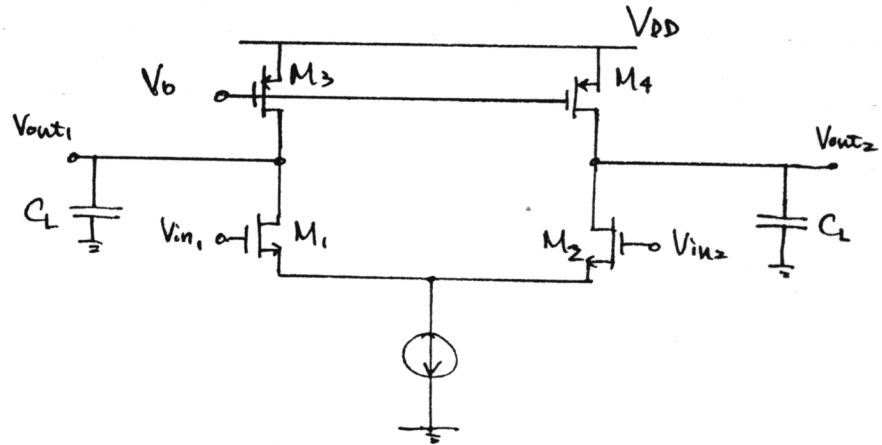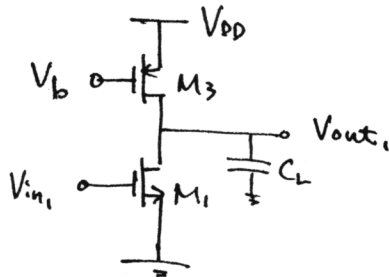

$$A_v = g_{m1} (r_{o1} \parallel r_{o2})$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \quad \text{where } I_D = \frac{I_{SS}}{2} = 0.5 \text{ mA}$$

$$C_{ox} (@ t_{ox} = 400 \text{ \AA}) = 0.863 \text{ fF}/\mu\text{m}^2 = 86.3 \times 10^{-9} \text{ F}/\text{cm}^2$$

$$C_{ox} (@ t_{ox} = 9 \times 10^{-9} \text{ m}) = \frac{86.3 \times 10^{-9}}{9 \times 10^{-9}} \times 400 \times 10^{-10} = 383.56 \text{ nF}/\text{cm}^2$$

$$g_{m1} = \left[2 \times (350 \text{ cm}^2/\text{V} \cdot \text{sec}) (383.56 \times 10^{-9} \text{ F}/\text{cm}^2) \left(\frac{50}{0.5 - 0.08 \times 2} \right) (0.5 \times 10^{-3} \text{ A}) \right]^{\frac{1}{2}}$$

$$= 4.443 \text{ m}\Omega^{-1}$$

$$r_{o1} = \frac{1}{\lambda_1 I_{D1}} = \frac{1}{(0.1)(1\text{V})(0.5 \text{ mA})}$$

$$= 20 \text{ k}\Omega$$

$$r_{o3} = \frac{1}{\lambda_3 I_{D3}} = \frac{1}{(0.2)(4\text{V})(0.5 \text{ mA})}$$

$$= 10 \text{ k}\Omega$$


$$A_v = g_{m1} (r_{o1} \parallel r_{o3})$$

$$= (4.443 \times 10^{-3} \Omega^{-1}) \left[\frac{20 \text{ k} \cdot 10 \text{ k}}{20 \text{ k} + 10 \text{ k}} \right] (\Omega)$$

$$= 29.6 = A_v$$

To find maximum output swing

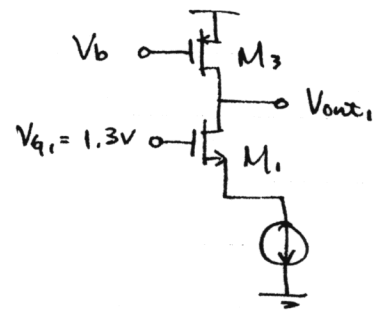If we require both transistors are in saturation,



$$V_{DS1} \geq V_{GS1} - V_T$$

$$V_{D1} - V_{S1} \geq V_{G1} - V_{S1} - V_T$$

$$V_{D1} \geq V_{G1} - V_T = 1.3 - 0.7 = 0.6 \text{ V.}$$

$$\Rightarrow V_{out1 \min} = 0.6 \text{ V}$$

For M_3 : $I_{D3} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L_3} (V_{GS3} - V_{TP})^2 (1 + \lambda V_{DS})$

For simplicity, assume channel length modulation is negligible, $\lambda \rightarrow 0$.

$$k_p' = \mu_p C_{ox}$$

$$= (100 \text{ cm}^2/\text{V}\cdot\text{sec}) (3.836 \times 10^{-7} \text{ F/cm}^2)$$

$$= 3.836 \times 10^{-5} \text{ A/V}^2$$

$$I_{D3} = 0.5 \text{ mA} = \frac{1}{2} k_p' \left(\frac{W}{L_{eff}} \right) (V_{GS3} - V_{TP})^2$$

$$V_{GS3} - V_{TP} = \left[\frac{(0.5 \text{ mA})(2)}{(3.836 \times 10^{-5} \text{ A/V}^2) \left(\frac{50}{0.5 - 0.09 \times 2} \right)} \right]^{\frac{1}{2}} = 0.408$$

$$V_{DS3} \geq V_{GS3} - V_{TP} = 0.408 \text{ V.}$$

$$V_{out1 \max} = V_{DD} - V_{DS3} = 3 \text{ V} - 0.408 \text{ V}$$

$$= 2.59 \text{ V.}$$

$$0.6 \text{ V} \leq V_{out1} \leq 2.59 \text{ V}$$

$$\therefore \text{One sided output swing} = 2.59 - 0.6 = 1.99 \text{ V.}$$

$$\boxed{\begin{aligned} \text{Differential output swing} &= (1.99 \times 2) \text{ V} \\ &= 3.98 \text{ V} \end{aligned}}$$

9.1 (c). From part (b), M_3 will enter the triode region when $V_{DS3} < V_{GS3} - V_{TP} = 0.408 \text{ V}$.

At the peak of the output swing $V_{DS3} = 0.408 - 50 \text{ mV}$
 $= 0.358 \text{ V}$

$$r_{o3} = \frac{1}{\mu_p C_{ox} \frac{W}{L_{eff}} (V_{GS3} - V_{TP} - V_{DS})} \quad (\text{from part a}).$$

$$= \left[(3.836 \times 10^{-5} \text{ A/V}^2) \left(\frac{50}{0.32} \right) (0.408 - 0.358) \right]^{-1}$$

$$= 3.337 \text{ k}\Omega.$$

$$A_v = g_{m1} (r_{o1} \parallel r_{o3})$$

$$= (4.443 \times 10^{-3} \text{ S}) \left(\frac{20 \times 3.337}{20 + 3.337} \text{ k}\Omega \right)$$

$$A_v = 12.7$$

Problem 9.2

(a) $V_b = 1.4V$ $I_{SS} = 1mA$ $(\frac{W}{L})_{1-4} = \frac{100}{0.5}$

To keep M_3 in saturation,

$$V_A > V_b - V_{THn} = 1.4V - 0.7V = 0.7V.$$

Assume $M_5 - M_8$ are identical,

So $V_{GS5} = V_{GS7}$

$$V_{GS5} = \frac{V_{DD} - V_A}{2} = \frac{3 - 0.7}{2} = 1.15V.$$

$$I_{D5} = \frac{1}{2} \mu_p C_{ox} (\frac{W}{L})_5 (V_{GS5} - V_{THp})^2 (1 + \lambda V_{DS5})$$


$$(\frac{W}{L})_{5, \text{eff}} = \frac{2I_{D5}}{\mu_p C_{ox} (V_{GS5} - V_{THp})^2 (1 + \lambda V_{DS})}$$

$$= \frac{2(0.5mA)}{(100)(3.836 \times 10^{-7})(1.15 - 0.8)^2 (1 + 0.2(1.15))} = 173.$$

$$W_5 = 173 \times L_{\text{eff}} = 173 \times (0.5 - 0.09 \times 2).$$

$$W_5 \approx 56 \mu m$$

$$W_{5-8} = 56 \mu m$$

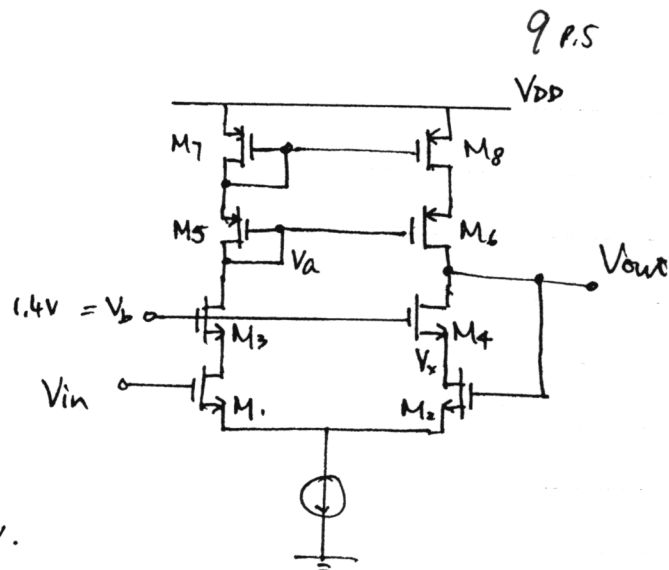

b, Max. output swing $= V_{TH4} - (V_{GS4} - V_{TH2}) = V_{TH4} + V_{TH2} - V_{GS4}$

$$I_{D4} = \frac{1}{2} \mu_n C_{ox} (\frac{W}{L})_4 (V_{GS4} - V_{TH4})^2 (1 + \lambda V_{DS4}) \quad \text{assume } \lambda \rightarrow 0 \text{ for simplicity}$$

$$V_{GS4} - V_{TH4} \approx \left[\frac{2I_D}{\mu_n C_{ox} (\frac{W}{L})_4} \right]^{\frac{1}{2}}$$

$$= \left[\frac{2(0.5mA)}{(350)(3.836 \times 10^{-7})(\frac{100}{0.34})} \right]^{\frac{1}{2}} = 0.159V$$

$$V_{GS4} = V_{TH4} + 0.159 = 0.859V$$

$$\text{Max. Output swing} = 0.7 + 0.7 - 0.859 = 0.541V$$

9.2 (c). $A_{v \text{ open loop}} = g_{m1} (g_{m4} r_{o4} r_{o2} \parallel g_{m6} r_{o6} r_{o8})$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_{\text{eff}} I_D}$$

$$= \sqrt{2(350)(383.6 \times 10^{-9}) \left(\frac{100}{0.34}\right) (0.5 \text{ mA})}$$

$$= 6.28 \text{ m}\Omega^{-1}$$

$$g_{m4} = g_{m1} = 6.28 \text{ m}\Omega^{-1}$$

$$g_{m6} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_{\text{eff}} I_D}$$

$$= \sqrt{2(100)(383.6 \times 10^{-9}) \left(\frac{56}{0.5 - 0.09 \times 2}\right) (0.5 \text{ mA})}$$

$$= 2.59 \text{ m}\Omega^{-1}$$

$$r_{o2} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(0.5 \text{ mA})} = 20 \text{ k}\Omega$$

$$r_{o4} = r_{o2} = 20 \text{ k}\Omega$$

$$r_{o6} = r_{o8} = \frac{1}{(0.2)(0.5 \text{ mA})} = 10 \text{ k}\Omega$$

$$A_v = (6.28 \text{ m}) [(6.28 \text{ m} \times 20 \text{ k} \times 20 \text{ k}) \parallel (2.59 \text{ m} \times 10 \text{ k} \times 10 \text{ k})]$$



$$A_v = 1474$$

(d) Since this is a cascode configuration, the noise due to $M_{3,4,5,6}$ can be neglected.



$$\overline{V_{n \text{ input}}^2} \text{ due to } M_{1,2} = 4kTY \frac{1}{g_{m1,2}}$$

$$\overline{V_{n \text{ input}}^2} \text{ due to } M_8 = 4kTY \frac{g_{m8}}{g_{m1,2}^2} \text{ same as in cascode.}$$
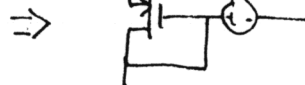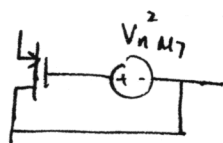
$$\overline{V_{n \text{ input}}^2} \text{ due to } M_7$$



Consider M_7 :

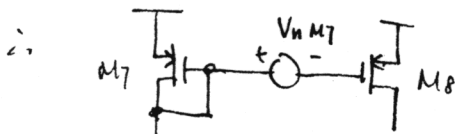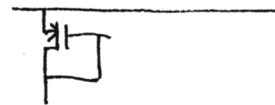

M_7 will induce the same noise as M_8 .

$\therefore$ input-referred noise voltage

$$\overline{V_n^2} = \left[4kTY \frac{1}{g_{m1,2}} + 4kTY \frac{g_{m7,8}}{g_{m1,2}^2} \right] \times 2 \quad \text{where } \gamma = \frac{2}{3}$$

9.2 (d) cont.

$$\overline{V_n^2} = 4 \times 1.38 \times 10^{-23} \times 300 \times \frac{2}{3} \times 2 \left[\frac{1}{6.28 \text{ m}} + \frac{2.59 \text{ m}}{(6.28 \text{ m})^2} \right]$$

$$\overline{V_n^2} = 4.966 \times 10^{-18} \text{ V}^2/\text{Hz}$$

$$\text{or} = 2.23 \times 10^{-9} \text{ V}/\sqrt{\text{Hz}}$$

Problem 9.3

Requirements: Max. diff. swing 2.4V

$$P_{\text{total}} = 6\text{mW}$$

Max diff swing =

$$= 2[V_{DD} - (V_{DD3} + V_{DD5} + |V_{DD7}| + |V_{DD9}|)]$$

$$= 2.4\text{V}$$

$$V_{DD3} + V_{DD5} + |V_{DD7}| + |V_{DD9}| = V_{DD} - 1.2 = 1.8$$

In general, assign $|V_{DD7}|$ & $|V_{DD9}|$ to be large than V_{DD3} as PMOS has a smaller μ_p . Also M_5 need large V_{DD} as I_{D5} is larger.

Let the followings:

$$V_{DD3} = 0.3\text{V}, \quad V_{DD5} = 0.44\text{V} \quad |V_{DD7}| = |V_{DD9}| = 0.53\text{V} \quad |V_{DD1}| = 0.53\text{V}$$

$$P_{\text{total}} = 6\text{mW} = V_{DD} \times (I_{D5} + I_{D6})$$

$$I_{D5} = I_{D6} = \frac{6\text{mW}}{(3)(2)} = 1\text{mA}$$

$$I_D = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$\left(\frac{W}{L}\right) = \frac{2I_D}{\mu C_{ox} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})}$$

$$\left(\frac{W}{L}\right)_{5,6} = \frac{2(1\text{mA})}{(350)(383.6 \times 10^{-9})(0.44)^2 (1 + (0.1)(0.44))}$$

$$= 74$$

(Assume $V_{DS} \approx V_{GS} - V_{TH}$,

Since λ is small, the result will not be affected too much.)

$$W_{5,6} = (74)(0.34\mu\text{m}) = 25.16\mu\text{m}$$

$$\text{Let } I_{D1,2} = 0.5\text{mA}, \quad I_{D3,4} = 0.5\text{mA}$$


$$\left(\frac{W}{L}\right)_{1,2} = \frac{2(0.5\text{mA})}{(100)(383.6 \times 10^{-9})(0.53)^2 (1 + (0.2)(0.53))} = 84$$

$$W_{1,2} = 84(0.32\mu\text{m}) = 26.88\mu\text{m}$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{2(0.5\text{mA})}{(350)(383.6 \times 10^{-9})(0.3)^2 (1 + (0.1)(0.3))} = 80$$

$$W_{3,4} = 80 \times 0.34\mu\text{m} = 27.2\mu\text{m}$$
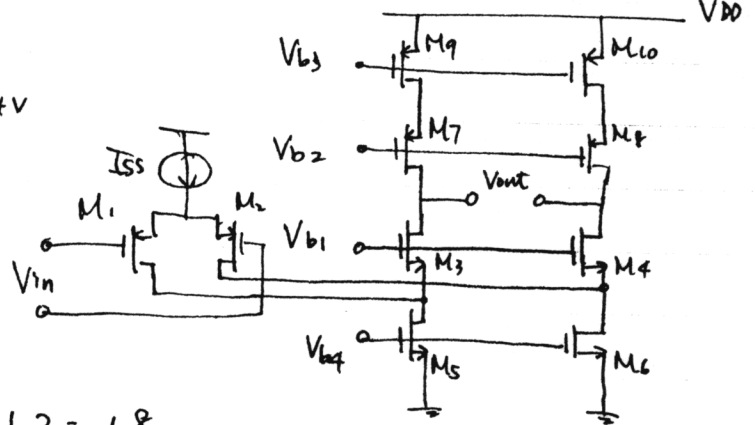
$$\left(\frac{W}{L}\right)_{7,9} = \frac{2(0.5\text{mA})}{(100)(383.6 \times 10^{-9})(0.53)^2 (1 + (0.2)(0.53))} = 84$$



9.3 cont.

$$W_{7,9} = 84 \times 0.32 \mu\text{m} = 26.88 \mu\text{m}.$$

$$V_{b4} = V_{GS5} = V_{DD5} + V_{TH5} = 0.44 + 0.7$$

$$V_{b4} = 1.14 \text{ V}$$

$$\begin{aligned} V_{b1} &= V_{DD5} + V_{GS3} = V_{DD5} + V_{DD3} + V_{TH3} = V_{DD5} + V_{DD3} + V_{TH0} + \gamma(\sqrt{1 - 2\phi_F + V_{SB1}} - \sqrt{1 - 2\phi_F}) \\ &= 0.44 + 0.3 + 0.7 + 0.45(\sqrt{0.9 + 0.44} - \sqrt{0.9}) \\ &= 1.53 \text{ V} \end{aligned}$$

$$V_{b3} = V_{DD} - |V_{GS9}| = V_{DD} - [|V_{DD9}| + |V_{TH9}|] = 3 - 0.53 - 0.8$$

$$V_{b3} = 1.67 \text{ V}$$

$$\begin{aligned} V_{b2} &= V_{DD} - |V_{DD9}| - |V_{GS7}| = V_{DD} - |V_{DD9}| - |V_{DD7}| - |V_{TH7}| \\ &= 3 - 0.53 - 0.53 - [0.8 + 0.4(\sqrt{0.8 + 0.53} - \sqrt{0.8})] \end{aligned}$$

$$V_{b2} = 1.04 \text{ V}$$

$$\begin{aligned} V_{in, \text{common mode}} &\leq V_{DD} - V_{ISS} - V_{GS1} = 3 - 0.3 - 0.8 - 0.53 = 1.37 \text{ V} \\ &\geq V_{DD5} - V_{TH1} = 0.44 - 0.8 = -0.36 \text{ V} \end{aligned} \quad \left. \begin{array}{l} V_{in, \text{common mode}} \\ \text{can be zero} \\ (V_{in, CM} = 0) \end{array} \right\}$$

$$A_V = g_{m1} [(g_{m7} r_{O7} r_{O9}) // (g_{m3} r_{O3} (r_{O1} // r_{O5}))]$$

$$g_{m1} = \frac{2I_{D1}}{V_{GS} - V_{TH}} = \frac{2(0.5 \text{ mA})}{0.53} = 1.89 \text{ m}\Omega^{-1}$$

$$g_{m7} = g_{m1} = 1.89 \text{ m}\Omega^{-1}$$

$$g_{m3} = \frac{2I_{D3}}{V_{GS} - V_{TH}} = \frac{2(0.5 \text{ mA})}{0.3} = 3.33 \text{ m}\Omega^{-1}$$

$$r_{O7} = r_{O9} = \frac{1}{\lambda I_D} = \frac{1}{(0.2)(0.5 \text{ mA})} = 10 \text{ k}\Omega = r_{O1}$$

$$r_{O3} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(0.5 \text{ mA})} = 20 \text{ k}\Omega$$

$$r_{O5} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(1 \text{ mA})} = 10 \text{ k}\Omega$$

$$\begin{aligned} A_V &= (1.89 \text{ m}) [(1.89 \text{ m} (10 \text{ k})^2) // (3.33 \text{ m} (20 \text{ k}) (10 \text{ k} // 2))] \\ &= 228 \end{aligned}$$

$$W_{4,2} = 26.88 \mu\text{m}$$

$$V_{b1} = 1.53 \text{ V}$$

$$A_V = 228$$

$$W_{3,4} = 27.2 \mu\text{m}$$

$$V_{b2} = 1.04 \text{ V}$$

$$W_{5,6} = 25.16 \mu\text{m}$$

$$V_{b3} = 1.67 \text{ V}$$

$$W_{7,8,9,10} = 26.88 \mu\text{m}$$

$$V_{b4} = 1.14 \text{ V}$$

$$-0.36 \leq V_{in, CM} \leq 1.37 \text{ V}$$

(A) $V_{in, CM, min} = V_{ISS} + V_{GS1}$

$$= V_{ISS} + V_{THN} + V_{OD1}$$


where V_{Igs} is the voltage across I_{ss} .

$$V_{in, CM, max} = V_Y + V_{TH}, \quad ;$$

$$V_Y = V_{b1} - V_{gs3} = V_{b1} - V_{TH3} - V_{OD3}$$

$$V_{in, CM, max} = V_{b1} - V_{TH3} - V_{OD3} + V_{TH1} \quad \text{Assume } V_{TH3} = V_{TH1}$$

$$V_{in-CM, \max} = V_{B1} - V_{OD3}$$

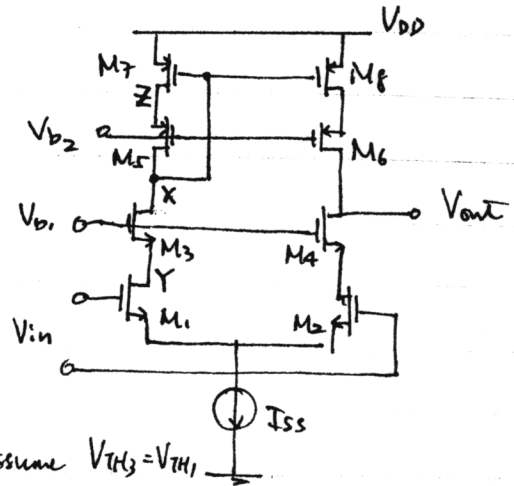

To calculate V_{OD3} , $I_{D3} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_3 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$ Assume $\lambda \rightarrow 0$

$$V_{OD3} = V_{GS3} - V_{TH} = \left[\frac{2 I_{D3}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_3} \right]^{\frac{1}{2}}$$

$$= \left[\frac{2 (0.5 \text{ mA})}{350 (383.6 \times 10^{-9}) \left(\frac{100}{0.34}\right)} \right]^{\frac{1}{2}} = 0.159 \text{ V.}$$

$$\therefore V_{in, CM, max} = 1.7 - 0.159 = 1.541 \text{ V}$$

b, $V_x = ?$. To find V_x , we can find V_{os7}

$$V_{GS7} - V_{THP} = \left[\frac{2 I_{D7}}{\mu_r C_{ox} \left(\frac{W}{L} \right)_7} \right]^{\frac{1}{2}}$$

$$= \left[\frac{2(0.5 \text{ mA})}{(100)(383.6 \times 10^{-9}) \left(\frac{100}{0.32} \right)} \right]^{\frac{1}{2}} = 0.289$$

$$V_{GS7} = 0.289 + V_{THP} = 1.089V$$

$$V_x = V_{DD} - V_{GS7} = 3 - 1.089V$$

$$V_x = 1.911 \text{ V}$$

c, For details, please see page 284 (chapter 9).

$$\text{Max. output swing} = V_{TH4} - (V_{DS4} - V_{TH2})$$

$$V_{GS3} = V_{GS4} \quad \text{by symmetry,} \quad V_{GS3} - V_{THn} = V_{GS4} - V_{THn} = 0.159 \text{ V}$$

$$V_{GS4} = 0.7 + 0.159 = 0.859 \text{ V}$$

$$\text{Max output swing} = 0.7 - (0.859 - 0.7) =$$

Max output swing = 0.541 V.

9.4 cont.

(d). We know $V_x = 1.911V$, $V_{GS5} = V_{GS7} = 1.089V$

To keep M_7 in saturation,

$$V_Z < V_x + V_{THP} \quad ; \quad V_{b2} > V_Z - |V_{GS5}|$$

$$V_{b2} < V_x + V_{THP} - |V_{GS5}| = 1.911V + 0.8 - 1.089$$

$$V_{b2} < 1.622V$$

$$V_{b2} > V_x - V_{TH5} = 1.911 - 0.8 \Rightarrow V_{b2} > 1.111V$$

$$\therefore \boxed{1.111V < V_{b2} < 1.622V}$$


e. As this is a cascode configuration, M_3, M_4, M_5, M_6 have negligible.

Input referred noise voltage due to M_1, M_2

$$\overline{V_n^2}_{\text{input}} = 4kTY \frac{1}{g_{m1,2}}$$

$$\overline{V_n^2}_{\text{input } M_8} = 4kTY \frac{g_{m8}}{g_{m1,2}^2}$$
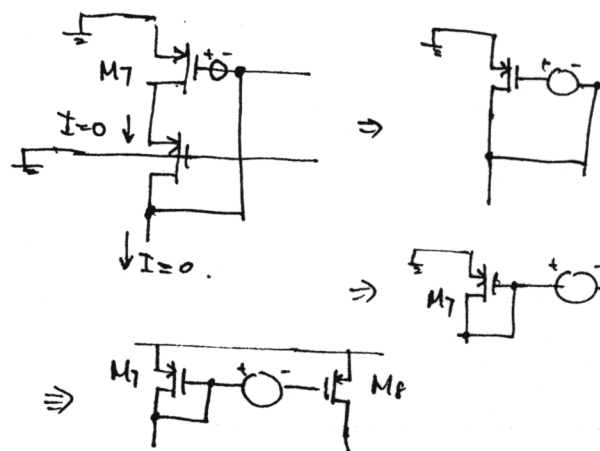
$$\begin{aligned} \overline{V_n^2}_{\text{input } M_7} &= \overline{V_n^2}_{\text{input due to } M_8} \\ &= 4kTY \frac{g_{m7}}{g_{m1,2}^2} \end{aligned}$$



$\therefore$ Input referred noise voltage

$$= \left[4kTY \left(\frac{1}{g_{m1,2}} + \frac{g_{m7,8}}{g_{m1,2}^2} \right) \right] \times 2$$

$$\begin{aligned} g_{m1,2} &= \sqrt{2\mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) I_D} \\ &= \left[2(350)(383.6 \times 10^{-9}) \left(\frac{100}{0.34} \right) (0.5mA) \right]^{\frac{1}{2}} \\ &= 6.28 \times 10^{-3} \Omega^{-1} \end{aligned}$$

$$\begin{aligned} g_{m7,8} &= \left[2(100)(383.6 \times 10^{-9}) \left(\frac{100}{0.32} \right) (0.5mA) \right]^{\frac{1}{2}} \\ &= 3.46 m\Omega^{-1} \end{aligned}$$

$$\text{Input referred noise voltage} = \left[4 \times (1.38 \times 10^{-23}) \times 300 \times \frac{2}{3} \times \left(\frac{1}{6.28m} + \frac{3.46m}{6.28m^2} \right) \right] \times 2$$

$$= 5.45 \times 10^{-18} V^2/Hz$$

$$\sigma = 2.34 \times 10^{-9} V/\sqrt{Hz}$$

Problem 9.6

(a) Given: $\left(\frac{W}{L}\right)_{1-8} = \frac{100}{0.5}$ $I_{SS} = 1\text{mA}$

$$I_{D5,6} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_{5,6} (V_{GS5,6} - V_{THp})^2 (1 + \lambda V_{DS5,6})$$

$$V_{GS5,6} - V_{THp} = \left[\frac{2I_{D5,6}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{5,6}} \right]^{\frac{1}{2}}$$

$$= \left[\frac{2(1\text{mA})}{(100)(383.6 \times 10^{-9}) \left(\frac{100}{0.32}\right)} \right]^{\frac{1}{2}} = 0.408\text{V}$$

$$V_{GS5,6} = 0.408 + 0.8 = 1.208\text{V}$$

$$V_{X,Y} = V_{DD} - V_{GS5,6} = 3 - 1.208\text{V}$$

$$V_{X,Y} = 1.792\text{V}$$

In order to keep M_1, M_2 in saturation,

$$V_{in,CM} < V_{X,Y} + V_{TH} = 1.792 + 0.7 = 2.492\text{V}$$

$$\therefore V_{in,CM,max} = 2.49\text{V}$$

(b) A_v of 1st stage = $g_{m1}(r_{o1} \parallel r_{o3})$

A_v of 2nd stage = $g_{m5}(r_{o5} \parallel r_{o7})$

$$A_{v,tot} = g_{m1}(r_{o1} \parallel r_{o3}) g_{m5}(r_{o5} \parallel r_{o7})$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_{1,2} (I_{D1})} = \left[2(350)(383.6 \times 10^{-9}) \left(\frac{100}{0.34}\right) (0.5\text{mA}) \right]^{\frac{1}{2}}$$

$$= 6.28\text{m}\Omega^{-1}$$

$$g_{m5} = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2(1\text{mA})}{0.408}$$

$$g_{m5} = 4.90\text{m}\Omega^{-1}$$

$$r_{o1} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(0.5\text{mA})} = 20\text{k}\Omega$$

$$r_{o3} = \frac{1}{\lambda I_D} = \frac{1}{(0.2)(1\text{mA})} = 10\text{k}\Omega$$


$$r_{o5} = \frac{1}{\lambda I_D} = \frac{1}{(0.2)(1\text{mA})} = 5\text{k}\Omega$$

$$r_{o7} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(1\text{mA})} = 10\text{k}\Omega$$

$$A_v = (6.28\text{m}) [20\text{k} \parallel 10\text{k}] (4.90\text{m}) [5\text{k} \parallel 10\text{k}]$$

$$A_v = 684$$

$$\text{Max output swing} = 2(V_{DD} - |V_{DS5}| - V_{DS7})$$

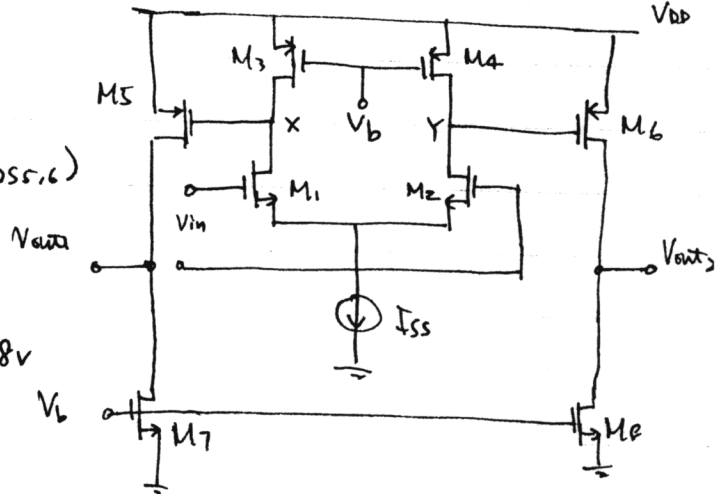

$$|V_{DS}| = |V_{GS}| - |V_{THP}| = 0.408V$$

$$V_{GS7} = V_{THN} = \left[\frac{2 I_D}{(M_n) C_{ox} \left(\frac{W}{L}\right)_7} \right]^{\frac{1}{2}}$$

$$= \left[\frac{2 (1mA)}{(350)(383.6 \times 10^{-9}) \left(\frac{100}{0.34}\right)} \right]^{\frac{1}{2}} = 0.225$$

$$\boxed{\begin{aligned} \text{Max output swing} &= 2(3 - 0.408 - 0.225) \\ &= 4.734V. \end{aligned}}$$

Problem 9.7

Design the op amp of fig. 9.21

Max diff. swing = 4V

total Power = 6mW $I_{SS} = 0.5\text{mA}$ Total current driven by $V_{DD} = \frac{6\text{mW}}{3\text{V}} = 2\text{mA}$

$$I_{D5} + I_{D6} = 2\text{mA} - I_{SS} = 1.5\text{mA} \Rightarrow I_{D5} = I_{D6} = 0.75\text{mA}$$

$$\text{Max diff swing} = 2[V_{DD} - |V_{D05}| - V_{D07}] = 4\text{V}$$

$$\Rightarrow |V_{D05}| + |V_{D07}| = 1 \quad \text{choose } V_{D05} = 0.6\text{V}, \quad V_{D07} = 0.4\text{V}$$

$$I_D = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$\left(\frac{W}{L_{eff}} \right)_5 = \frac{2I_D}{\mu_p C_{ox} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})} = \frac{2(0.75\text{mA})}{(100)(383.6 \times 10^{-9})(0.6)^2 (1 + 0.2 \times 0.6)}$$

$$\left(\frac{W}{L_{eff}} \right)_5 = 97 \Rightarrow W_{5,6} = 97 \times 0.32\mu = 31\mu\text{m}$$

$$\left(\frac{W}{L_{eff}} \right)_7 = \frac{2(0.75\text{mA})}{(350)(383.6 \times 10^{-9})(0.4)^2 (1 + 0.1(0.4))}$$

$$= 67 \Rightarrow W_{7,8} = 67 \times 0.34\mu = 23\mu\text{m}$$

We are generally not worried about the swing of 1st stage, assume $|V_{D03}| = 1\text{V}$, $V_{D01} = 1\text{V}$.

$$\left(\frac{W}{L_{eff}} \right)_3 = \frac{2(0.25\text{mA})}{(100)(383.6 \times 10^{-9})(1)^2 (1 + 0.2(1))} = 10.86$$

$$W_{3,4} = 3.5\mu\text{m}$$

$$\left(\frac{W}{L_{eff}} \right)_1 = \frac{2(0.25\text{mA})}{(350)(383.6 \times 10^{-9})(1)^2 (1 + 0.1)} = 3.4$$

$$W_{1,2} = 1.2\mu\text{m}$$

$$V_{b1} = V_{DD} - |V_{D03}| - V_{TH3} = 3 - 1 - 0.8 = 1.2\text{V}$$

$$V_{in,CM} = V_{SS} + V_{TH1} + V_{D01} = 0.3 + 0.7 + 1.0 = 2\text{V}$$

$$V_{b2} = V_{TH7} + V_{D07} = 0.7 + 0.4 = 1.1\text{V}$$

Summary $L = 0.5\mu\text{m}$

$$W_{1,2} = 1.2\mu\text{m}$$

$$V_{b1} = 1.2\text{V}$$


$$W_{3,4} = 3.5\mu\text{m}$$

$$V_{b2} = 1.1\text{V}$$

$$W_{5,6} = 31\mu\text{m}$$

$$V_{in,CM} = 2\text{V}$$

$$W_{7,8} = 23\mu\text{m}$$

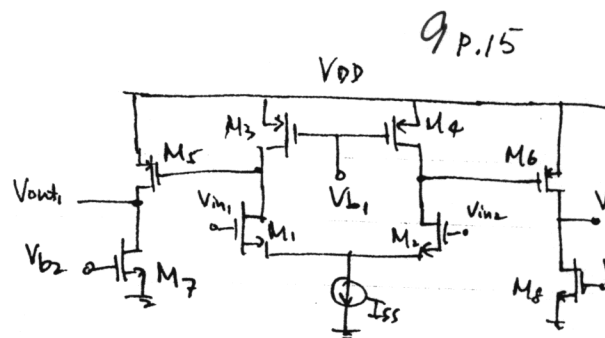

$$1c) A_v = g_{m1} (g_{m3} r_{o3} r_{o1} \parallel g_{m5} r_{o5} r_{o7}) g_{m9} (r_{o9} \parallel r_{o11})$$

$$g_{m1} = \frac{2 I_D}{V_{GS1} - V_{TH}} = \frac{2(0.5mA)}{0.7055} = 1.417 m\Omega^{-1}$$

$$g_{m3} = g_{m1} = 1.417 m\Omega^{-1}$$

$$g_{m5} = \frac{2 I_D}{V_{GS5} - V_{THp}} = \frac{2(0.5mA)}{0.495} = 2.022 m\Omega^{-1}$$

$$g_{m9} = \frac{2(0.5mA)}{0.289} = 3.46 m\Omega^{-1}$$

$$r_{oN} = r_{o1} = r_{o3} = r_{o11} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(0.5mA)} \\ = 20 k\Omega$$

$$r_{op} = r_{o5} = r_{o7} = r_{o9} = \frac{1}{\lambda I_D} = \frac{1}{(0.2)(0.5mA)} \\ = 10 k\Omega$$

$$A_v = (1.417m) [1.417m \times 20k \times 20k \parallel 2.022m \times 10k \times 10k] \times 3.46m \times (10k \parallel 20k)$$

$$A_v = 4871$$

Problem 9.9

$$\overline{V_n^2}_{\text{input}}|_{M_1} = 4kT\gamma \frac{1}{g_{m1}}$$

$$\overline{V_n^2}_{\text{input}}|_{M_2} \approx 0$$

$$\overline{V_n^2}_{\text{out}}|_{M_5} = 4kT\gamma g_{m5} R_{\text{out}}^2$$

$$\begin{aligned} \overline{V_n^2}_{\text{out}}|_{M_5} &= \frac{4kT\gamma g_{m5} R_{\text{out}}^2}{(g_{m1} R_{\text{out}})^2} \\ &= 4kT\gamma \frac{g_{m5}}{g_{m1}^2} \end{aligned}$$

Noise due to M_3, M_4 :

$$I_{n,34} = 4kT\gamma (g_{m3} + g_{m4})$$

$$R_{034} = r_{03} \parallel r_{04}$$

$$V_x = r_{01} \left(-\frac{V_{\text{out}}}{r_{05}} \right)$$

$$I_{D3} = g_{m3} V_x = -\frac{g_{m3} r_{01} V_{\text{out}}}{r_{05}}$$

$$V_Y = R_{034} \left(I_{n,34} + \frac{g_{m3} r_{01}}{r_{05}} V_{\text{out}} \right)$$

neglect the r_{02} to approximate the result,

$$V_{\text{out}} = \frac{-r_{05}}{\frac{1}{g_{m2}} + r_{01}} V_Y = \frac{-r_{05}}{\frac{1}{g_{m2}} + r_{01}} R_{034} \left(I_{n,34} + \frac{g_{m3} r_{01}}{r_{05}} V_{\text{out}} \right)$$



$$V_{\text{out}} \left(\frac{\frac{1}{g_{m2}} + r_{02}}{1 + r_{05} R_{034}} + \frac{g_{m3} r_{01}}{r_{05}} \right) = -I_n$$

$$V_{\text{out}} = \frac{-I_n r_{05} R_{034}}{\frac{1}{g_{m2}} + r_{02} + g_{m3} r_{01} R_{034}} \approx \frac{-I_n r_{05} R_{034}}{g_{m3} r_{01} R_{034}} = \frac{-r_{05}}{r_{01} g_{m3}} I_n$$

$$\begin{aligned} \overline{V_n^2}_{\text{input}}|_{M_3, M_4} &= \frac{\left(\frac{r_{05}}{r_{01} g_{m3}} \right)^2 I_n^2}{g_{m1}^2 (r_{05} \parallel [g_{m1} r_{02} r_{01} g_{m3} (r_{03} \parallel r_{04})])^2} \approx \frac{I_n \left(\frac{r_{05}}{g_{m3} r_{01}} \right)^2}{g_{m1}^2 r_{05}^2} \\ &= 4kT\gamma (g_{m3} + g_{m4}) \left[\frac{1}{g_{m1}^2 g_{m3}^2 r_{01}^2} \right] \end{aligned}$$

This is negligible compared with the noise due to M_1, M_5

$$\boxed{\therefore \overline{V_n^2}_{\text{in total}} = 4kT\gamma \left[\frac{1}{g_{m1}} + \frac{g_{m5}}{g_{m1}^2} \right]}$$

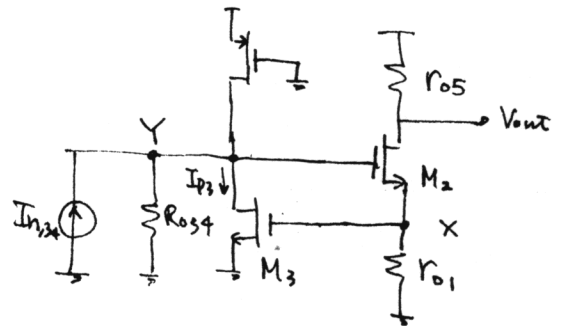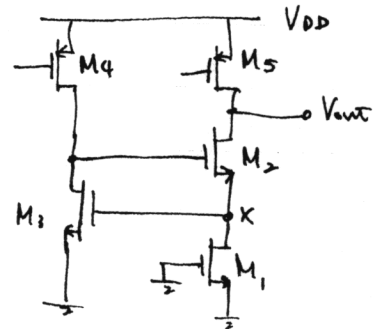

Problem 9.10

(a) $I_1 = 100 \mu A$, $I_2 = 0.5 mA$, $(\frac{W}{L})_{1-3} = \frac{100}{0.5}$

$$(\frac{W}{L})_p = \frac{50}{0.5}$$

$$I_{D3} = I_1 = \frac{1}{2} \mu_n C_{ox} (\frac{W}{L})_3 (V_{G3} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$V_{G3} - V_{TH} = \left[\frac{2I_1}{\mu_n C_{ox} (\frac{W}{L})_{eff3}} \right]^{\frac{1}{2}}$$

$$= \left[\frac{2(100 \mu A)}{350 \times (383.6 n) (\frac{100}{0.34})} \right]^{\frac{1}{2}} = 0.0712$$

$$V_{G3} = 0.7712 V = V_{G3} = V_X$$

$$V_{G2} = V_{THn} = \left[\frac{2I_2}{\mu_n C_{ox} (\frac{W}{L})_{eff2}} \right]^{\frac{1}{2}}$$

$$= \left[\frac{2(0.5 mA)}{(350)(383.6 n) (\frac{100}{0.34})} \right]^{\frac{1}{2}} = 0.159 V$$

$$V_{G2} = 0.859 V$$

$$V_{G2} = V_{G2} + V_X = 1.630 V$$

b, Max output swing:

$$V_{outmax} = V_{DD} - |V_{DS5}|$$

$$V_{outmin} = V_X + V_{DS2} = V_{G3} + V_{DS2}$$

$$\text{Max output swing} = V_{DD} - |V_{DS5}| - V_{DS2} - V_{G3}$$

$$|V_{GS5}| - |V_{TH}| = \left[\frac{2I_D}{\mu_p C_{ox} (\frac{W}{L})_{eff5}} \right]^{\frac{1}{2}} = \left[\frac{2(0.5 mA)}{(100)(383.6 n) (\frac{50}{0.32})} \right]^{\frac{1}{2}}$$

$$= 0.408 V = |V_{DS5}|$$

$$\text{Max output swing} = 3 - 0.408 - 0.159 - 0.7712$$

$$= 1.6618 V$$

c, $A_v = g_{m1} [r_{o5} \parallel (g_{m2} r_{o2} r_{o1} g_{m3} (r_{o3} \parallel r_{o4}))]$ Note: r_{o5} is limiting the gain.



$$\approx g_{m1} r_{o5}$$

$$g_{m1} = \sqrt{2 \mu_n C_{ox} (\frac{W}{L})_1 I_{D1}} = \sqrt{2(350)(383.6 n) (\frac{100}{0.34})(0.5 mA)}$$

$$= 6.28 mS^{-1}$$

$$r_{o5} = \frac{1}{\lambda I_D} = \frac{1}{(0.2)(0.5 mA)} = 10 k\Omega$$

$$A_v = 62.8$$

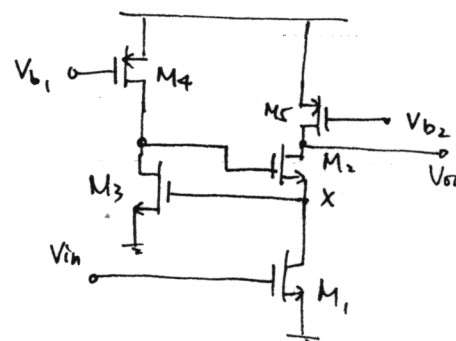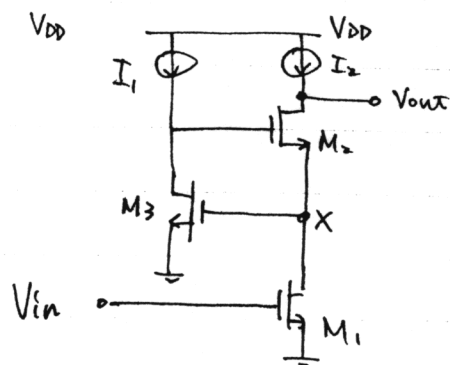

9.10 cont.

$$(c) \quad \overline{V_{n,in}} = 4kTR \left[\frac{1}{g_{m1}} + \frac{g_{m5}}{g_{m1}^2} \right] + 4kTR \left(\frac{1}{g_{m3}} + \frac{g_{m4}}{g_{m3}^2} \right) \left[\frac{g_{m2} r_{o2} g_{m3} (r_{o3} \parallel r_{o4})}{g_{m1} (r_{o1} + r_{o2} + r_{o5})} \right]^2 \quad (\text{see ...})$$

$$g_{m1} = g_{m2} = 6.28 \text{ m}\Omega^{-1}$$

$$g_{m5} = \left[2(100)(383.6 \text{ n}) \left(\frac{50}{0.32} \right) (0.5 \text{ m}) \right]^{\frac{1}{2}} = 2.45 \text{ m}\Omega^{-1}$$

$$g_{m3} = \left[2(350)(383.6 \text{ n}) \left(\frac{100}{0.34} \right) (100 \mu) \right]^{\frac{1}{2}} = 2.81 \text{ m}\Omega^{-1}$$

$$g_{m4} = \left[2(100)(383.6 \text{ n}) \left(\frac{50}{0.32} \right) (100 \mu) \right]^{\frac{1}{2}} = 1.09 \text{ m}\Omega^{-1}$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(0.5 \text{ m})} = 20 \text{ k}\Omega$$

$$r_{o3} = \frac{1}{(0.1)(100 \mu)} = 100 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{(0.2)(100 \mu)} = 50 \text{ k}\Omega$$

$$r_{o5} = \frac{1}{(0.2)(0.5 \text{ m})} = 10 \text{ k}\Omega$$


$$\overline{V_{n,in}} = 4(1.38 \times 10^{-23})(300) \left(\frac{2}{3} \right) \left[\frac{1}{6.28 \text{ m}} + \frac{2.45 \text{ m}}{6.28 \text{ m}^2} \right]$$

$$= 2.444 \times 10^{-18} \text{ V}^2/\text{Hz}$$

$$\overline{V_{n,in}} = 1.56 \times 10^{-9} \text{ V} \sqrt{\text{Hz}}$$


Problem 9.12

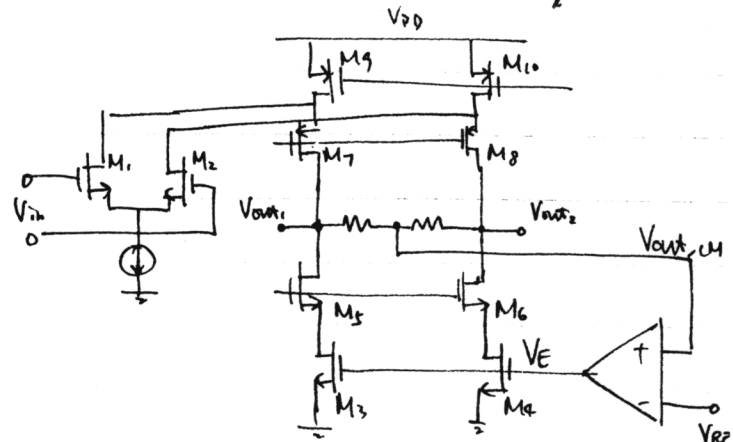- (A) PMOS devices should be used.
 Since $V_{out,CM}$ is in the middle voltage range, (around 1.5V), and $V_{GS,4}$ are in low voltage range, (around 0.7 - 0.8V), we should use PMOS to bring down the voltage.



$$A_1 = g_{m13} (r_{o12} \parallel r_{o14})$$

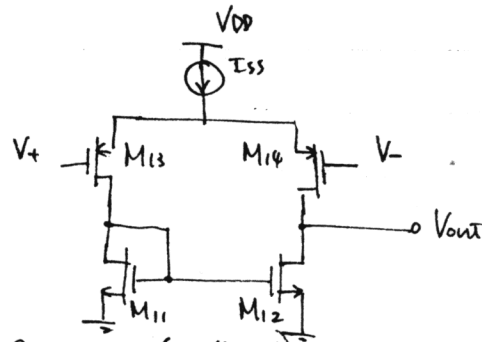
$$\frac{V_{out,CM}}{V_E} = -g_{m3,4} (g_{m5} r_{o5} r_{o3} \parallel g_{m7} r_{o7} (r_{o1} \parallel r_{o9}))$$




$$\text{Loop gain} = -g_{m3,4} \left[(g_{m5} r_{o5} r_{o3}) \parallel (g_{m7} r_{o7} (r_{o1} \parallel r_{o9})) \right] g_{m13} (r_{o12} \parallel r_{o14})$$

Problem 9.13

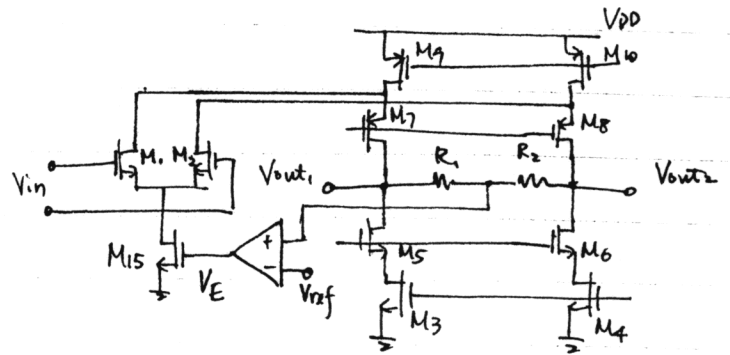
- (a) Since we need to bring down $V_{out,CM}$ to fit the bias voltage of NMOS, which is relatively low, we should use PMOS for the input pair of amplifier.



(b)

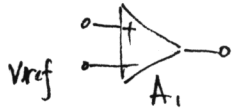

=

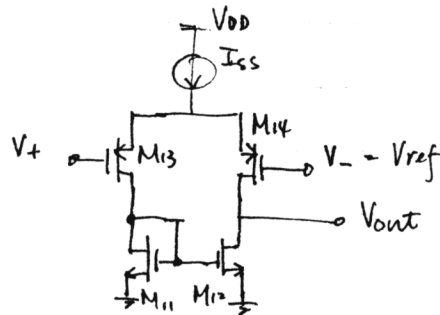

$$A_1 = g_{m13} (r_{o12} \parallel r_{o14})$$

$$\frac{V_{out1}}{V_E} = -g_{m15} \left[(g_{m5} r_{o5} r_{o3}) \parallel (g_{m7} r_{o7} (r_{o9} \parallel g_{m1} r_{o1} r_{o15})) \right]$$

$$\text{loop gain} = -g_{m15} \left[(g_{m5} r_{o5} r_{o3}) \parallel (g_{m7} r_{o7} (r_{o9} \parallel g_{m1} r_{o1} r_{o15})) \right] g_{m13} (r_{o12} \parallel r_{o14})$$

Problem 9.14

(a) $(\frac{W}{L})_{1-4} = \frac{100}{0.5}$, $C_1 = C_2 = 0.5 \text{ pF}$, $I_{SS} = 1 \text{ mA}$

$$A_v = g_{m1} (r_{o2} \parallel r_{o4})$$



$$R_{out} = r_{o2} \parallel r_{o4}$$

$$V_{in} = V_i + V_x$$

$$V_x = V_{out} \frac{C_1}{C_1 + C_2}$$

$$V_{out} = A_v V_i \left[\frac{\frac{1}{C_1 \parallel C_2 s}}{R_{out} + \frac{1}{C_1 \parallel C_2 s}} \right] = A_v V_i \frac{1}{(C_1 \parallel C_2) R_{out} s + 1}$$
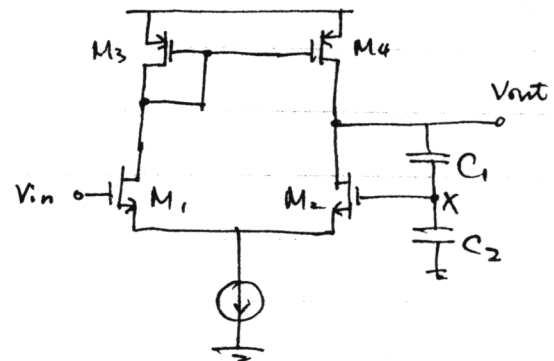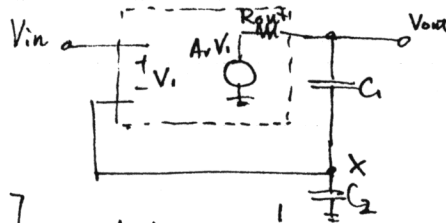
$$= \frac{A_v}{1 + (C_1 \parallel C_2) R_{out} s} (V_{in} - V_{out} \frac{C_1}{C_1 + C_2})$$



$$(1 + (C_1 \parallel C_2) R_{out} s + A_v \frac{C_1}{C_1 + C_2}) V_{out} = A_v V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_v}{1 + A_v \frac{C_1}{C_1 + C_2} + (C_1 \parallel C_2) R_{out} s} = \frac{\frac{A_v}{1 + A_v \frac{C_1}{C_1 + C_2}}}{1 + \frac{(C_1 \parallel C_2) R_{out} s}{1 + A_v \frac{C_1}{C_1 + C_2}}}$$

$$\tau = \frac{\frac{C_1 C_2}{C_1 + C_2} R_{out}}{1 + A_v \frac{C_1}{C_1 + C_2}}$$

(b) $I_{D2} = 0.1 I_{SS}$,

Since I_{D2} is still small, we can solve this problem by assuming the current through C_1 & C_2 roughly equal to I_{SS}

$$V_x(t) - V_x(0) = \frac{I_{SS}}{C_2} t$$

At $t = 0^-$ $I_{D1} = I_{D2} = 0.5 \text{ mA}$

$$V_{GS1,2} - V_{TH} = \left[\frac{2 I_D}{\mu_n C_{ox} (\frac{W}{L})_{eff}} \right]^{\frac{1}{2}} = \left[\frac{2(0.5 \text{ mA})}{(350)(303.6 \mu\text{m}) (\frac{100}{0.34})} \right]^{\frac{1}{2}}$$

$$= 0.159 \text{ V}$$

At time = t , when $I_{D2} = 0.1 I_{SS} \Rightarrow I_{D1} = 0.9 I_{SS}$

$$I_D = \frac{1}{2} k_n C_{ox} (\frac{W}{L}) (V_{GS} - V_T)^2$$

$$\frac{I_{D1}}{I_{D2}} = \frac{0.9 I_{SS}}{0.1 I_{SS}} = \frac{(V_{GS1} - V_T)^2}{(V_{GS2} - V_T)^2} \Rightarrow \frac{(V_{GS1} - V_T)}{(V_{GS2} - V_T)} = 3$$

$$V_{GS1}(t) - V_T = 3(V_{GS2} - V_T)$$

$$(V_{GS1}(t) - V_T) = (V_{GS1}(0) - V_T) + 1 \text{ V} = 0.159 + 1 \text{ V} = 1.159 \text{ V} = 3(V_{GS2} - V_T)$$

$$V_{GS2}(t) - V_T = 0.386 \text{ V}$$

Q.14 cont.


$$[V_{GS_2}(t) - V_T] - [V_{GS_2}(0) - V_T] = V_X(t) - V_X(0) = \frac{I_{SS}}{C_e} t$$

$$0.386 - 0.159 = 0.227 = \frac{1 \text{ mA}}{0.5 \text{ pF}} (t)$$

$$\boxed{t = 113.5 \text{ ps.}}$$

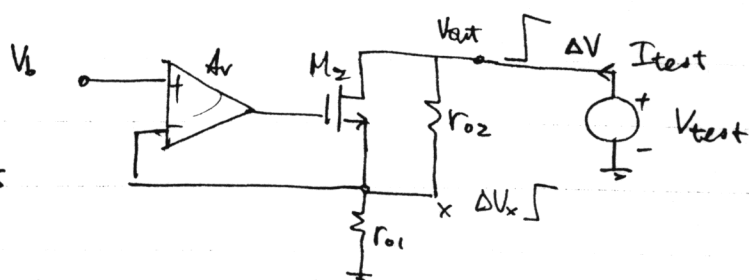Problem 9.15

The mistake is made when we say the current from V_{test} is equal to $\Delta V / r_{o2}$.



We can see it when we start from the amplifier.

If we ~~assume~~ assume current from V_- is very small or negligible, the current through r_{o1} is equal to I_{test} , the current driven from V_{test} . The current through r_{o1} is $\frac{\Delta V_x}{r_{o1}}$, which is a much smaller value than $\Delta V / r_{o2}$.

The mistake is made because the current through r_{o2} is actually equal to $\Delta V / r_{o2}$ or $\approx \frac{\Delta V + \Delta V_x}{r_{o2}}$. This current is larger ~~than~~ than I_{test} since some extra current from M_2 makes the current through r_{o2} larger. As a result, ΔV_{ro2} (Δ voltage across r_{o2}) increases by about ΔV , but the current from V_{test} ~~only~~ increases only by $\frac{\Delta V_x}{r_{o1}}$.

Problem 9.16

$$CMRR = \frac{\text{diff. gain}}{\text{CM. gain.}}$$

$$\text{diff. gain} = g_{m1}(r_{o2} \parallel r_{o4})$$

CM gain: let R is the resistance of current source

$$\Delta V_{in1} = \Delta V_{in2} = V_{CM}$$

$$\frac{V_{out}}{\Delta V_{in1}} = \frac{-\frac{1}{g_{m3}}}{\frac{R}{2} + \frac{1}{g_{m1}}} g_{m4}(R_{out})$$



$$\frac{V_{out}}{\Delta V_{in2}} = \frac{-R_{out}}{\frac{R}{2} + \frac{1}{g_{m2}}}$$

$$\left| \frac{V_{out}}{V_{CM}} \right| = \frac{2R_{out}}{\frac{R}{2} + \frac{1}{g_{m1}}} \approx \frac{4R_{out}}{R}$$


$$\text{where } R_{out} = r_{o4} \parallel r_{o2}$$

$$\text{CM gain} = \frac{4(r_{o4} \parallel r_{o2})}{R}$$

$$CMRR = \frac{g_{m1}(r_{o2} \parallel r_{o4})}{\frac{4(r_{o2} \parallel r_{o4})}{R}} = \boxed{\frac{g_{m1}R}{4} = CMRR}$$

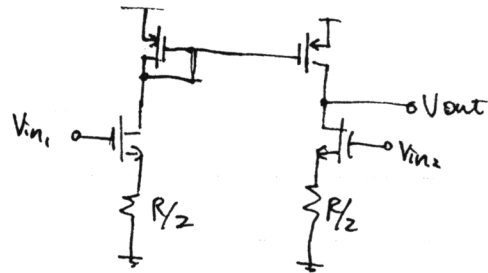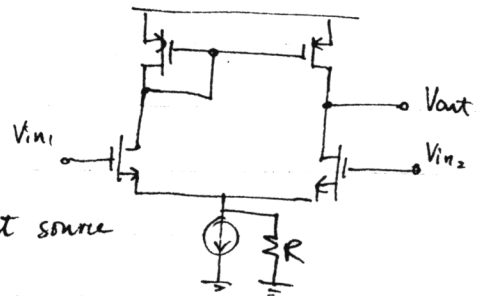

Problem 9.17

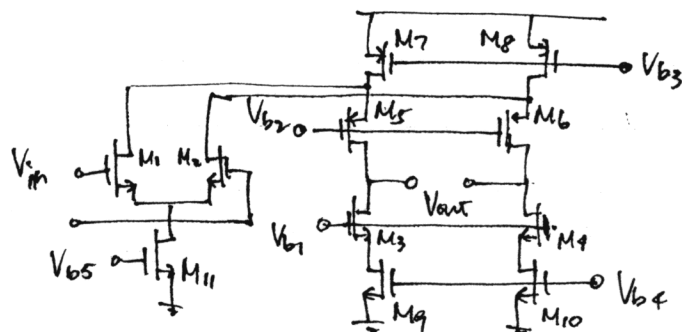

Neglect the noise due to $M_{11}, M_3, M_4, M_5, M_6$.

$$\text{Input-referred flicker noise due to } M_{7,8} = \frac{2 \left[\overline{V_{n,7,8}}^2 \cdot g_{m7,8}^2 R_{out}^2 \right]}{A_v}$$

$$\text{where } A_v = g_{m1} (R_{out}), \quad \overline{V_{n,7,8}}^2 = \frac{K_p}{C_{ox} (WL)_{7,8}} \cdot \frac{1}{f}$$

$$\overline{V_{n, \text{input}}|_{M_{9,10}}} = \frac{\overline{V_{n,9,10}}^2 \cdot g_{m9,10}^2 R_{out}^2}{g_{m1}^2 R_{out}^2} = 2 \left[\overline{V_{n,9,10}}^2 \frac{g_{m9,10}^2}{g_{m1,2}^2} \right]$$

Total Input-referred flicker noise

$$= \frac{2K_N}{C_{ox} f} \left[\frac{1}{(WL)_{1,2}} + \frac{1}{(WL)_{9,10}} \frac{g_{m9,10}^2}{g_{m1,2}^2} \right] + \frac{2K_p}{C_{ox} f} \frac{1}{(WL)_{7,8}} \frac{g_{m7,8}^2}{g_{m1,2}^2}$$

Problem 9.18

$$P = 6mW, \text{ output swing} = 2.5V$$

$$L_{eff} = 0.5\mu m$$

$$(a) I_{D5,6} = 1mA. V_{D5} \approx V_{D6} = \frac{V_{DD} - \text{Output Swing}}{2} = \frac{3 - 2.5}{2} = 0.25V$$

$$I_D = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$\left(\frac{W}{L}\right)_{eff} = \frac{2I_D}{\mu C_{ox} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})}$$

$$\left(\frac{W}{L}\right)_5 = \frac{2(1mA)}{(350)(383.6n)(0.25)^2(1 + (0.1)(0.25))}$$

$$I_{D5} = I_{D6} = 1mA$$

$$= 233$$

$$\left(\frac{W}{L}\right)_6 = \frac{2(1mA)}{(100)(383.6n)(0.25)^2(1 + 0.2(0.25))}$$

$$= 795$$

$$\boxed{\left(\frac{W}{L}\right)_5 = 233 \quad \left(\frac{W}{L}\right)_6 = 795}$$

$$b. A_v \text{ of 1st stage} = g_{m1} (r_{o2} \parallel r_{o4})$$

$$A_v \text{ of 2nd stage} = g_{m5} (r_{o5} \parallel r_{o6})$$

$$g_{m5} = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2(1mA)}{0.25} = 8mS^{-1}$$

$$r_{o5} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(1mA)} = 10k\Omega$$

$$r_{o6} = \frac{1}{\lambda I_D} = \frac{1}{(0.2)(1mA)} = 5k\Omega$$

$$\boxed{A_v \text{ of output stage} = (8m)(10k \parallel 5k) = 26.67}$$

$$(c) I_{D7} = 1mA \rightarrow I_{D3} = I_{D4} = 0.5mA$$

$$V_{GS5} - V_{TH} = 0.25V \Rightarrow V_{GS5} = 0.25 + V_{TH} = 0.95V$$

$$V_{GS3} - V_{TH} = 0.25$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{2(0.5mA)}{(350)(383.6n)(0.25)^2(1 + 0.1 \times 0.25)}$$

$$\boxed{\left(\frac{W}{L}\right)_{3,4} = 116}$$

9.18

$$(a) \quad A_{v_{tot}} = g_{m1}(r_{o2} \parallel r_{o4}) g_{m5}(r_{o5} \parallel r_{o6})$$

$$r_{o2} = \frac{1}{\lambda I_D} = \frac{1}{(0.2)(0.5\text{mA})} = 10\text{k}\Omega.$$

$$r_{o4} = \frac{1}{(0.1)(0.5\text{mA})} = 20\text{k}\Omega.$$

$$r_{o2} \parallel r_{o4} = 6.67\text{k}\Omega$$

$$A_{v_{tot}} = g_{m1}(6.67\text{k})(26.7) = 500$$

$$g_{m1} = 2.81\text{mA/V}$$

$$g_{m1} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right) I_D} \Rightarrow \left(\frac{W}{L}\right) = \frac{g_{m1}^2}{2\mu_p C_{ox} I_D}$$

$$\left(\frac{W}{L}\right)_{1,2} = \frac{(2.81\text{mA/V})^2}{2(100)(383.6\text{n})(0.5\text{mA})}$$

$$\boxed{\left(\frac{W}{L}\right)_{1,2} = 206}$$

Problem 9.19

$$A_v \text{ of 2nd stage} = 20 \quad I_{D5,6} = 1\text{mA}$$

$$(a), V_{DS} = V_{DS6}$$

$$A_v \text{ of 2nd stage} = g_{m5} (r_{o5} \parallel r_{o6})$$

$$= \frac{2I_D}{V_{GS} - V_{TH}} \cdot \left[\frac{1}{\lambda_n I_{D5}} \parallel \frac{1}{\lambda_p I_{D6}} \right] = 20.$$

$$r_{o5} = \frac{1}{(0.1)(1\text{mA})} = 10\text{k}\Omega \quad r_{o6} = \frac{1}{(0.2)(1\text{mA})} = 5\text{k}\Omega \quad r_{o5} \parallel r_{o6} = 3.33\text{k}\Omega$$

$$V_{GS} - V_{TH} = \frac{2I_D (r_{o5} \parallel r_{o6})}{A_v} = \frac{2(1\text{mA})(3.33\text{k}\Omega)}{20} = 0.333\text{V}$$

$$\left(\frac{W}{L}\right)_5 = \frac{2(1\text{mA})}{(350)(383.6\text{n})(0.33)^2(1 + 0.1 \times 0.33)} = 132 = (W/L)_5$$

$$\left(\frac{W}{L}\right)_6 = \frac{2(1\text{mA})}{(100)(383.6\text{n})(0.33)^2(1 + 0.2 \times 0.33)} = 449 = (W/L)_6$$

$$(b), r_{o6} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right) (V_{GS6} - V_{THp} - V_{DS})}$$

$$= \frac{1}{(100)(383.6\text{n})(449)(50\text{m})} = 1.16\text{k}\Omega$$

$$V_{GS6} - V_{THp} - V_{DS} = 50\text{mV}$$

$$A_v \text{ of 2nd stage} = \left[\frac{2(1\text{mA})}{0.333} \right] [10\text{k} \parallel 1.16\text{k}]$$

$$= 6.24 = A_v$$

Problem 9.20

$$a) |V_{GS7} - V_{TH7}| = 0.4V = V_{OD7}$$

$$V_{in\ max} = V_{DD} - |V_{OD7}| - |V_{OD1}| - |V_{TH1}|$$

$$\text{In part 1d, Prob 9.18. } g_{m1} = 2.81\text{ mS} = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2(0.5\text{ m})}{V_{OD1}}$$

$$|V_{OD1}| = 0.356V$$

$$V_{in\ max} = 3 - 0.4V - 0.356V - 0.8 = 1.444V$$

$$V_{in\ min} = |V_{OD3}| = 0.25 \quad \text{from Prob 9.18 (c)}$$

$$\text{Allowable input voltage range: } \boxed{0.25 \leq V_{in} \leq 1.44V}$$

b, At $V_{in} = V_{out}$, $V_{in1} = V_{in2}$ since V_{in2} is connect to V_{out}

$$\text{Since } V_{in1} = V_{in2}, I_{D1} = I_{D2} \Rightarrow V_X = V_Y.$$

$$\Rightarrow I_{D5} = 1\text{ mA} \Rightarrow I_{D1} = I_{D2} = 0.5\text{ mA}.$$

$$I_D = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$V_{GS1} - V_{TH} = \sqrt{\frac{2I_D}{\mu C_{ox} \left(\frac{W}{L}\right) (1 + \lambda V_{DS})}}$$

$$= \left[\frac{2(0.5\text{ m})}{(100)(383.6\text{ n})(206)(1 + 0.2 \times 1.3)} \right]^{\frac{1}{2}}$$

$$= 0.317V$$

$$V_{GS1} = 0.317 + 0.7 = 1.017V$$

$$V_{in} = V_{GS3} + V_{GS1} = 0.95 + 1.017V$$

$$V_{in} = 1.97V$$

$$V_{GS3} - V_{TH} = 0.25 \Rightarrow V_{GS3} = 0.95$$

$$\Rightarrow V_{DS} \cong V_{DD} - V_{DS7} - V_{GS3} \cong 3 - 0.7 - 0.95 \cong 1.3V$$

Problem 9.21

Noise due to M_7 is negligible since induce common mode gain, which is very small.

Consider 1st stage:

$$\overline{V_{n, \text{input}}}^2 | \text{1st stage} = \left[4kT \left(\frac{1}{g_{m1,2}} + \frac{g_{m3,4}}{g_{m1,2}^2} \right) \right] \times 2$$

Consider 2nd stage

$$\overline{V_{n, \text{output}}}^2 | \text{2nd stage} = [4kT \gamma (g_{m5} + g_{m6})] (r_{o5} \parallel r_{o6})^2$$

Overall:

$$\overline{V_{n, \text{input}}}^2 = \left[4kT \gamma \left(\frac{1}{g_{m1,2}} + \frac{g_{m3,4}}{g_{m1,2}^2} \right) \right] \times 2 + \frac{[4kT \gamma \left(\frac{1}{g_{m5}} + \frac{g_{m6}}{g_{m5}^2} \right)]}{[g_{m1} (r_{o2} \parallel r_{o4})]^2}$$

From Prob. 9.18

$$g_{m1,2} = 2.81 \text{ mS}, \quad g_{m3,4} = \frac{2I_D}{V_{DS3} - V_{TH}} = \frac{2(0.5 \text{ m})}{0.25} = 4 \text{ mS}^{-1}$$

$$g_{m5} = 8 \text{ mS}^{-1}, \quad g_{m6} = 8 \text{ mS}^{-1}, \quad r_{o2} = 10 \text{ k}\Omega, \quad r_{o4} = 2 \text{ k}\Omega, \quad r_{o2} \parallel r_{o4} = 6.67 \text{ k}\Omega$$

$$\overline{V_{n, \text{input}}}^2 = \left[4 \times 1.38 \times 10^{-23} \times 300 \times \frac{2}{3} \times \left(\frac{1}{2.81 \text{ m}} + \frac{4 \text{ m}}{2.81 \text{ m}^2} \right) \right] \times 2 + \frac{4 \times 1.38 \times 10^{-23} \times 300 \times \frac{2}{3} \times \left(\frac{1}{8 \text{ m}} + \frac{1}{8 \text{ m}} \right)}{[2.81 \text{ m} (6.67 \text{ k})]^2}$$


$$= 1.905 \times 10^{-17} \text{ V}^2/\text{Hz}$$

$$\overline{V_{n, \text{input}}}^2 = 4.36 \times 10^{-9} \text{ V}^2/\text{Hz}$$

9.22.

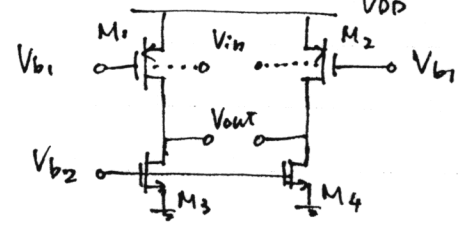(a) $A_v = g_{mb1,2} (r_{o1} \parallel r_{o3})$

b, $V_{in} > V_{DD} - V_{D1}$ where V_{D1} is the diode junction voltage of the diode between source and body.



(c) $g_{mb} = g_m \frac{\gamma}{2\sqrt{|\phi_F| + |V_{SB}|}}$

As $V_{in,cm}$ decreases, $|V_{SB}| \uparrow$, g_{mb} decreases.

More accurately, $g_{mb} \propto \frac{1}{\sqrt{|\phi_F| + |V_{SB}|}}$

As a result, A_v decreases.

(d)

$$\begin{aligned} \overline{V_{n,out}^2} &= [4kT\gamma (g_{m1} + g_{m3}) R_{out}^2] \times 2 \\ \overline{V_{n,in}^2} &= \frac{4kT\gamma (g_{m1} + g_{m3}) R_{out}^2 \times 2}{[g_{mb1,2} (R_{out})]^2} \\ &= \left[4kT\gamma \frac{g_{m1} + g_{m3}}{(g_{mb1,2})^2} \right] \times 2 \end{aligned}$$

Problem 9.23

a, Av of 1st stage = $g_{m1,2} (r_{o1} // r_{o3})$

Av of 2nd stage = $[g_{m5,9} (r_{o7} // r_{o5})] \times 2$

$A_{v-tot} = g_{m1,2} (r_{o1} // r_{o3}) g_{m5,9} (r_{o5} // r_{o7}) \times 2$

b, 1st major pole:

$$\omega_1 = \frac{1}{(r_{o9} // r_{o11}) [C_{DG9} + C_{DB9} + C_{GS11} + C_{DB11} + C_{GS7} + C_{GD7} (1 + g_{m7} (r_{o5} // r_{o7}))]}$$

2nd major pole: node X, Y

$$\omega_x = \frac{1}{(r_{o1} // r_{o3}) \left[C_{DG1} + C_{DB1} + C_{DG3} + C_{DB3} + C_{GS10} + C_{GD10} \left(1 + \frac{g_{m10}}{g_{m12}} \right) + C_{GS5} \right. \\ \left. + C_{GD5} (1 + g_{m5} (r_{o5} // r_{o7})) \right]}$$

3rd major pole: node output

$$\omega_{out} = \frac{1}{(r_{o5} // r_{o7}) (C_{GD5} + C_{DB5} + C_{GD7} + C_{DB7})}$$

Prob. 9.24.

A_v of fast path: $g_{m1}' (r_{o5} \parallel r_{o7})$

A_v of slow path: $g_{m1} (r_{o1} \parallel r_{o3}) g_{m5} (r_{o5} \parallel r_{o7})$.

Overall gain $A_{v\text{tot}} = \left[\frac{g_{m1}' + g_{m1} g_{m5} (r_{o1} \parallel r_{o3})}{2} \right] (r_{o5} \parallel r_{o7})$

The output swing is usually limited by M_{5-8} , i.e.
 $V_{DS} - |V_{DD7}| - V_{DD5}$.

Problem 9.25

Noise due to $M_{1,2}$

$$\overline{V_{n, \text{input}}^2} | M_{1,2} = 4kTY \left(\frac{1}{g_{m1,2}} \right) \times 2$$

$$\overline{V_{n, \text{input}}^2} | M_{1,2} = 4kTY \left(\frac{1}{g_{m1,2}} \right) \times 2$$

$$\overline{V_{n, \text{input}}^2} | M_{3,4} = 4kTY \left(\frac{g_{m3,4}}{g_{m1,2}^2} \right) \times 2$$

$$\overline{V_{n, \text{output}}^2} | M_{5,6} = 4kTY g_{m5,6} R_{out} \times 2$$

$$\overline{V_{n, \text{output}}^2} | M_{7,8} = 4kTY g_{m7,8} R_{out} \times 2$$

$$\overline{V_{n, \text{input}}^2} | M_{5-8} = \frac{4kTY (g_{m5,6} + g_{m7,8}) \times 2}{\left(\frac{g_{m1} + g_{m1} g_{m5} (R_{o1} // R_{o3})}{2} \right)^2}$$

$$\overline{V_{n, \text{input}}^2} |_{\text{tot}} = 2 \left[4kTY \left(\frac{1}{g_{m1,2}} + \frac{1}{g_{m1,2}} + \frac{g_{m3,4}}{g_{m1,2}^2} + \frac{4(g_{m5,6} + g_{m7,8})}{(g_{m1} + g_{m1} g_{m5} (R_{o1} // R_{o3}))^2} \right) \right]$$

CHAPTER 10

10.1

10.1 Two poles $\omega_{p1} = 10 \text{ MHz}$ $\omega_{p2} = 500 \text{ MHz}$

First find ω_1 ($= G \times$) that gives phase $= -120^\circ$ (P.M. of 60°)

$$-120^\circ = -\tan^{-1} \frac{\omega_1}{\omega_{p1}} - \tan^{-1} \frac{\omega_1}{\omega_{p2}} \longrightarrow \omega_1 \cong 311 \text{ MHz}$$

$$A_o = (\log \frac{\omega_1}{\omega_{p1}}) (20 \text{ dB/dec}) = (\log \frac{311}{10}) (20) = \underline{\underline{29.9 \text{ dB}}}$$


10.2 $\omega_{p1} = \omega_{p2} = \omega_p$

a) $60^\circ \cdot \frac{1}{90^\circ/\text{dec}} = 0.67 \text{ decade}$

$$\log \frac{10\omega_p}{\omega_1} = 0.67 \text{ dec} \quad (\omega_1 \text{ is } G \times)$$

$$\Rightarrow \omega_1 = 2.14 \omega_p$$
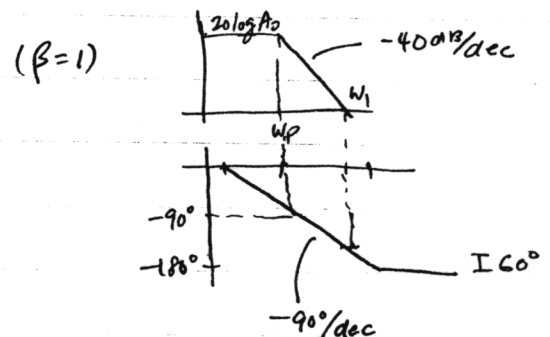
$$A_o = (\log \frac{2.14\omega_p}{\omega_p}) (40 \text{ dB/dec}) = \underline{\underline{13.2 \text{ dB}}}$$



b) For closed-loop gain $= 4 \Rightarrow \beta \approx \frac{1}{4}$

Thus A_o can increase by a factor of 4 to maintain 60° P.M.

$$\Rightarrow A'_o = 13.2 \text{ dB} + 20 \log 4 = \underline{\underline{25.2 \text{ dB}}}$$

10.3 $A_o = 1000$ $\omega_{p1} = 1 \text{ MHz}$

a) 60 dB $= 60 \text{ dB} - (\log \frac{2 \text{ MHz}}{1 \text{ MHz}}) (20 \frac{\text{dB}}{\text{dec}}) = \underline{\underline{54 \text{ dB}}}$

$$\log \frac{\omega_1}{2 \text{ MHz}} = 54 \text{ dB} \frac{1}{40 \text{ dB/dec}} = 1.35 \text{ dec}$$

$$\omega_1 = \underline{\underline{44.8 \text{ MHz}}}$$

$$\angle H(j\omega_1) = -\tan^{-1} \frac{\omega_1}{1 \text{ MHz}} - \tan^{-1} \frac{\omega_1}{2 \text{ MHz}} = -176.2^\circ \Rightarrow \text{P.M.} = 180^\circ - 176.2^\circ = \underline{\underline{3.8^\circ}}$$

b) $\omega'_{p2} = 4 \text{ MHz}$

$$\log \frac{\omega'_1}{4 \text{ MHz}} = [60 \text{ dB} - (\log \frac{4 \text{ MHz}}{1 \text{ MHz}}) (20 \text{ dB/dec})] \frac{1}{40 \text{ dB/dec}} = 1.199 \text{ dec}$$

$$\Rightarrow \omega'_1 = 63.2 \text{ MHz}$$

$$\angle H(j\omega'_1) = -175.5^\circ \Rightarrow \underline{\underline{\text{P.M.} = 4.5^\circ}}$$

10.4



$$\beta = 1$$

$$\text{At } \omega_1, H(j\omega_1) = 1 \cdot e^{j\theta_1}$$


$$\text{Closed loop: } \left| \frac{Y}{X}(j\omega_1) \right| = \left| \frac{H(j\omega_1)}{1 + H(j\omega_1)} \right| = 1.5$$

$$\left| \frac{1}{1 + e^{j\theta_1}} \right| = 1.5$$


$$\rightarrow \frac{1}{\sqrt{1 + 2\cos\theta_1 + 1}} \rightarrow \frac{1}{2 + 2\cos\theta_1} = 1.5^2 \rightarrow \theta_1 = -141.1^\circ$$

$$\underline{\underline{P.M. = 38.9^\circ}}$$

10.5

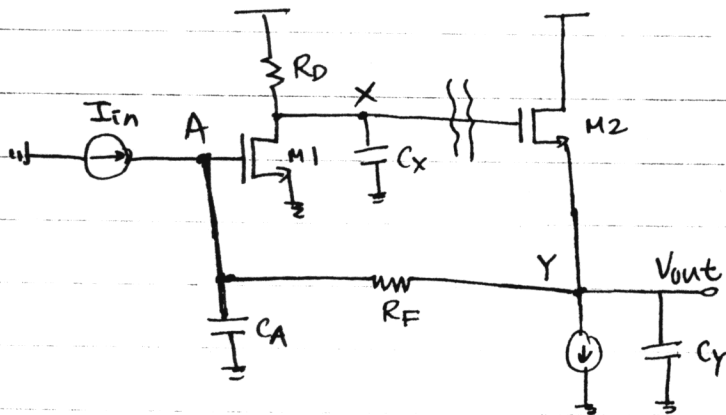

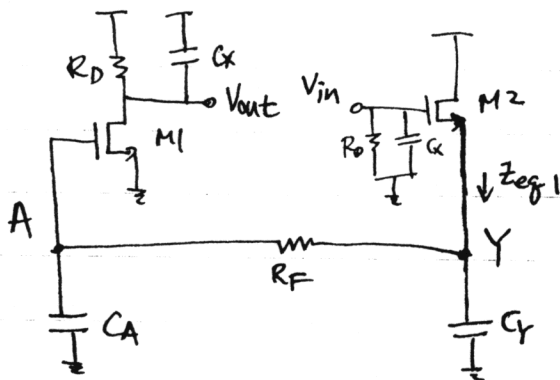Breaking the loop at node X as shown by $\{\}$ and replacing each end by the impedance each sees, we get the next circuit:



Next, calculate the loop gain

$$\frac{V_{out}}{V_{in}}(s) = \frac{V_Y}{V_{in}} \cdot \frac{V_A}{V_Y} \cdot \frac{V_{out}}{V_A} = A_{v1} \cdot A_{v2} \cdot A_{v3}$$


$$Z_{eg1} \approx \frac{1}{sC_Y} \text{ since } R_F = 10 \text{ k}\Omega \gg \frac{1}{g_{m2}}$$

$$A_{v1} = \frac{g_{m2} Z_{eg1}}{1 + g_{m2} Z_{eg1}} \approx \frac{g_{m2} \frac{1}{sC_Y}}{1 + g_{m2} \frac{1}{sC_Y}} = \frac{1}{s\left(\frac{C_Y}{g_{m2}}\right) + 1}$$

$$A_{v2} = \frac{\frac{1}{sC_A}}{R_F + \frac{1}{sC_A}} = \frac{1}{sC_A R_F + 1}$$

$$A_{v3} = -g_{m1} (R_D \parallel \frac{1}{sC_X}) = \frac{-g_{m1} R_D}{1 + sC_X R_D}$$

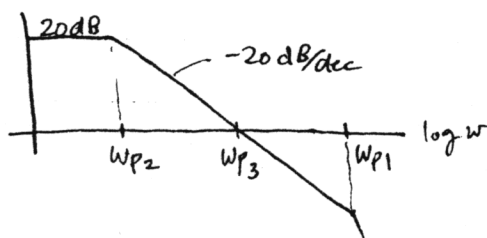Hence $\omega_{p1} = \frac{g_{m2}}{C_Y} = 1 \times 10^{11} \text{ rad/s}$, $\omega_{p2} = \frac{1}{C_A R_F} = 1 \times 10^9 \text{ rad/s}$, $\omega_{p3} = \frac{1}{C_X R_D} = 1 \times 10^{10} \text{ rad/s}$
and $g_{m1} R_D = 10 \rightarrow 20 \text{ dB}$



$$\Rightarrow \underline{\underline{P.M. = 45^\circ}}$$

10.6 $R_D' = 2 \text{ k}\Omega$

$\rightarrow g_{m1} R_D' = 20 \Rightarrow \underline{26.0 \text{ dB}}$, $\omega_{P3}' = \frac{1}{C_X R_D'} = \underline{5 \times 10^9 \text{ rad/s}}$.

$\omega_i' \Rightarrow 26 \text{ dB} - \left(\log \frac{\omega_{P3}'}{\omega_{P2}'} \right) (20 \text{ dB/dec}) - \left(\log \frac{\omega_i'}{\omega_{P3}'} \right) (40 \text{ dB/dec}) = 0 \text{ dB}$
 $\omega_i' = \underline{9.99 \times 10^9 \text{ rad/s}}$


$\phi = -\tan^{-1} \frac{\omega_i'}{1 \times 10^9} - \tan^{-1} \frac{\omega_i'}{5 \times 10^9} - \tan^{-1} \frac{\omega_i'}{1 \times 10^{11}} = -153.4^\circ$

P.M. = 26.6°

10.7 From 10.5 $\omega_{P1} = \frac{g_{m2}}{C_Y}$ $\omega_{P2} = \frac{1}{C_A R_F}$ $\omega_{P3} = \frac{1}{C_X R_D}$

- Increasing C_Y causes ω_{P1} to move towards ω_{P3} and will be less than 1 decade from ω_{P3} . This will reduce the already 45° -phase margin. Hence $C_{Y \max} = 100 \text{ fF}$.
- Increasing C_A will increase phase margin.
Hence $C_{A \max} = 100 \text{ fF}$.
- $C_{X \max} = 100 \text{ fF}$ since increasing C_X will reduce phase margin.

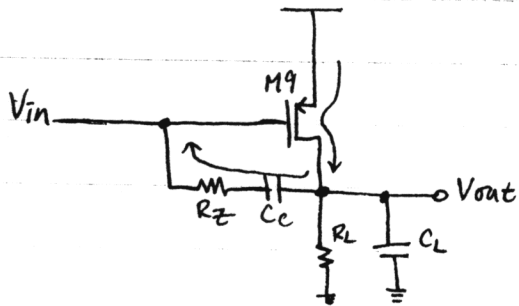10.8 The approximation can be derived from the ideal case in which the circuit looks like the following:



At the zero, $V_{out} = 0$. and

$$\frac{-V_{th}}{R_Z + \frac{1}{s_z C_c}} = -g_{m9} V_{in}$$

$$\left(\frac{1}{g_{m9}} - R_Z \right)^{-1} = s_z C_c$$

$$\therefore s_z = \frac{1}{C_c (g_{m9}^{-1} - R_Z)}$$

10.9 $\left(\frac{W}{L}\right)_{1-4} = \frac{50}{0.5}$ $I_{SS} = I_1 = 0.5 \text{ mA}$ $C_X = C_Y = 0.5 \text{ pF}$

a)

$$\omega_{PX} \approx \frac{1}{C_X (r_{op3} \parallel r_{op2})}$$

$$\omega_{PY} \approx \frac{1}{C_Y \cdot (g_{m4}^{-1})}$$

In saturation :

$$r_o = \frac{1}{\lambda I_D}$$

$$\lambda_P = 0.2 \quad \lambda_n = 0.1 \quad \text{from Table 2.1}$$

$$r_{op3} = \frac{1}{0.2 (0.25 \text{ mA})} = 20 \text{ k}\Omega$$

$$r_{on2} = 2 r_{op3} = 40 \text{ k}\Omega$$


$$g_{m4} = \sqrt{2 I_D \mu_n C_{ox} \frac{W}{L}} = \sqrt{2 (0.5 \text{ mA}) (1.34 \times 10^{-4}) \left(\frac{50}{0.5}\right)} = \frac{1}{273} \text{ A/V}$$

$$g_{m4}^{-1} = 273.0 \Omega$$

$$\Rightarrow \omega_{PX} = 150 \times 10^6 \text{ rad/s}, \quad \omega_{PY} = 7.33 \times 10^9 \text{ rad/s} //$$

$$| \text{Low frequency gain} | \approx g_{m2} (r_{on2} \parallel r_{op3}) \cdot (1) \quad (g_{m2} = \frac{g_{m4}}{\sqrt{2}})$$
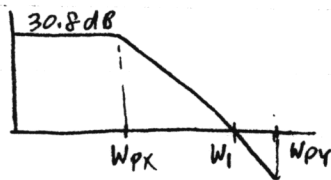
$$\approx 34.5 \text{ V/V} \Rightarrow 30.8 \text{ dB} //$$



$$30.8 \text{ dB} - \left[\log \left(\frac{7.33 \times 10^9}{150 \times 10^6} \right) \right] (20 \text{ dB/dec}) = -3.78 \text{ dB}$$

$$\left(\log \frac{\omega_1}{150 \times 10^6} \right) (20 \text{ dB/dec}) = 30.8 \text{ dB}$$

$$\Rightarrow \omega_1 = 5.20 \times 10^9 \text{ rad/s} //$$

$$\phi = -\tan^{-1} \frac{\omega_1}{\omega_{PX}} - \tan^{-1} \frac{\omega_1}{\omega_{PY}} = -123.7^\circ$$

$$\Rightarrow \underline{\underline{\text{P.M.} = 56.3^\circ}}$$

b)

$$\phi = -\tan^{-1} \frac{\omega_1}{150 \times 10^6} - \tan^{-1} \frac{\omega_1}{\omega_{PY}} = -120^\circ$$

$$\text{If } \omega_1 \text{ is same as (a), then } \omega_{PY} = 8.43 \times 10^9 \text{ rad/s}$$

$$= \frac{1}{C_{Y\max} g_{m4}^{-1}}$$


$$\underline{\underline{C_{Y\max} = 434 \text{ fF}}}$$

10.10

For large positive step in V_{in} :

M_2 turns off. M_3 charges C_x and M_4 charges C_y .

(M_4 also provides I_1 .)

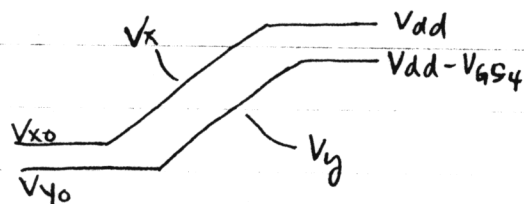

The slew rates of V_x and V_y (or V_{out}) must be exactly the same — regardless of C_x or C_y .

Hence slew rate due to positive step input $\cong \frac{I_{p3}}{C_x}$ for both parts (a) and (b) of 10.9.

$$\text{slew rate} \cong \frac{I_{p3}}{C_x} \cong \frac{0.25 \text{ mA}}{0.5 \text{ pF}} = 5.00 \times 10^8 \text{ V/s} //$$

For large negative step in V_{in} :

Again, V_{out} tracks V_x — as V_x drops, V_{out} drops at the same rate.

$$\text{Slew rate} \cong -\frac{I_{cx}}{C_x}, \quad I_{p3} \cong 0.25 \text{ mA}, \quad I_{cx} \cong 0.5 \text{ mA} - I_{p3} = 0.25 \text{ mA}$$

$$\text{For both } C_y\text{'s}, \quad \text{slew rate} \cong -\frac{0.25 \text{ mA}}{0.5 \text{ pF}} = -5.00 \times 10^8 \text{ V/s} //$$

$$\boxed{10.11} \quad \left(\frac{W}{L}\right)_{5,6} = \frac{60}{0.5} \quad I_{SS} = 0.25 \text{ mA}$$

a) CM level $V_x = V_y = V_{DD} - V_{GS5} = V_{DD} - V_{GS6}$
 $I = 1 \text{ mA} = \frac{1}{2} \mu_p C_{ox} \left(\frac{60}{0.5}\right) (|V_{GS6}| - |V_{tp}|)^2$
 $V_{GS6} = 1.46 \text{ V} \rightarrow V_x = V_y = 3 - 1.46 = 1.54 \text{ V}$

b) Max. output swing:

$$V_{out, \max} = V_{DD} - V_{overdrive6} = 3 - (1.46 - 0.8) = \underline{2.34 \text{ V}}$$

$$V_{out, \min} = V_{overdrive8} = V_b - V_{tn} = \underline{0.39 \text{ V}}$$

$$(\text{since } V_b = 1.09 \text{ V from } 1 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - 0.7)^2)$$

$$\text{Total max. swing} = 2.34 - 0.39 = \underline{1.95 \text{ V}}$$

c) $r_{on2} = \frac{1}{(0.1)(0.125 \text{ mA})} = 80 \text{ k}\Omega$
 $r_{op4} = 40 \text{ k}\Omega$ } $\rightarrow r_{on2} \parallel r_{op4} = 26.67 \text{ k}\Omega$
 $r_{on8} = 10 \text{ k}\Omega, r_{op6} = 5 \text{ k}\Omega$ } $\rightarrow r_{on8} \parallel r_{op6} = 3.33 \text{ k}\Omega$
 $g_{m2} = \sqrt{2(0.125 \text{ mA})(1.34 \times 10^{-4})(\frac{50}{0.5})} = 1.83 \times 10^{-3} \text{ A/V}$
 $g_{m6} = \mu_p C_{ox} \frac{W}{L} (V_{GS6} - V_{th}) = (3.83 \times 10^{-5})(\frac{60}{0.5})(1.46 - 0.8) = 3.03 \times 10^{-3} \text{ A/V}$
 $A_{v2} = g_{m6}(3.33 \text{ k}\Omega) = -10.09 \text{ V/V}$
 $A_{v1} = g_{m2}(26.67 \text{ k}\Omega) = -48.8 \text{ V/V}$ } $\rightarrow A_{v1}, A_{v2} = 492.4 \rightarrow \underline{53.8 \text{ dB}}$

$$C_{out} = C_L + [C_{db6} + (1 + \frac{1}{|A_{v2}|}) C_{gd6}] + (C_{db8} + C_{gd8})$$

$$\approx 1 \text{ pF} + 52.1 + (1 + \frac{1}{10.09}) 0.18 + 23.4 + 0.2 = \underline{1.076 \text{ pF}}$$

$$C_Y = C_{gd4} + C_{db4} + C_{gd2} + C_{db2} + C_{gs6} + C_{gd6}(1 + |A_{v2}|)$$

$$\approx 0.15 + 43.8 + 0.2 + 23.4 + 76.6 + 0.18(11.09) = \underline{146.1 \text{ fF}}$$

Using:

$$C_{overlap} = C_{GD0} \cdot W, \quad C_{db} = \frac{(C_J)(W \cdot 1.5 \mu\text{m})}{[1 - \frac{V_D}{V_{PB}}]_{MJS}} + \frac{C_{JSW}(2W + 3 \mu\text{m})}{[1 - \frac{V_D}{V_{PB}}]_{MJSW}}$$

(V_D = reverse bias junction voltage.)

10.11c) cont. $C_{gs} = \frac{2}{3} C_{ox} W \cdot L$, Values from Table 2.1.

Before Compensation:

$$\text{Dominant Pole: } \omega_p = \frac{1}{C_y R_y} = \frac{1}{(146.1 \text{ fF})(26.67 \text{ k}\Omega)} = 2.57 \times 10^8 \text{ rad/s}$$

$$\text{2nd Pole: } \omega_{out} = \frac{1}{C_{out} R_{out}} = \frac{1}{(1.076 \text{ pF})(3.33 \text{ k}\Omega)} = 2.79 \times 10^8 \text{ rad/s}$$

★ After compensation:

$$\text{2nd Pole: } \omega'_{out} \approx \frac{g_{m6}}{C_y + C_{out}} = \frac{3.03 \times 10^{-3}}{146.1 \text{ fF} + 1.076 \text{ pF}} = \underline{\underline{2.48 \times 10^9 \text{ rad/s}}}$$

$$\text{Dominant Pole: } \omega'_y = \frac{1}{[C_y + (1 + |A_{vsl}|)C_c] R_y}$$

(For 60° P.M.)

$$90^\circ + \tan^{-1} \frac{\omega'_y}{\omega'_{out}} = 120^\circ \rightarrow \omega'_y = \omega'_{out} \tan 30^\circ = 1.43 \times 10^9 \text{ rad/s}$$

$$\log \frac{\omega'_y}{\omega_y} = \frac{53.8 \text{ dB}}{20 \text{ dB/dec}} \rightarrow \omega'_y = \frac{1}{10^{53.8/20}} \cdot \omega_y = \underline{\underline{2.91 \times 10^6 \text{ rad/s}}}$$


$$C_c = \frac{[(2.91 \times 10^6)(26.67 \text{ k}\Omega)]^{-1} - 146.1 \text{ fF}}{1 + 10.08} = \underline{\underline{1.15 \text{ pF}}}$$

(So $C_c \gg C_y$)

$$\text{Zero: } \omega'_z = \frac{g_{m6}}{C_c + C_{gd6}} = \frac{3.03 \times 10^{-3}}{1.15 \text{ pF} + 0.18 \text{ fF}} = \underline{\underline{2.63 \times 10^9 \text{ rad/s}}} \quad (> \omega'_y, \omega'_{out})$$

$$d) \omega_z = \frac{1}{C_c (\frac{1}{g_{m6}} + R_z)} = -|\omega'_{out}|$$

$$\rightarrow R_z = \frac{1}{g_{m6}} + \frac{1}{|\omega'_{out}| \cdot C_c} = \underline{\underline{680.7 \Omega}}$$

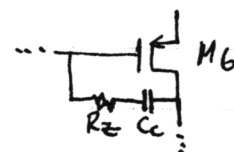


e) Slew rate: Symmetrical for large positive V_{in} or large negative V_{in} .

Large + V_{in} :

$$\text{Slew rate of } V_{out2} \approx -\frac{I_{D4}}{C_c} \approx -\frac{0.125 \text{ mA}}{1.15 \text{ pF}} = \underline{\underline{1.09 \times 10^8 \text{ V/s}}}$$

$$\text{Slew rate of } V_{out1} = -(\text{slew rate of } V_{out2}) = \underline{\underline{1.09 \times 10^8 \text{ V/s}}}$$

10.12

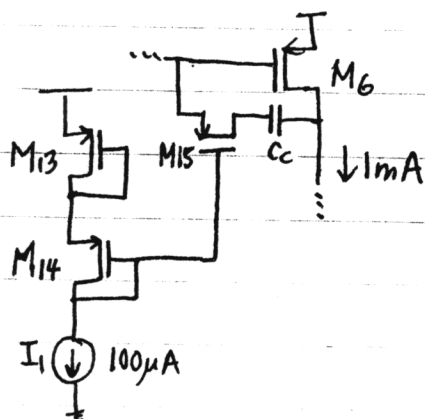

Want $|V_{gs13}| = |V_{gs6}| = 1.46 \text{ V}$ (from 10.11a)

$$100 \mu\text{A} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_{13} (|V_{gs6}| - |V_{tp}|)^2$$

$$\hookrightarrow \left(\frac{W}{L}\right)_{13} = \frac{2(100 \mu\text{A})}{(3.83 \times 10^{-5})(1.46 - 0.8)^2} = \underline{\underline{120}} \quad \text{e.g. } \left(\frac{W}{L}\right)_{13} = \frac{6}{0.5}$$

Allowing 0.5V across I_1 and maximizing $V_{gs14} = V_{gs15}$,

We get $V_{gs14} = V_{gs15} = V_{DD} - 0.5 = 1.54 - 0.5 = \underline{\underline{1.04 \text{ V}}}$


$$R_{on15} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{15} (1.04 - 0.8)} = 680.7 \Omega$$

$$\hookrightarrow \left(\frac{W}{L}\right)_{15} = \underline{\underline{384}} \quad \text{e.g. } \frac{192}{0.5}$$

$$I_{D14} = 100 \mu\text{A} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_{14} (1.04 - 0.8)^2$$

$$\hookrightarrow \left(\frac{W}{L}\right)_{14} = \underline{\underline{90.7}} \quad \text{e.g. } \frac{45.5}{0.5}$$

10.13

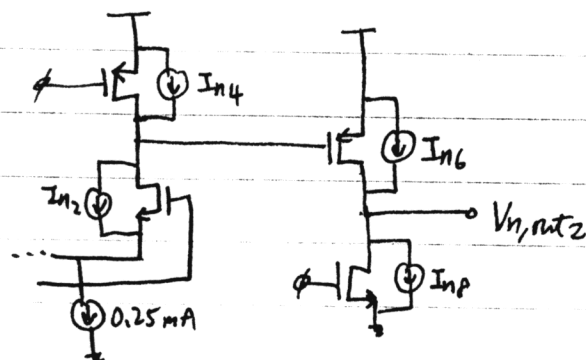

$$\overline{I_n^2} = 4kT \frac{2}{3} g_m$$

$$V_{n,out2} = (I_{n2} + I_{n4})(r_{o2} \parallel r_{o4}) \cdot A_{v2} + (I_{n6} + I_{n8})(r_{o6} \parallel r_{o8})$$

$$\overline{V_{n,out2}^2} = (\overline{I_{n2}^2} + \overline{I_{n4}^2}) [(r_{o2} \parallel r_{o4}) A_{v2}]^2 + (\overline{I_{n6}^2} + \overline{I_{n8}^2}) (r_{o6} \parallel r_{o8})^2$$

$$\overline{V_{n,out1}^2} = (\overline{I_{n1}^2} + \overline{I_{n3}^2}) [(r_{o2} \parallel r_{o4}) A_{v2}]^2 + (\overline{I_{n5}^2} + \overline{I_{n7}^2}) (r_{o6} \parallel r_{o8})^2$$

$$\overline{V_{n,out}^2} = \overline{V_{n,out2}^2} + \overline{V_{n,out1}^2}$$

$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{(A_{v1} A_{v2})^2}$$

$$= \left(\frac{1}{A_{v1} A_{v2}} \right)^2 \left\{ [(r_{o2} \parallel r_{o4}) A_{v2}]^2 [\overline{I_{n1}^2} + \overline{I_{n2}^2} + \overline{I_{n3}^2} + \overline{I_{n4}^2}] + (r_{o6} \parallel r_{o8})^2 (\overline{I_{n5}^2} + \overline{I_{n6}^2} + \overline{I_{n7}^2} + \overline{I_{n8}^2}) \right\}$$

Aside


$$\begin{cases} g_{m1} = g_{m2} = 1.83 \times 10^{-3} \text{ A/V} \\ g_{mP1} = g_{m4} = \sqrt{2 I_{PP} \mu_n \frac{W}{L}} = \sqrt{2 (0.125 \text{ mA}) (3.83 \times 10^{-5}) \left(\frac{50}{0.5} \right)} = 9.79 \times 10^{-4} \text{ A/V} \\ g_{mN2} = g_{m8} = 5.18 \times 10^{-3} \text{ A/V} ; & A_{v1} = 48.8, A_{v2} = 10.09 \\ g_{mP2} = g_{m6} = 3.03 \times 10^{-3} \text{ A/V} ; & r_{o2} \parallel r_{o4} = 26.67 \text{ k}\Omega, r_{o6} \parallel r_{o8} = 3.33 \text{ k}\Omega \end{cases}$$

$$\overline{V_{n,in}^2} = 4kT \frac{2}{3} [1678.1 + 0.7511] = 4kT \frac{2}{3} [1678.85]$$


$$(4kT = 1.658 \times 10^{-20})$$

$$= 1.86 \times 10^{-17} \text{ V}^2/\text{Hz}$$


10.14

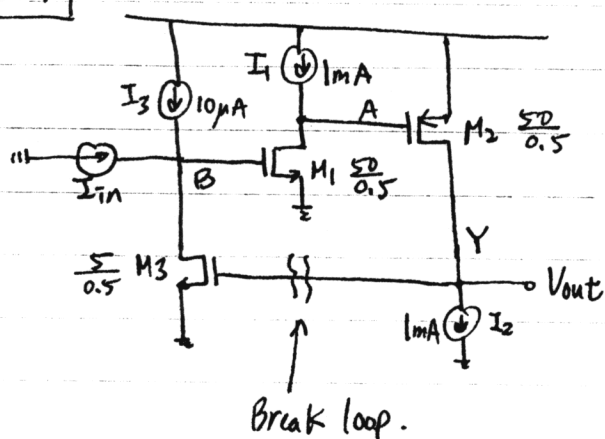

a)

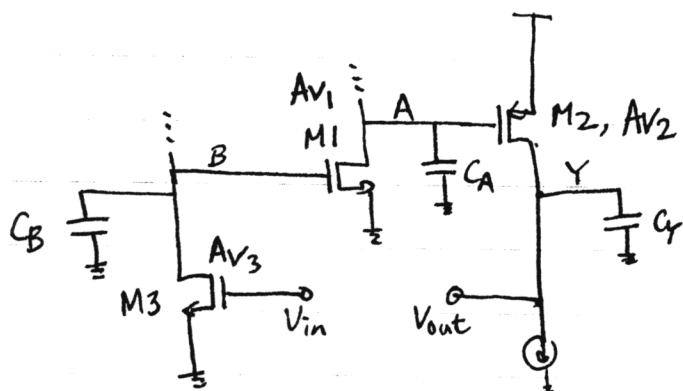

Cap's:

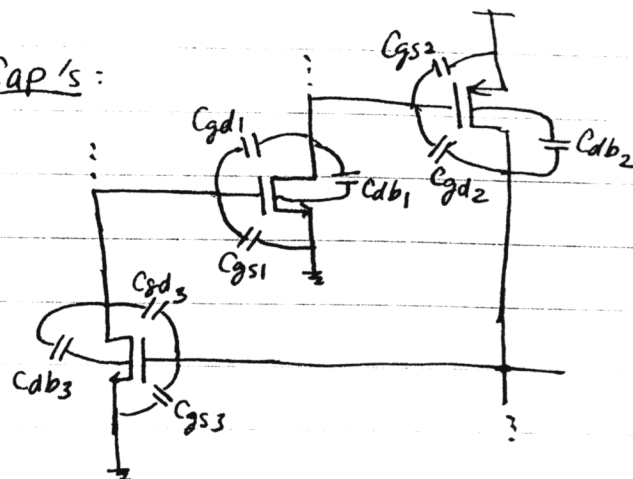

$$C_B = C_{db3} + \left(1 + \frac{1}{|A_{v3}|}\right) C_{gd3} + C_{gs1} + (1 + |A_{v1}|) C_{gd1}$$

$$C_A = (1 + |A_{v1}|) C_{gd1} + C_{gs2} + (1 + |A_{v2}|) C_{gd2} + C_{db1}$$

$$C_Y = C_{db2} + \left(1 + \frac{1}{|A_{v2}|}\right) C_{gd2} + C_{gs3} + (1 + |A_{v3}|) C_{gd3}$$

$$r_{o1} = \frac{1}{(0.1)(1\text{mA})} = 10\text{ k}\Omega$$

$$r_{o2} = 5\text{ k}\Omega$$

$$r_{o3} = 1\text{ M}\Omega$$

Using capacitance formulas of (10.11), we get:

$$C_A = 80.4\text{ fF}$$

$$C_B = 77.1\text{ fF}$$

$$C_Y = 105.6\text{ fF}$$

$$V_A = 1.48\text{ V}$$

$$V_B = 1.09\text{ V}$$

$$V_Y = 0.822\text{ V}$$

Also,

$$g_{m1} = \sqrt{2(1\text{mA})(1.34 \times 10^{-4})(50/0.5)} = 5.18 \times 10^{-3}\text{ A/V}$$

$$g_{m2} = 2.77 \times 10^{-3}\text{ A/V}$$

$$g_{m3} = 1.64 \times 10^{-4}\text{ A/V}$$

$$A_{v1} = g_{m1} r_{o1} = -51.8\text{ V/V}$$


$$A_{v2} = g_{m2} r_{o2} = -13.85\text{ V/V}$$

$$A_{v3} = g_{m3} r_{o3} = -164.0\text{ V/V}$$

$$\left|A_{v1} A_{v2} A_{v3}\right| = 1.18 \times 10^5 \rightarrow \underline{\underline{101.4\text{ dB}}}$$

10.14 a) cont.

$$\begin{aligned}
 W_A &= \frac{1}{C_A r_{o1}} = 1.24 \times 10^9 \text{ rad/s} && \leftarrow \text{2nd} \\
 W_B &= \frac{1}{C_B r_{o3}} = 1.30 \times 10^7 \text{ rad/s} && \leftarrow \text{Dominant} \\
 W_Y &= \frac{1}{C_Y r_{o2}} = 1.89 \times 10^9 \text{ rad/s} && \leftarrow \text{3rd}
 \end{aligned}$$

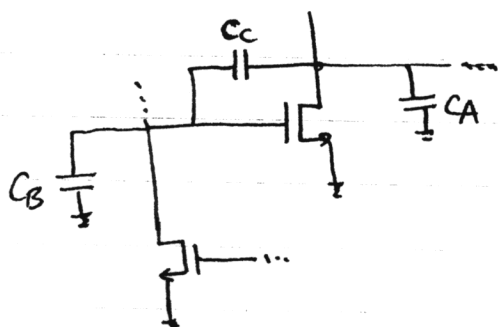(Phase Margin is $-78.3^\circ \rightarrow$ unstable system.)b) Compensate by adding C_c across G and D of M_1 .

$$\rightarrow W_A' \approx \frac{g_{m1}}{C_B + C_A} = \frac{5.18 \times 10^{-3}}{77.1 \text{ fF} + 80.4 \text{ fF}} = \underline{\underline{3.3 \times 10^{10} \text{ rad/s}}}$$

$$\rightarrow W_Y \text{ unchanged} = \underline{\underline{1.89 \times 10^9 \text{ rad/s}}}$$

$$90^\circ + \tan^{-1} \frac{W_1}{W_Y} = 120^\circ \quad (\text{For } 60^\circ \text{ P.M.})$$

$$\tan^{-1} \frac{W_1}{W_Y} = 30^\circ$$

$$\underline{\underline{W_1 = 1.09 \times 10^9 \text{ rad/s}}}$$

$$\left(\log \frac{W_1}{W_B'} \right) \frac{20 \text{ dB}}{\text{dec}} = 101.4 \text{ dB}$$

$$\rightarrow \underline{\underline{W_B' = 9.28 \times 10^3 \text{ rad/s}}}$$

Dominant = W_B' , 2nd: W_Y , 3rd: W_A'

$$W_B' = \frac{1}{[C_B + (1 + |A_{v1}|) C_c] r_{o3}} \rightarrow C_c = \frac{1}{\frac{W_B' (1 \times 10^6)}{52.8} - 77.1 \text{ fF}} = \underline{\underline{2.04 \text{ pF}}}$$

$$W_Z' \approx \frac{g_{m1}}{C_c} = \frac{5.18 \times 10^{-3}}{2.04 \text{ pF}} = \underline{\underline{2.54 \times 10^9 \text{ rad/s}}} \quad (> W_Y)$$

10.14 c)

$$W_z = \frac{1}{C_c (g_{m1}^{-1} - R_z)} = -|W_g| = -1.89 \times 10^9$$

$$\hookrightarrow R_z = \frac{1}{g_{m1}} + \frac{1}{|W_g| C_c} = \underline{\underline{452.4 \Omega}}$$

10.15 a) Before compensation:

$$C_A = 80.4 \text{ fF}$$

$$C_B = 77.1 \text{ fF}$$

$$C_Y = 105.6 \text{ fF} + 0.5 \text{ pF} = 605.6 \text{ fF}$$

$$\omega_A = 1.24 \times 10^9 \text{ rad/s}$$

$$\omega_B = 1.30 \times 10^7 \text{ rad/s}$$


$$\omega_Y = \frac{1}{(605.6 \text{ fF})(5 \times 10^3)} = 3.30 \times 10^8 \text{ rad/s}$$

← 3rd

← Dominant

← 2nd

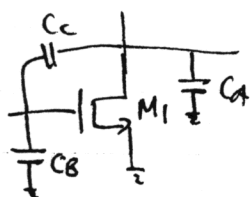b) Two choices: We can put C_c across G & D of M_1 OR just add a C from G of M_1 to ground. Cannot take advantage of splitting 1st and 2nd pole here since 1st pole is at B and 2nd pole is at Y and the gain between those two nodes is > 0 .
Choose to put C_c across M_1 : Splits 1st and 3rd poles,
2nd pole unchanged.



$$\text{3rd: } \omega'_A \cong \frac{g_{m1}}{C_A + C_B} = 3.30 \times 10^{10} \text{ rad/s}$$

$$\text{2nd: } \omega_Y = 3.30 \times 10^8 \text{ rad/s (unchanged)}$$

$$\omega'_1 = \omega_Y \cdot \tan 30^\circ = 1.91 \times 10^8 \text{ rad/s}$$

$$\text{Dominant: } \omega'_B = \frac{1}{10^{(101.4/20)}} \cdot \omega'_1 = 1.63 \times 10^3 \text{ rad/s}$$

$$C_c = \frac{1}{\frac{(1.63 \times 10^3)(1 \times 10^6)}{52.8} - 77.1 \text{ fF}} = \underline{\underline{11.6 \text{ pF}}}$$

10.16

10.15c)

$$W_z = \frac{1}{C_c(g_{m1}^{-1} - R_z)} = -|W_y| = -3.30 \times 10^8 \text{ rad/s}$$

$$\hookrightarrow R_z = \frac{1}{g_{m1}} + \frac{1}{|W_y| \cdot C_c}$$

$$R_z = \frac{1}{5.18 \times 10^{-3}} + \frac{1}{(3.3 \times 10^8)(11.6 \text{ pF})}$$

$$\underline{\underline{R_z = 454.3 \Omega}}$$

10.16

If M_1 turns off momentarily, I_1 causes a positive jump in voltage at node A. This causes M_2 to shut off momentarily so the slew rate is determined by I_2 and C_y .

$$i) \text{ Slew rate} = -\frac{I_2}{C_y} = -\frac{1 \text{ mA}}{105.6 \text{ fF}} = \underline{\underline{-9.47 \times 10^9 \text{ V/s}}}$$

(If unloaded)

$$ii) \text{ Slew rate} = -\frac{I_2}{C_y + C_L} = -\frac{1 \text{ mA}}{105.6 \text{ fF} + 0.5 \text{ pF}} = \underline{\underline{-1.65 \times 10^9 \text{ V/s}}}$$

(loaded.)


10.17

For problem 10.14, C_c should not be placed "across" M_2 or M_3 because of the location of the poles. Since the dominant pole was at node B, the 2nd pole at node A, and the 3rd pole at node Y, we need to split the 1st two poles by placing C_c across M_1 .

Putting C_c "across" M_2 only splits the 2nd and 3rd pole keeping the dominant pole unchanged. It moves the 2nd pole toward the dominant pole and the 3rd pole away. That cannot give a 60° phase margin.

Putting C_c "across" M_3 only affects the dominant pole and we cannot take advantage of pole-splitting to widen the bandwidth.

10.18

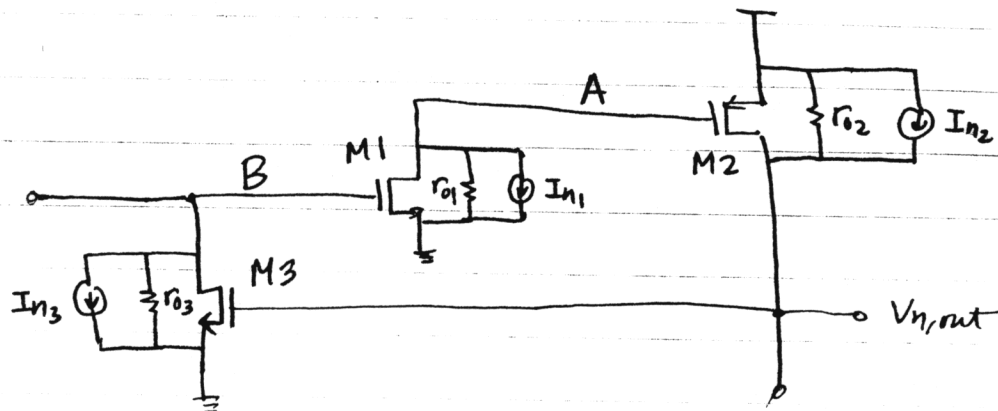

$$V_B = -r_{03}(g_{m3}V_{n,out} + I_{n3})$$


$$V_A = -r_{01}(g_{m1}V_B + I_{n1}) = -r_{01}(-g_{m1}g_{m3}r_{03}V_{n,out} - g_{m1}r_{03}I_{n3} + I_{n1})$$

$$V_{n,out} = -r_{02}(g_{m2}V_A + I_{n2})$$

$$= -r_{02}[I_{n2} + g_{m1}g_{m2}g_{m3}r_{01}r_{03}V_{n,out} + g_{m1}g_{m2}r_{01}r_{03}I_{n3} - g_{m2}r_{01}I_{n1}]$$

$$\overline{V_{n,out}^2} = \frac{\overline{I_{n2}^2} + (g_{m1}g_{m2}r_{01}r_{03})^2 \overline{I_{n3}^2} + (g_{m2}r_{01})^2 \overline{I_{n1}^2}}{(\frac{1}{r_{02}} + g_{m1}g_{m2}g_{m3}r_{01}r_{03})^2}$$

Trans resistance of the circuit is :

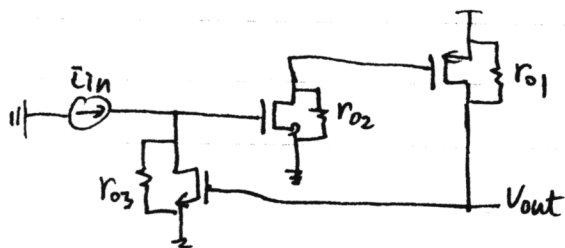

$$\frac{V_{out}}{\bar{i}_{in}} = \frac{1}{g_{m3} + [g_{m1}g_{m2}r_{01}r_{02}r_{03}]^{-1}}$$

$$\star \text{ Input referred noise current: } \underline{\underline{\overline{\bar{i}_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{\left(\frac{V_{out}}{\bar{i}_{in}}\right)^2} = 7.25 \times 10^{-24} \text{ A}^2/\text{Hz}}}}$$

Aside { Since from (10.14) : $g_{m1} = 5.18 \times 10^{-3} \text{ A/V}$, $g_{m2} = 2.77 \times 10^{-3} \text{ A/V}$, $g_{m3} = 1.64 \times 10^{-4} \text{ A/V}$.
 $r_{01} = 10 \text{ k}\Omega$, $r_{02} = 5 \text{ k}\Omega$, $r_{03} = 1 \text{ M}\Omega$.
 $\overline{I_{n2}^2} = 4kT \frac{2}{3} g_{m2} = 3.062 \times 10^{-23} \text{ A}^2/\text{Hz}$, $\overline{I_{n3}^2} = 1.813 \times 10^{-24} \text{ A}^2/\text{Hz}$,
 $\overline{I_{n1}^2} = 5.726 \times 10^{-23} \text{ A}^2/\text{Hz}$.

$$\boxed{10.19} \quad H_{open}(s) = \frac{A_0 \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)} \quad \omega_z \approx \omega_{p2}$$

a)

$$\begin{aligned} H_{closed}(s) &= \frac{A}{1 + A\beta} = \frac{A_0 \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) + A_0 \left(1 + \frac{s}{\omega_z}\right)} \\ &= \frac{A_0 \left(1 + \frac{s}{\omega_z}\right)}{\frac{s^2}{\omega_{p1}\omega_{p2}} + s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \frac{A_0}{\omega_z}\right) + A_0 + 1} \quad \text{Q.E.D.} \end{aligned}$$

$$b) \quad D(s) = \left(1 + \frac{s}{\omega_{pA}}\right) \left(1 + \frac{s}{\omega_{pB}}\right) \approx 1 + \frac{s}{\omega_{pB}} + \frac{s^2}{\omega_{pA}\omega_{pB}} \quad (\omega_{pB} \ll \omega_{pA})$$

$$\omega_{pB} = \frac{A_0 + 1}{\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \frac{A_0}{\omega_z}} //$$

$$\omega_{pA} = (1 + A_0) \omega_{p1} \omega_{p2} \cdot \frac{1}{\omega_{pB}} = \omega_{p2} + \omega_{p1} + \frac{A_0}{\omega_z} \omega_{p1} \omega_{p2} //$$

$$c) \quad \text{Using } \omega_z \approx \omega_{p2}, \omega_{p2} \ll (1 + A_0) \omega_{p1} \text{ or } \frac{1}{\omega_{p1}} \ll \frac{A_0 + 1}{\omega_{p2}}$$

$$\omega_{pB} = \frac{A_0 + 1}{\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \frac{A_0}{\omega_z}} \approx \frac{A_0 + 1}{\frac{1}{\omega_{p1}} + \frac{A_0 + 1}{\omega_{p2}}} \approx \underline{\underline{\omega_{p2}}}$$

$$\omega_{pA} = \omega_{p2} + \omega_{p1} + \frac{A_0}{\omega_z} \omega_{p1} \omega_{p2} \approx \omega_{p2} + (A_0 + 1) \omega_{p1} \approx \underline{\underline{(A_0 + 1) \omega_{p1}}}$$

$$H_{closed}(s) \approx \frac{\frac{A_0}{A_0 + 1} \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{(A_0 + 1) \omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)} //$$

10.19 d) Step response: $Y(s)$

$$\begin{aligned}
 Y(s) &= \frac{1}{s} \frac{A(1 + \frac{s}{\omega_z})}{(1 + \frac{s}{\omega_{PA}})(1 + \frac{s}{\omega_{PB}})} & A &= \frac{A_0}{1+A_0}, \quad \omega_{PA} = (1+A_0)\omega_{P1}, \\
 & & & \omega_{PB} = \omega_{P2}. \\
 &= \frac{K_1}{s} + \frac{K_2}{(1 + \frac{s}{\omega_{PA}})} + \frac{K_3}{(1 + \frac{s}{\omega_{PB}})} \\
 &= \frac{s^2 \left(\frac{K_1}{\omega_{PA}\omega_{PB}} + \frac{K_2}{\omega_{PB}} + \frac{K_3}{\omega_{PA}} \right) + s \left(\frac{K_1}{\omega_{PA}} + \frac{K_1}{\omega_{PB}} + K_2 + K_3 \right) + K_1}{s \left(1 + \frac{s}{\omega_{PA}} \right) \left(1 + \frac{s}{\omega_{PB}} \right)}
 \end{aligned}$$

$$\boxed{K_1 = A}$$

$$\frac{A}{\omega_{PA}} + \frac{A}{\omega_{PB}} + K_2 + K_3 = \frac{A}{\omega_z} \longrightarrow K_2 + K_3 = A \left(\frac{1}{\omega_z} - \frac{1}{\omega_{PA}} - \frac{1}{\omega_{PB}} \right) \quad \dots (1)$$

$$\frac{A}{\omega_{PA}\omega_{PB}} + \frac{K_2}{\omega_{PB}} + \frac{K_3}{\omega_{PA}} = 0 \longrightarrow \omega_{PA}K_2 + \omega_{PB}K_3 = -A \quad \dots (2)$$

$$\begin{aligned}
 - (1) \times \omega_{PA} + (2) &\longrightarrow - \left[\omega_{PA}K_2 + \omega_{PA}K_3 = A \left(\frac{\omega_{PA}}{\omega_z} - 1 - \frac{\omega_{PA}}{\omega_{PB}} \right) \right] \\
 &+ \omega_{PA}K_2 + \omega_{PB}K_3 = -A \\
 \hline
 K_3(\omega_{PB} - \omega_{PA}) &= A \left(\frac{\omega_{PA}}{\omega_{PB}} - \frac{\omega_{PA}}{\omega_z} \right)
 \end{aligned}$$

$$K_3 = \frac{A \left(\frac{\omega_{PA}}{\omega_{PB}} - \frac{\omega_{PA}}{\omega_z} \right)}{\omega_{PB} - \omega_{PA}}$$

Plug back into (2) to get K_2 :

$$\omega_{PA}K_2 + \omega_{PB} \left[\frac{A \omega_{PA} \left(\frac{1}{\omega_{PB}} - \frac{1}{\omega_z} \right)}{\omega_{PB} - \omega_{PA}} \right] = -A$$

$$\omega_{PA}K_2 = -A \left[1 + \frac{\omega_{PA} - \frac{\omega_{PA}\omega_{PB}}{\omega_z}}{\omega_{PB} - \omega_{PA}} \right] = -A \cdot \frac{\omega_{PB} - \frac{\omega_{PA}\omega_{PB}}{\omega_z}}{\omega_{PB} - \omega_{PA}}$$

$$K_2 = -A \frac{\omega_{PB} \left(1 - \frac{\omega_{PA}}{\omega_z} \right)}{\omega_{PA}(\omega_{PB} - \omega_{PA})}$$

10.19d) (cont)

can simplify:

$$K_3 = \frac{A W_P A \left(\frac{1}{W_{PB}} - \frac{1}{W_Z} \right)}{W_{PB} - W_P A} \cong \frac{\frac{A_0}{A_0+1} (A_0+1) W_{P1} \left(\frac{1}{W_{P2}} - \frac{1}{W_Z} \right)}{W_{P2} - (A_0+1) W_{P1}}$$

$$\cong \underline{\underline{-\frac{A_0}{A_0+1} \left(\frac{1}{W_{P2}} - \frac{1}{W_{P2}} \right) = K_3}}$$

$$K_2 = -A \frac{W_{P2} \left(1 - \frac{(A_0+1) W_{P1}}{W_Z} \right)}{(A_0+1) W_{P1} (W_{P2} - (A_0+1) W_{P1})} \cong \frac{-\frac{A_0}{A_0+1} \frac{-(A_0+1) W_{P1}}{-(A_0+1)^2 W_{P1}^2}}{\cong \underline{\underline{\frac{-A_0}{(A_0+1)^2 W_{P1}} = K_2}}}$$

$$Y(s) = \frac{A}{s} + \frac{\frac{A_0}{(A_0+1)^2 W_{P1}} \cdot W_{P1}}{W_{P1} + s} + \frac{-\frac{A_0}{A_0+1} \left(\frac{1}{W_{P2}} - \frac{1}{W_Z} \right) \cdot W_{PB}}{s + W_{PB}}$$

$$\cong \frac{A}{s} + \frac{-\frac{A_0}{A_0+1}}{s + (A_0+1) W_{P1}} + \frac{-\frac{A_0}{A_0+1} \left(1 - \frac{W_{P2}}{W_Z} \right)}{s + W_{P2}}$$

$$\star y(t) = \frac{A_0}{1+A_0} \left[1 - \left(1 - \frac{W_{P2}}{W_Z} \right) e^{-W_{P2}t} - e^{-(A_0+1)W_{P1}t} \right] u(t)$$

= small signal step response.

$$\star y(t) \cong \frac{A_0}{1+A_0} \left[1 - \left(1 - \frac{W_{P2}}{W_Z} \right) e^{-W_{P2}t} \right] u(t) \text{ since } (1+A_0)W_{P1} \gg W_{P2}.$$

Hence if W_Z and W_{P2} do not exactly cancel, there is an exponential term $\left(1 - \frac{W_{P2}}{W_Z} \right) e^{-W_{P2}t}$ with a time constant $\frac{1}{W_{P2}} \approx \frac{1}{W_Z}$. Q.E.D.


10.20

a) Perfect pole-zero cancellation.

Then

$$y(t) \cong \frac{A_0}{1+A_0} [1 - 0 - e^{-\omega_{p1}(A_0+1)t}] u(t)$$

$$\cong \frac{A_0}{1+A_0} u(t)$$

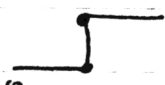$\Rightarrow$ Step. 

b) 10% mismatch.

$$y(t) \cong \frac{A_0}{1+A_0} [1 - 0.9 e^{-\omega_{p2}t}] u(t)$$

$\Rightarrow$  $\tau = \frac{1}{\omega_{p2}}$