
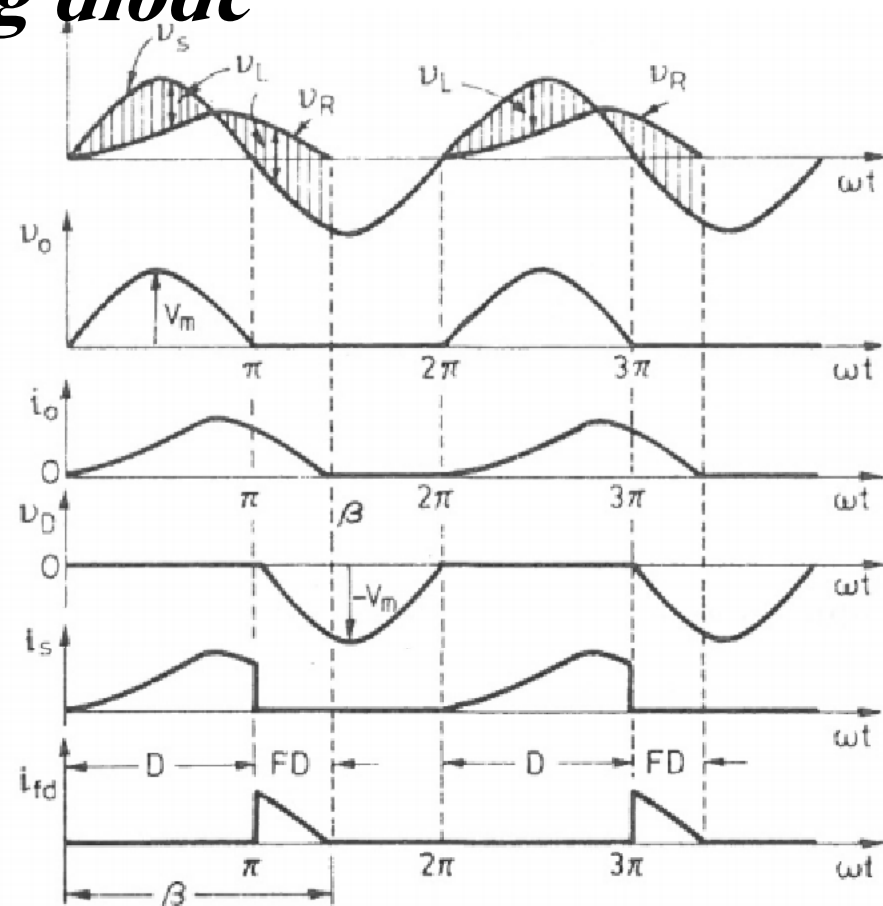


RL Load with freewheeling diode

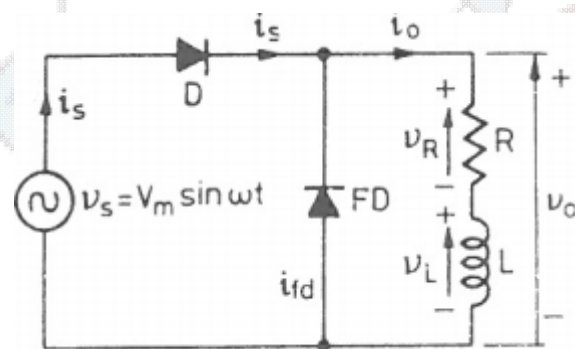

Output voltage is $v_o = v_s$ for $0 \leq \omega t \leq \pi$. At $\omega t = \pi$, source voltage v_s is zero, but output current i_o is not zero because of L in the load circuit. Just after $\omega t = \pi$, as v_s tends to reverse, negative polarity of v_s reaches cathode of FD through conducting diode D , whereas positive polarity of v_s reaches anode of FD direct. Freewheeling (or flywheel) diode FD , therefore, gets forward-biased. As a result, load current i_o is immediately transferred from D to FD as v_s tends to reverse. After $\omega t = \pi$, diode current $i_s = 0$ and it is subjected to reverse voltage with PIV equal to V_m .

After $\omega t = \pi$, current freewheels through circuit RL and FD. The energy stored in L is now dissipated in R . When energy stored in $L =$ energy dissipated in R , current falls to zero at $\omega t = \beta < 2\pi$. Depending upon the value of R and L , the current may not fall to zero even when $\omega t = 2\pi$, this is called continuous conduction. load current decays to zero before $\omega t = 2\pi$; load current is therefore discontinuous.

The effects of using freewheeling diode are as under :

- (i) It prevents the output (or load) voltage from becoming negative.
- (ii) As the energy stored in L is transferred to load R through FD , the system efficiency is improved.
- (iii) The load current waveform is more smooth, the load performance is therefore improved.

average output voltage,

$$V_0 = \frac{1}{2\pi} \int_0^\pi V_m \sin \omega t d(\omega t) = \frac{V_m}{\pi}$$

and average load current,

$$I_0 = \frac{V_m}{\pi R}$$

Power Electronic by M. H. Rashid

The effect of this diode is to prevent a negative voltage appearing across the load; and as a result, the magnetic stored energy is increased. At $t = t_1 = \pi/\omega$, the current from D_1 is transferred to D_m and this process is called *commutation of diodes*.

Depending on the load time constant, the load current may be discontinuous. Load current i_0 is discontinuous with a resistive load and continuous with a very high inductive load. The continuity of the load current depends on its time constant $\tau = \omega L/R$.

The performance of a half-wave rectifier that is measured by certain parameters is poor. The load current can be made continuous by adding an inductor and a freewheeling diode. The output voltage is discontinuous and contains harmonics at multiples of the supply frequency.

Example Finding the Fourier Series of the Output Voltage for a Half-Wave Rectifier

The single-phase half-wave rectifier of Figure is connected to a source of $V_s = 120 \text{ V}$, 60 Hz. Express the instantaneous output voltage $v_o(t)$ in Fourier series.

Solution

The rectifier output voltage v_o may be described by a Fourier series as

$$v_o(t) = V_{dc} + \sum_{n=1,2,\dots}^{\infty} (a_n \sin n\omega t + b_n \cos n\omega t)$$

$$V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} v_o d(\omega t) = \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t) = \frac{V_m}{\pi}$$

$$a_n = \frac{1}{\pi} \int_0^{2\pi} v_o \sin n\omega t d(\omega t) = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \sin n\omega t d(\omega t)$$

$$= \frac{V_m}{2} \quad \text{for } n = 1$$

$$= 0 \quad \text{for } n = 2, 3, 4, 5, 6, \dots$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} v_o \cos n\omega t d(\omega t) = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \cos n\omega t d(\omega t)$$



$$= \frac{V_m}{\pi} \frac{1 + (-1)^n}{1 - n^2} \quad \text{for } n = 2, 4, 6, \dots$$

$$= 0 \quad \text{for } n = 1, 3, 5, \dots$$

Substituting a_n and b_n , the instantaneous output voltage becomes


$$v_o(t) = \frac{V_m}{\pi} + \frac{V_m}{2} \sin \omega t - \frac{2V_m}{3\pi} \cos 2\omega t - \frac{2V_m}{15\pi} \cos 4\omega t - \frac{2V_m}{35\pi} \cos 6\omega t - \dots$$

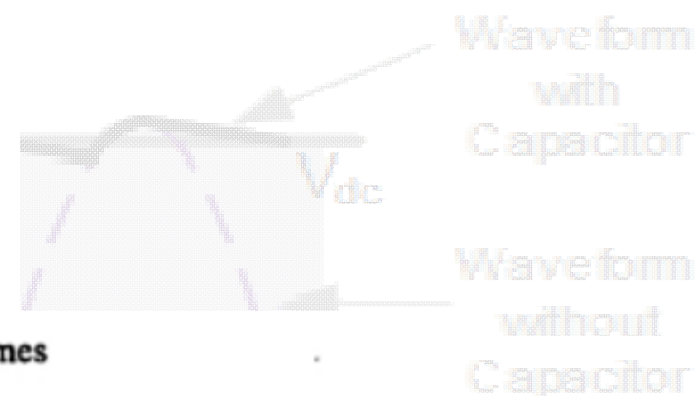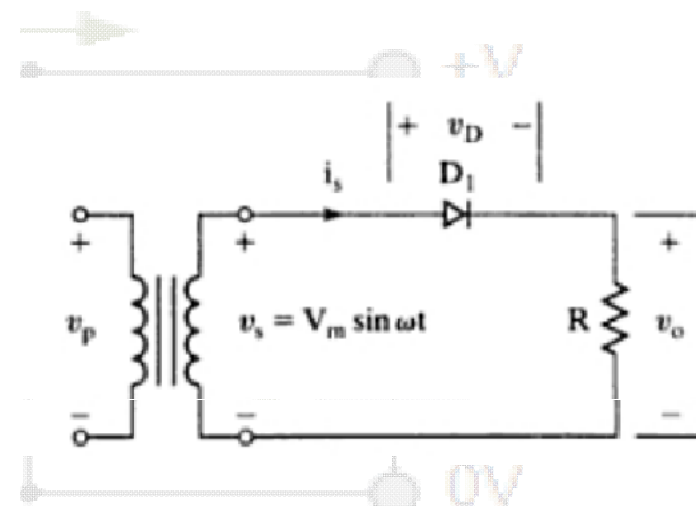where $V_m = \sqrt{2} \times 120 = 169.7 \text{ V}$ and $\omega = 2\pi \times 60 = 377 \text{ rad/s}$.





Single Phase Full Wave Diode Rectifiers

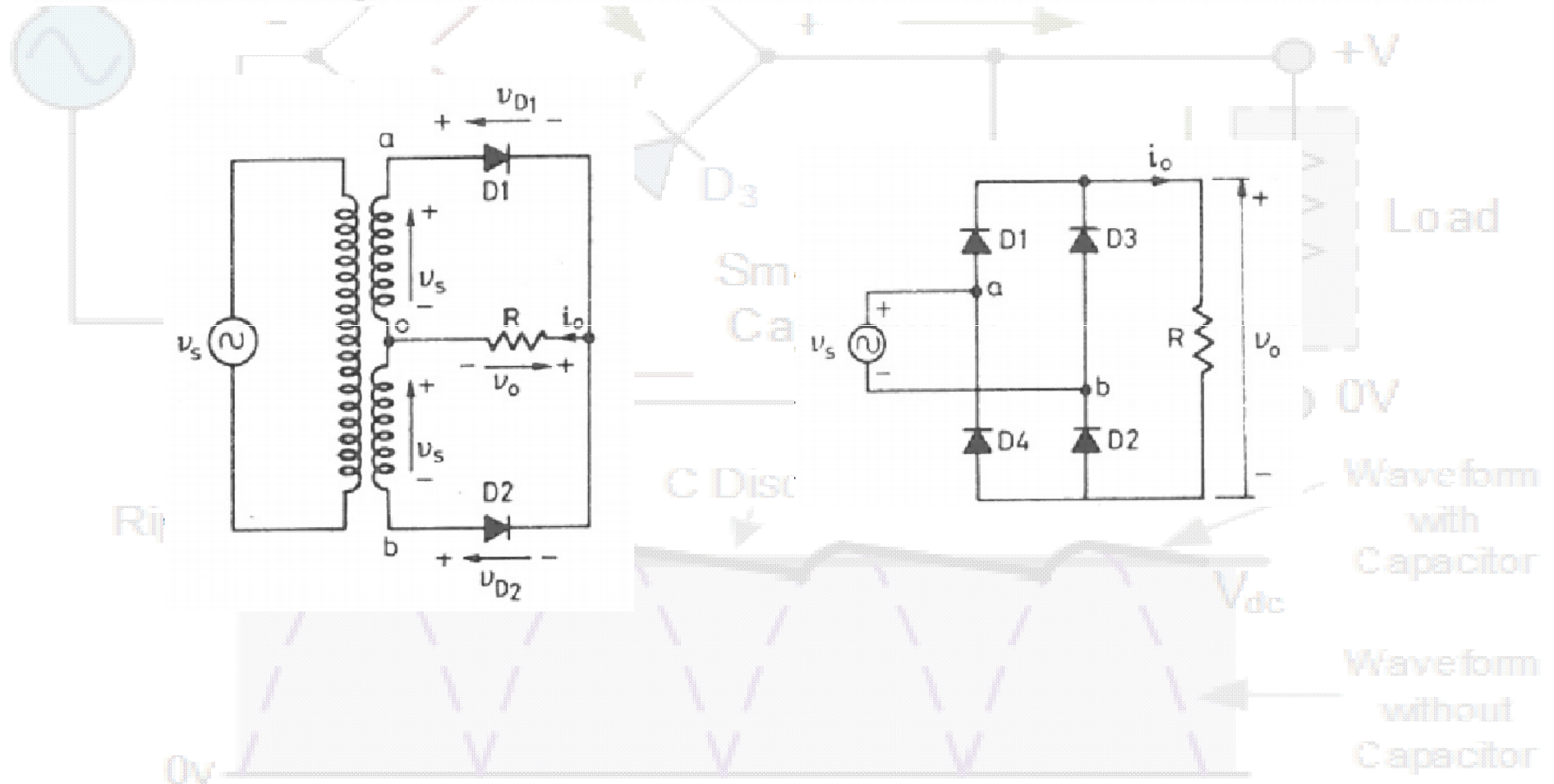There are two types of full-wave diode rectifiers, one is centre-tapped (or mid-point) full-wave diode rectifier and the other is full-wave diode bridge rectifier. These are now described briefly.



Resultant Output Waveform

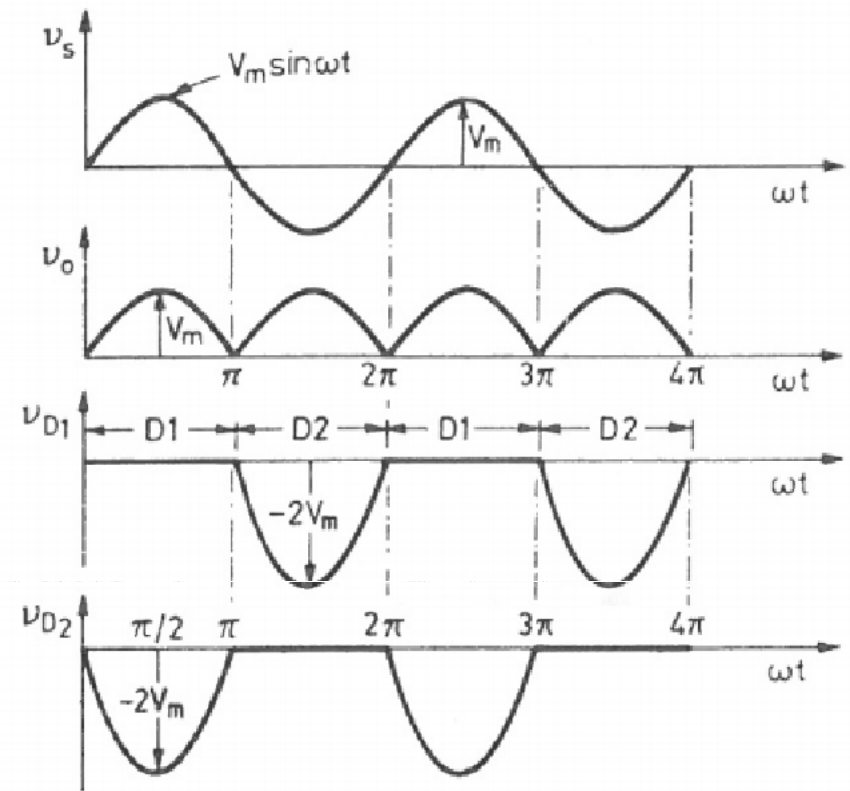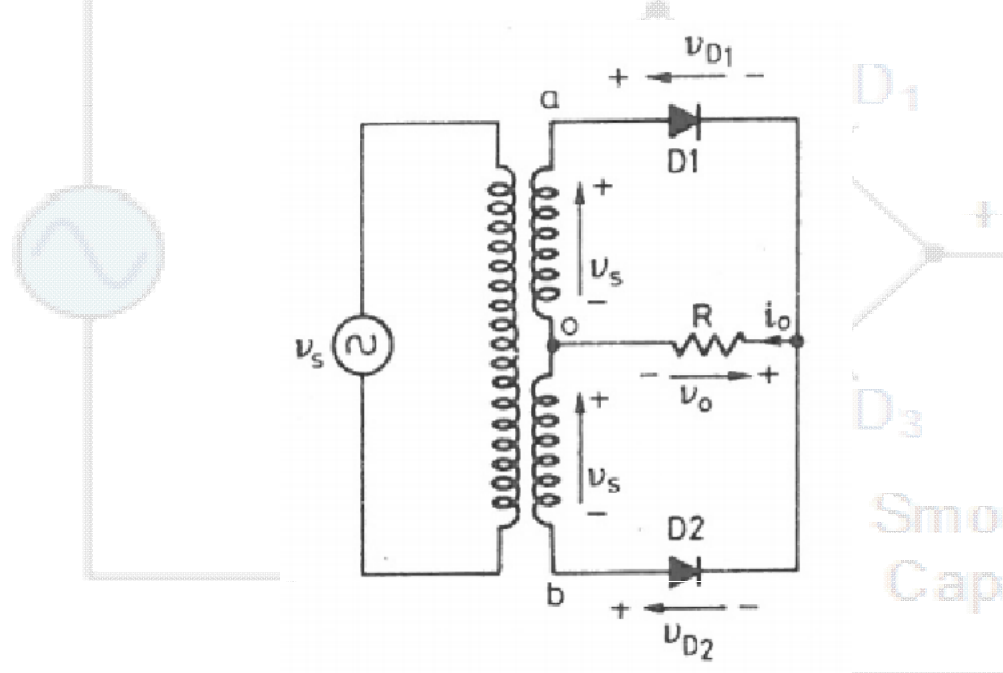Single Phase Full Wave mid point Diode Rectifiers



Each half of the transformer with its associated diode acts as a half-wave rectifier

The turns ratio from each secondary to primary is taken as unity for simplicity. When 'a' is positive with respect to 'b'; diode D1 conducts for π radians. In the next half cycle, 'b' is positive with respect to 'a' and therefore diode D2 conducts.

Resultant Output Waveform

The waveform for output current i_o (not shown in the figure) is similar to v_o waveform. When 'a' is positive with respect to 'b', diode D2 is subjected to a reverse voltage of $2v_s$. In the next half cycle, diode D1 experiences a reverse voltage of $2v_s$. Thus, for diodes

D1 and D2, peak inverse voltage is $2V_m$.

for one cycle

of source voltage, there are two pulses of output voltage. So single-phase full-wave diode rectifier can also be called *single-phase two-pulse* diode rectifier.


Average output voltage

$$V_0 = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t) = \frac{2V_m}{\pi}$$

Average output current, $I_0 = \frac{V_0}{R}$

Rms value of output voltage,
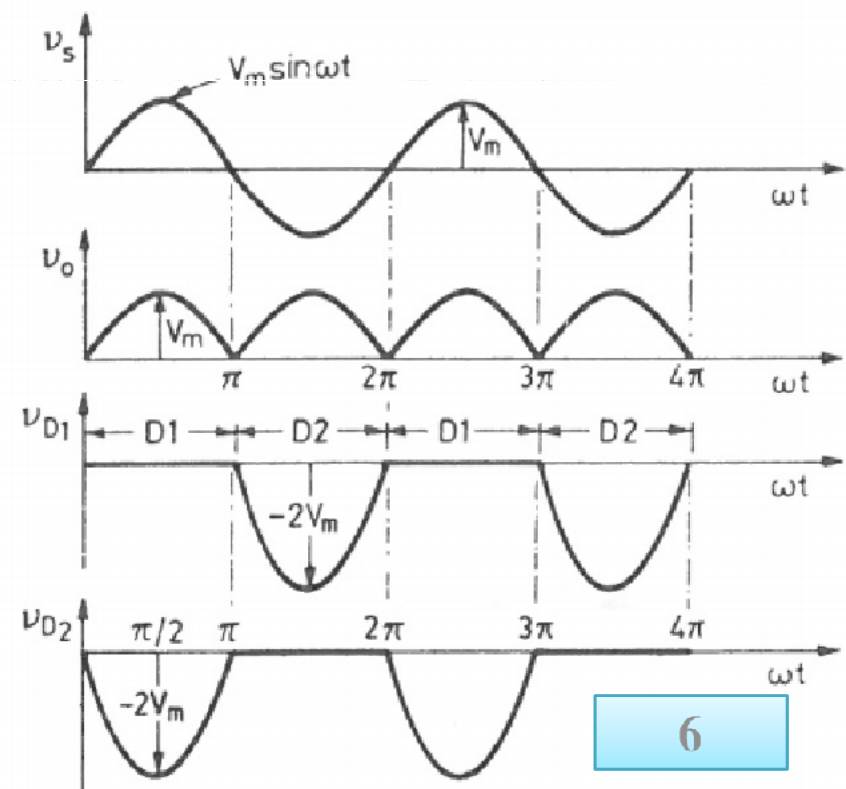
$$V_{or} = \left[\frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t d(\omega t) \right]^{1/2} \\ = \frac{V_m}{\sqrt{2}} = V_s$$



Bridge

Rms value of load current,

$$I_{or} = \frac{V_s}{R}$$

Power delivered to load



$$= V_{or} \cdot I_{or} = I_{or}^2 \cdot R$$

Input voltamperes

$$= V_s \cdot I_{or}$$



∴ Input
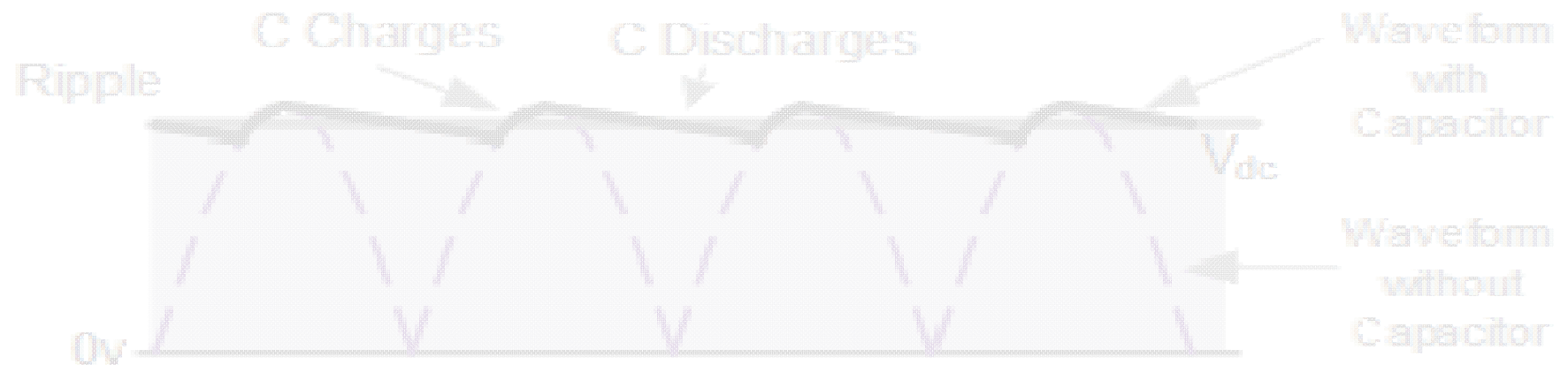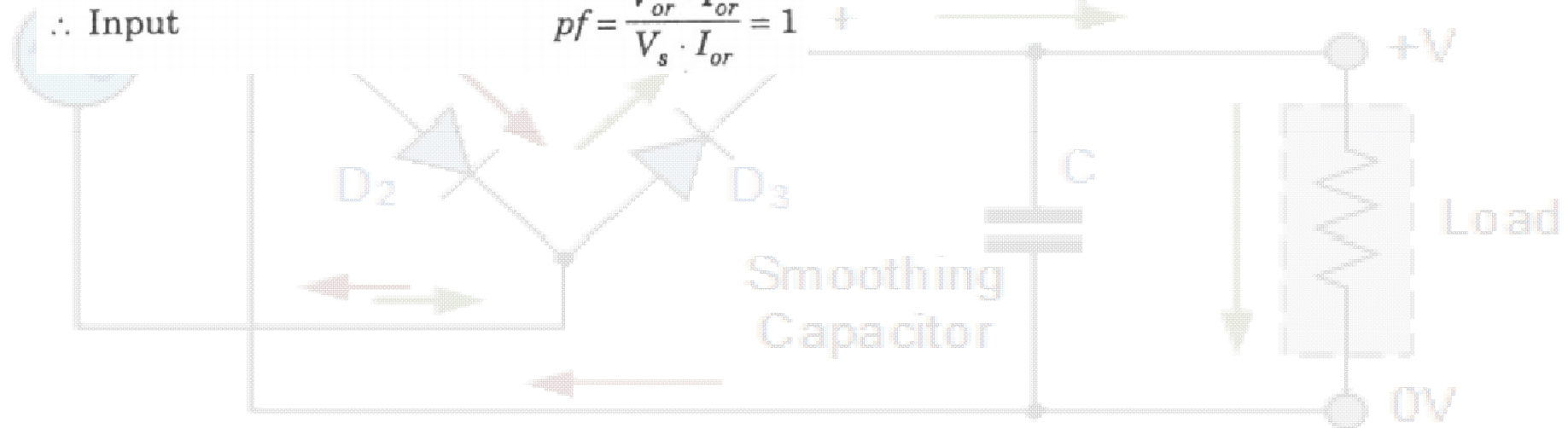
$$pf = \frac{V_{or} \cdot I_{or}}{V_s \cdot I_{or}} = 1$$



Resultant Output Waveform

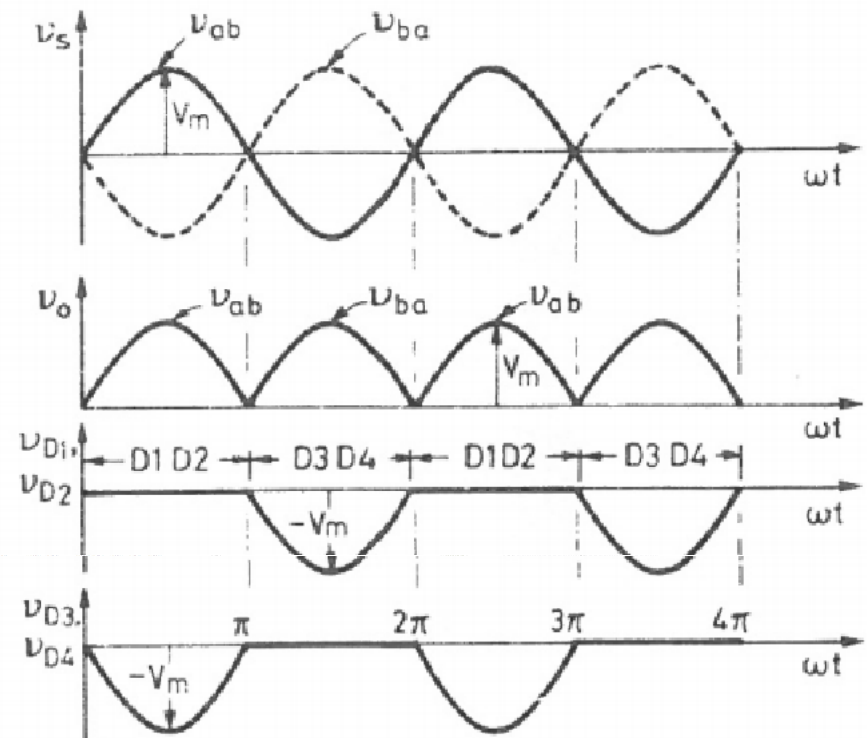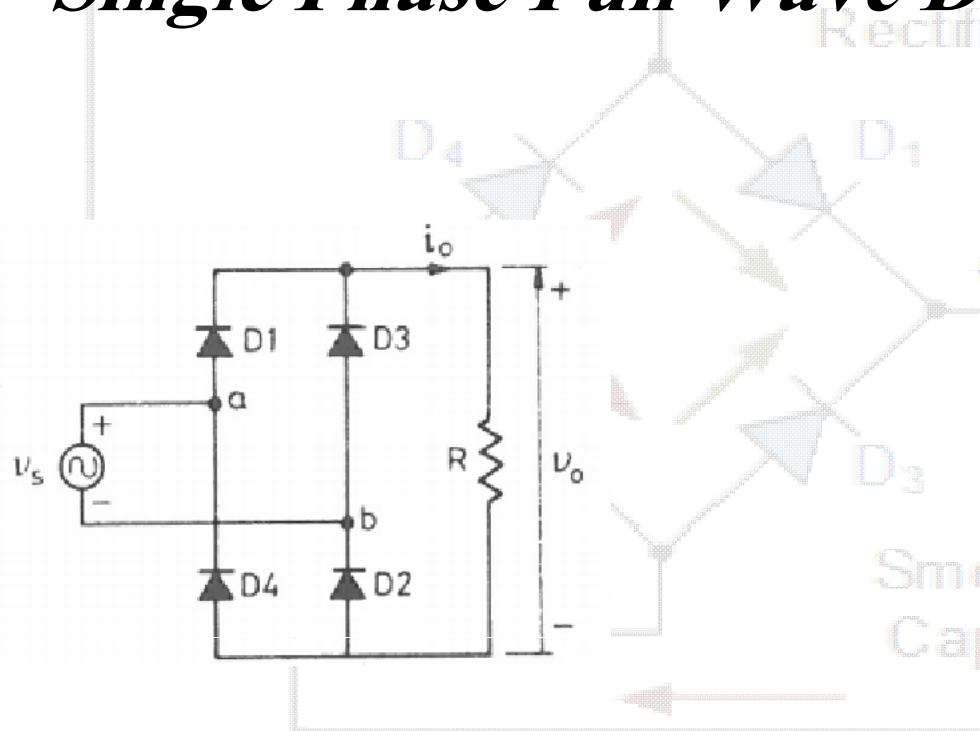Single Phase Full Wave Diode Bridge Rectifiers



When 'a' is positive with respect to 'b', diodes D1, D2 conduct together so that output voltage is v_{ab} . Each of the diodes D3 and D4 is subjected to a reverse voltage of v_s . When 'b' is positive with respect to 'a', diodes D3, D4 conduct together and output voltage is v_{ba} . Each of the two diodes D1 and D2 experience a reverse voltage of v_s as shown.

a diode in mid-point full-wave rectifier is subjected to PIV of $2V_m$ whereas a diode in full-wave bridge rectifier has PIV of V_m only.

Example In a single-phase full-wave diode bridge rectifier, the diodes have a reverse recovery time of $40 \mu\text{s}$. For an ac input voltage of 230 V , determine the effect of reverse recovery time on the average output voltage for a supply frequency of (a) 50 Hz and (b) 2.5 kHz .

If reverse recovery time is taken into consideration, the diodes D1 and D2 will not be off at $\omega t = \pi$, but will continue to conduct until $t = \frac{\pi}{\omega} + t_{rr}$

The reduction in output voltage is given by the cross-hatched area. Average value of this reduction in output voltage is given by

$$V_r = \frac{1}{\pi} \int_0^{t_{rr}} V_m \sin \omega t d(\omega t)$$


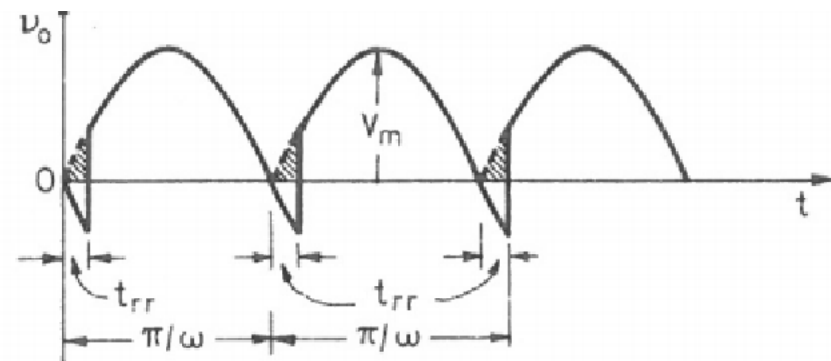


Fig. 3.20. Effect of reverse recovery time on output voltage.

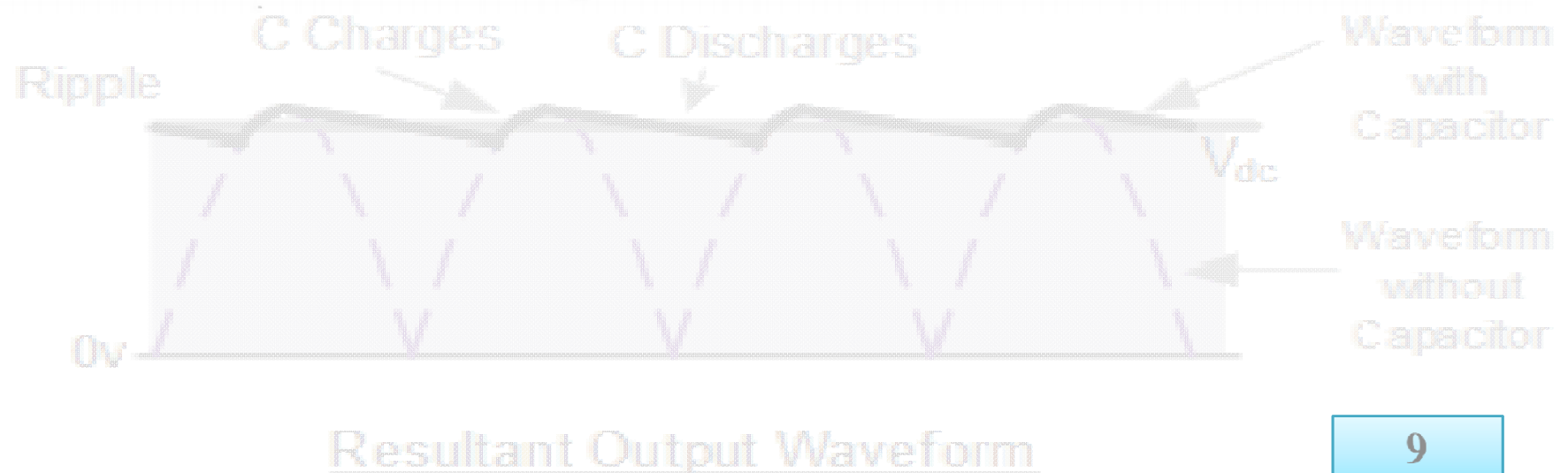

$$= \frac{V_m}{\pi} (1 - \cos \omega t_{rr})$$

With zero reverse recovery time, average output voltage,

is

$$V_0 = \frac{2\sqrt{2} \times 230}{\pi} = 207.04 \text{ V}$$

(a) For $f = 50 \text{ Hz}$ and $t_{rr} = 40 \mu\text{s}$, the reduction in the average output voltage, is

$$\begin{aligned} V_r &= \frac{V_m}{\pi} (1 - \cos 2\pi f t_{rr}) \\ &= \frac{\sqrt{2} \times 230}{\pi} \left(1 - \cos 2\pi \times 50 \times 40 \times 10^{-6} \times \frac{180}{\pi} \right) \\ &= 8.174 \text{ mV} \end{aligned}$$

Percentage reduction in average output voltage

$$= \frac{8.174 \times 10^{-3}}{207.04} \times 100 = 3.948 \times 10^{-3} \%$$

(b) For $f = 2500 \text{ Hz}$, the reduction in the average output voltage,

is



$$\begin{aligned} V_r &= \frac{\sqrt{2} \times 230}{\pi} \left(1 - \cos 2\pi \times 2500 \times 40 \times 10^{-6} \times \frac{180}{\pi} \right) \\ &= 19.77 \text{ V} \end{aligned}$$

Percentage reduction in average output voltage = $\frac{19.77}{207.04} \times 100 = 9.594\%$.

It is seen from above that the effect of reverse recovery time is negligible for diode operation at 50 Hz, but for high-frequency operation of diodes, the effect is noticeable.

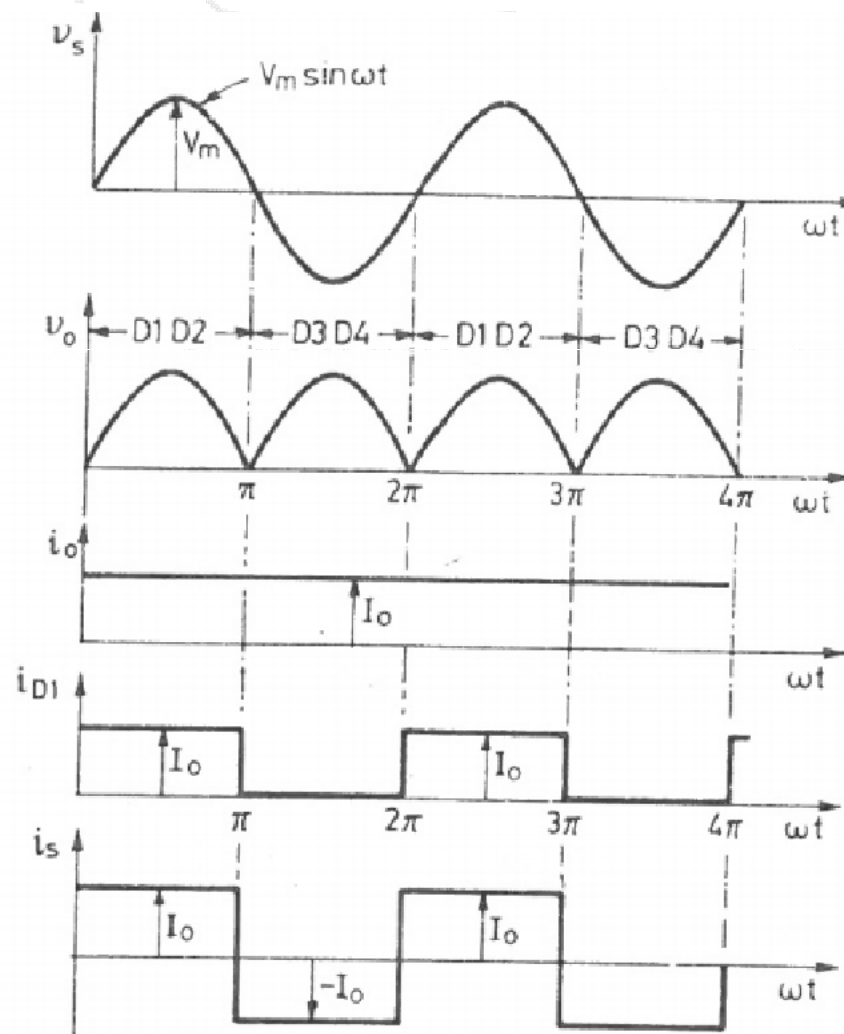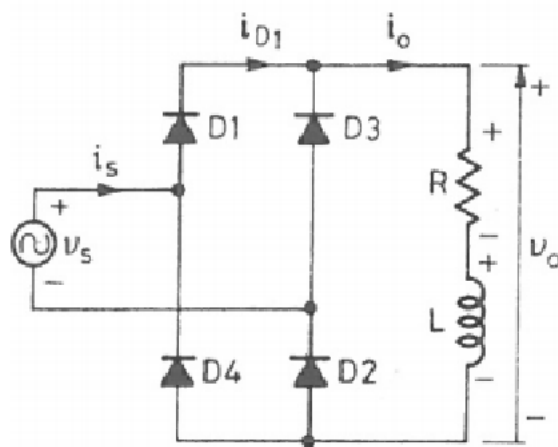Example A single-phase full bridge diode rectifier is supplied from 230 V, 50 Hz source. The load consists of $R = 10 \Omega$ and a large inductance so as to render the load current constant. Determine

- average values of output voltage and output current,
- average and rms values of diode currents,
- rms values of output and input currents, and supply pf.



Load

Wave form

with
Capacitor

Wave form
without
Capacitor

(a) Average value of output voltage,

$$V_0 = \frac{2V_m}{\pi} = \frac{2\sqrt{2} \times 230}{\pi} = 207.04 \text{ V}$$

Average value of output current,

$$I_0 = \frac{V_0}{R} = \frac{207.04}{10} = 20.704 \text{ A}$$

(b) Average value of diode current,

$$I_{DAV} = \frac{I_0 \cdot \pi}{2\pi} = \frac{I_0}{2} = \frac{20.704}{2} = 10.352 \text{ A}$$

Rms value of diode current, $I_{Dr} = \sqrt{\frac{I_0^2 \pi}{2\pi}} = \frac{I_0}{\sqrt{2}} = \frac{20.704}{\sqrt{2}} = 14.642 \text{ A}$

As load, or output, current is ripple free, rms value of output current

= average value of output current = $I_0 = 20.704 \text{ A}$

Rms value of source current, $I_s = \sqrt{\frac{I_0^2 \pi}{\pi}} = I_0 = 20.704 \text{ A}$

Load power = $V_0 I_0 = 207.04 \times 20.704 \text{ W}$

Input power = $V_s I_s \cos \phi$

$$\therefore 230 \times 20.704 \times \cos \phi = 207.04 \times 20.704$$

$$\therefore \text{Supply pf} = \cos \phi = \frac{207.04}{230} = 0.90 \text{ lagging.}$$

Resultant Output Waveform

Example Finding the Fourier Series of the Output Voltage for a Full-Wave Rectifier

The rectifier in Figure 3.5a has an RL load. Use the method of Fourier series to obtain expressions for output voltage $v_0(t)$.

Solution

The rectifier output voltage may be described by a Fourier series (which is reviewed in Appendix E) as

$$v_0(t) = V_{dc} + \sum_{n=2,4,\dots}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

$$V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} v_0(t) d(\omega t) = \frac{2}{2\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t) = \frac{2V_m}{\pi}$$

$$a_n = \frac{1}{\pi} \int_0^{2\pi} v_0 \cos n\omega t d(\omega t) = \frac{2}{\pi} \int_0^{\pi} V_m \sin \omega t \cos n\omega t d(\omega t)$$

$$= \frac{4V_m}{\pi} \sum_{n=2,4,\dots}^{\infty} \frac{-1}{(n-1)(n+1)} \quad \text{for } n = 2, 4, 6, \dots$$

$$= 0 \quad \text{for } n = 1, 3, 5, \dots$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} v_0 \sin n\omega t d(\omega t) = \frac{2}{\pi} \int_0^{\pi} V_m \sin \omega t \sin n\omega t d(\omega t) = 0$$

Substituting the values of a_n and b_n , the expression for the output voltage is

$$v_0(t) = \frac{2V_m}{\pi} - \frac{4V_m}{3\pi} \cos 2\omega t - \frac{4V_m}{15\pi} \cos 4\omega t - \frac{4V_m}{35\pi} \cos 6\omega t - \dots$$

0V



Resultant Output Waveform