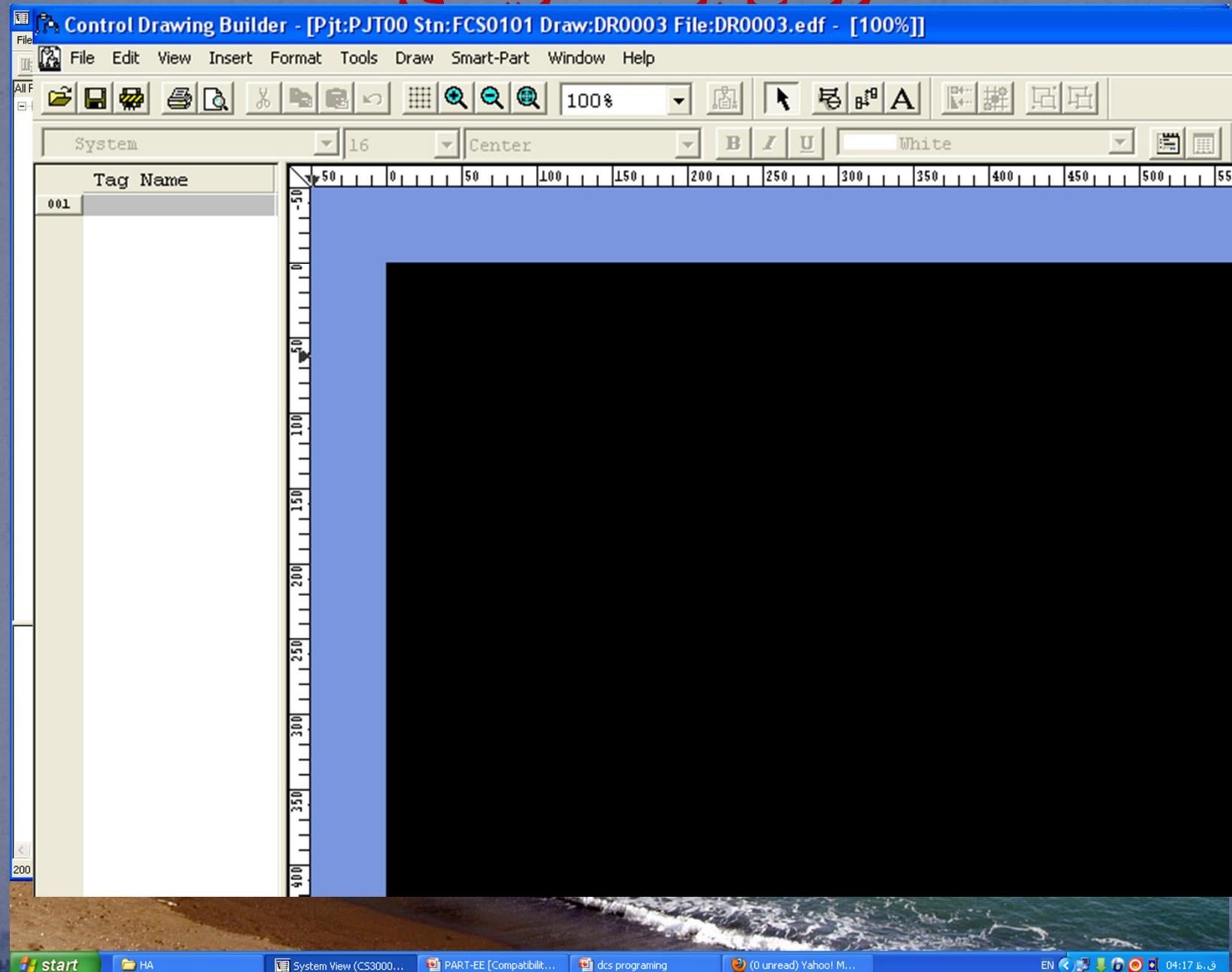


Yokogawa cs3000 Programming

ارائه دهنده: مهندس حمید کتیرائی

روش، برنامه نویسی،




Logic Chart Block (LC64)

فضائی است که در آن لاجیک سیستم کنترلی نوشته می شود، دارای ۳۲ ورودی و ۳۲ خروجی و دارای ۶۴ گیت است

سوئیچها در سیستم CS3000 به دو دسته تقسیم می شود که عبارتند از:

۱ - سوئیچ های نرم افزاری: در صورتی که بخواهیم در اتاق کنترل فرمان start,stop بدهیم از این سوئیچها استفاده می شود

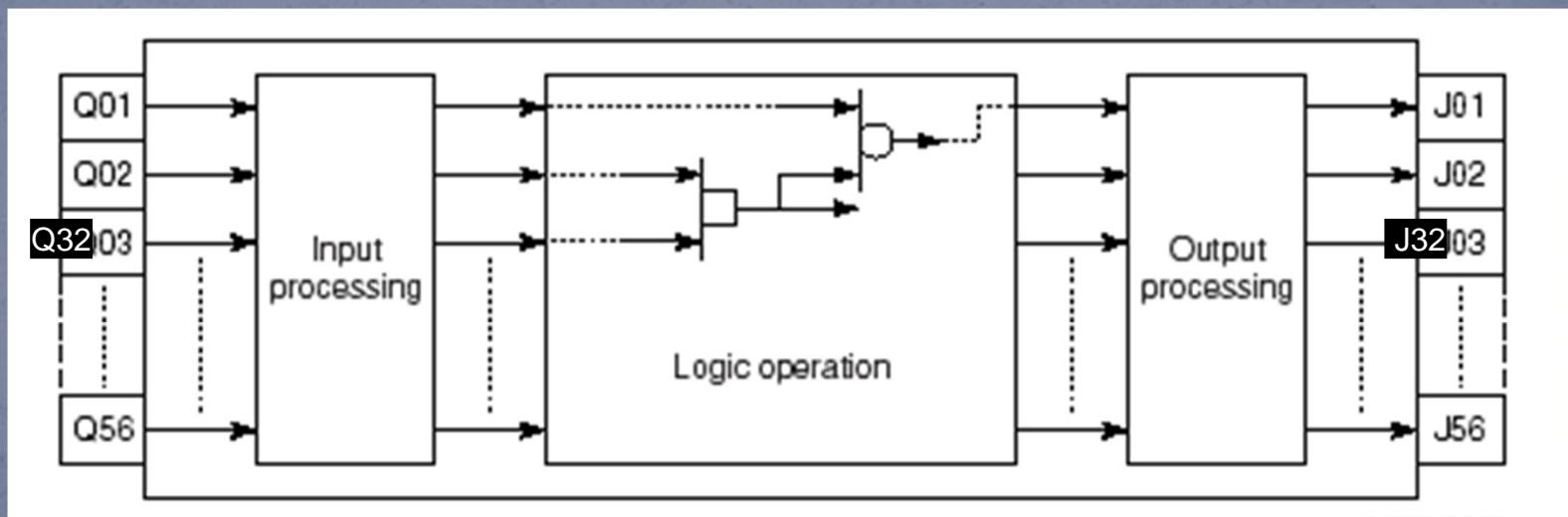۲ - سوئیچهای سخت افزاری: در صورتی که بخواهیم در سایت فرمان start,stop بدهیم از این سوئیچها استفاده می شود



A logic chart block LC64 has 32 inputs, 32 outputs and 64 logic elements.

سوئیچ های نرم افزاری به دو دسته تقسیم می شود که عبارتند از:


-1 **Global Switch**: تعداد آنها 256 تا است، سوئیچ هایی که در همه FCS استفاده می شود در یک FCS تعریف ولي در همه آنها استفاده می شود

-2 **Common Switch**: تعداد آنها 4000 تا است و سوئیچ هایی است که در هر FCS تعریف شود در همان FCS استفاده می شود

-جهت تعریف سوئیچها نرم افزاری از قسمت Switch استفاده می شود

-در قسمت Switch Def 200 تا 400 سوئیچ مخصوص خود سیستم است و نباید استفاده شود

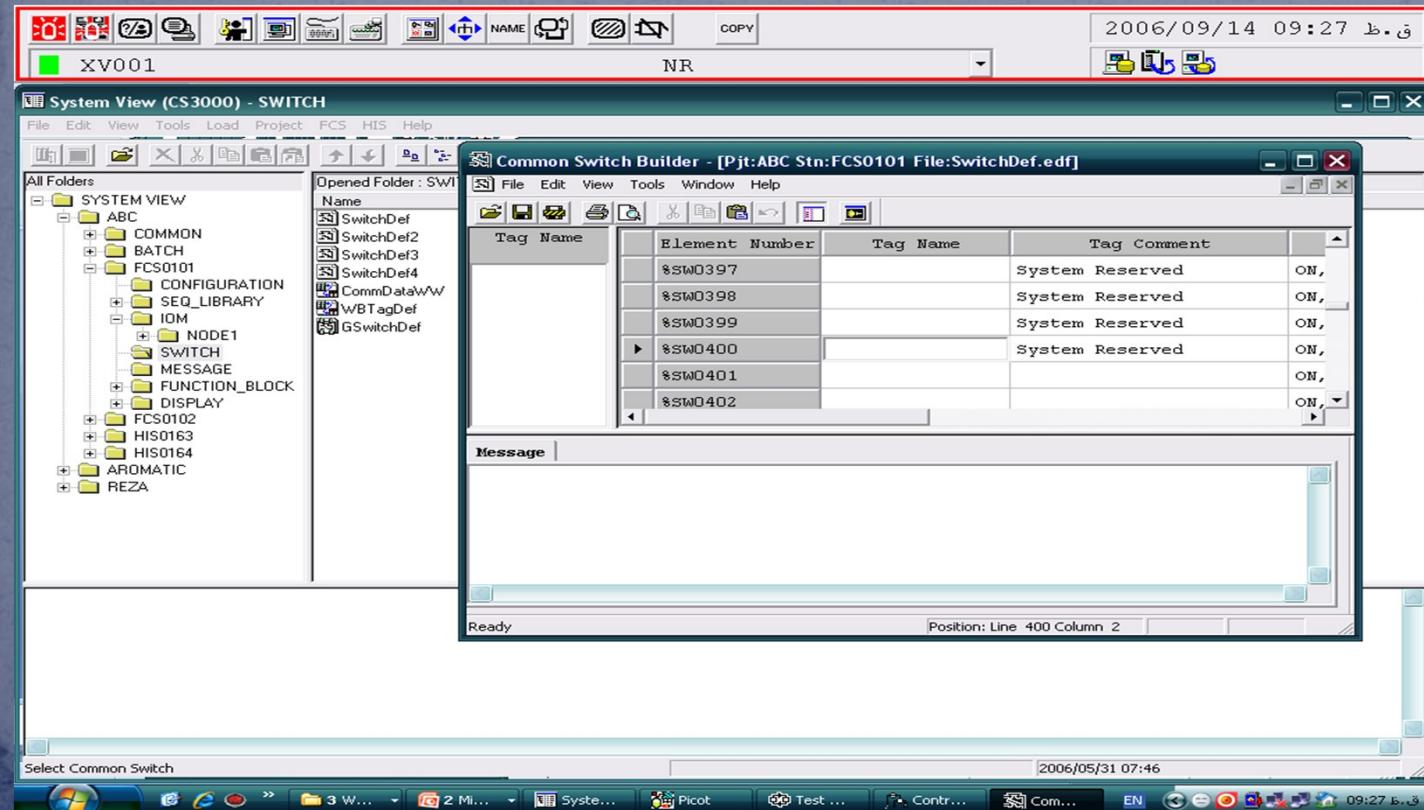
-Gswitch Def ها را در قسمت Global Switch تعریف می شود



Global Switch Builder - [Pjt:ABC Stn:FCS0101 File:GSwitchDef.edf]

Element Number	Tag Name	Tag Comment	Switch Position Label	Label	Btn1	Btn2	Lvl	Tag M
...			ON,,OFF,ON	Direct	Red	Red	4	General
ON,,OFF,ON								
RUN,,STOP,RU								
OPEN,,CLOSE,								
HIGH,MIDDLE,								
RIGHT,MIDDLE								
DIRECT,STOP,								
START,HOLD,S								
3,2,1,0								
STOP,PAUSE,S								
UP,,DOWN,UP								
RUN,PAUSE,ST								
START,PAUSE,								
LSH001			OPEN,,CLOSE,OPEN	Direct	Red	Red	4	General
%GS001			ON,,OFF,ON	Direct	Red	Red	4	General
%GS002	LSH001		OPEN,,CLOSE,OPEN	Direct	Red	Red	4	General
%GS003			ON,,OFF,ON	Direct	Red	Red	4	General
%GS004			ON,,OFF,ON	Direct	Red	Red	4	General
%GS005			ON,,OFF,ON	Direct	Red	Red	4	General
%GS006			ON,,OFF,ON	Direct	Red	Red	4	General
%GS007			ON,,OFF,ON	Direct	Red	Red	4	General
%GS008			ON,,OFF,ON	Direct	Red	Red	4	General
%GS009			ON,,OFF,ON	Direct	Red	Red	4	General
%GS010			ON,,OFF,ON	Direct	Red	Red	4	General
%GS011			ON,,OFF,ON	Direct	Red	Red	4	General
%GS012			ON,,OFF,ON	Direct	Red	Red	4	General
%GS013			ON,,OFF,ON	Direct	Red	Red	4	General
%GS014			ON,,OFF,ON	Direct	Red	Red	4	General
%GS015			ON,,OFF,ON	Direct	Red	Red	4	General
%GS016			ON,,OFF,ON	Direct	Red	Red	4	General
%GS017			ON,,OFF,ON	Direct	Red	Red	4	General
%GS018			ON,,OFF,ON	Direct	Red	Red	4	General
%GS019			ON,,OFF,ON	Direct	Red	Red	4	General
%GS020			ON,,OFF,ON	Direct	Red	Red	4	General
%GS021			ON,,OFF,ON	Direct	Red	Red	4	General


برنامه های Sequence

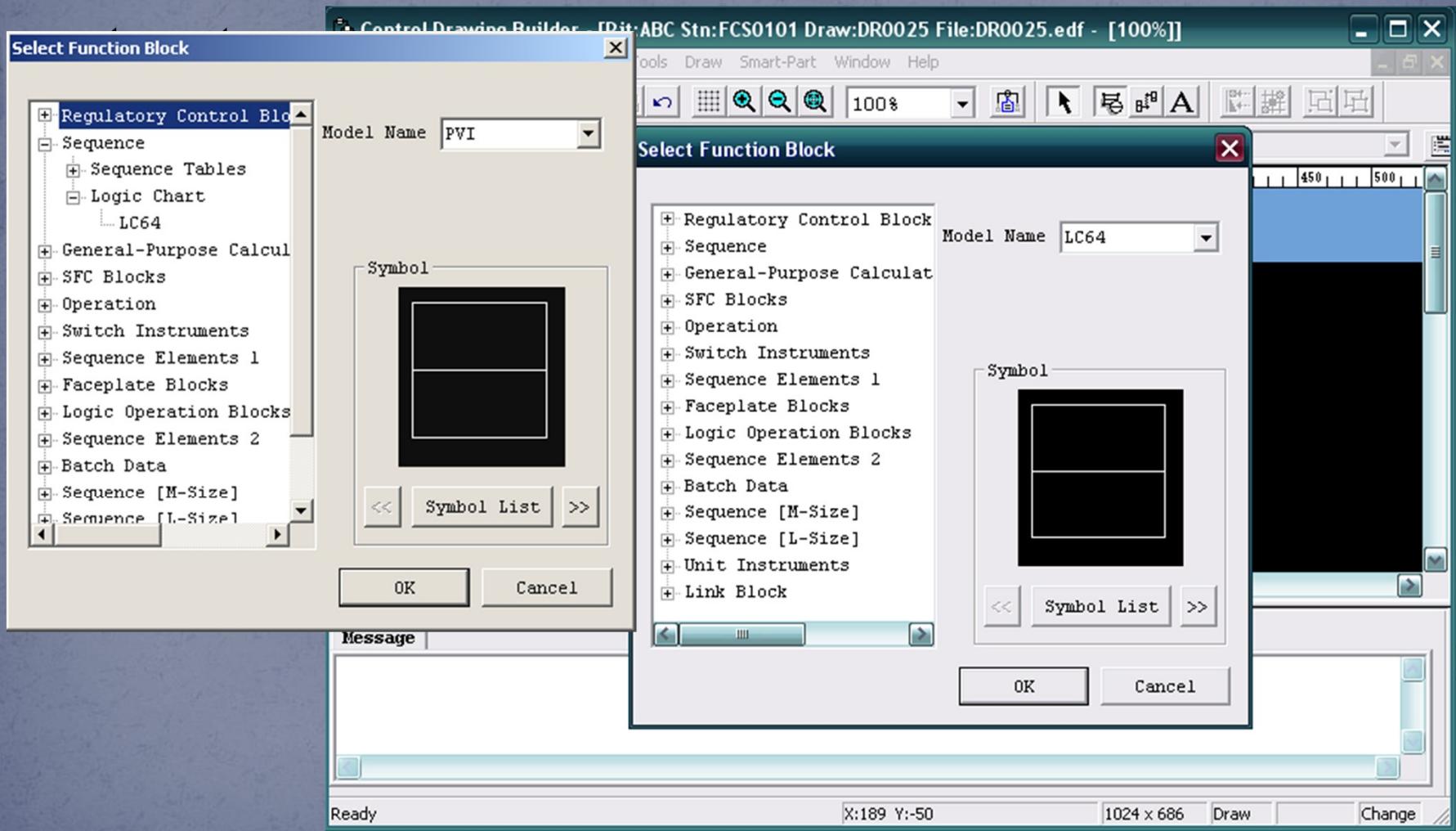


Process timing

Scan period



Order of execution




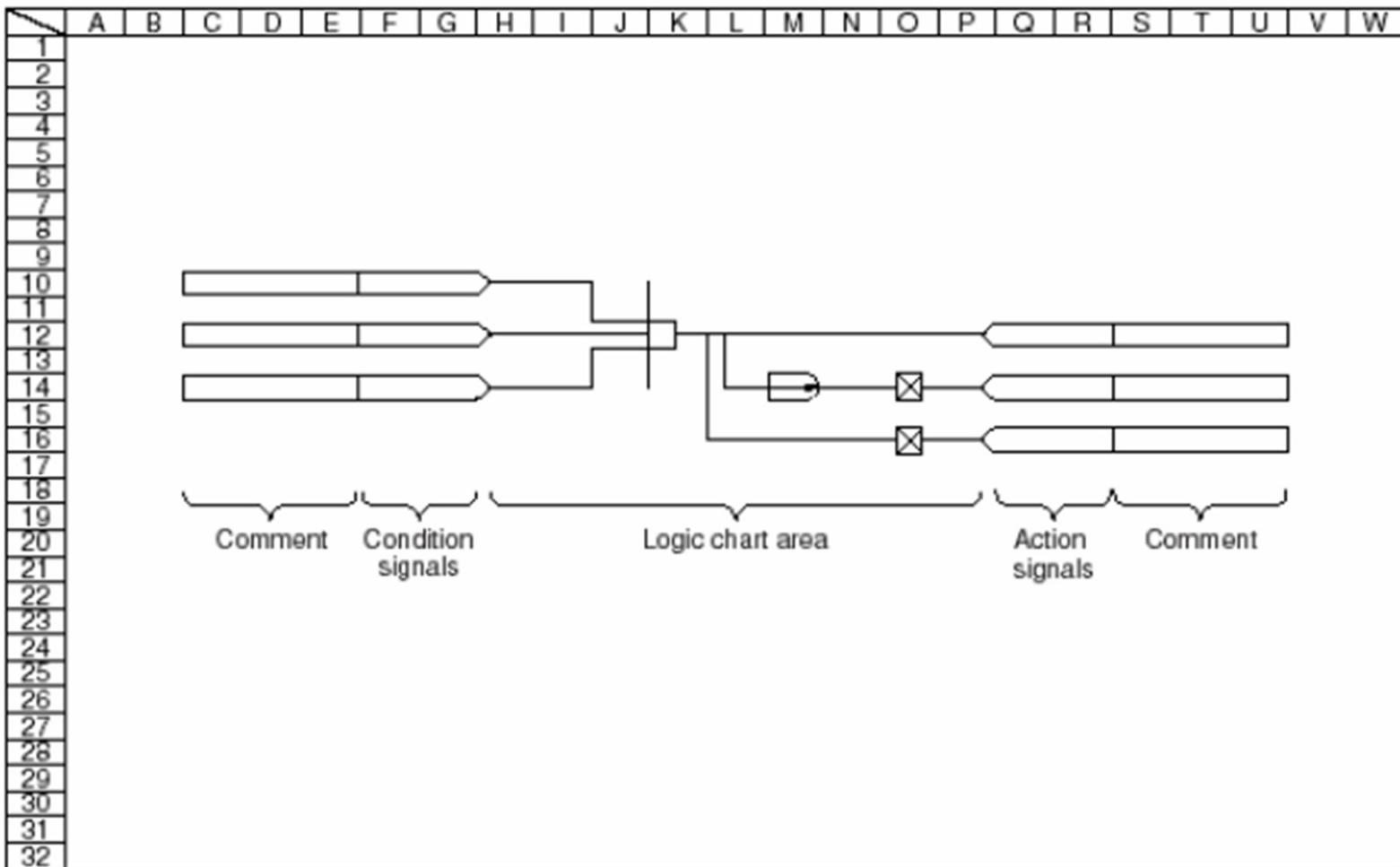






Client area


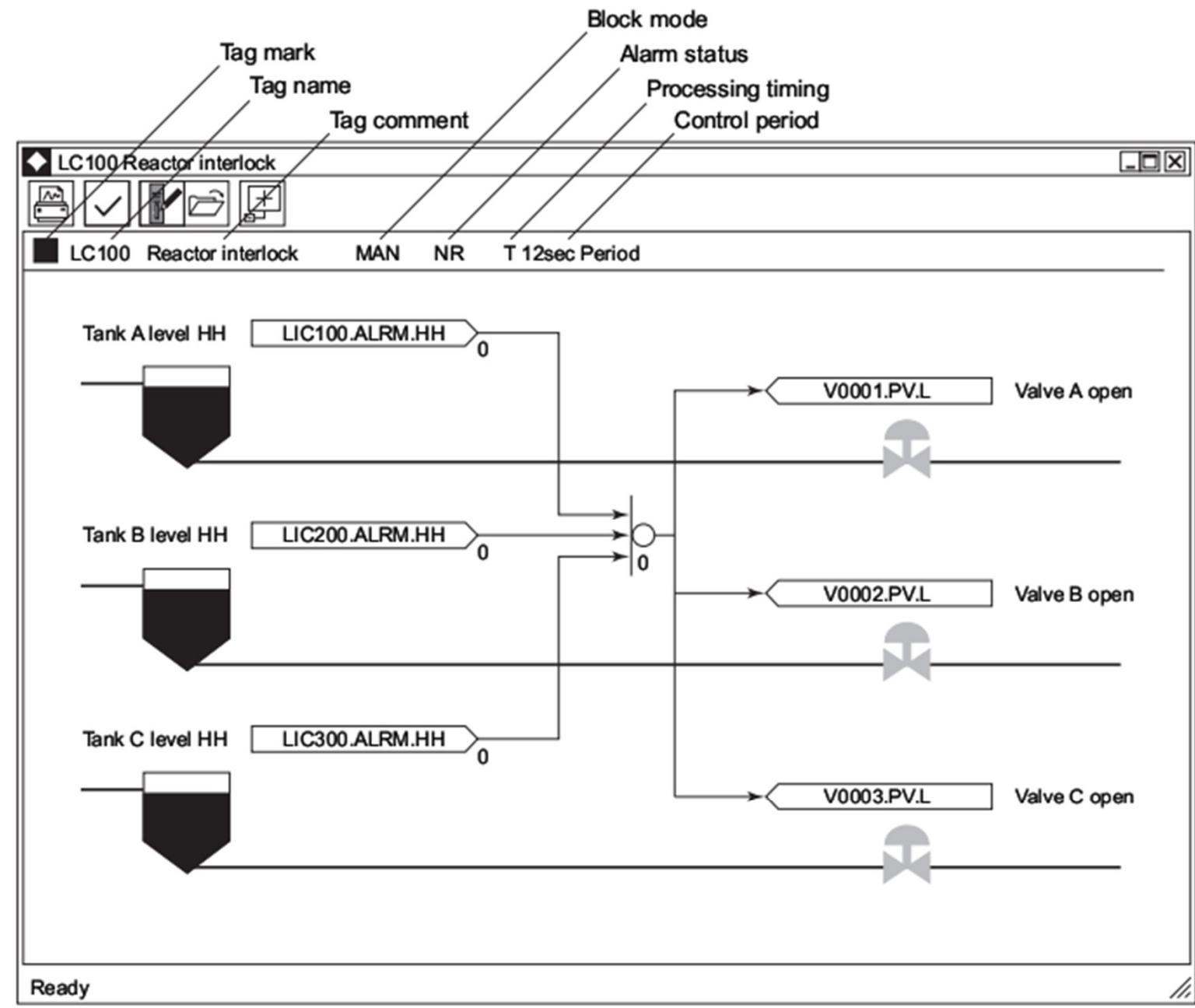






Logic Operation Elements

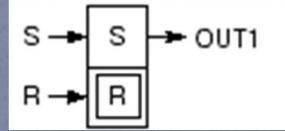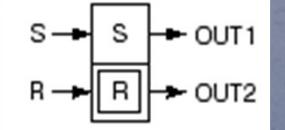Logic operator	Symbol	Action	Notes																								
AND	$\wedge, \text{且}, \sqcap, \sqcap$	Logic product (Max. inputs 21.)																									
OR	$\vee, \text{或}, \sqcup, \sqcup$	Logic sum (Max. inputs 21)																									
NOT	\boxtimes	Negation																									
SRS1-R		<table border="1"> <tr> <td>Input</td> <td>S</td> <td>0</td> <td>1</td> <td>0</td> <td></td> </tr> <tr> <td></td> <td>R</td> <td>0</td> <td>0</td> <td>1</td> <td></td> </tr> <tr> <td>Output</td> <td>OUT1</td> <td>Latched</td> <td>1</td> <td>0</td> <td></td> </tr> <tr> <td></td> <td>OUT2</td> <td>Latched</td> <td>0</td> <td>1</td> <td></td> </tr> </table>	Input	S	0	1	0			R	0	0	1		Output	OUT1	Latched	1	0			OUT2	Latched	0	1		Flip-flop (Reset dominant)
Input	S	0	1	0																							
	R	0	0	1																							
Output	OUT1	Latched	1	0																							
	OUT2	Latched	0	1																							
SRS2-R																											

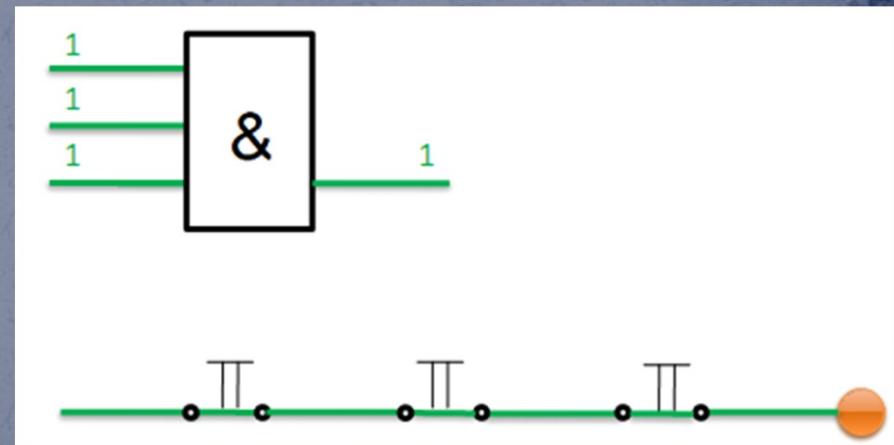
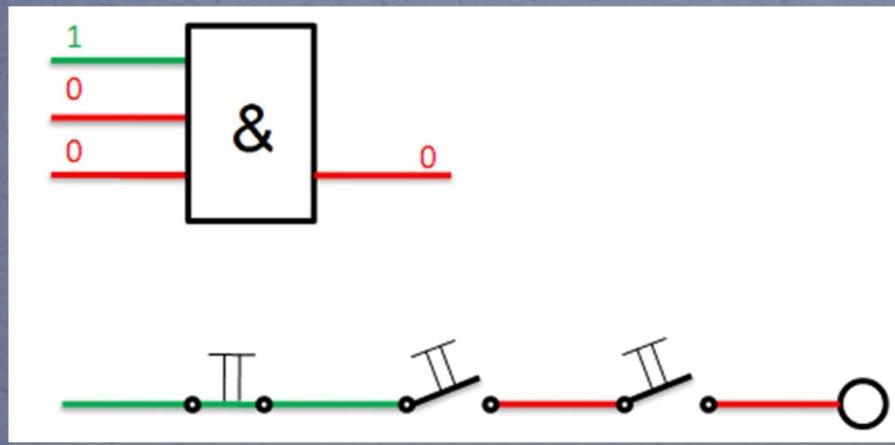
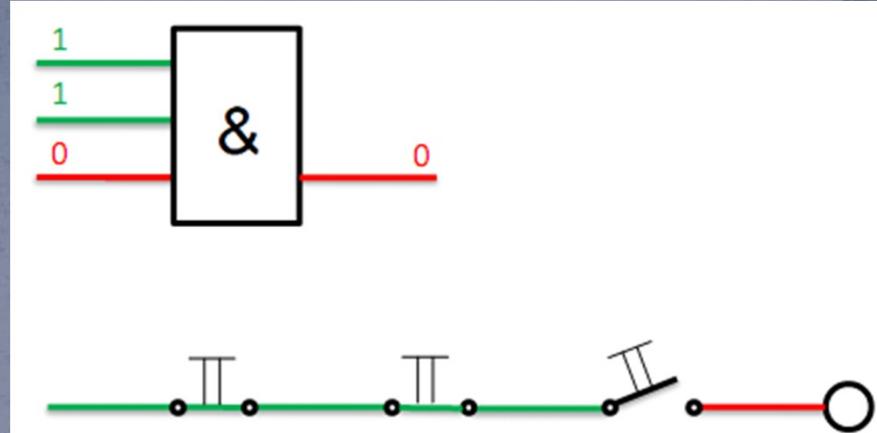
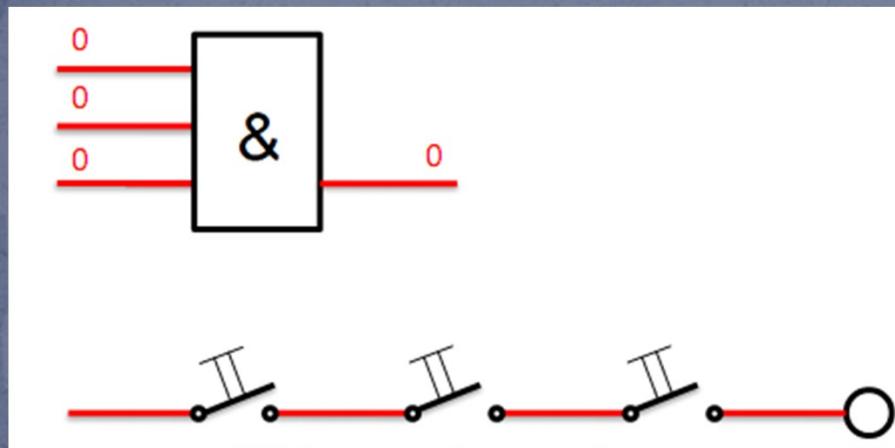


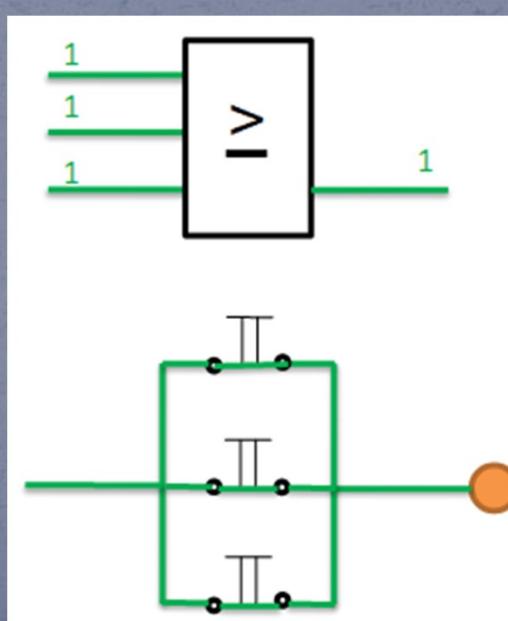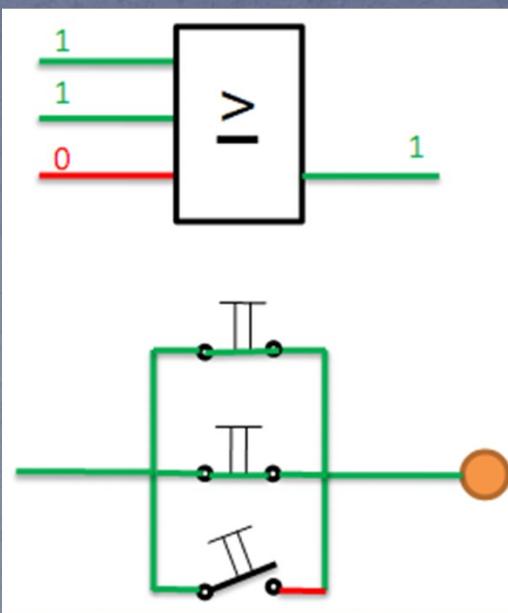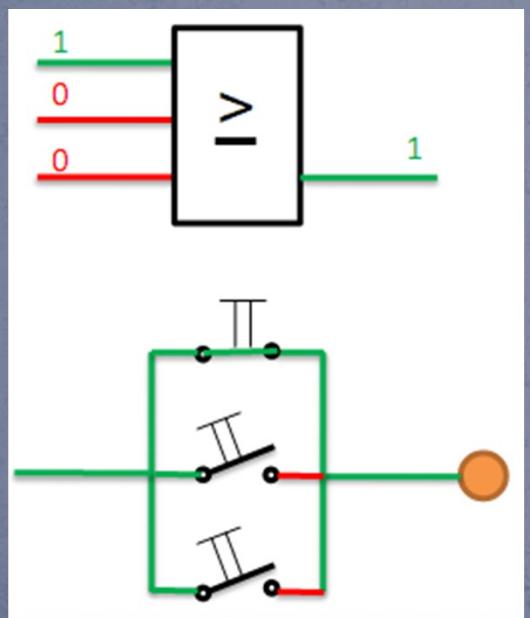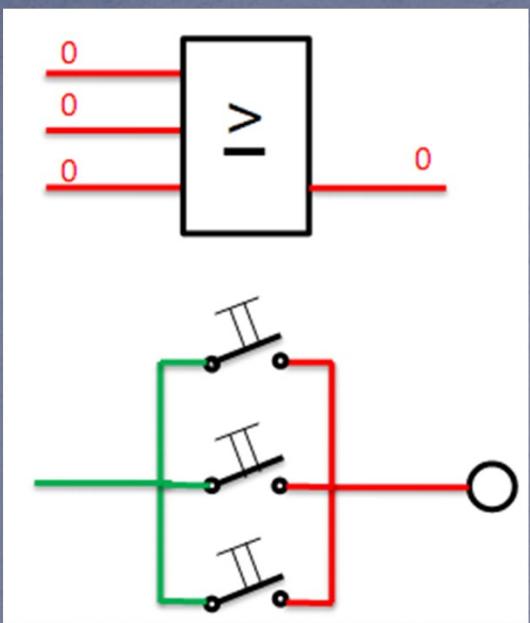

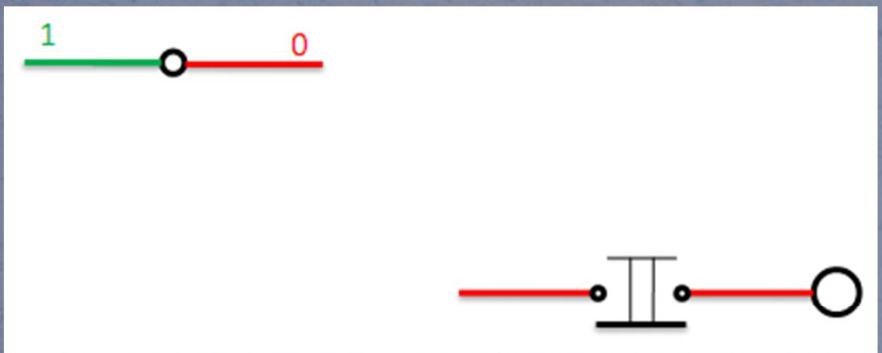
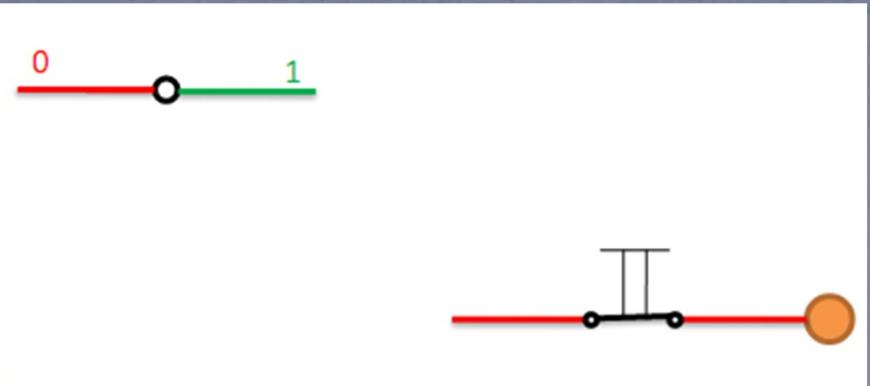


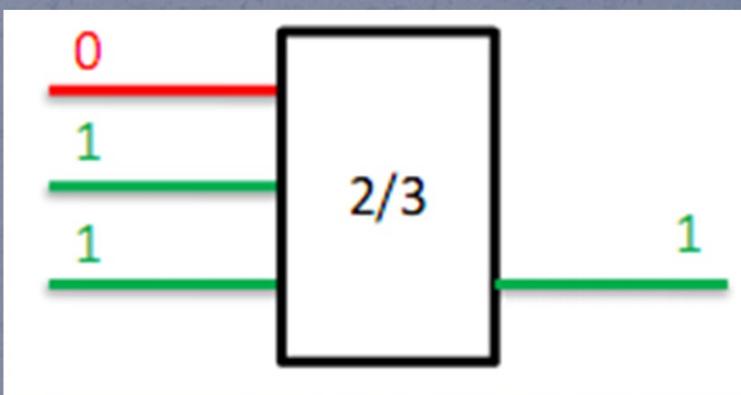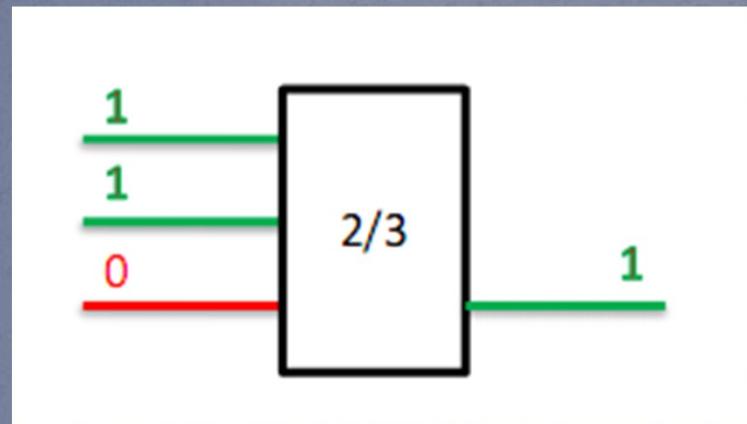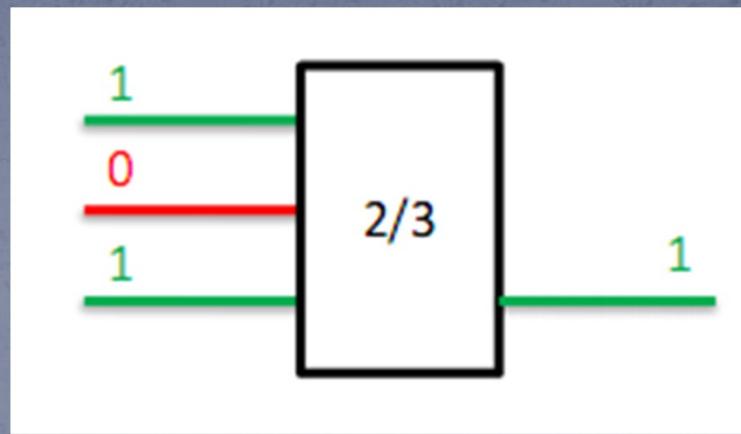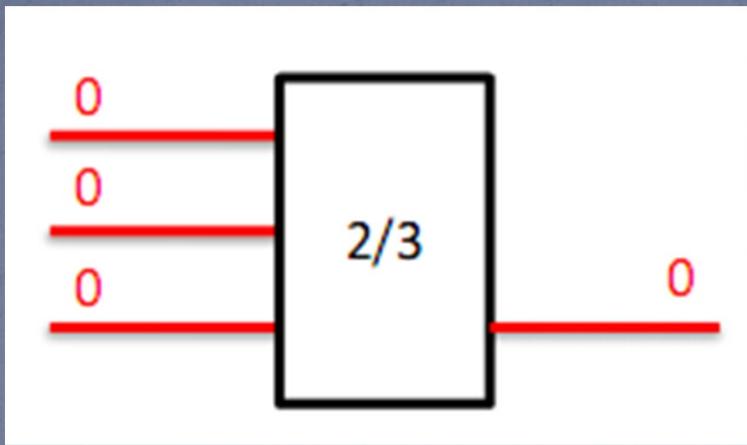



Logic Operation Elements

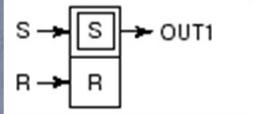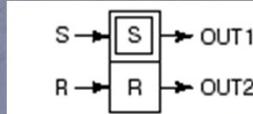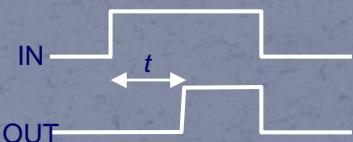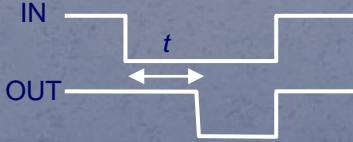Logic operator	Symbol	Action	Notes																				
SRS1-S		<table border="1"> <tr> <td rowspan="2">Input</td> <td>S</td> <td>0</td> <td>1</td> <td>0</td> <td rowspan="2"></td> </tr> <tr> <td>R</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td rowspan="2">Output</td> <td>OUT1</td> <td>Latched</td> <td>1</td> <td>0</td> <td rowspan="2"></td> </tr> <tr> <td>OUT2</td> <td>Latched</td> <td>0</td> <td>1</td> </tr> </table>	Input	S	0	1	0		R	0	0	1	Output	OUT1	Latched	1	0		OUT2	Latched	0	1	Flip-flop (Set dominant)
Input	S	0		1	0																		
	R	0	0	1																			
Output	OUT1	Latched	1	0																			
	OUT2	Latched	0	1																			
SRS2-S																							
WOUT	(W.O)	<table border="1"> <tr> <td rowspan="2">Input</td> <td>S</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> <td rowspan="2"></td> </tr> <tr> <td>R</td> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>Output</td> <td>OUT</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td></td> </tr> </table>	Input	S	0	1	0	1		R	0	0	1	1	Output	OUT	0	1	0	0		Wipeout	
Input	S	0		1	0	1																	
	R	0	0	1	1																		
Output	OUT	0	1	0	0																		
OND			ON-delay timer																				
OFFD			OFF-delay timer																				



- On Delay Timer

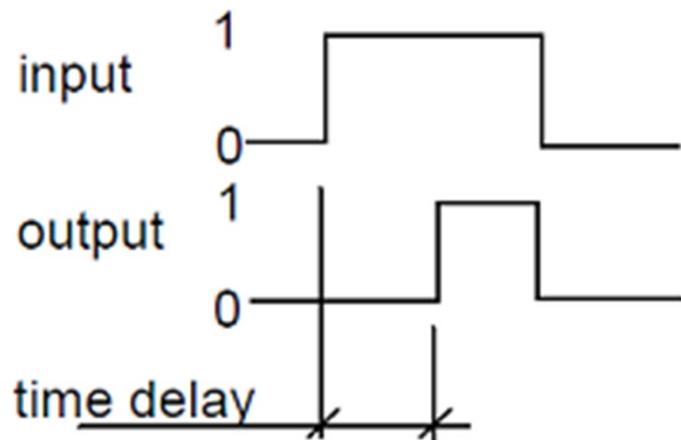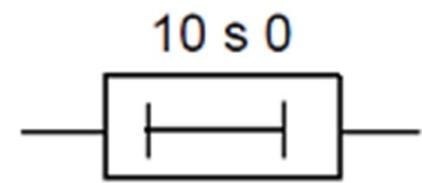


- Off Delay Timer

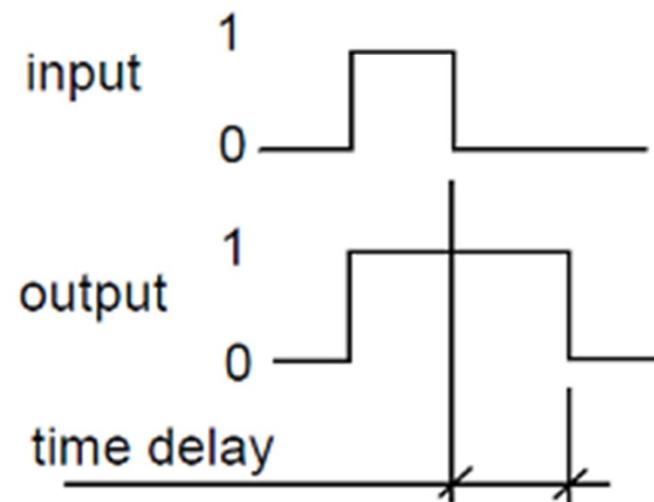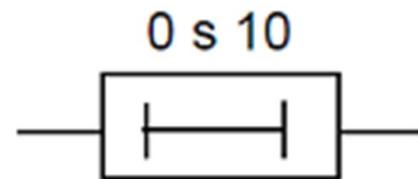


Logic Operation Elements

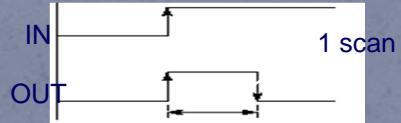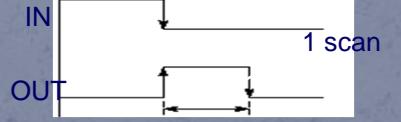Logic operator	Symbol	Action	Notes																		
TON		 IN OUT 1 scan	One-shot (Rise trigger)																		
TOFF		 IN OUT 1 scan	One-shot (Fall trigger)																		
CMP-GE		<table border="1" data-bbox="854 888 1360 1018"> <thead> <tr> <th>Input</th><th>IN1</th><th>0</th><th>0</th><th>1</th><th>1</th></tr> </thead> <tbody> <tr> <th>IN2</th><td>0</td><td>1</td><td>0</td><td>1</td><td></td></tr> <tr> <th>Output</th><th>OUT</th><td>1</td><td>0</td><td>1</td><td>1</td></tr> </tbody> </table>	Input	IN1	0	0	1	1	IN2	0	1	0	1		Output	OUT	1	0	1	1	Comparator
Input	IN1	0	0	1	1																
IN2	0	1	0	1																	
Output	OUT	1	0	1	1																
CMP-GT		<table border="1" data-bbox="854 1075 1360 1206"> <thead> <tr> <th>Input</th><th>IN1</th><th>0</th><th>0</th><th>1</th><th>1</th></tr> </thead> <tbody> <tr> <th>IN2</th><td>0</td><td>1</td><td>0</td><td>1</td><td></td></tr> <tr> <th>Output</th><th>OUT</th><td>0</td><td>0</td><td>1</td><td>0</td></tr> </tbody> </table>	Input	IN1	0	0	1	1	IN2	0	1	0	1		Output	OUT	0	0	1	0	Comparator
Input	IN1	0	0	1	1																
IN2	0	1	0	1																	
Output	OUT	0	0	1	0																
CMP-EQ		<table border="1" data-bbox="854 1263 1360 1393"> <thead> <tr> <th>Input</th><th>IN1</th><th>0</th><th>0</th><th>1</th><th>1</th></tr> </thead> <tbody> <tr> <th>IN2</th><td>0</td><td>1</td><td>0</td><td>1</td><td></td></tr> <tr> <th>Output</th><th>OUT</th><td>1</td><td>0</td><td>0</td><td>1</td></tr> </tbody> </table>	Input	IN1	0	0	1	1	IN2	0	1	0	1		Output	OUT	1	0	0	1	Comparator
Input	IN1	0	0	1	1																
IN2	0	1	0	1																	
Output	OUT	1	0	0	1																


Pull up Edge Detector

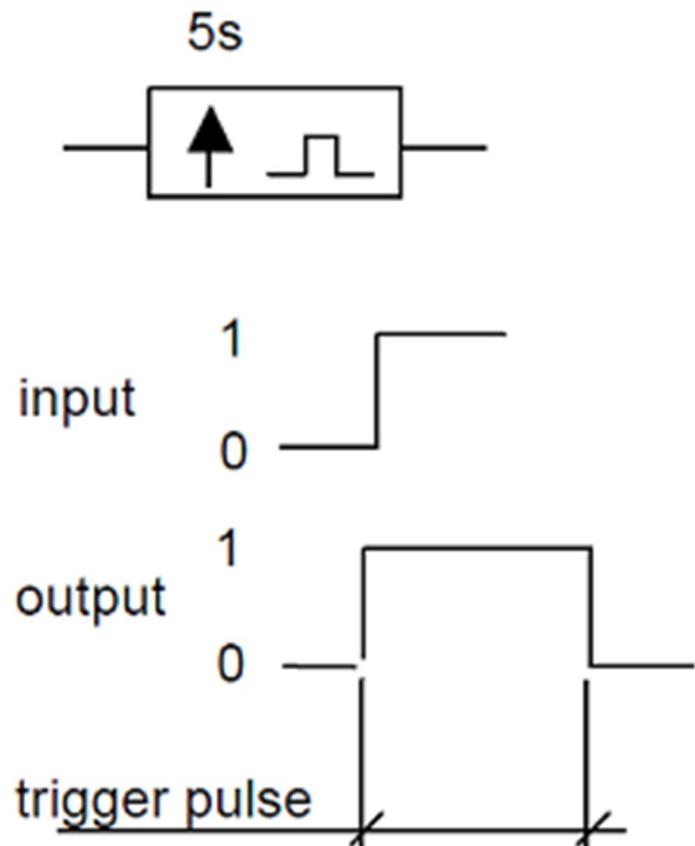

Drop Out Edge Detector

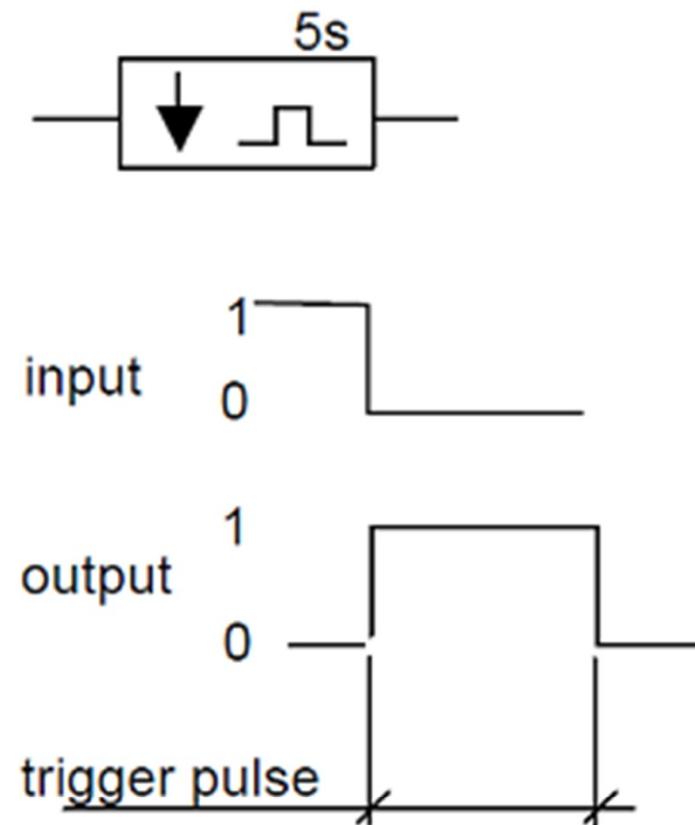


S/R-flip/flop with reset dominant input.

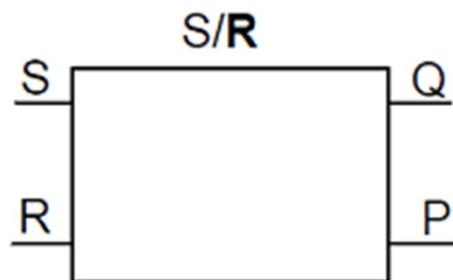

S	R	Q	P
0	0	Y*	Y*
0	1	0	1
1	0	1	0
1	1	0	1

Y: Previous state is retained.*

S/R-flip/flop with set dominant input.

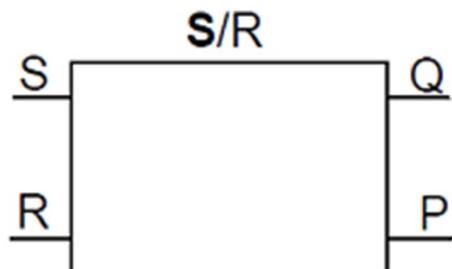


S	R	Q	P
0	0	Y*	Y*
0	1	0	1
1	0	1	0
1	1	1	0

Y: Previous state is retained.*

Wipeout Operation

در این عملگر ورودی را با NOT ورودی دوم AND می نماید

Input	S	0	1	0	1
	R	0	0	1	1
Output	OUT	0	1	0	0

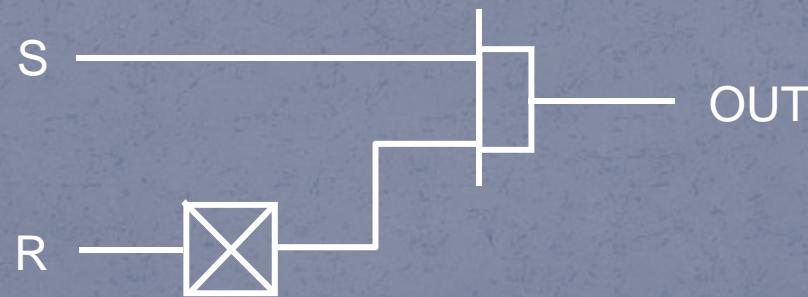

One wipeout operation is counted as two logic operation elements.



42X2002005LC LOGIC


42X2002005LC

AUT

NR


T 1sec Period


SECOND OUTPUT

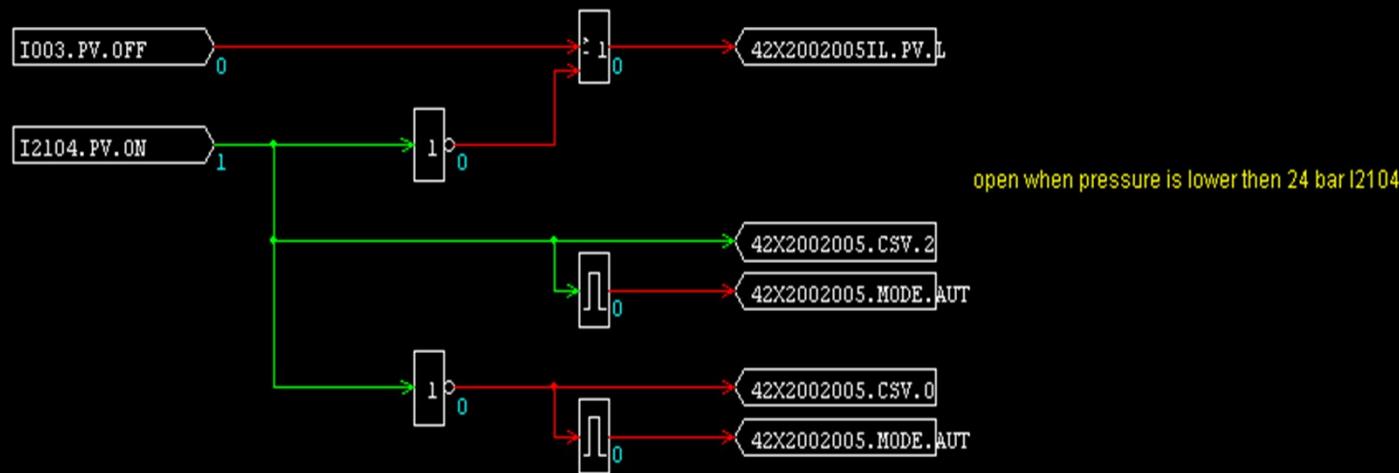

SECOND OUTPUT






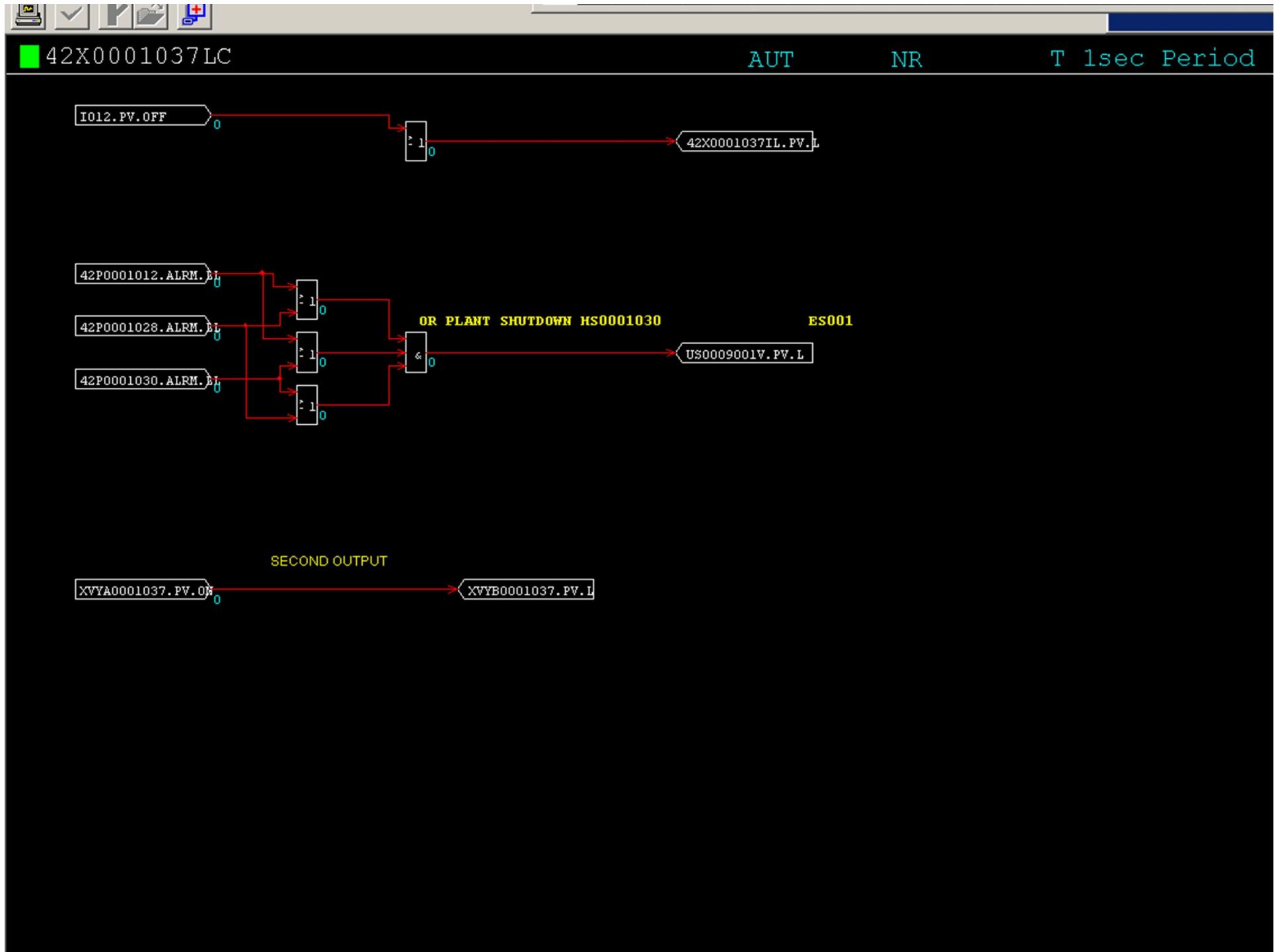


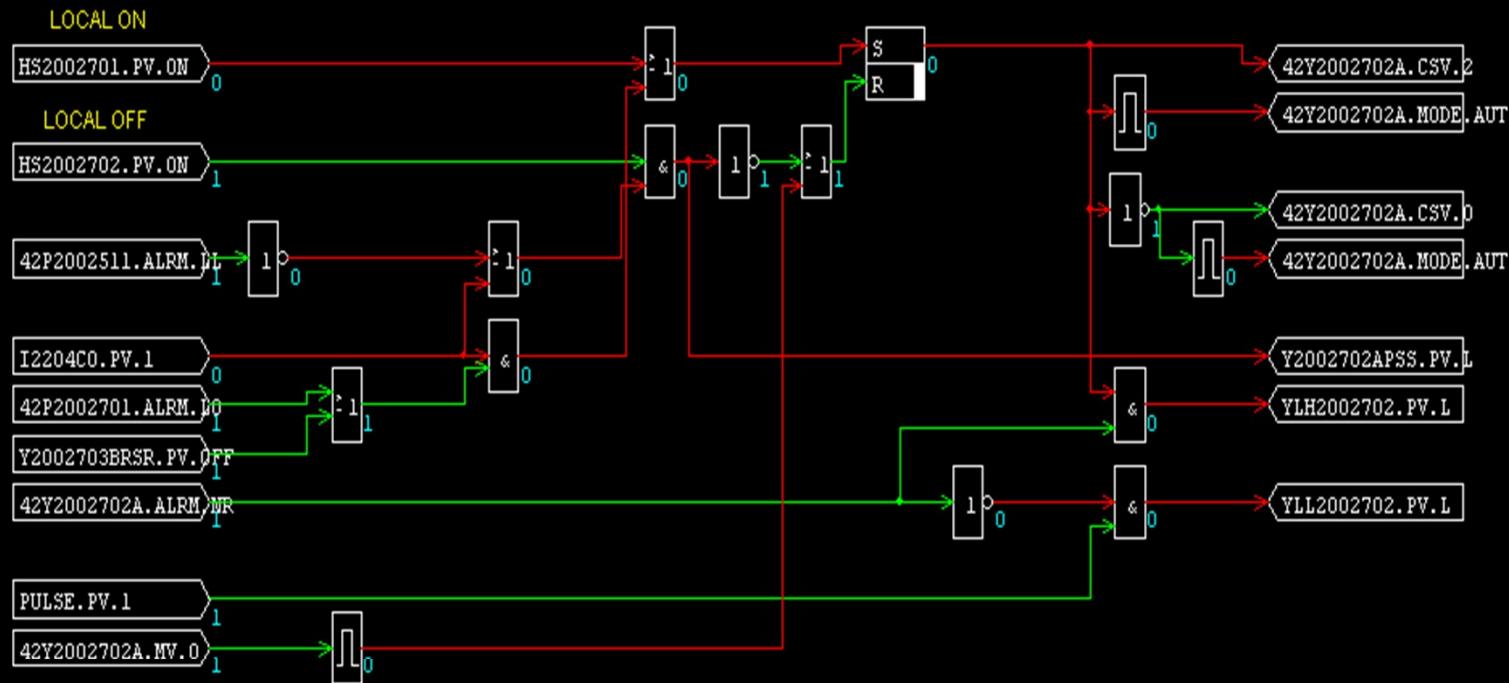



TRACKING




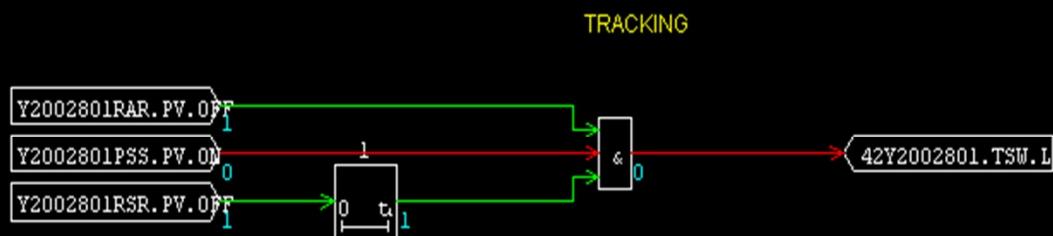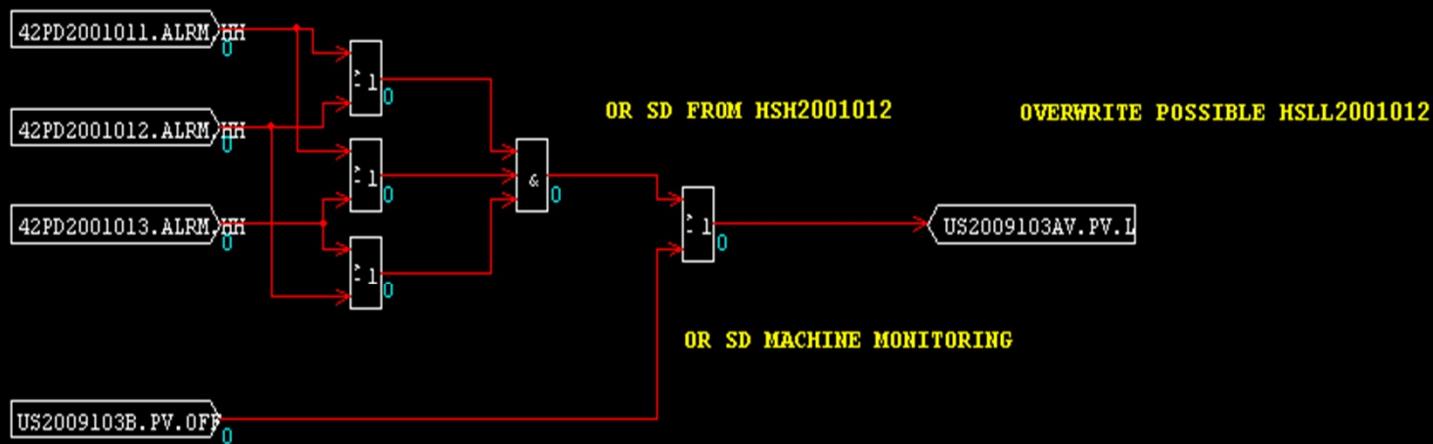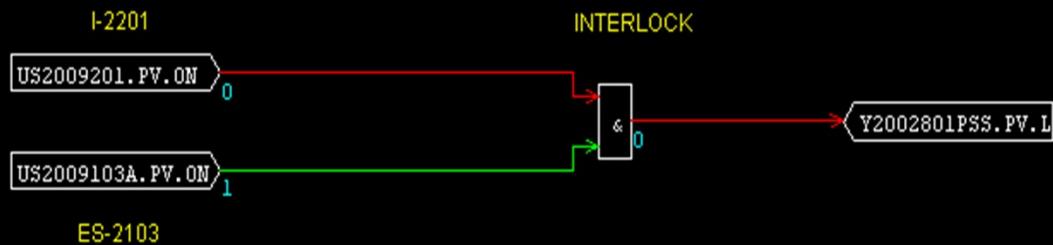

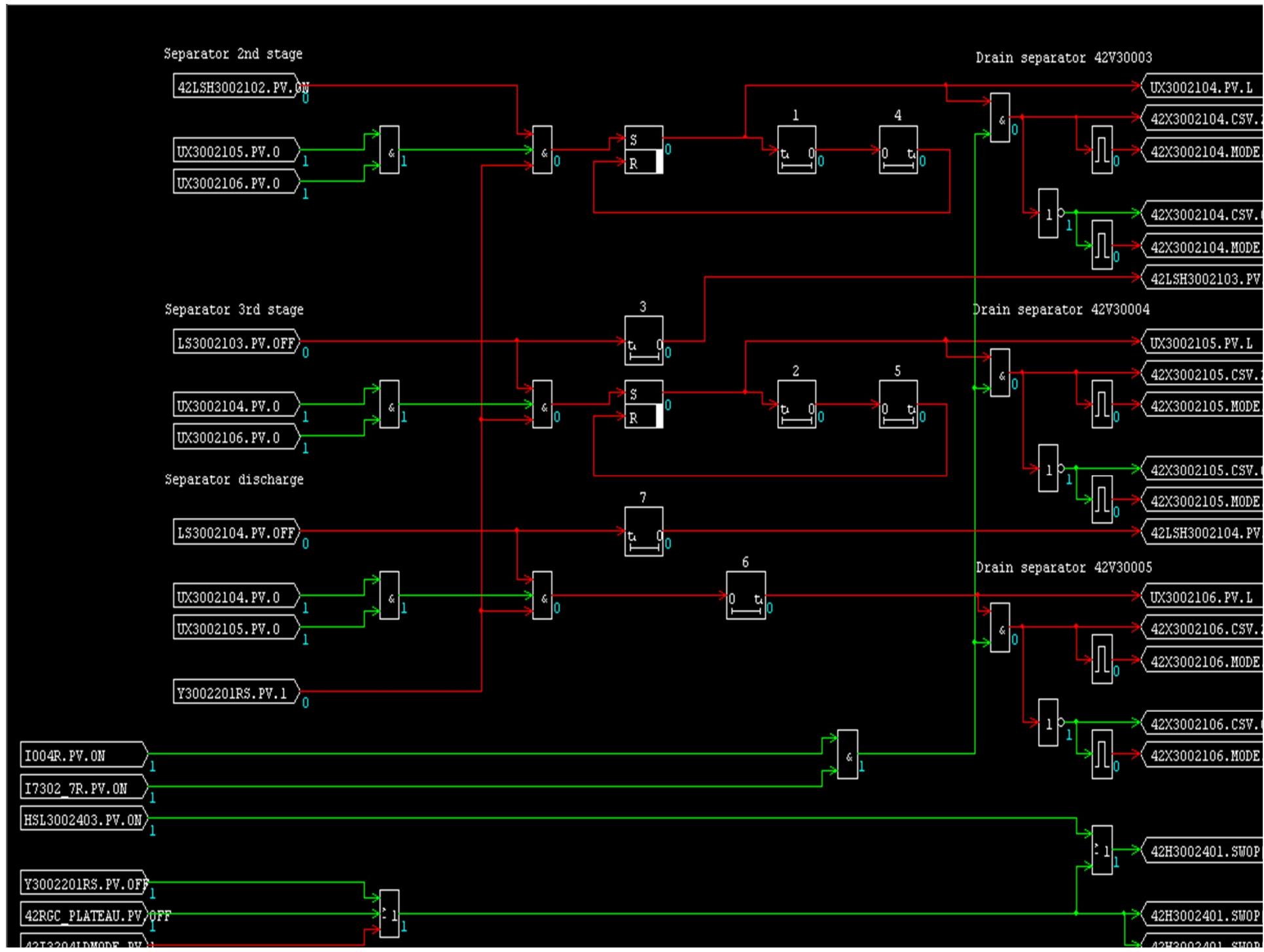

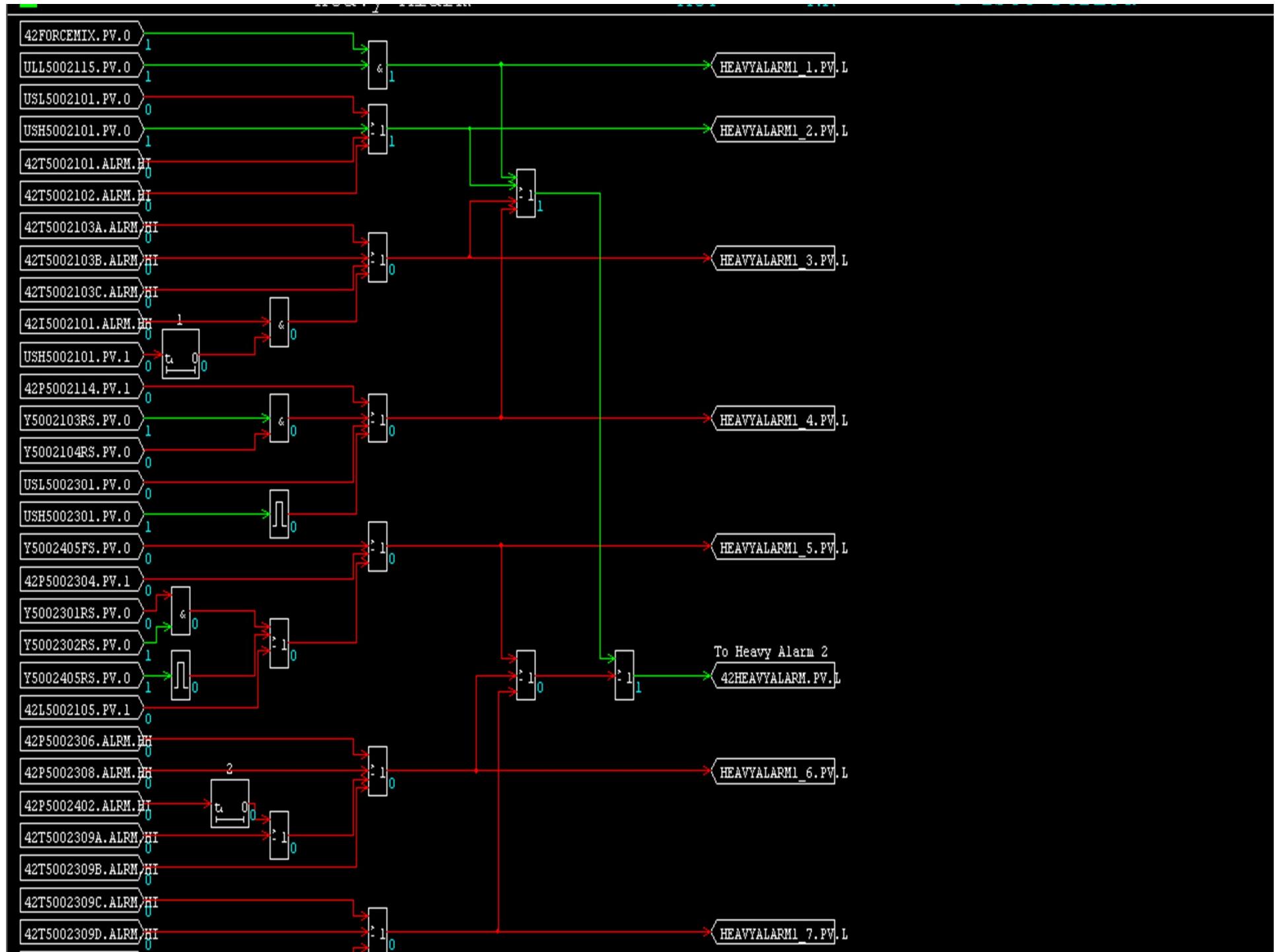

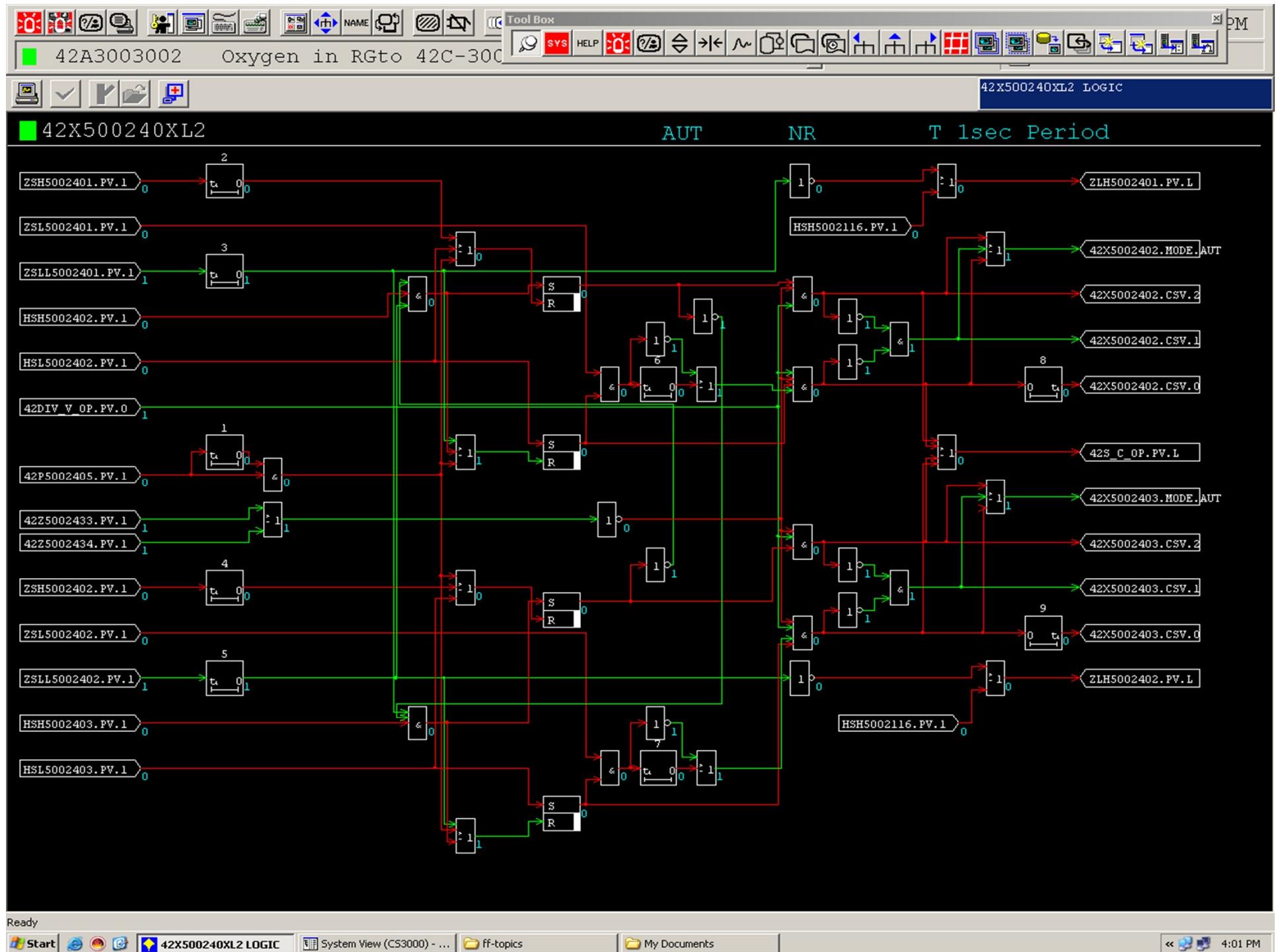

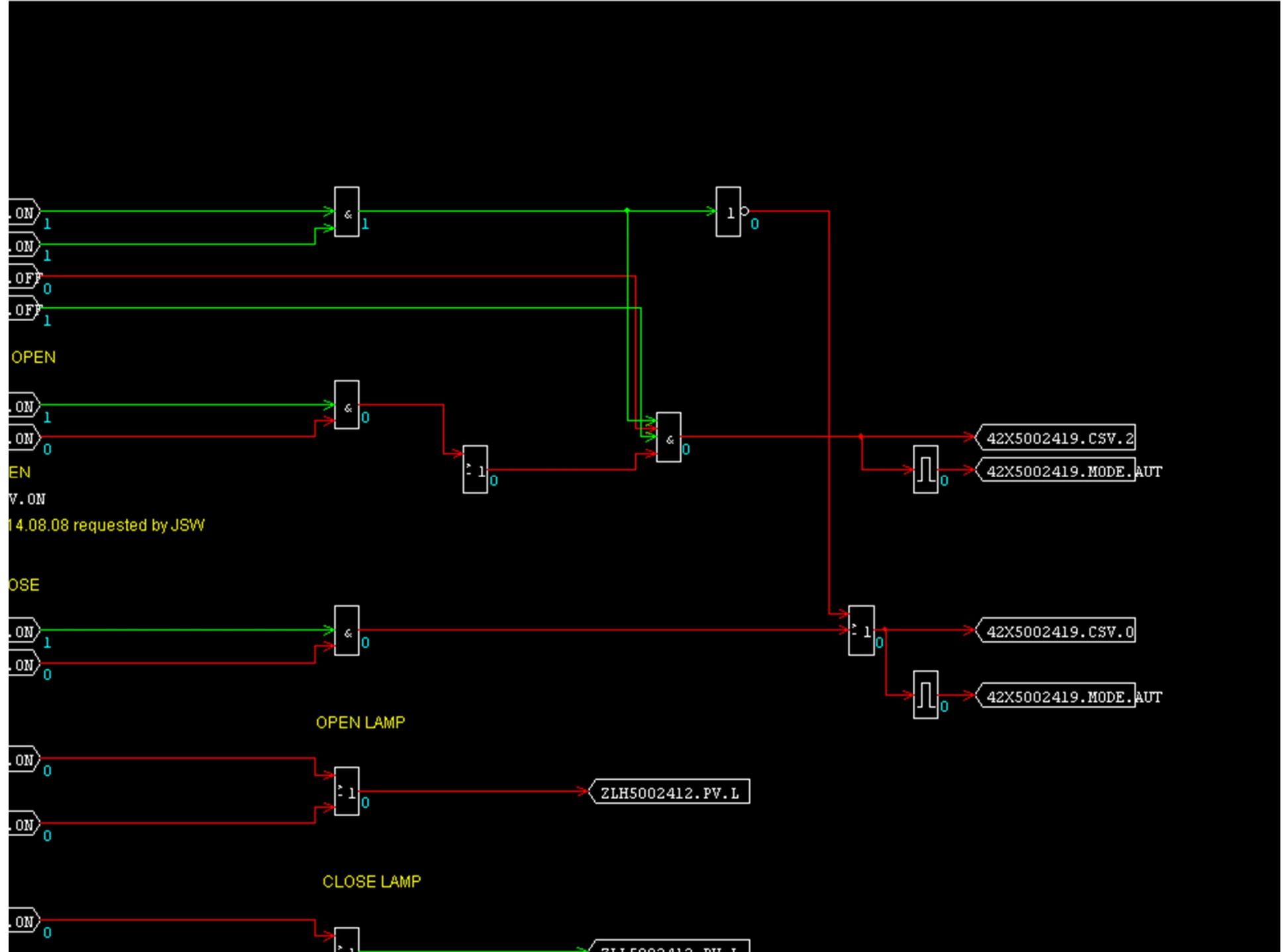


تمرین ۱:


- با استفاده از LC64 مدار گیت های زیر را طراحی نمایید
 - الف) گیت AND
 - ب) گیت OR
 - ج) گیت SR-FF


در این تمرین ورودی ها را LSL0011.FSL0012 و خروجی PUMP001 را بنامید

تمرین ۲:

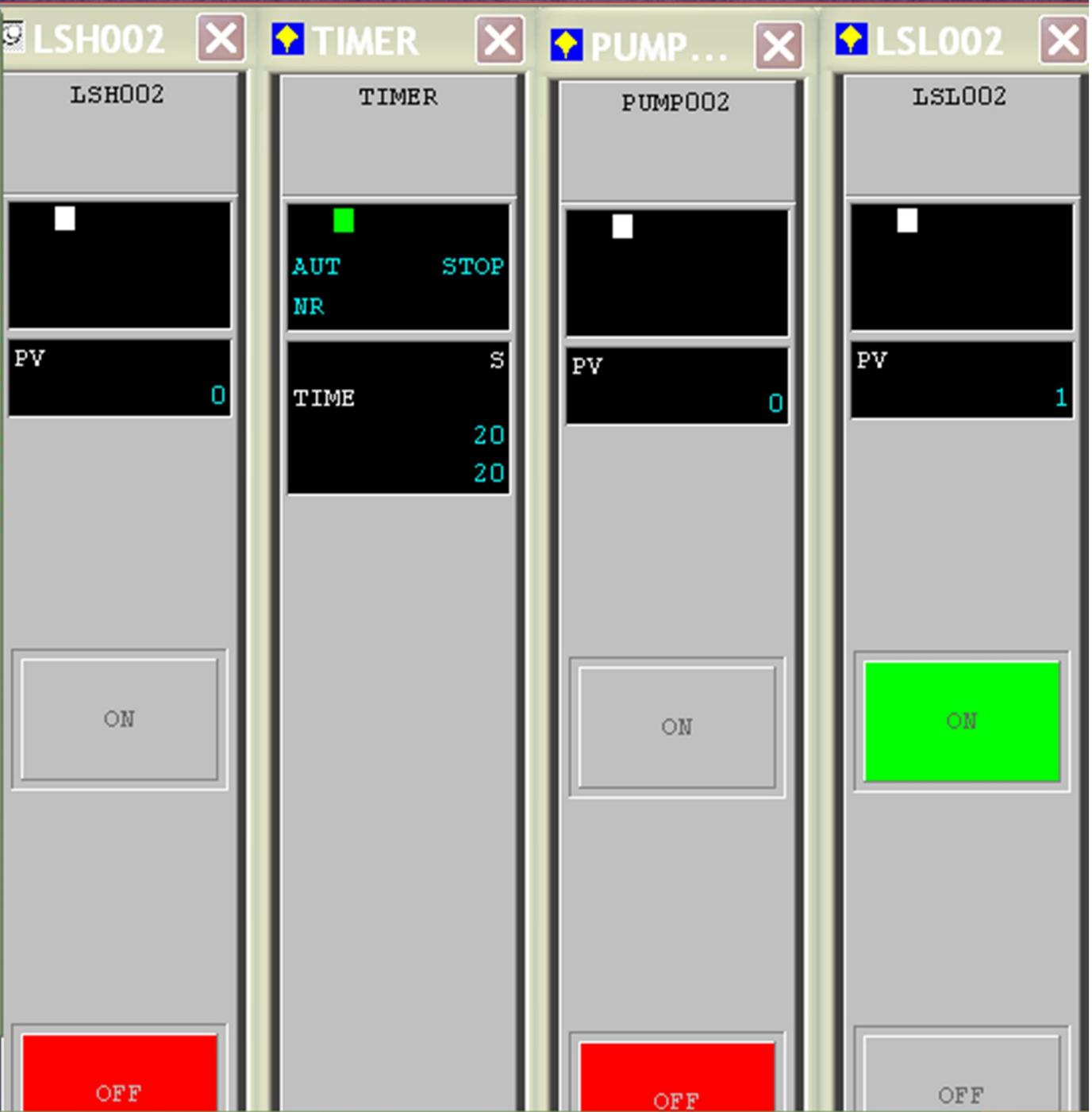- با استفاده تایمر و LC64 مداری طراحی کنید که:
 - الف) با فعال شدن سوئیچ LSL002 پمپ ۲۰ روشن شده و به مدت ۲۰ ثانیه مخزن را پر نماید با فعال شدن سوئیچ LSH002 یا گذشت زمان ۲۰ ثانیه پمپ خاموش شود
 - ب) مدار را طوری اصلاح نمایید که بطور متناوب شمارش را داشته باشد ولی در صورت عمل سوئیچ LSH002 سیستم از کار افتاده و منتظر فرمان سوئیچ LOW باشد.
 - ج) مدار قسمت ب را با استفاده از فلیپ فلاپ SR طراحی نمایید




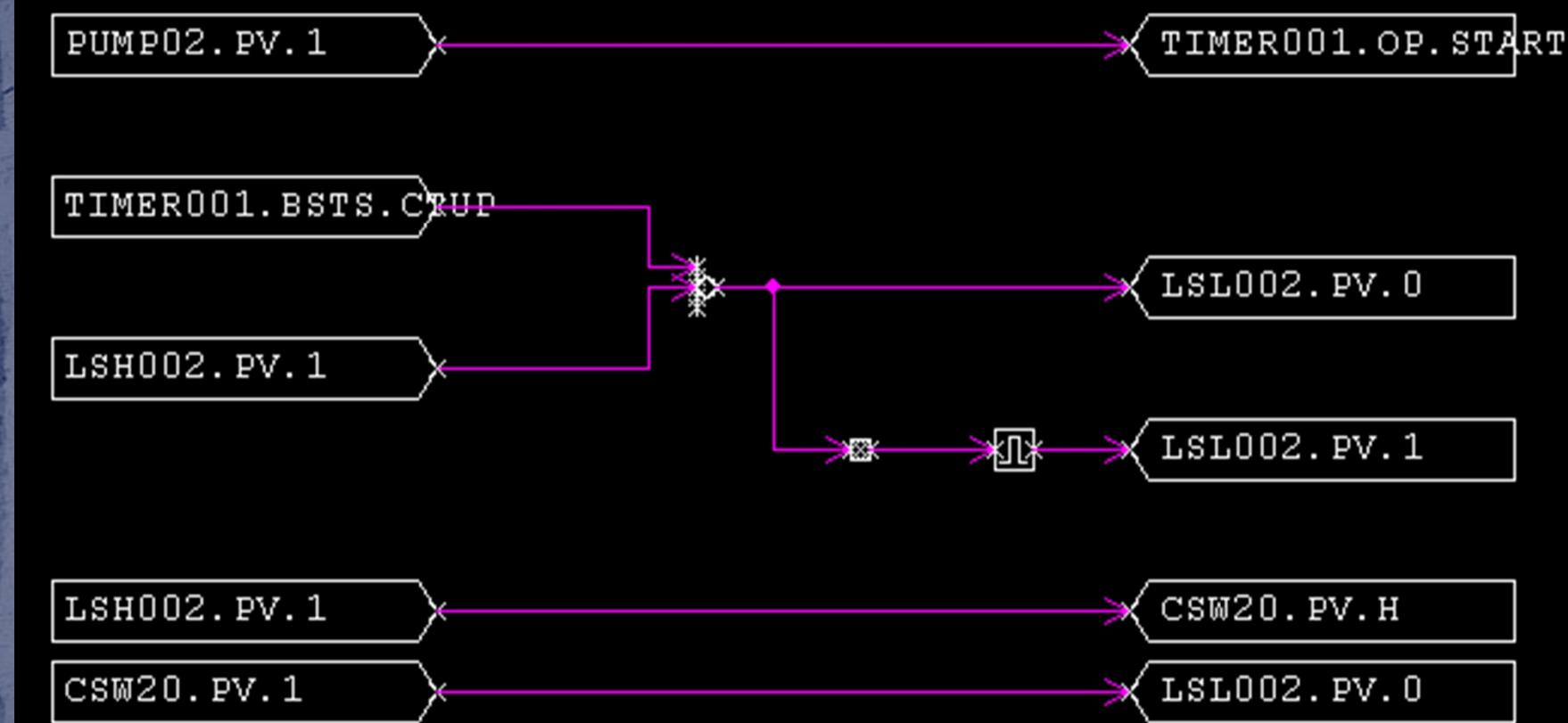

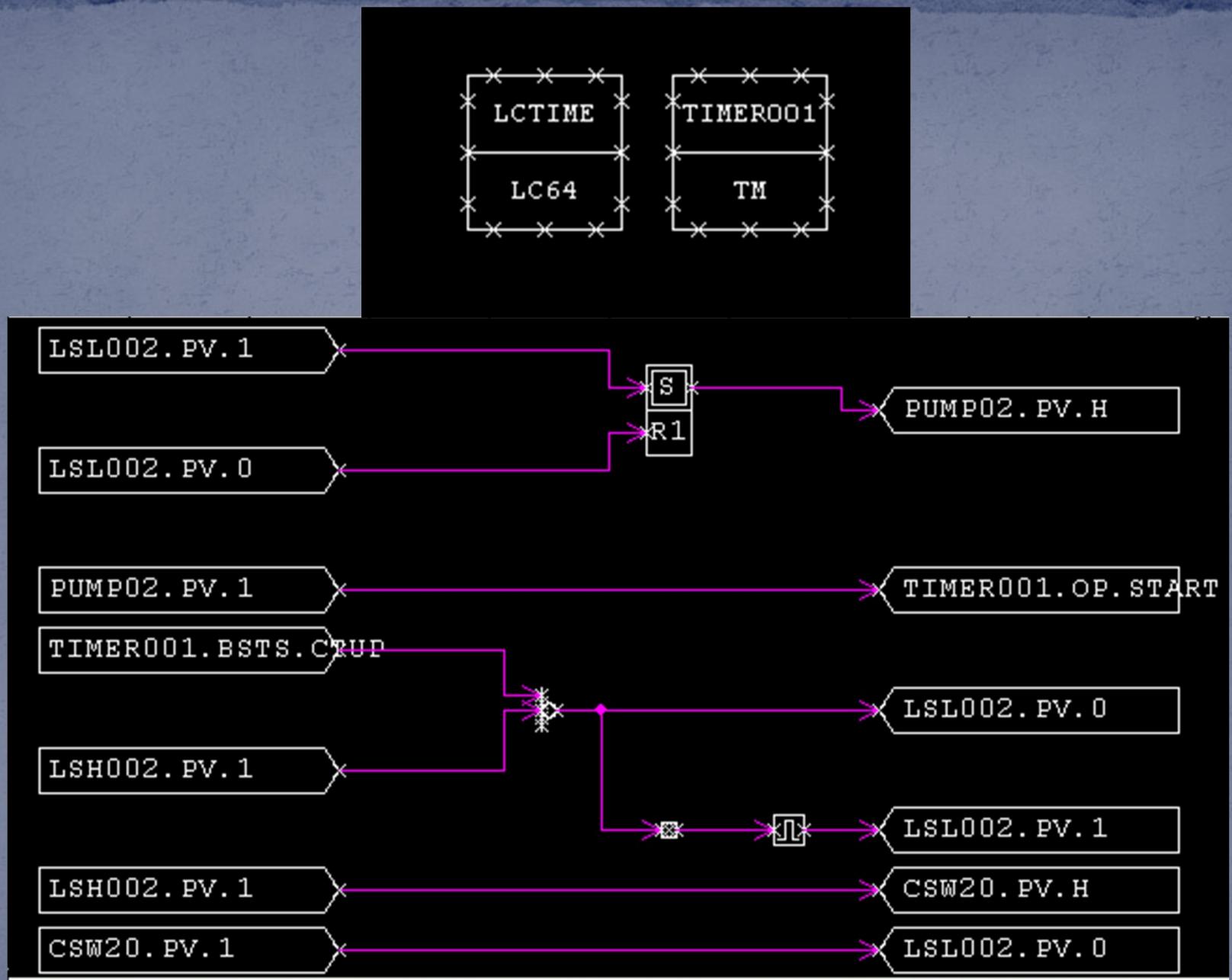

Sequence Table Blocks

Select Function Block

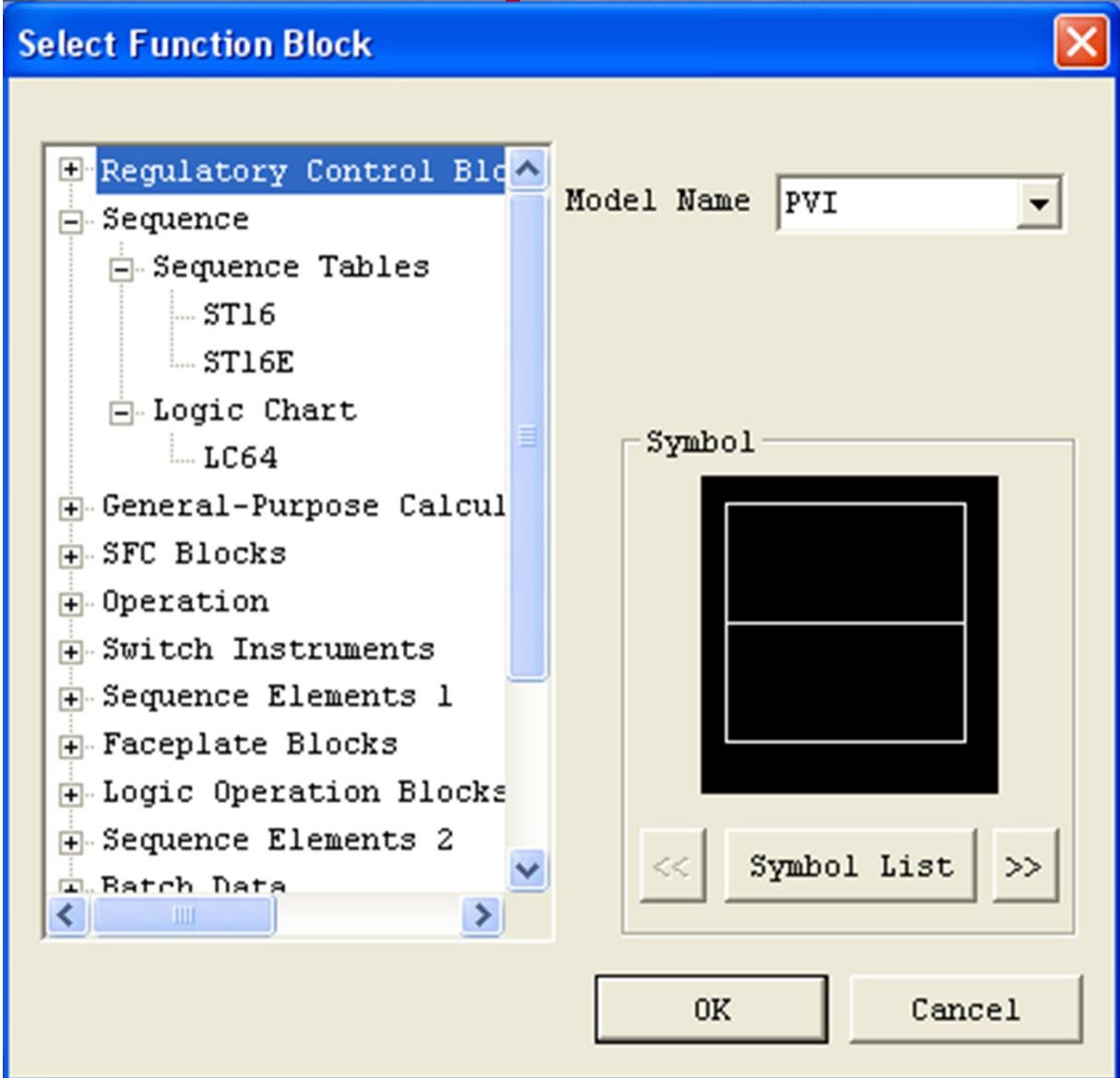

- برای لاجیکها پیچیده ای
- در صورتی که بخواهیم آنها را همزمان معکوس شود
- در LC64 در انتهای فرمت Table صورتیکه در Sequence Elements 1 تغییرات خروجی رو به ازای هر تغییر در Sequence Table ST16E ,ST16E

Sequence Table Blocks

در Sequence Table یک جدول وجود دارد که شامل دو قسمت است قسمت شرطها و قسمت

1-ST16	No. of condition signals	No. of action signals	اجرای شد
تائی می ۸	8	56	دارای ۴
Total points	16	48	توان در
	24	40	→
(2) ST16E	32 (default)	32 (default)	قابل
	40	24	با
Total points	48	16	→
	56	8	
Output action		Y N	Action values

M- and L- Size Sequence Tables

دو سایز بزرگتر از Sequence Table ها عبارتند از:

Middle size table: M-ST16, M-ST16E

Large size table: L-ST16, L-ST16E


(1) M-ST16, M-ST16E:

دو مدل فوق ۹۶ سیگنال I/O و ۳۲ ستون را ساپورت می کند

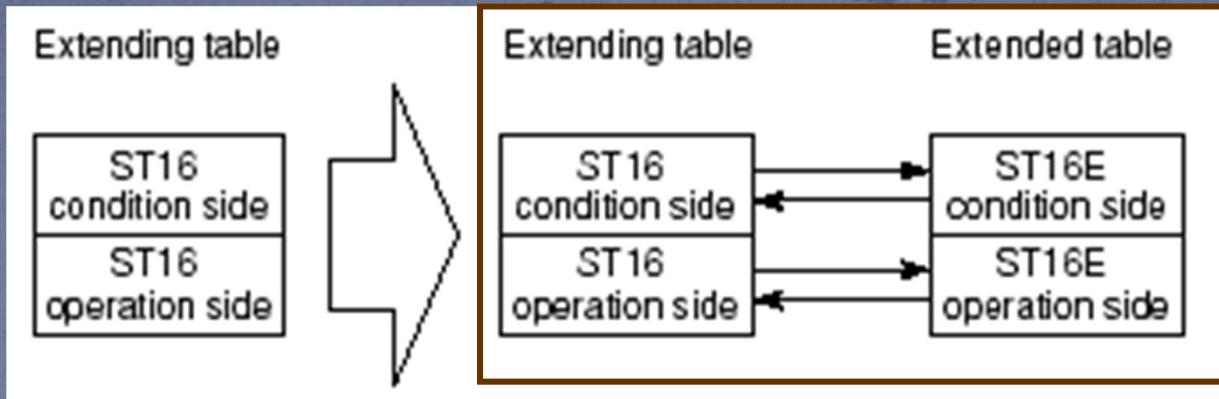(2) L-ST16, L-ST16E:

دارای ۱۲۸ سیگنال I/O و ۳۲ ستون می باشد

* در Sequence Table تعداد ستون ها همواره ثابت است برای افزایش آنها دو عدد ST16E را با ST16 سری می کنیم



Sequence table group

-قا ۱۰۰ را با STEP می توان ساپورت نمود
-های یکسان نمی توانند بعنوان یک step در نظر گرفته شوند

Sequen انها

شوند

		Symbol	Rule	ST16															
	Step			01	32		
C01	E1	Step 1 to 15															G1		
A01	H1																J1		
		THEN															ELSE		
		ELSE																	


NEXT Expansion destination sequence table name

Expansion source sequence table


		Symbol	Rule	ST16E															
	Step			01	31	32	
C01	E1	Step 16 to 35															G2		
A01	H1																J2		
		THEN															ELSE		
		ELSE																	

Expansion destination sequence table

Sequence Table Block

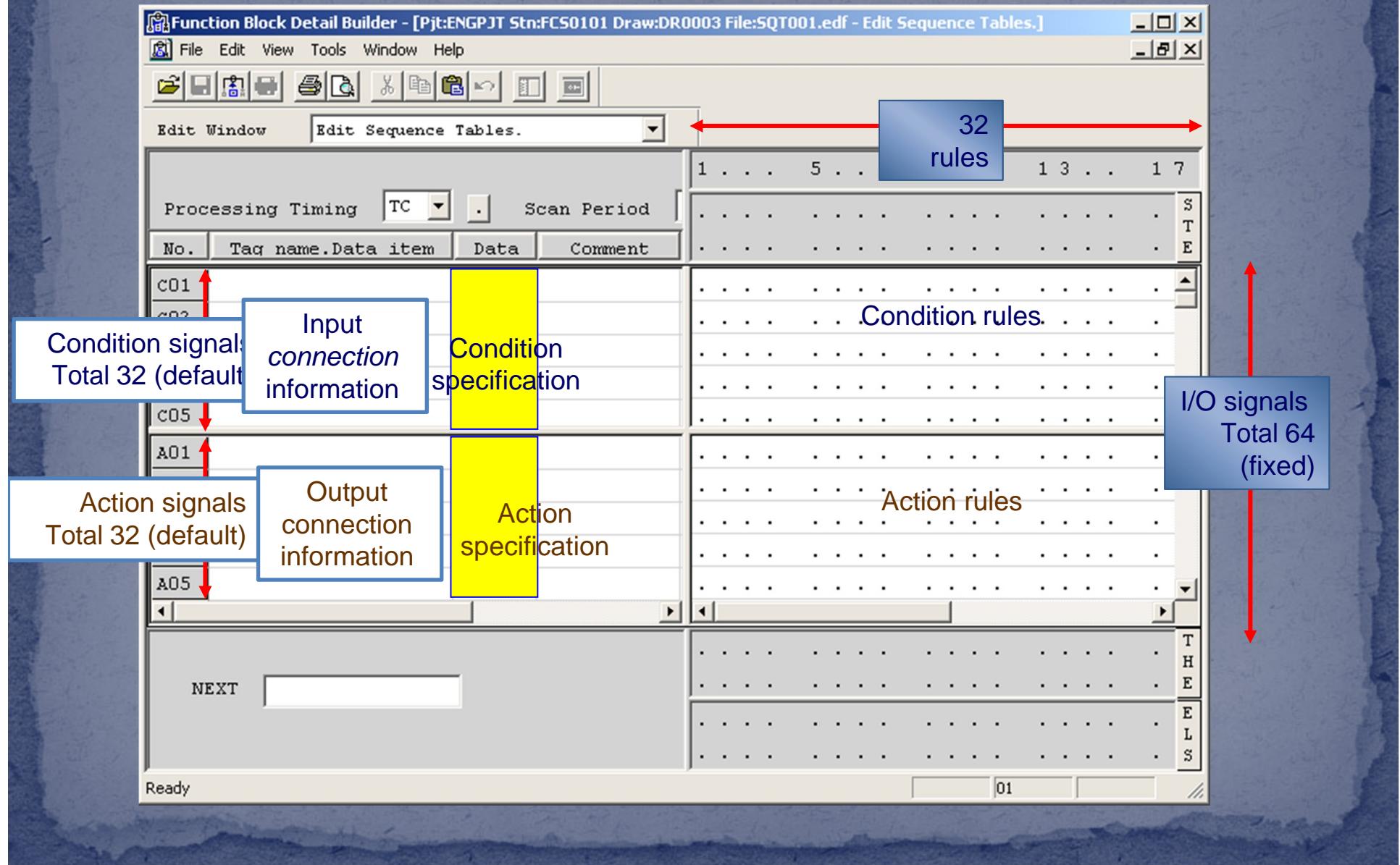


Sequence Table Block

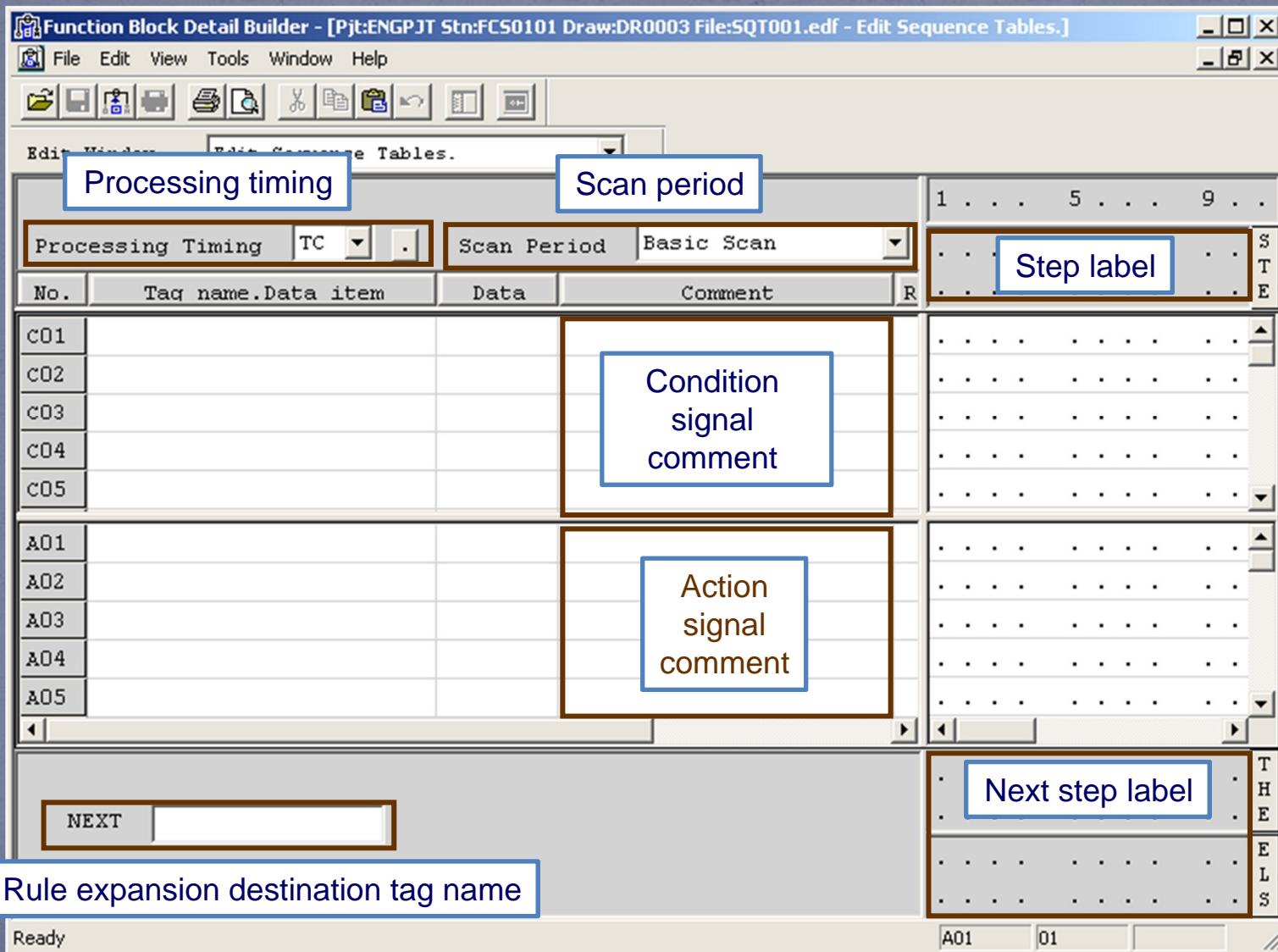

Example of Sequence Description

روش اجرای گیتهای مختلف در ST16

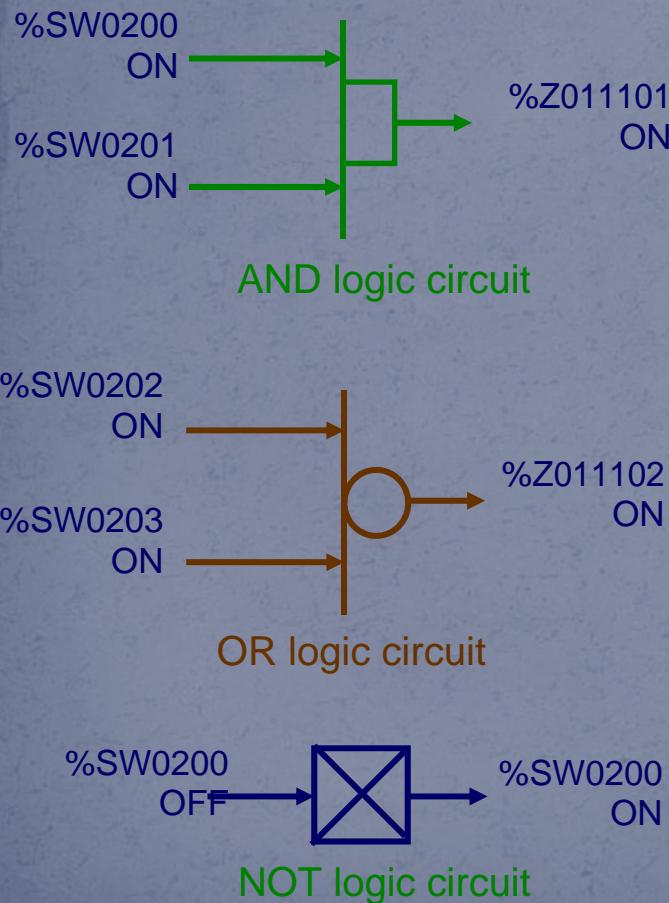

	Rule	Step	01	02	03	32
C01	%SW0200.PV	ON	Y					
.	%SW0201.PV	ON	Y					
.	%SW0202.PV	ON						
.	%SW0203.PV	ON						
C32	(Condition signals)							
A01	%Z011101.PV	H		Y				
.	%Z011102.PV	H						
.	%SW0200.PV	H						
A32	(Action signals)							
	THEN							
	ELSE							

تنظیم عملکرد خروجی

دارای چهار حالت تنظیم خروجی دارد که عبارتند از:

- تنظیم و اجرای پریودیک (T):
اجرا و تنظیم سیکل از قبل تنظیم شده بصورت پریودیک
- اجرا و تنظیم یک دفعه ای (one-shot)(O):
بکار اجراء با درخواست یک function block دیگر.
- (I) **Initial execution/Restart execution**:
در این مدتی به هر عنوان سیستم restart شود تنظیمات sequence table را به حالت اول یا cold restart خود برمی گرداند
- (B) **Initial execution**:
وقتی FCS در وضعیت RESTART قرار می گیرد اجراء می شود تنظیمات خروجی
- دو نوع تنظیم خروجی دارد که عبارتند از:
وقتی تغییرات وضعیت داشته باشیم خروجی داریم یعنی می توان بطور دستی تغییر وضعیت بدھیم (C)
- تغییرات خروجی تابع تغییرات ورودی است و بطور دستی نمی توان تغییرات داد (E)

Processing Timing

تنظیمات اجراء و خروجی را می توان بصورت ترکیبی نیز درنظر گرفت که با استفاده از آن می توان تنظیمات فرآیند کنترلی را انجام داد

Default

Execution Timing	Output Timing	Symbol
Periodic Execution (T)	Conditional Output (C)	TC
	Each time Output (E)	TE
One-Shot Execution (O)	Conditional Output (C)	OC
	Each time Output (E)	OE
Startup at Initial Cold Start/Restart (I)	-	I
Restricted Initial Execution (B)	-	B

:وقتی بطور دستی بخواهیم خروجی را صفر کنیم استفاده می شود معمولا برای کنترل آلارم ها **TC** استفاده می شود بطوری که بخواهیم همه آنها را همزمان **acknowledge** کنیم **TE**: خروجی بطور دستی صفر نمی شود و تابع ورودی است

Non-step Type Sequence Table

		Rule	01	32
		Step			
C01	%SW0200	Y			
.	%SW0201	Y			
.	%SW0202				
.	%SW0203				
C32	Condition signals				
A01	%Z011101	Y			
.	%Z011102	Y			
.	%Z011103	N			
A32	Action signals				
		THEN			
		ELSE			

		Rule	01	32
		Step			
C01	%SW0200	Y			
.	%SW0201	Y			
.	%SW0202				
.	%SW0203				
C32	Condition signals				
A01	%Z011101		Y		
.	%Z011102				
.	%Z011103				
A32	Action signals				
		THEN			
		ELSE			

Actions are executed in order of %Z011101, %Z011102, %Z011103.

%SW0200 and %SW0201 are ON and then %Z011101 turns ON.

%SW0201 and %SW0202 are OFF and then %Z011102 turns ON.

Non-step Type Sequence Table

		Rule	01	32
		Step								
C01	%SW0200	Y								
.	%SW0201	Y								
.	%SW0202		Y							
.	%SW0203			Y						
C32	Condition signals									
A01	%Z011101	Y	N	N						
.	%Z011102									
.	%Z011102									
A32	Action signals									
		THEN								
		ELSE								

When conditions in 3 rules are satisfied,
Y is executed. (Y has a priority.)

When conditions in 2 rules are satisfied, Y and
then N is executed. (Executed from top to
down.)

Step Type Sequence Table

		Rule	04	05	08
		Step			
C01	%SW0200			Y	
.	%SW0201			Y	
.	%SW0202		Y		
.	%SW0203			Y	
C32	Condition signals				
A01	%Z011101			Y	
.	%Z011102		Y		
.	%Z011103			Y	
A32	Action signals				
		THEN	05		
		ELSE	08		

Step label → Step label (THEN label) → Next step label (ELSE label)

Tested rules ←

Step Type Sequence Table

		Rule	04	05	08
		Step	04	05	08
C01	%SW0200			Y	
.	%SW0201			Y	
.	%SW0202		Y		
.	%SW0203			Y	
C32	Condition signals				
A01	%Z011101			Y	
.	%Z011102		Y		
.	%Z011103			Y	
A32	Action signals				
		THEN	05		
		ELSE	08		

When the condition of the rule in step 04 is satisfied, the step advances to 05.

Step Type Sequence Table

Rule		04	05	08
	Step			
C01	%SW0200		Y	
.	%SW0201		Y	
.	%SW0202	Y		
.	%SW0203		Y	
C32	Condition signals			
A01	%Z011101		Y	
.	%Z011102	Y		
.	%Z011103		Y	
A32	Action signals			
THEN		05		
ELSE		08		

When the condition of the rule in step 04 is not satisfied, the step advances to 08.

Diagram illustrating the structure of a process configuration table for the ST100 Wash Line Accept Processing.

The table is organized into several sections:

- Header Row:** Rule no., Step label, Rule true/false status, Rule.
- Control Period Row:** Tag comment, Control period.
- Block Mode Row:** Tag name, Block mode, Alarm status.
- Step Processing Section:** Contains rows for C01-C04, C06-C08, C10-C12, A01-A04, A05-A10, and an extended table label section.
- Action Processing Section:** Contains rows for A05-A10.
- Bottom Row:** Table name of extention destination, Ready, *1, *2, Label for next step.

Annotations point to specific fields and sections:

- Tag name: Points to the first column of the Block Mode row.
- Block mode: Points to the second column of the Block Mode row.
- Alarm status: Points to the third column of the Block Mode row.
- Label name of the step currently in progress: Points to the first column of the Step Processing section.
- Process timing: Points to the second column of the Step Processing section.
- Condition signal no.: Points to the third column of the Step Processing section.
- Condition signal: Points to the fourth column of the Step Processing section.
- Signal comment/tag comment: Points to the fifth column of the Step Processing section.
- Action signal no.: Points to the first column of the Action Processing section.
- Action signal: Points to the second column of the Action Processing section.
- Extended table label: Points to the extended table label section at the bottom.
- Table name of extention destination: Points to the first column of the bottom row.
- *1: Can drag to change (relative) display area for conditions/actions.
- *2: Can drag to change display area for signals & comments/rules.
- Label for next step: Points to the last column of the bottom row.

Table Data (Step Processing Section):

No	Comment	1..4	5..8	9..2	3..6	7..9	1..4	5..8	9..2
C01	SW0012.PV	ON	Line stop	Y...	Y...
C02	SW0010.PV	ON	Washing start	.N.Y
C03	TM0003.BSTS	CTUP	Process timer 1	Y... N.
C04	TM0004.BSTS	CTUP	Process timer 2	.. Y.	Y...
C06	R0001.X01	GE		N..Y	N..
C07			
C08			
C10			
C11			
C12			

Table Data (Action Processing Section):

A01	%OG0001.PV	NON	Washing process start	Y...	Y...
A02	SW0011.PV	H	Washing complete	.Y.	N..
A03	TM0003.OP	START	Process timer 1	..Y
A04	CL0020.ACT	ON	Flow calculation 1	.. Y.
A05	FIC003.MODE	MAN		Y...	Y...
A06	FIC005.MODE	MAN		.. Y.
A07	FIC007.MODE	MAN	Inlet flow Y.
A08	CL0021.ACT	ON	Flow calculation 2	.. Y.
A09	CL0022.ACT	ON	Flow calculation 3	.. Y.
A10	CL0023.ACT	ON	Flow calculation 4	.. Y.

Extended Table Label Section:


YN	ST101	THEN	AAAA	AAAA
YN			2345	6789
		ELSE A
		 1

*1: Can drag to change (relative) display area for conditions/actions

*2: Can drag to change display area for signals & comments/rules


تمرین ۱:

- با استفاده از ST16 مدارات گیت های NOT و OR و AND را بندید

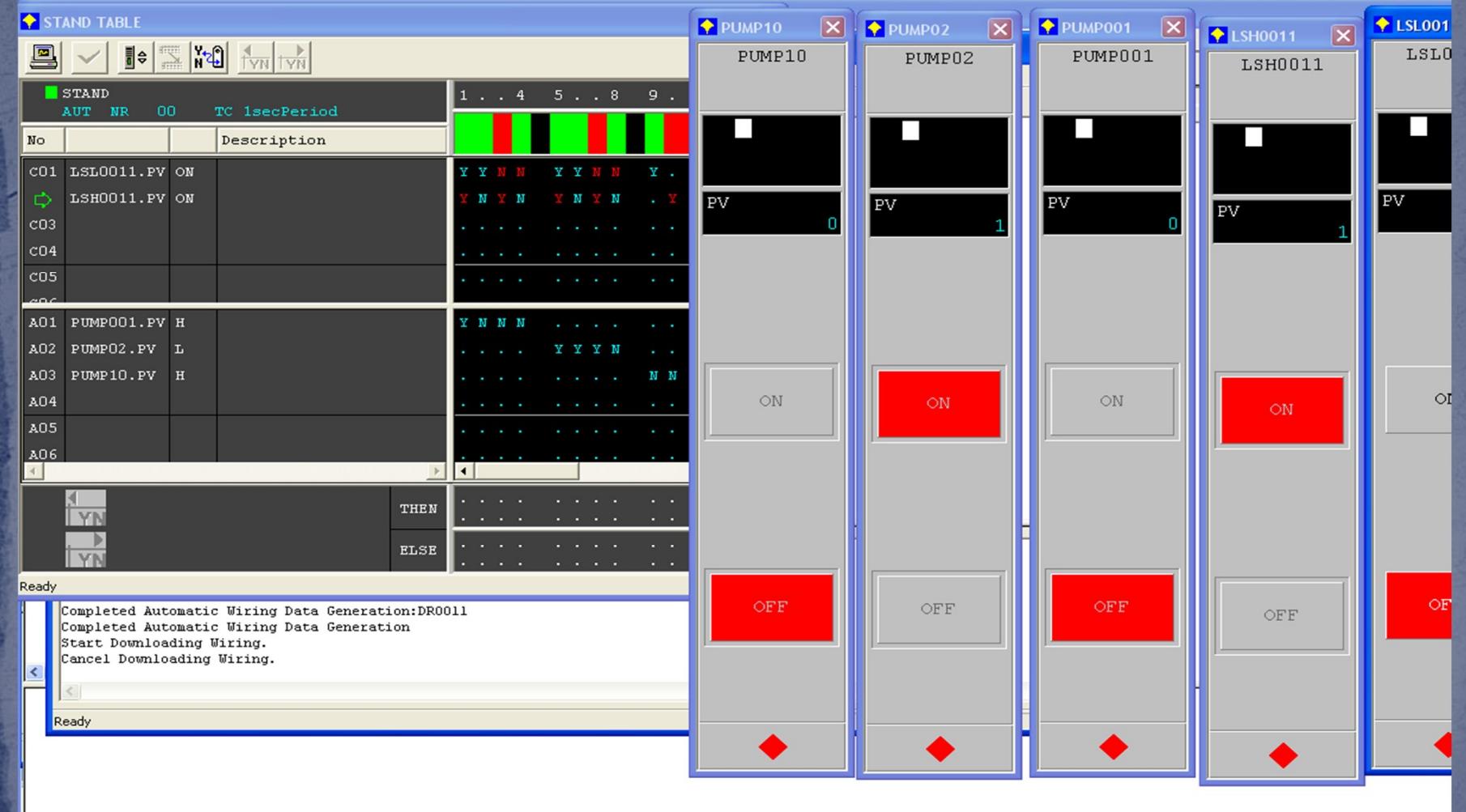


تمرین 2

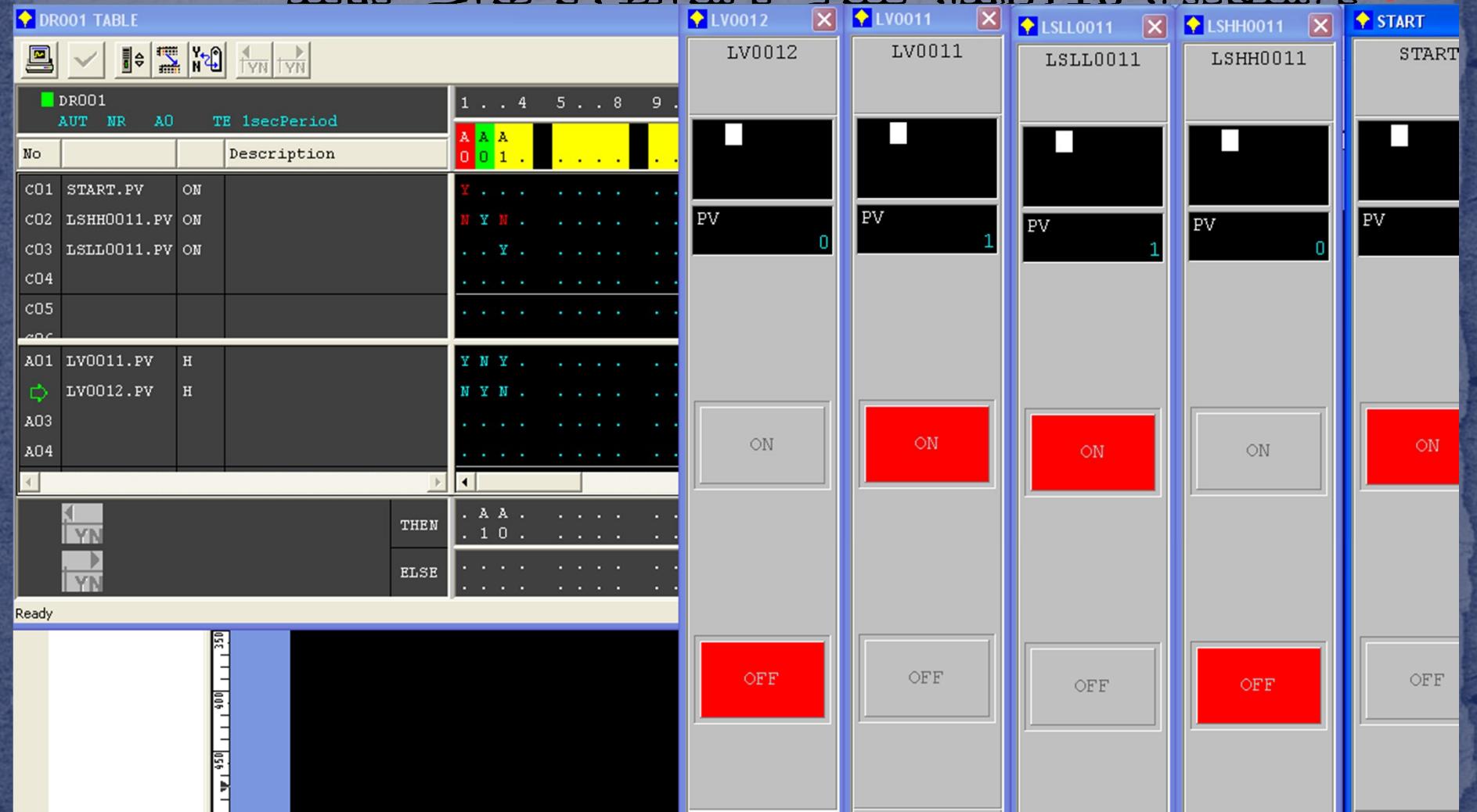● با استفاده از مدار کنترل با شابط زد طاح نمائید



Timer Block (TM)

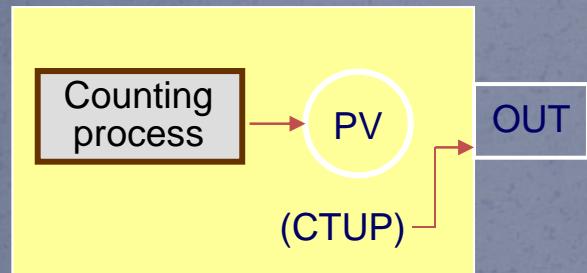بلوک تایمر زمان را بر حسب ثانیه و دقیقه اندازه گیری می کند و دارای قابلیت فرمان های پریودیک را دارد



Function block diagram Timer count-up

BSTS: Block status
CTUP: Count-up
OP: Operation
TART: Start/stop action

An example of the timer block operation.

Processing Timing: TC		
%SW0500.PV	ON	Y
TM100.BSTS	CTUP	Y
TM100.OP	START	Y
%SW0500.PV	H	N
	Start command	
	Stop command	

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.